

1. a. Take 3.8 (a) and find equivalent impedance, using 3.8 (b); That is,

$$R_s + jX_s = \frac{jR_p X_p}{R_p + jX_p} \frac{R_p - jX_p}{R_p - jX_p} = \frac{R_p X_p^2 - jR_p^2 X_p}{R_p^2 + X_p^2}$$

so

$$R_s = \frac{R_p X_p^2}{R_p^2 + X_p^2} = \frac{R_p}{Q_p^2 + 1}, \text{ since } Q_p = \frac{R_p}{X_p}$$

and

$$X_s = \frac{R_p^2 X_p}{R_p^2 + X_p^2} = \frac{X_p}{1 + Q_p^{-2}}$$

$$Q_s = \frac{X_s}{R_s} = \frac{X_p}{1 + Q_p^{-2}} \frac{Q_p^2 + 1}{R_p} = \frac{Q_p^2 + 1}{1 + Q_p^{-2}} \frac{1}{Q_p}$$

$$= \frac{(Q_p^2 + 1) \cdot Q_p}{(Q_p^2 + 1)}$$

$$= Q_p$$

b. $R_s \sim R_p$ when $Q = Q_p$ is small
 $X_s \sim X_p$ when $Q = Q_p$ is large.



want $\text{Re} \left[\frac{-jX_c R_L}{R_L - jX_c} \cdot \frac{R_L + jX_c}{R_L + jX_c} \right] = 5j$.

$$\frac{X_c^2 R_L}{R_L^2 + X_c^2} = 5 \Omega$$

$$\frac{R_L}{5} = \frac{R_L^2}{X_c^2} + 1$$

$$\frac{1}{X_c^2} = \frac{1}{R_L^2} \left[\frac{R_L}{5} - 1 \right]$$

$$\text{for } R_L = 50 \Omega, \quad X_c = \frac{50}{3} \Omega$$

$$\text{imaginary part: } -\frac{X_c R_L^2}{R_L^2 + X_c^2}$$

so


$$X_L = \frac{X_c R_L^2}{R_L^2 + X_c^2} = \frac{X_c}{1 + \frac{X_c^2}{R_L^2}} = \frac{X_c}{1 + \left(\frac{1}{3}\right)^2} = \frac{50}{3 + \frac{1}{3}}$$

example $f = 7 \text{ MHz}$

$$X_c = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega X_c} = \frac{3}{2\pi(7 \cdot 10^6) 50} = 1.36 \text{ nF}$$

$$X_L = \omega L$$
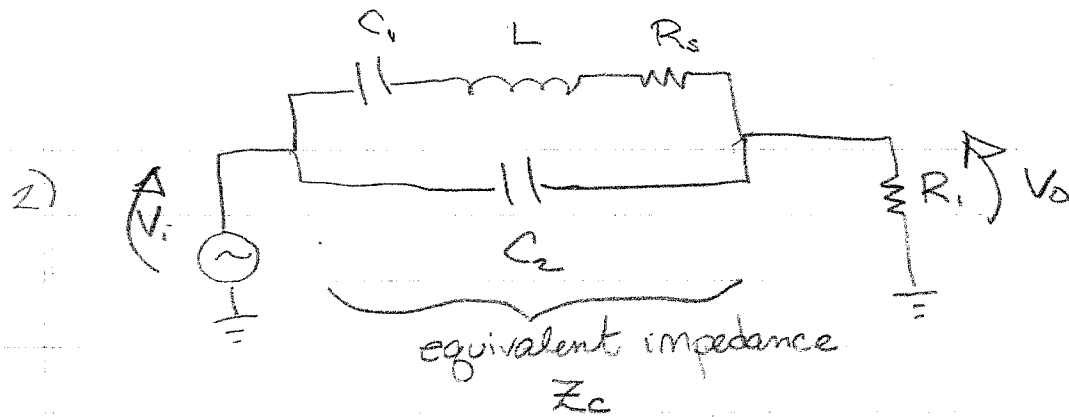
$$\Rightarrow L = \frac{X_L}{2\pi(7 \cdot 10^6)} = 341 \text{ nH}$$




$$Z_c = \frac{\left(\frac{1}{j\omega C_1} + j\omega L + R_s\right) \frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + j\omega L + R_s + \frac{1}{j\omega C_2}}$$

$$\text{Im}(Z_c) = \frac{-R_s^2}{\omega C_2} + \frac{1}{\omega C_2} \left(\omega L - \frac{1}{\omega C_1}\right) \left(\frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L\right)$$

condition for $\text{Im}(Z_c) = 0$

$$R_s^2 = \left(\omega L - \frac{1}{\omega C_1}\right) \left(\frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L\right)$$

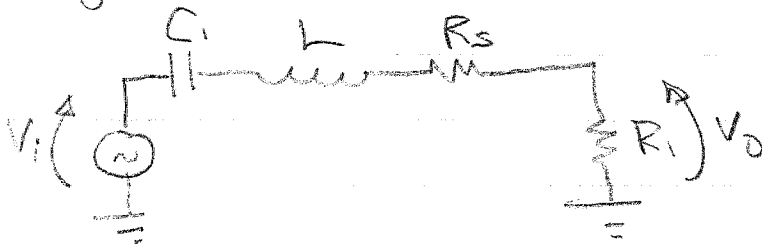2b equivalent circuit if C_2 can be neglected.



series resonance

$$\frac{V_o}{V_i} = \frac{R_L}{R_i + R_s + j\omega L + \frac{1}{j\omega C_1}} = \frac{R_L \left[(R_i + R_s) - j \left(\omega L - \frac{1}{\omega C_1} \right) \right]}{(R_i + R_s)^2 + \left(\omega L - \frac{1}{\omega C_1} \right)^2}$$

at resonance,

$$\omega L = \frac{1}{\omega C_1}, \text{ so}$$

$$\frac{V_o}{V_i} = \frac{R_L}{(R_i + R_s)} \quad \text{at resonance.}$$

|reactance| = resistance condition:

$$R_i + R_s = \left| \omega L - \frac{1}{\omega C_1} \right|$$

$$(R_i + R_s)^2 = \left(\omega L - \frac{1}{\omega C_1} \right)^2$$

$$\omega^2 (R_i + R_s)^2 = \left(\omega^2 L - \frac{1}{C_1} \right)^2$$

2 solutions for $x = \omega^2$:

$$0 = x^2 L^2 - \frac{2}{C_1} L \cdot x - (R_i + R_s)^2 x + \frac{1}{C_1^2}$$

$$x = \frac{\left(\frac{2L}{C_1} + (R_i + R_s)^2 \right)}{2L^2} \pm \sqrt{\frac{\left(\frac{2L}{C_1} + (R_i + R_s)^2 \right)^2}{4L^4} - \frac{1}{C_1^2 L^2}}$$

$$\text{or } \omega^2 = \frac{1}{LC_1} + \frac{(R_i + R_s)^2}{2L^2} \pm \sqrt{\left(\frac{1}{LC_1} + \frac{(R_i + R_s)^2}{2L^2} \right)^2 - \frac{1}{L^2 C_1^2}}$$

|reactance| = resistance condition

3dB condition :

find ω

$$\left| \frac{V_o}{V_i} \right|^2 = \frac{1}{2} \frac{R_i^2}{(R_i + R_s)^2} = \frac{R_i^2 \cdot \left[(R_i + R_s)^2 + (\omega L - \frac{1}{\omega C})^2 \right]}{\left[(R_i + R_s)^2 + (\omega L - \frac{1}{\omega C})^2 \right]^2}$$

or


$$(R_i + R_s)^2 + (\omega L - \frac{1}{\omega C})^2 = 2 (R_i + R_s)^2$$

$$(\omega L - \frac{1}{\omega C})^2 = (R_i + R_s)^2$$

so 3dB condition is identical to the
|reactance| = resistance condition

— // —

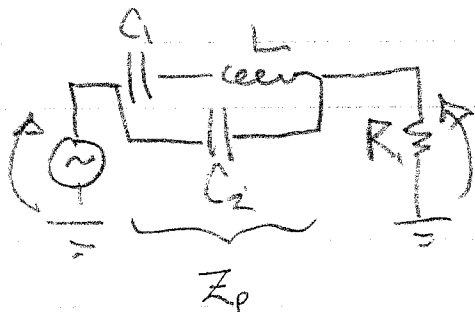2b) contd) equivalent circuit if R_s can be neglected



$$Z_p = \frac{\left[\frac{1}{j\omega C_1} + j\omega L \right] \frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j\omega L} = j \frac{\left[\omega L - \frac{1}{\omega C_1} \right]}{\frac{C_2}{C_1} + 1 - \omega^2 L C_2}$$

purely reactive

resonance condition

$$Z_p = 0 \Rightarrow \omega L = \frac{1}{\omega C_1}$$

$$\frac{V_o}{V_i} = 1 \text{ at resonance}$$

cut off condition

$$|Z_p| = R_1$$

$$\text{get } \left[\omega L - \frac{1}{\omega C_1} \right]^2 = R_1^2 \left(\frac{C_2}{C_1} + 1 - \omega^2 LC_2 \right)^2$$

consider ω such that $\omega^2 LC_2 \ll \frac{C_1 + C_2}{C_1}$
(low frequencies)

Then, the equation becomes
$$\left[\omega L - \frac{1}{\omega C_1} \right]^2 \approx R_1^2 \left(\frac{C_1 + C_2}{C_1} \right)^2$$

or

$$\omega^4 L^2 - 2\omega^2 \frac{L}{C_1} + \frac{1}{C_1^2} - \omega^2 R_1^2 \left(\frac{C_1 + C_2}{C_1} \right)^2 + \frac{1}{C_1^2} = 0$$

or ($X = \omega^2$):

$$L^2 X^2 - \left(\frac{2L}{C_1} + R_1^2 \left(\frac{C_1 + C_2}{C_1} \right)^2 \right) X + \frac{1}{C_1^2} = 0$$

2 solutions

$$X = \frac{\frac{2L}{C_1} + R_1^2 \left(\frac{C_1 + C_2}{C_1} \right)^2}{2L^2 C_1^2} \pm \sqrt{\left(\frac{\frac{2L}{C_1} + R_1^2 \left(\frac{C_1 + C_2}{C_1} \right)^2}{2L^2 C_1^2} \right)^2 - \frac{1}{L^2 C_1^2}}$$

approximate
cut off
frequencies

$$\text{or } \omega^2 = \frac{1}{LC_1} + \frac{R_1^2}{2L^2} \left(1 + \frac{C_2}{C_1} \right)^2 \pm \sqrt{\left\{ \frac{1}{LC_1} + \frac{R_1^2}{2L^2} \left(1 + \frac{C_2}{C_1} \right)^2 \right\}^2 - \frac{1}{L^2 C_1^2}}$$


now consider frequencies such that $\omega^2 LC_2 \sim \frac{C_1 + C_2}{C_1}$

then $|Z_p| = \infty$, and $\frac{V_o}{V_i} \approx 0$ @ $\omega^2 \sim \frac{C_1 + C_2}{LC_1 C_2}$

and around this frequency there are
2 more cutoffs

for all crystals of interest, $\underbrace{\frac{1}{LC_1}}_{\text{resonant freq}^2} \ll \underbrace{\frac{C_1 + C_2}{C_2} \frac{1}{LC_1}}_{\text{notch freq}^2}$

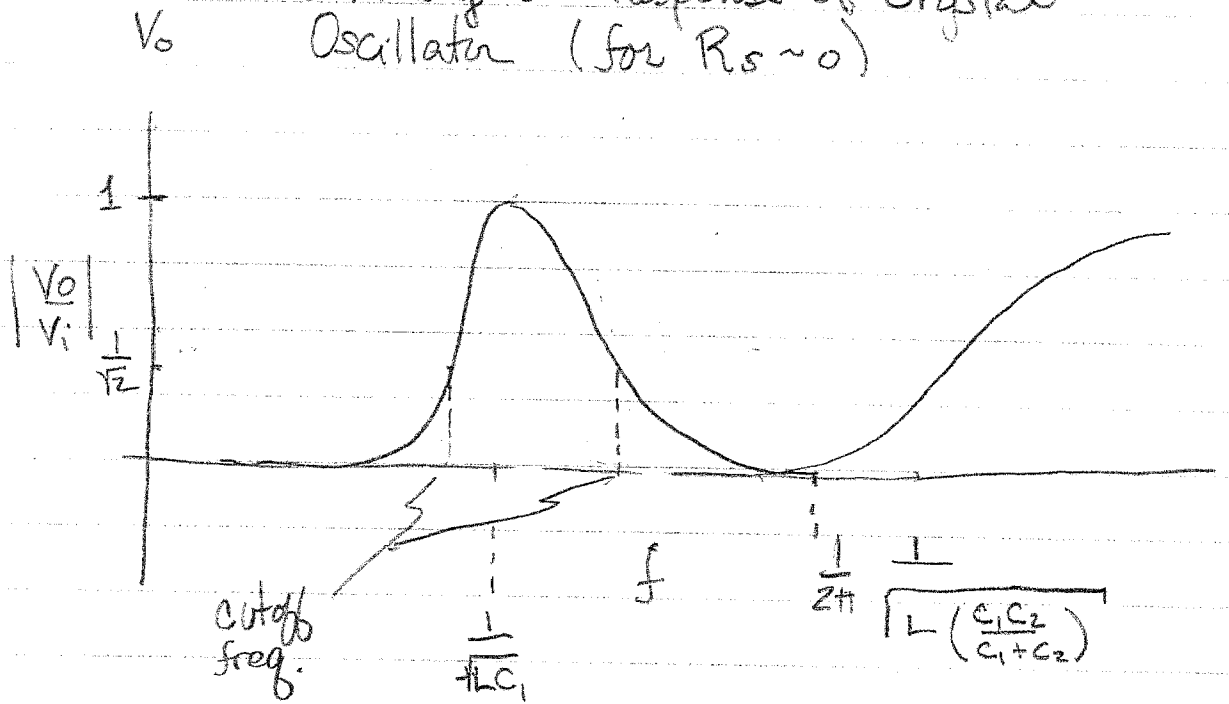Summary of Response of Crystal Oscillator (for $R_s \sim 0$)




2c) if C_2 can be neglected, then this circuit acts like a series resonance device.

Use the formulas developed in 2b for $C_2=0$, setting $R_s=0$ in the formulas. So.

$$\omega^2 = \frac{1}{LC_1} \quad \text{resonance}$$

$$\omega^2 = \frac{1}{LC_1} + \frac{R_1^2}{2L^2} \pm \sqrt{\left(\frac{1}{LC_1} + \frac{R_1^2}{2L^2}\right)^2 - \frac{1}{L^2C_2}} \quad \text{cutoff}$$

3

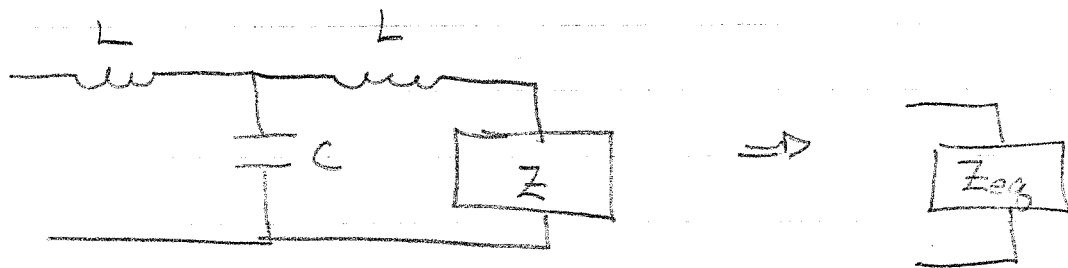

$$a.) \quad Z_{eq} = j\omega L + \frac{\frac{1}{j\omega C} [j\omega L + Z]}{Z + j\omega L + \frac{1}{j\omega C}}$$

$$b.) \quad \text{at } \omega = \frac{1}{\sqrt{LC}},$$

$$Z_{eq} = j\sqrt{\frac{L}{C}} + \frac{\left[\frac{L}{C} - jZ\sqrt{\frac{L}{C}}\right]}{Z + 0}$$

$$= j\sqrt{\frac{L}{C}} + \frac{1}{C} \cdot \frac{1}{Z} - j\sqrt{\frac{L}{C}}$$

So, this circuit inverts the impedance Z , and is called an impedance inverter.