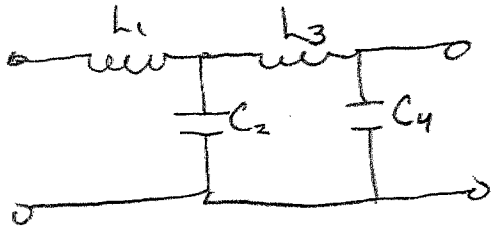


$$1.) L(f) = 1 + \left(\frac{f}{f_c}\right)^{2n} \geq 100 \quad @ \quad f = 56 \text{ Hz}$$

$$n \geq 4 \Rightarrow n = 4.$$



$$a_1 = x_1 = \frac{X_1}{75} = \frac{\omega_c L_1}{75}$$

$$L_1 = \frac{(0.765) 75}{2\pi \cdot 2.5 \cdot 10^9}$$

$$L_1 = 3.65 \text{ nH}$$

$$a_2 = b_2 = \omega_c C_2 \cdot 75$$

$$C_2 = \frac{1.848}{75 \cdot 2 \cdot \pi \cdot 2.5 \cdot 10^9} = 1.57 \text{ pF}$$

$$a_3 = x_3 = \frac{\omega_c L_3}{75}$$

$$L_3 = \frac{(1.848)(75)}{2\pi \cdot 2.5 \cdot 10^9} = 8.8 \text{ nH}$$


$$a_4 = b_4 = \omega_c C_4 \cdot 75$$

$$C_4 = \frac{0.765}{75 (2\pi) 10^9} = 1.6 \text{ pF}$$

2.  $C_0(x) = 1$   $L(f) = 1 + \alpha C_n^2\left(\frac{f}{f_c}\right)$   
 $C_1(x) = x$   $1 + \alpha = 10^{\frac{1}{20}}$   
 $C_2(x) = 2x^2 - 1$   $\alpha = 0.122$   
 $C_3(x) = 4x^3 - 3x$

$n, \text{ odd}$	$L(5\text{GHz})$
1	1.7
3	2.83
5	

$\rightarrow n = 3$

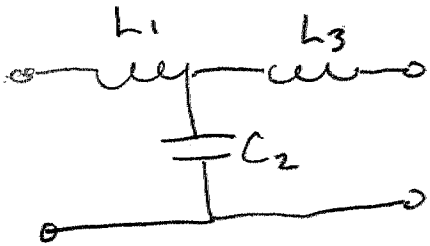

$$\beta = \sinh\left(\frac{\tanh^{-1}\left(\frac{1}{\sqrt{1+\alpha}}\right)}{n}\right)$$

$\beta = 0.52$

table coefficients:

$$C_1 = \frac{a_1}{\beta} = \frac{1}{0.52} = 1.92$$

$$C_2 = \frac{a_2 a_1}{C_1 (\beta^2 + \sin^2[\frac{\pi}{3}])}$$

$$= \frac{2}{1.92} \cdot \frac{1}{(0.52)^2 + 0.75}$$

$$C_2 = 1.04 \cdot (0.98) = 1.02$$

$$C_3 = \frac{2}{(1.02) \left( (0.52)^2 + \sin^2\left(\frac{2\pi}{3}\right) \right)}$$

$$= (1.96)(0.98) = 1.92$$

$$C_1 = \frac{\omega_c L_1}{75} \Rightarrow L_1 = \frac{(1.92)(75)}{2\pi(2.5)10^9}$$


$$L_1 = 9.2 \text{ nH}$$

$$C_2 = 75 \omega_c C_2 \Rightarrow C_2 = \frac{1.02}{(75)(2\pi)(2.5)10^9} = 0.86 \text{ pF}$$

$$L_3 = L_1$$

3.

$$|L(1.25 \text{ GHz})| = 1 + (2)^{2n} \geq 100 \Rightarrow n = 4$$

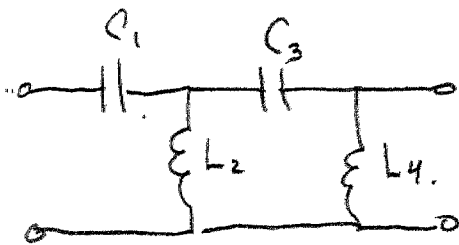

$$a_1 = 0.765$$

$$a_3 = 1.848$$

$$a_2 = 1.848$$

$$a_4 = 0.765$$

$$a_1 = \frac{1}{\omega_c C_1} \frac{1}{75} \Rightarrow C_1 = \frac{1}{2\pi(2.5)10^9 (0.765)(75)} = 0.9 \mu\text{F}$$

$$a_2 = \frac{75}{\omega_c L_2} \Rightarrow L_2 = \frac{75}{2\pi(2.5)10^9 (1.848)} = 2.6 \text{ nH}$$

$$a_3 = \frac{1}{\omega_c C_3} \Rightarrow C_3 = C_1 \cdot \frac{(0.765)}{1.848} = 37 \text{ nF}$$

$$a_4 = \frac{75}{\omega_c L_4} \Rightarrow L_4 = \frac{75}{\omega_c a_4} = L_2 \cdot \frac{a_2}{a_4} = 6.3 \text{ nH}$$

4.)

$$\alpha = 0.122$$

$$C_0(z) = 1$$


$$C_1(z) = 2$$

$$C_2(z) = 4 \cdot 2 - 1 = 7$$

$$C_3(z) = 4(7) - 2 = 26$$

$$C_4(z) = 4(26) - 7 = 97$$

$$C_5(z) = 4(97) - 26 = 362$$

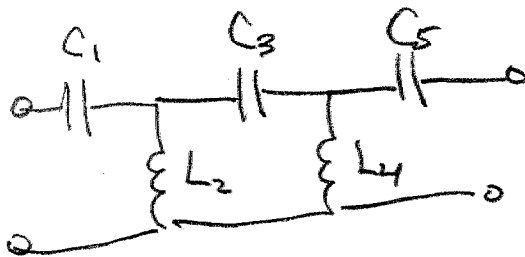

$$C_1 = \frac{1}{\omega_c C_1} \frac{1}{75} \Rightarrow C_1 = \frac{1}{(2\pi)(2.5)10^9(1.7)(75)}$$

$$C_1 = \frac{1}{2} \text{ pF}$$

$$C_2 = \frac{75}{\omega_c L_2} \Rightarrow L_2 = \frac{75}{2\pi(2.5)10^9(1.23)}$$

$$L_2 = 3.88 \text{ nH}$$

$$C_3 = \frac{1}{\omega_c C_3} \frac{1}{75} \Rightarrow C_3 = C_1 \cdot \frac{C_1}{C_3}$$

$$= 0.33 \text{ pF}$$

$$C_4 = \frac{75}{\omega_c L_4} \Rightarrow L_4 = L_2 \cdot \frac{C_2}{C_4} = 3.88 \text{ nH}$$

$$C_5 = \frac{1}{\omega_c C_5} \frac{1}{75} \Rightarrow C_5 = C_1 \cdot \frac{C_1}{C_5}$$

$$= \frac{1}{2} \text{ pF}$$

$$L(1.25) = 1 + \alpha C_n^2(z)$$

n	
1	1.48
3	83
5	~16000

$$n = 5$$

$$\beta = \sinh \left( \frac{\tanh^{-1} \left( \frac{1}{11.22} \right)}{5} \right)$$

$$\beta = 0.362$$

$$C_1 = \frac{Q_1}{\beta} = \frac{0.618}{0.362} = 1.7$$

$$C_2 = \frac{(0.618)(1.618)}{(1.7)} \frac{1}{\left[ (0.362)^2 + \sin^2 \left( \frac{\pi}{5} \right) \right]}$$

$$C_2 = 1.23$$

$$C_3 = \frac{2(1.618)}{1.23} \frac{1}{\left[ (0.362)^2 + \sin^2 \left( \frac{2\pi}{5} \right) \right]}$$


$$C_3 = 2.54$$

$$C_4 = \frac{(1.618)(2)}{(2.54)} \frac{1}{\left[ (0.362)^2 + \sin^2 \left( \frac{3\pi}{5} \right) \right]}$$

$$C_4 = 1.23$$

$$C_5 = 1.7$$

5)

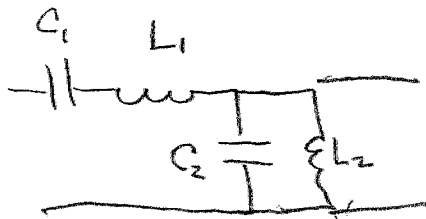

$$n=2 \quad \Delta\omega = 2\pi (50 \text{ kHz})$$

$$a_1 = \sqrt{2} \quad \omega_0 = 2\pi (300 \text{ kHz})$$

$$a_2 = \sqrt{2}$$

$$a_1 = \frac{\Delta\omega L_1}{75} \Rightarrow L_1 = \frac{a_1 \cdot 75}{\Delta\omega} = \frac{\sqrt{2} \cdot 75}{2\pi \cdot 50 \cdot 10^3} = \frac{1}{3} \text{ mH}$$


$$C_1 = \frac{1}{\omega_0^2 L_1} = \frac{1}{(2\pi)^2 (3)^2 (10^5)^2 \cdot 0.33 \cdot 10^{-3}}$$

$$C_1 = 853 \mu\text{F}$$

$$a_2 = \frac{75}{\Delta\omega C_2} \Rightarrow C_2 = \frac{75}{\Delta\omega a_2} = \frac{75}{2\pi \cdot 50 \cdot 10^3 \cdot \sqrt{2}} = 168 \mu\text{F}$$

$$L_2 = \frac{1}{\omega_0^2 C_2} = \frac{1}{(2\pi)^2 (3)^2 (10^5)^2 \cdot 168 \cdot 10^{-6}}$$

$$L_2 = 1.67 \text{ nH}$$

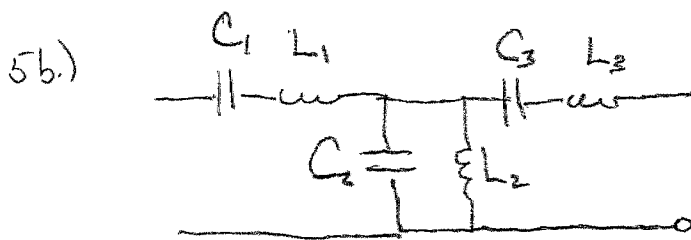

$$a_1 = 1$$

$$a_3 = 1$$

$$a_2 = 2$$

$$a_1 = \frac{\Delta\omega L_1}{75} \Rightarrow L_1 = \frac{75}{2\pi \cdot 5 \cdot 10^4} = 239 \mu\text{H}$$

$$C_1 = \frac{1}{\omega_0^2 L_1} = \frac{1}{(355 \cdot 10^{10}) (239 \cdot 10^{-6})} = 1.18 \text{ nF}$$

$$a_2 = \Delta\omega C_2 \cdot 75 \Rightarrow C_2 = \frac{2}{2\pi \cdot 5 \cdot 10^4 (75)} = 85 \text{ nF}$$

$$h_2 = \frac{1}{\omega_0^2 C_2} = \frac{1}{355 \cdot 10^{10} (85 \cdot 10^{-9})}$$

$$h_2 = 3.3 \mu\text{H}$$

$$h_3 = L_1$$

$$C_3 = C_1$$

3rd order filter requires smaller inductances.