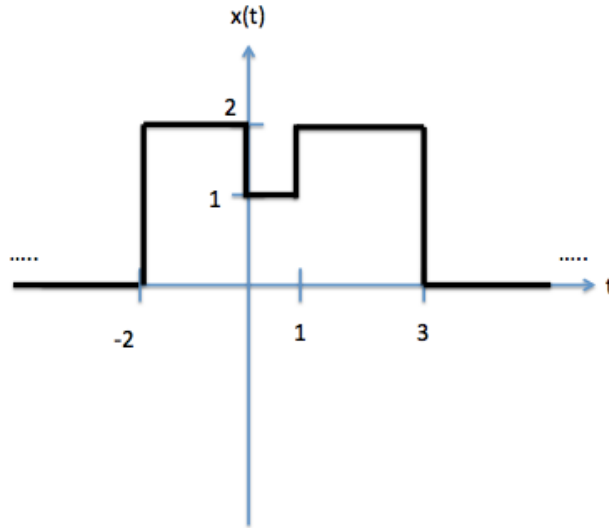


Answers to Practice Final. F14 Section 1

P1.  $v_c(t) = 5(1 + \exp(-100t))$  for  $t > 0$

P2  
(a)



(b-1)  $3\sin((2\pi/3)n + \pi/3) + 4\cos((\pi/2)n - \pi/6)$

(b-2)  $3\sin(4000\pi t \pi/3) + 4\cos((3000\pi t - \pi/6)$

(b-3) No because the 2<sup>nd</sup> term is aliased as the sampling rate is  $< 2x$  the frequency of 4500Hz.

(c-1)  $6/(2^{10}-1) \approx 6\text{mV}$

(c-2)  $\sim 3\text{mV}$

(c-3) 1 V

(d)  $X(\omega) = 2\exp(-j2\omega)(1/1 + j2\omega)$

P3

(a) At DC and as  $\omega \rightarrow \infty$   $v_0(t) = 0$

(b)  $R + j(\omega L + (1/\omega C))$

(c) Call the result in (b)  $Z_T(\omega)$ . Then  $\mathbf{V}_o = R/Z_T(\omega)$ .

(d) Yes. At DC, the first term in the denominator = 0 but the 2<sup>nd</sup>  $\rightarrow \infty$  so the fraction = 0. As  $\omega \rightarrow \infty$  the 2<sup>nd</sup> term in the denominator goes to 0 but the 1<sup>st</sup>  $\rightarrow \infty$  so the fraction  $\rightarrow 0$ .

(e)  $R_{eq} = 20\text{k}\Omega$ ,  $L_{eq} = 15\text{mH}$

P4

(a) if we put ground at the node where the – side of the source, one of the  $20\Omega$  resistors and the  $40\Omega$  resistor are connected, and let  $V_a$  and  $V_b$  represent the node voltages at the nodes labeled as a and b, we get

$$\begin{bmatrix} 1/8 & -1/20 \\ -1/20 & 3/20 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

(b) If we let  $I_1$  be the mesh current for the loop that has the source, the  $20\Omega$ , and the  $40\Omega$  resistors,  $I_2$  be the mesh current for the loop that has the 3  $20\Omega$  resistors, and  $I_3$  be the mesh current for the loop that has the 2  $20\Omega$  resistors and one  $40\Omega$  resistor, we get

$$\begin{bmatrix} 60 & -20 & -40 \\ -20 & 60 & -20 \\ -20 & -40 & 80 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 0 \end{bmatrix}$$

(c)  $V_{th} = 10/3 \text{ V}$ ,  $R_{th} = 70/3$

P5

(a)  $1 + R_1 / (R_2 (1 + j\omega CR_1))$

(b)  $V_o(\omega) = V_s(\omega) (1 + R_1 / (R_2 (1 + j\omega CR_1)))$

(c)  $v_o(t) = 10 + 10/\sqrt{13} \cos(250t + 7\pi/12 - \tan^{-1}(5))$