

EECE 2150 – Circuits and Signals, Biomedical Applications
Final Exam

Name: _____


Instructions:

- Closed book, closed notes; Computers and cell phones are not allowed
- Equation sheet, 8.5x11 inches, both sides, permitted
- Scientific calculators are allowed
- **Complete all 6 problems**
- Show all work and **place a box around all your final answers**
- Include units with answers as appropriate
- Show your work for partial credit
- You may write on both sides of the pages

Question 1 (20 Points)

Name:

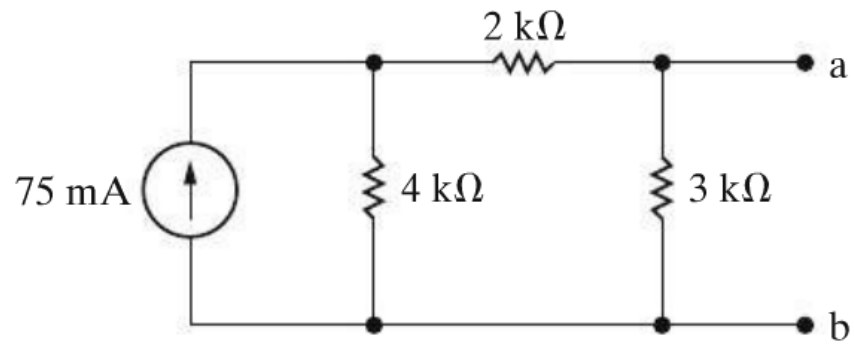1) Find the Thevenin equivalent circuit across terminals a,b for the circuit below:




Answers: $V_{Th} =$

$R_{Th} =$

Question 2 (20 Points)

Name:

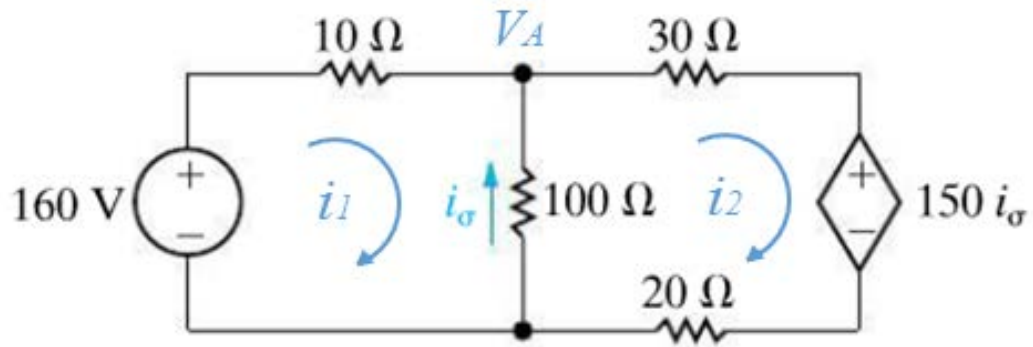

2A) Use either the node-voltage or the mesh-current technique to set up the matrix equations for either the currents i_1 and i_2 or for the voltage V_A .


2B) Solve the resulting equations to find the power dissipated in the 100 ohm resistor.

(extra space on the next page)

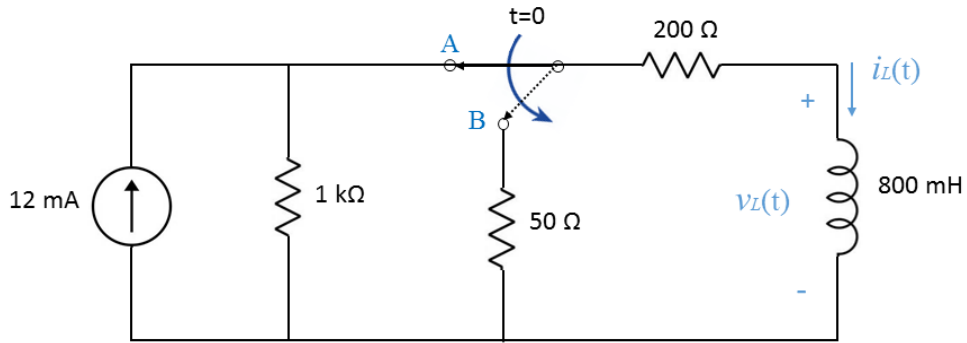Question 3 (20 Points)

Name:

In the circuit below, the switch has been in position A for a long time. At $t = 0$, it is switched to position B.




- 3A) Find the current through the inductor $i_L(0^-)$ and the voltage across the inductor $v_L(0^-)$ just before the switch is thrown.
- 3B) Find an expression for the current through the inductor as a function of time $i_L(t)$ for $t > 0$.
- 3C) Find the current through the inductor at $t = 1$ ms.
- 3D) Find the voltage across the inductor at $t = 1$ ms.

(extra space on the next page)

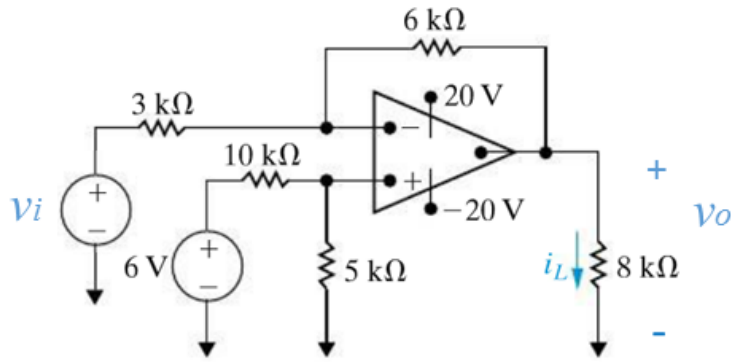Question 4 (20 Points)

Name:

Assuming the op amp is ideal, find i_L in the circuit below.




(extra space on the next page)

Question 5 (20 Points)

Name:

For the following circuit:

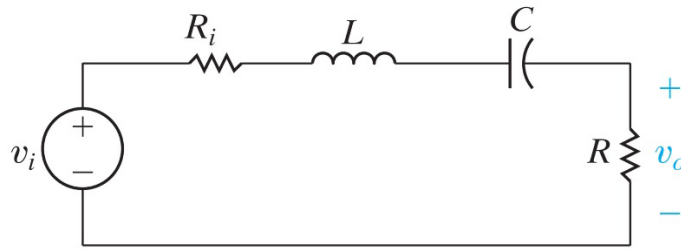


5A) Assuming that $R_i=100\Omega$, $L=100\text{mH}$, $C=1\mu\text{F}$, and $R=1\text{k}\Omega$, find the transfer function (v_o/v_i) at $\omega=1000$ rad/s.

5B) If $v_i=5\cos(1000t)$, what is the output voltage?

Question 6 (20 Points)

Name:

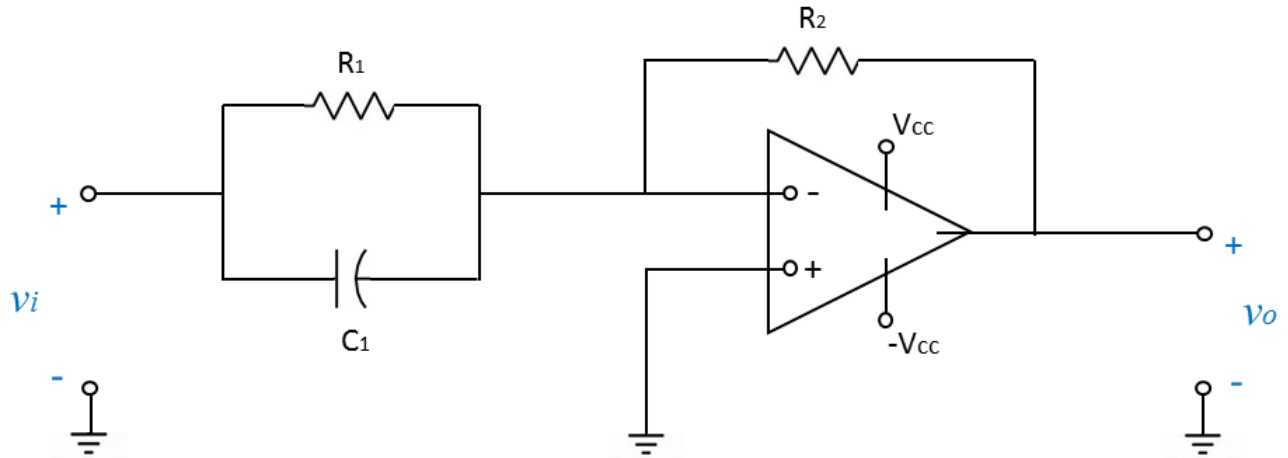

- 6A) If the op amp in the circuit above is ideal, find an expression for the transfer function $H(\omega) = v_o/v_i$
- 6B) If $R_1=5k\Omega$, $R_2=15k\Omega$, and $C=1\mu F$ and the input voltage is given by $v_i(t) = 0.5 \cos(200t)$, find the output voltage $v_o(t)$.
- 6C) If $R_1=5k\Omega$, $R_2=15k\Omega$, and $C=1\mu F$, sketch the magnitude of $H(\omega)$ vs. frequency on the axes shown. Label two values on each axis.



Question 6 (extra space)

Name: