

EECE 2510 – Circuits and Signals, Biomedical Applications
Final Exam – Section 2

Name:


Instructions:

- Closed book, closed notes; Computers and cell phones are not allowed
- Scientific calculators are allowed
- **Complete all 4 problems**
- Show all work and **place a box around all your final answers**
- Write your name on all pages
- You may write on both sides of the pages



Question 1 (32 Points)

Name:

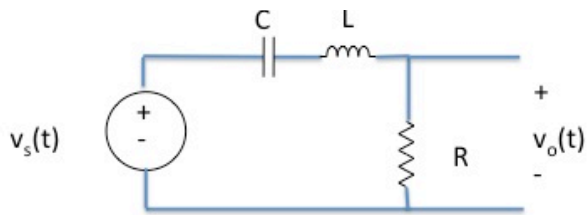1A) Consider the circuit below and given $C = 100 \mu\text{F}$, $L = 10 \text{ mH}$, $R = 10 \Omega$ give Z_c , Z_L , and $V_o(t)$ fori) $V_s(t) = 1\text{V}$ (3 points)

$Z_c =$	$Z_L =$	$V_o(t) =$
---------	---------	------------

ii) $V_s(t) = 1 \cos(10^{10}t) \text{ V}$ (3 points)

$Z_c =$	$Z_L =$	$V_o(t) =$
---------	---------	------------

iii) $V_s(t) = 1 \cos(10^3t) \text{ V}$ (5 points)

$Z_c =$	$Z_L =$	$V_o(t) =$
---------	---------	------------

Question 1 (continued)


Name:

1B) Write the following in complex exponential notation and write the associated phasor voltage (5 points):

i) $v(t) = 3 \cos(1000t + 45^\circ)$

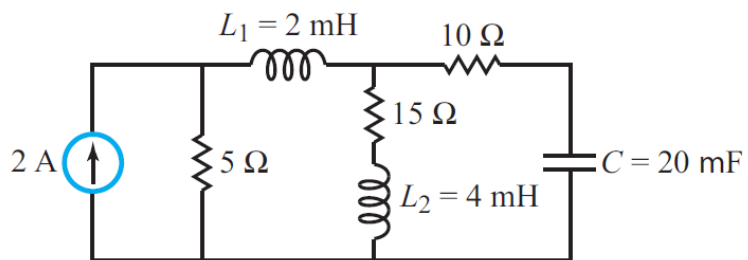ii) $v(t) = -6 \cos(100t - 30^\circ) + 4 \sin(100t + 45^\circ)$


1C) Find V_C (the voltage across the capacitor) in DC conditions for the circuit below: (5 Points)



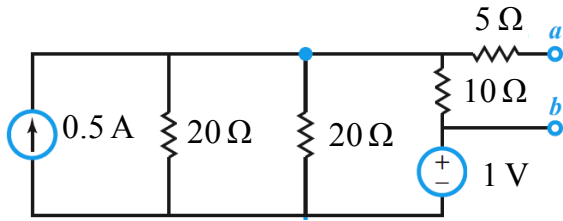
Question 1 (continued)

Name:

1D) Find the **Thevenin Equivalent** circuit of the following circuit across terminals (a,b): **(6 points)**



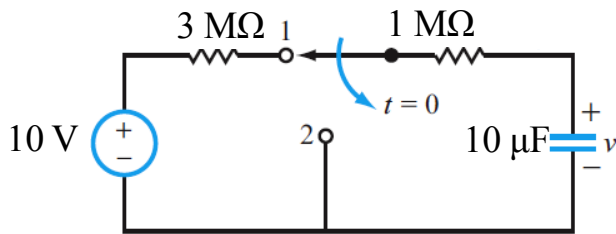1E) The switch in the figure below is at position 1 for a long time before it is thrown to position 2 at $t = 0$. Write an expression for i) V_c (voltage across the capacitor) at time $t=0^-$, and ii) $V_c(t)$ for $t>0$ **(5 points)**



Question 2 (22 Points)

Name:

2A) For the circuit below, find the equivalent phasor-domain quantities: (5 points)


$V_1 =$

$V_2 =$

$Z_L =$

$Z_C =$

$Z_R =$

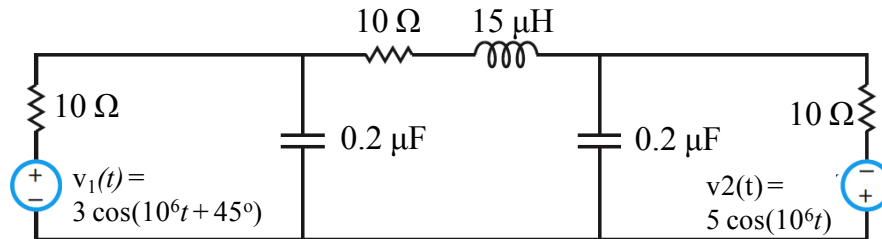

2B) For this circuit, apply the **Node-voltage method** in phasor domain to give two systems of equations and two unknowns node voltages **VN1** and **VN2** (indicate these on the figure above). Write these, simplify and put in **matrix form** below. Place a box around your final answer to make it easy for a grader to find. YOU DO NOT HAVE TO SOLVE VN1 and VN2. (8 Points)

Question 2 (continued)


Name:

- 2C) Now apply the **Mesh-current method** in phasor domain to give three systems of equations and three unknowns node voltages **I1, I2, and I3 (indicate these on the figure above)**. Write these, simplify and put in **matrix form** below. Place a box around your final answer to make it easy for a grader to find. **YOU DO NOT HAVE TO SOLVE** I1, I2 and I3. **(9 Points)**

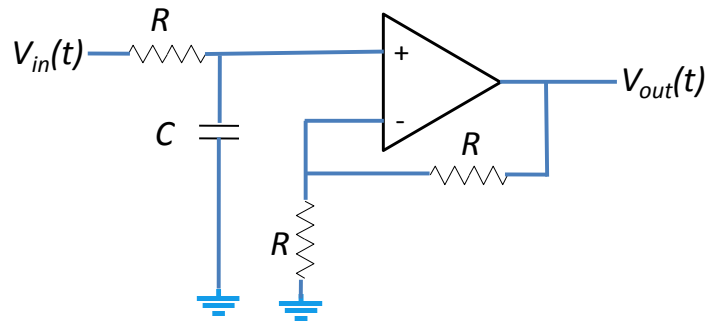Question 3 (22 Points)

Name:

3A) Use the ideal op-amp approximation (phasor domain) to solve the phasor quantity V_{out} as a function of V_{in} as a function of R and C . **(10 points)**



3B) What is the “in-band” gain of this circuit? What kind of filter is this? Justify your answer based directly on output expression in 3A, i.e. you should not require any explicit calculations **(4 points)**

Question 3 (continued)

Name:

3C) Using the expression you obtained in part 3A), if $R = 10\text{k}\Omega$ and $C = 1\mu\text{F}$,

What is $V_{\text{out}}(t)$ if $V_{\text{in}}(t) = 2 + 2 \cos(1000t + \pi/3)$?

If you could not obtain any expression for part (a) explain in as much detail as you can how you would solve this problem in order to get partial credit. **(8 points)**

Question 4 (24 Points)

Name:

(4A) Sketch the signal given by the following expression: $x(t) = 3u(t+1) - u(t) + u(t-2) - 3u(t-4)$. Be sure to label your sketch clearly for full credit. **(5 points)**

(4B) An analog-to-digital converter (also called ADC or A/D) uses a sampling rate of $F_s = 6000$ samples/second. An audio signal is recorded by a microphone to produce the electrical signal $x(t) = 3\sin(4000\pi t + \pi/3) + 6\cos(9000\pi t - \pi/6)$ volts and is then sampled by this ADC and stored on a computer.

(B-i) What is the resulting discrete time (DT) sinusoid? The frequencies of the DT sinusoid should be converted to the lowest equivalent frequency. **(6 points)**

(B-ii) If this DT sinusoid is played through speakers connected to a computer using the same sampling rate F_s to reconstruct the signal, what frequencies (itches) will be heard in the sound? **(3 points)**

(B-iii) Do these frequencies match those in the original signal? Why or why not? **(3 points)**

Question 4 (continued)

Name:

(4C) The ADC has a dynamic range of -5 to 5 volts and quantizes numbers to 12 bit accuracy.

(C-i) What is the amplitude resolution of this ADC in volts (that is, what is the equivalent in volts to a difference of one quantization level in the quantized signal)? **(3 points)**

(C-ii) Based on your answer to (C-i), for the first component of $x(t)$ (i.e. $3\sin(4000\pi t + \pi/3)$ volts), what is the maximum quantization error in volts for any given sample? **(2 points)**

(C-iii) For the second component of $x(t)$, (i.e. $6\cos(9000\pi t - \pi/6)$ volts), what is the maximum quantization error in volts for any given sample? **(2 points)**