

EECE 2510 – Circuits and Signals, Biomedical Applications
Final Exam – Section 3

Name:

Instructions:


- Closed book, closed notes; Computers and cell phones are not allowed
- Scientific calculators are allowed
- **Complete all 4 problems**
- Show all work and **place a box around all your final answers**
- Write your name on all pages
- You may write on both sides of the pages



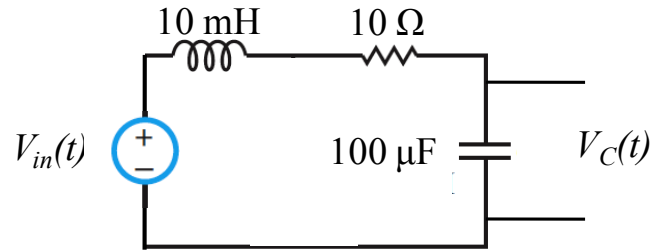Question 1 (32 Points)

Name:

1A) Consider the circuit below, give Z_c , Z_L , and $V_c(t)$ for



i) $V_{in}(t) = 1\text{V}$ (3 points)

$Z_c =$	$Z_L =$	$V_c(t) =$
---------	---------	------------

ii) $V_s(t) = 1 \cos(10^{10}t)$ V (3 points)

$Z_c =$	$Z_L =$	$V_c(t) =$
---------	---------	------------

iii) $V_s(t) = 1 \cos(10^3t)$ V (5 points)

$Z_c =$	$Z_L =$	$V_c(t) =$
---------	---------	------------

Question 1 (continued)


Name:

1B) Write the following phasor voltages in **complex exponential notation** and trigonometric form (4 points):


A) $V_1 = 2$, $f = 100$ Hz

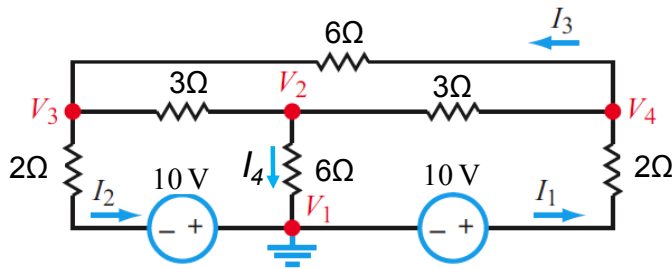B) $V_2 = -3e^{j55}$, $f = 200/\pi$ Hz


1C) Given that $I_4 = 0$ A, find V_1 , V_2 , V_3 , and V_4 and I_1 , I_2 , and I_3 in the circuit below: (6 Points)



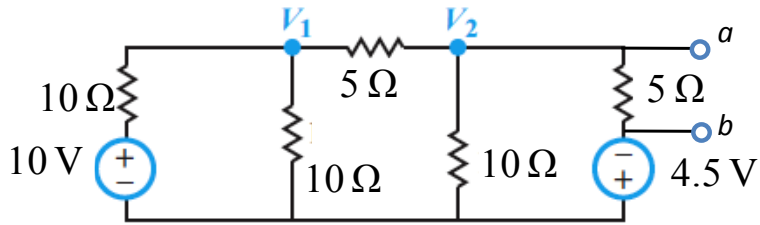1D) Find the **Thevenin Equivalent** circuit of the following circuit across terminals (a,b): **(8 points)**



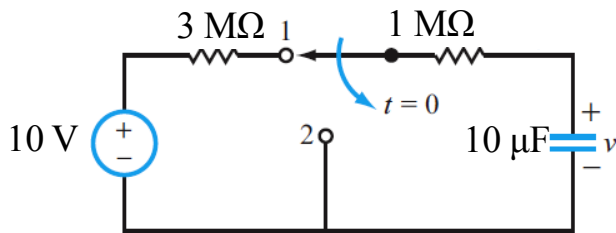1E) The switch in the figure below is at position 1 for a long time before it is thrown to position 2 at $t = 0$. Write an expression for i) V_c (voltage across the capacitor) at time $t=0^-$, and ii) $V_c(t)$ for $t>0$ **(4 points)**



Question 2 (22 Points)

Name:

2A) For the circuit below, find the equivalent phasor-domain quantities: (5 points)

$V_1 =$


$Z_{L1} =$

$Z_{L2} =$

$Z_C =$

$Z_{R1} =$

$Z_{R2} =$

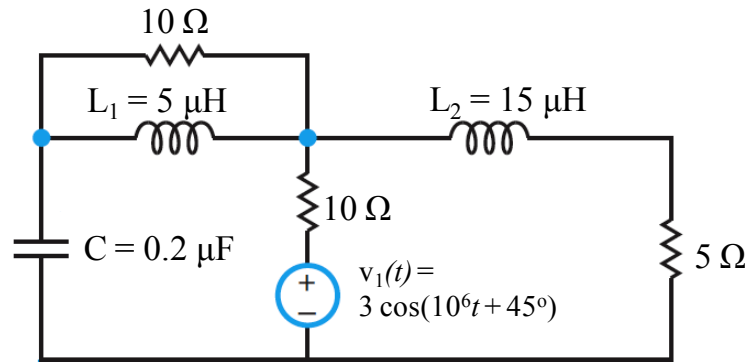

2B) For this circuit, apply the **Node-voltage method** in phasor domain to give two systems of equations and two unknowns node voltages **V1** and **V2**. Write these, simplify and put in **matrix form** below. Place a box around your final answer to make it easy for a grader to find. YOU DO NOT HAVE TO SOLVE V1 and V2. (8 Points)

Question 2 (continued)


Name:

- 2C) Now apply the **Mesh-current method** in phasor domain to give three systems of equations and three unknowns node voltages **I1, I2, and I3**. Write these, simplify and put in **matrix form** below. Place a box around your final answer to make it easy for a grader to find. YOU DO NOT HAVE TO SOLVE I1, I2 and I3. **(9 Points)**

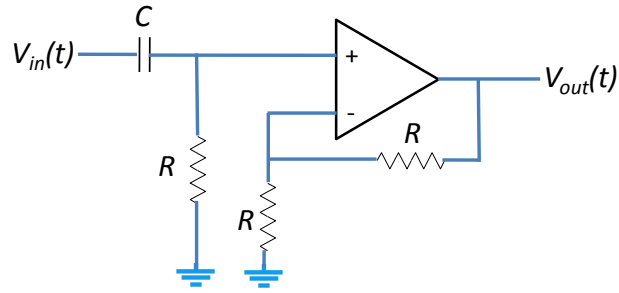Question 3 (22 Points)

Name:

- 3A)** Use the ideal op-amp approximation (phasor domain) to solve the phasor quantity V_{out} as a function of V_{in} as a function of R and C . **(10 points)**



- 3B)** What is the “in-band” gain of this circuit? What kind of filter is this? Justify your answer based directly on output expression in 3A, i.e. you should not require any explicit calculations **(4 points)**

Question 3 (continued)

Name:

3C) Using the expression you obtained in part 3A), if $R = 10\text{k}\Omega$ and $C = 1\mu\text{F}$,

What is $V_{\text{out}}(t)$ if $V_{\text{in}}(t) = 2 \cos(1000t + \pi/3) = 2 \cos(10^6 t)$?

If you could not obtain any expression for part (a) explain in as much detail as you can how you would solve this problem in order to get partial credit. **(8 points)**

Question 4 (24 Points)

Name:

(4A) Sketch the signal given by the following expression: $x(t) = 1u(t+2) - 2u(t) + 2u(t-3) - 1u(t-5)$. Be sure to label your sketch clearly for full credit. **(5 points)**

(4B) An analog-to-digital converter (also called ADC or A/D) uses a sampling rate of $F_s = 3000$ samples/second. An audio signal is recorded by a microphone to produce the electrical signal $x(t) = 0.5 \sin(2000\pi t + \pi/3) + 1.5 \cos(4500\pi t - \pi/6)$ volts and is then sampled by this ADC and stored on a computer.

(B-i) What is the resulting discrete time (DT) sinusoid? The frequencies of the DT sinusoid should be converted to the lowest equivalent frequency. **(6 points)**

(B-ii) If this DT sinusoid is played through speakers connected to a computer using the same sampling rate F_s to reconstruct the signal, what frequencies (itches) will be heard in the sound? **(3 points)**

(B-iii) Do these frequencies match those in the original signal? Why or why not? **(3 points)**

Question 4 (continued)

Name:

- (4C)** The ADC has a dynamic range of -1 to 1 volts and quantizes numbers to 14-bit accuracy (bit-depth).
- (C-i)** What is the amplitude resolution of this ADC in volts (that is, what is the equivalent in volts to a difference of one quantization level in the quantized signal)? **(3 points)**
- (C-ii)** Based on your answer to (C-i), for the first component of $x(t)$ (i.e. $0.5 \sin(2000\pi t + \pi/3)$ volts), what is the maximum quantization error in volts for any given sample? **(2 points)**
- (C-iii)** For the second component of $x(t)$, (i.e. $1.5 \cos(4500\pi t - \pi/6)$ volts), what is the maximum quantization error in volts for any given sample? **(2 points)**