

April 19, 2015, Final Exam

Answers

$$1) \begin{bmatrix} 0.0018 & -0.0010 \\ -0.0310 & 0.0011 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 0.0060 \\ 0 \end{bmatrix} \Rightarrow V_o = V_B = -6.428 \text{ V}$$

$$2) v_o = -2 \text{ V}$$

$$3) \text{ a) } V_{th} = 24 \text{ V}, R_{th} = 8\Omega$$

$$\text{ b) } C_T = 40 \mu\text{F}$$

$$\text{ c) } v_C(t) = 24e^{-t/1.8 \times 10^{-3}} \text{ V}$$

$$\text{ d) } v_C(4 \times 10^{-3} \text{ s}) = 2.6 \text{ V}$$

$$4) \text{ a) } i_o(t) = 0.2121 \cos(8000t + 45^\circ)$$

$$\text{ b) } P = \mathcal{R}e\left(\frac{1}{2} \underline{V} \underline{I}^*\right) = 0.225 \text{ W}$$

$$5) \text{ a) High-pass filter}$$

$$\text{ b) } R_1 = 100 \text{ k}\Omega, R_2 = 500 \text{ k}\Omega$$

$$\text{ c) } v_o(0.3) = 4.31 \text{ V}, v_o(1.0) = 10.6 \text{ V}, v_o(2.0) = 13.4 \text{ V}; v_o = 0 \text{ at all other frequencies.}$$

$$\text{Extra Credit: } \omega = 1/\sqrt{LC}$$