

EECE 2150 - Circuits and Signals: Biomedical Applications
Lab 9

Introduction to RC Circuits in the Time and Frequency Domains

Part 1. Transient Signals with an RC Circuit with Square Waves

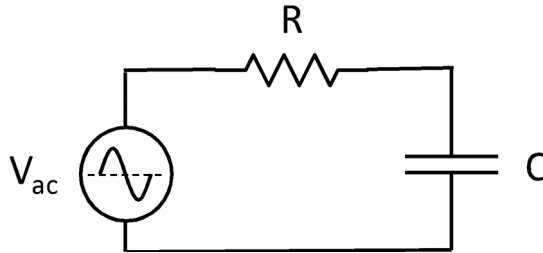


Figure 1. Simple RC circuit for Part 1.

1.1 Connect your function generator to a 20 k Ω resistor in series with a 0.1 μ F capacitor as in figure 1. Set your function generator to produce a 1 V amplitude square wave to charge and discharge the capacitor through the resistor.

1.2 What frequency should you use to observe the exponential decay behavior discussed in class? Hint: consider your **R and C** values, and the exponential **decay constant τ** . You will want at least 10-times this τ value between on-off cycles so that you can see the capacitor fully charge and discharge. Set up your function generator to produce this **square wave**.

1.3 Plot (by hand) the signal you expect to see on the oscilloscope. Use the oscilloscope to measure the voltage across the capacitor. Be sure to use the correct time-axis (horizontal control) to observe the decay effect, i.e. to “zoom” into the decay part of your square wave.

1.4 Calculate the time constant τ from your waveform. This is tricky – think about it. Recall that $V(t) = V_0 e^{-t/\tau}$. If you find a time and a voltage, you can calculate τ . Hint - the x and y cursors are useful for this measurement. **Q1:** What is τ , and is this consistent with what you expect from your circuit and what we discussed in class?

If needed you can change the frequency of your square wave.

Part 2. A Simple RC Circuit with Sine Waves

2.1 Use the same circuit and set your function generator to produce a 1 V amplitude sine wave with a frequency of 80 Hz. Verify that you have the correct signal by measuring it on your oscilloscope (using a BNC-BNC cable). Remember that the function generator will produce a center-to-peak amplitude of the set peak-to-peak amplitude, (**not** the peak-to-peak value) when driving a high-impedance load.

2.2 Measure the voltage across the capacitor using the other channel of the oscilloscope. Compare the sine waves at 80 Hz. **Prelab: Draw the signals you expect to see.** **Q2:** How do they compare in magnitude? **Q3:** How do they compare in phase (remember that the phase is an angle, in either radians or degrees, and that a whole cycle of the sine wave is 2π radians)? Work your way up in frequency from 80 Hz and record results for 100, 1000, and 10000 Hz. Then

work down to 10, 1, and 0.1 Hz. (Hint – be careful about using autoscale at the lowest frequencies – you may get unexpected results.) Record your results in a table. We will study phasor-domain analysis in the coming weeks that will allow us to explain these results. **Q4:** For now for now, what happens to the phase and amplitude as you go up in frequency? Down in frequency?

Part 3 - For the Write-Up.

As before, write a brief introduction and a brief conclusion describing, respectively, what the lab was about and what you learned. In between, just answer the questions in the document above.

IMPORTANT: BEFORE YOU LEAVE THE LAB:

- (a) Place all of the components that you removed from the red tool box back in that box and return it to the cabinet that houses them**
- (b) Collect all used components and wires from your bench and place them in your group's reusable plastic container. If you are not going to use these components or wires again please discard them in the trash bin located in your lab room.**
- (c) Turn off all of the equipment you have used on your workbench.**
- (d) Make sure you return your protoboard, the equipment wires and your reusable container to the front window.**
- (e) Make sure to have your notebook signed by an instructor or TA before you leave the lab.**

Department of Electrical Engineering, Northeastern University.

Last modified: N. McGruer, 2/16/16, 70 minutes; M.Niedre 8/10/15