

EECE 2150 - Circuits and Signals: Biomedical
Applications Fall 2018
Quiz 2

Prof. Charles A. DiMarzio

20 September 2018

Student Name: _____

Consider the circuit shown in the figure.


$$\begin{aligned}R_1 &= 10 \text{ kOhms} & R_2 &= R_1 \\R_3 &= 2 \text{ kOhms} & R_4 &= 5 \text{ kOhms} \\g &= 40 \mu\text{A/V} & V_s &= 10 \text{ V}\end{aligned}$$

1. Write two node equations for the unknown voltages V_1 and V_2 .

2. Simplify the equations.

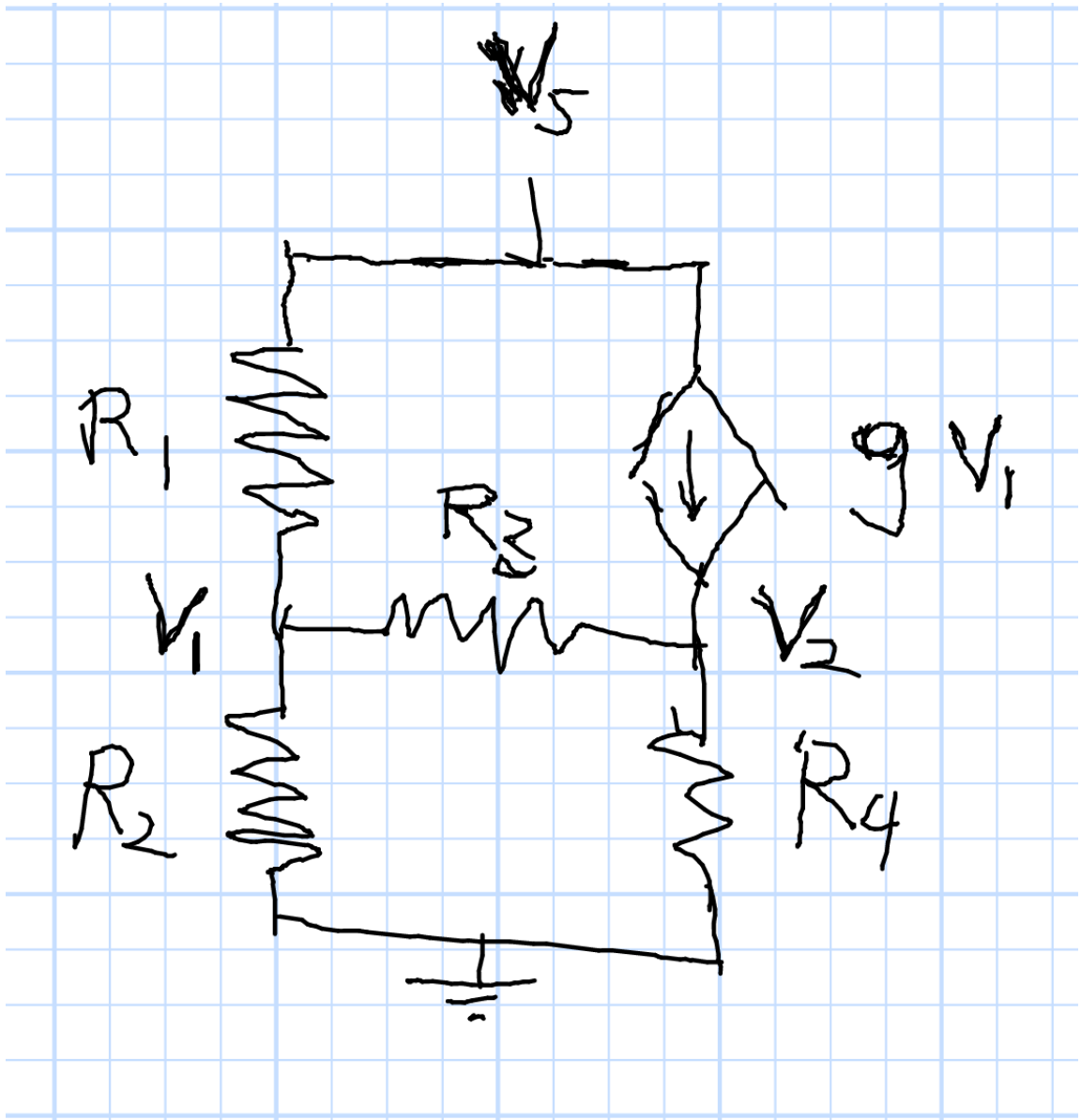3. Convert the equations to matrix form, $\mathcal{M}\mathbf{x} = \mathbf{y}$

You do not need to solve the matrix equation for \mathbf{x} .



1.

$$-\frac{V_s - V_1}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} = 0$$
$$-gV_1 + \frac{V_2}{R_4} + \frac{V_2 - V_1}{R_3} = 0.$$

2.

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)V_1 + \left(\frac{-1}{R_3}\right)V_2 = \frac{V_s}{R_1}$$
$$\left(-g - \frac{1}{R_3}\right)V_1 + \left(\frac{1}{R_4} + \frac{1}{R_3}\right)V_2 = 0.$$

3.

$$\begin{pmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) & \left(\frac{-1}{R_3}\right) \\ \left(-g - \frac{1}{R_3}\right) & \left(\frac{1}{R_4} + \frac{1}{R_3}\right) \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} \frac{V_s}{R_1} \\ 0 \end{pmatrix}$$

$$\begin{pmatrix} 0.7000 & -0.5000 \\ -0.5400 & 0.7000 \end{pmatrix} \times 10^{-3} \times \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 3.1818 \\ 2.4545 \end{pmatrix}$$

For your information, the solution is

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 3.1818 \\ 2.4545 \end{pmatrix}$$