

EECE 2150 - Circuits and Signals: Biomedical Applications Fall 2018, Quiz 8

Prof. Charles A. DiMarzio

8 November 2018

Student Name: _____

The top figures show the transfer function of some active filter.

1. Looking at the curves, how can you tell that it is an active filter?

2. What is the “passband” gain as a voltage ratio (not dB)?

$A_v =$ _____

3. What is the cutoff frequency?

$f_c =$ _____ Hz


4. The time constant is determined by a parallel RC circuit.

$C = 2 \text{ nF}$. What is R ?


$R =$ _____ Ω

5. The remaining figures show input and output voltages as functions of time for this filter. Which of the figures are correct? It might help to put a dot on the transfer function at the right frequency.


A B C D

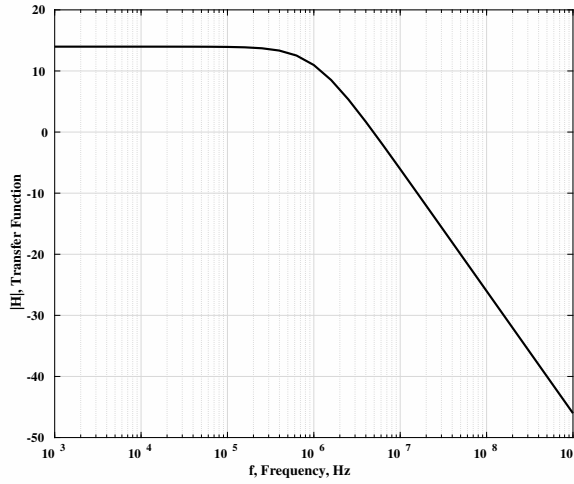


H Amplitude, dB

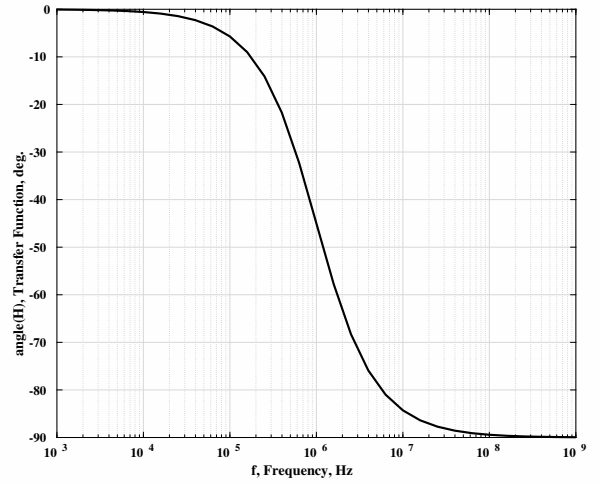


Phase, deg.

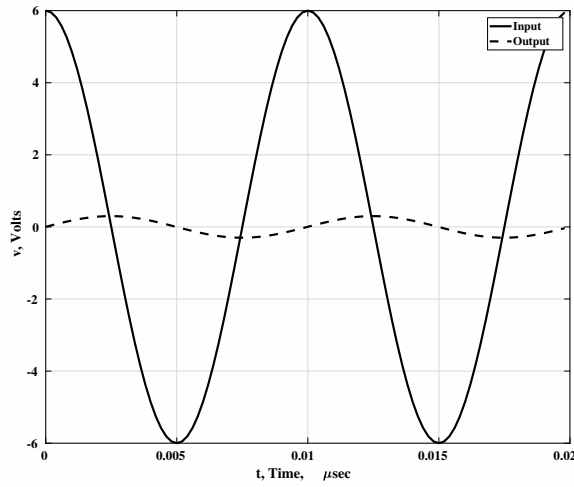


A

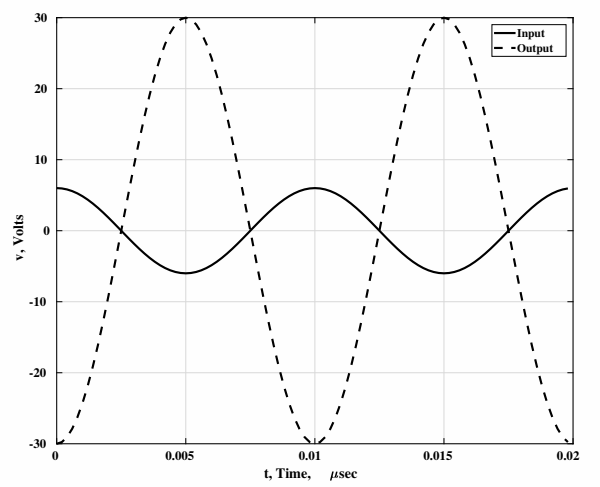

B

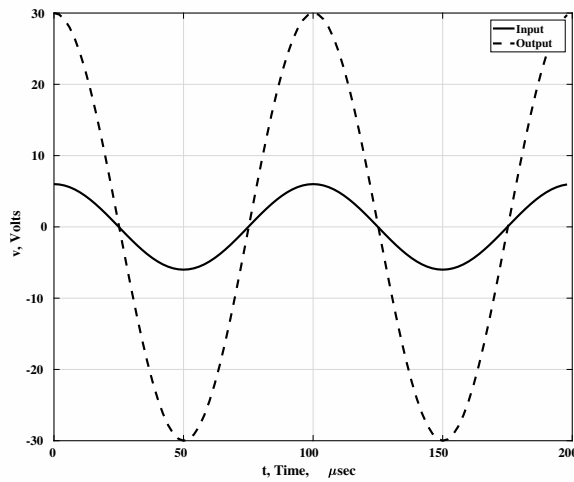


C

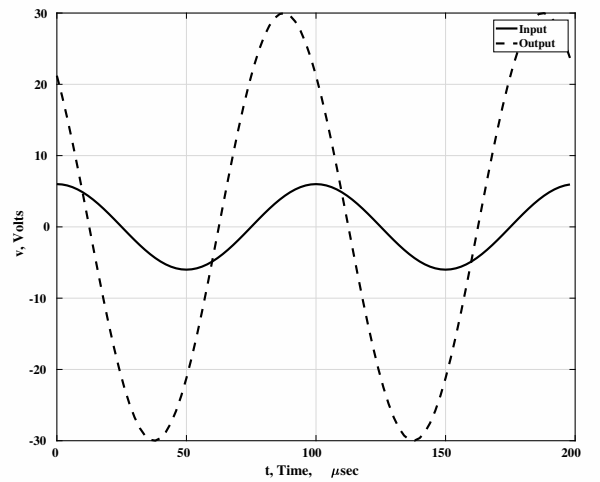

D

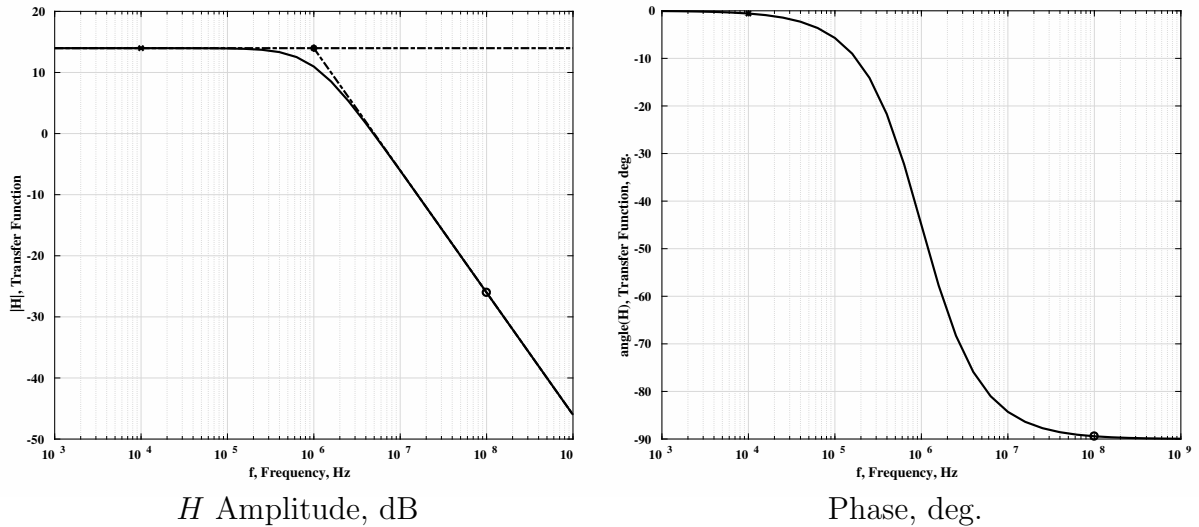1. The maximum gain is greater than one so it must be active.
2. The “passband” is low, all the way to DC, and the gain is 14 dB or a magnitude of 5. The phase is zero so the gain is plus 5.
3. Draw the 20dB/octave line and it intersects the low-frequency gain at $f_c = 10^6$ Hz.



4.

$$\tau = 1/\omega = \frac{1}{2\pi f_c}$$

$$RC = \frac{1}{2\pi f_c} = 0.16 \mu\text{s}$$

$$R = \tau/C = 79.5 \Omega$$

5.

- A (o on plots at 100 Mhz) is correct.
- B (same frequency) is wrong. The gain is the DC gain and the phase is wrong.
- C (x on plots at 10 kHz) is correct. The frequency is low so the output gain is about 5 and the phase is close to zero degrees.
- D (same frequenc) is wrong. The gain is right but there is a phase shift that is inconsistent with the zero phase at low frequencies.