

EECE 2150 - Circuits and Signals: Biomedical  
Applications Fall 2023  
Quiz 5

Prof. Charles A. DiMarzio

12 October 2023

Student Name: \_\_\_\_\_

The figure shows an amplifier circuit using an ideal op-amp, with the exception that the supply voltage rails are  $\pm 9\text{ V}$ . The resistors are  $R_1 = 2\text{ k}\Omega$  and  $R_2 = 30\text{ k}\Omega$ . The voltage source has  $R_s \approx 0\ \Omega$ .

1. What is the gain of the amplifier?

\_\_\_\_\_

2. If  $v_s = 0.3\text{ V}$ , what is the output voltage?

\_\_\_\_\_



3. If  $v_s = 0.3\text{ V} \times \cos 2\pi ft$  with  $f = 1000\text{ Hz}$ , write an equation for the output voltage.

\_\_\_\_\_

4. Now we change the input to  $v_s = 1\text{ V} \times \cos 2\pi ft$ , keeping the frequency the same. To view this signal on the oscilloscope, select the best time base of the following three for the horizontal setting.

$5\ \mu\text{sec/division}$      $500\ \mu\text{sec/division}$      $500\ \text{msec/division}$

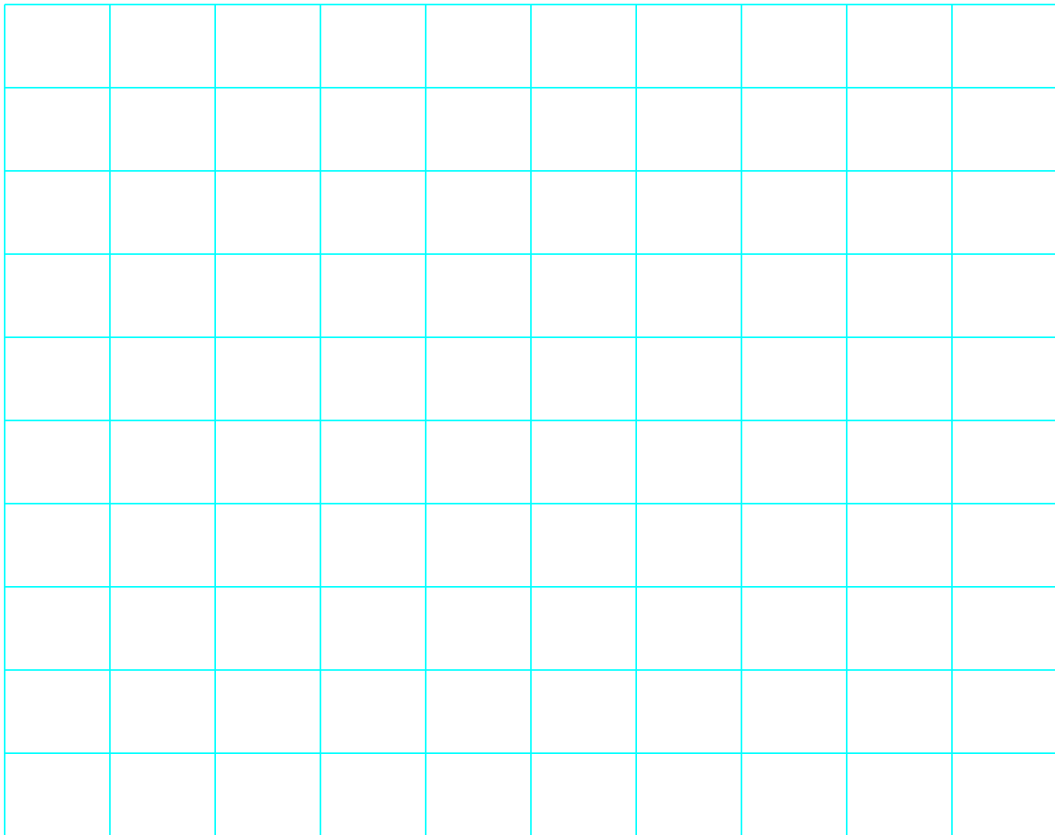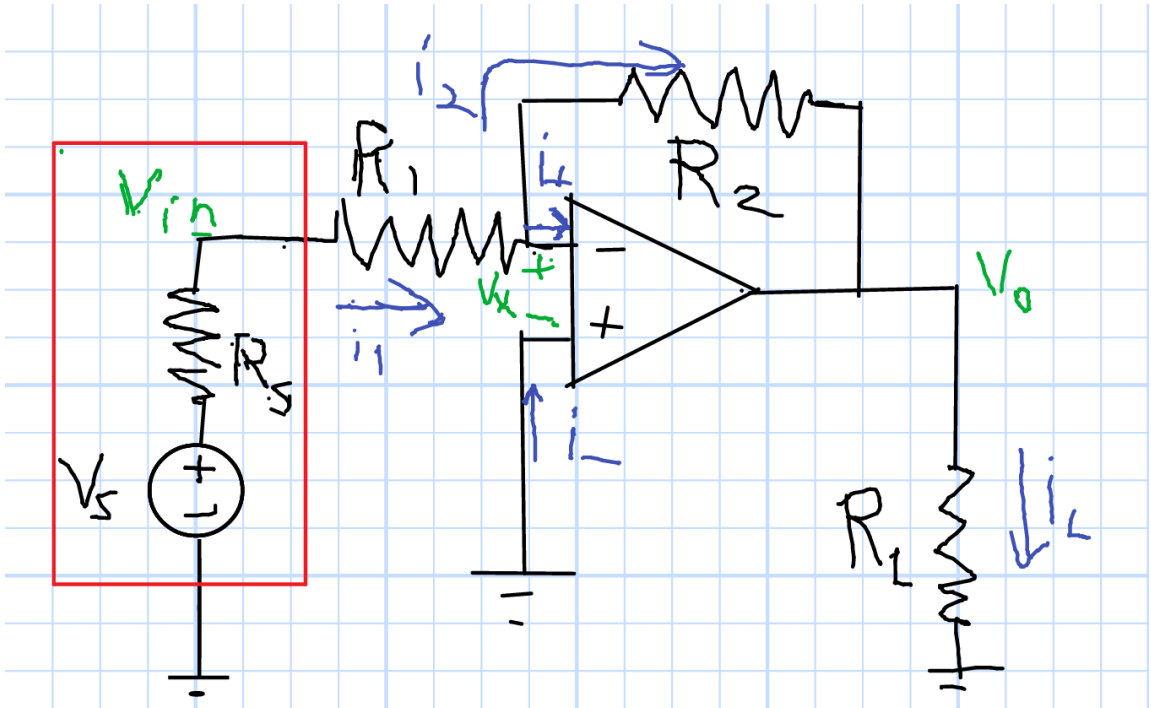5. We connect the input to Channel 1 of the oscilloscope with a setting of  $100\ \text{mV/division}$  and the output to Channel 2 at  $5\ \text{V/division}$ . Sketch what we would see on the oscilloscope.



# Solution

1.

$$-\frac{R_2}{R_1} = -15$$

2.

$$-15 \times v_s = -4.5 \text{ V}$$

3.

$$v_{out} = -4.5 \cos 2\pi ft.$$

4.  $500 \mu\text{sec/division}$ . This gives us 2 divisions per cycle.

5.

