

EECE 2150 - Circuits and Signals: Biomedical
Applications Fall 2022
Quiz 9

Prof. Charles A. DiMarzio

10 November 2022

Student Name: _____

In the figure, $R_1 = 2\text{ k}\Omega$ and $R_2 = 20\text{ k}\Omega$. We want to block power-line frequencies and we choose the cutoff frequency to be $f_c = 200\text{ Hz}$.

1. What type of filter is this?

Low Pass High Pass Band Pass Band Stop

2. What is the value of the capacitor?

$C =$ _____ .

3. What is the magnitude of the gain in dB at $f = 60\text{ Hz}$?


$H(60) =$ _____ .

4. What is the magnitude of the gain in dB at $f = 1\text{ kHz}$?

$H(1000) =$ _____ .

5. What is the magnitude of the gain in dB at very high frequencies?

$H(\infty) =$ _____ .

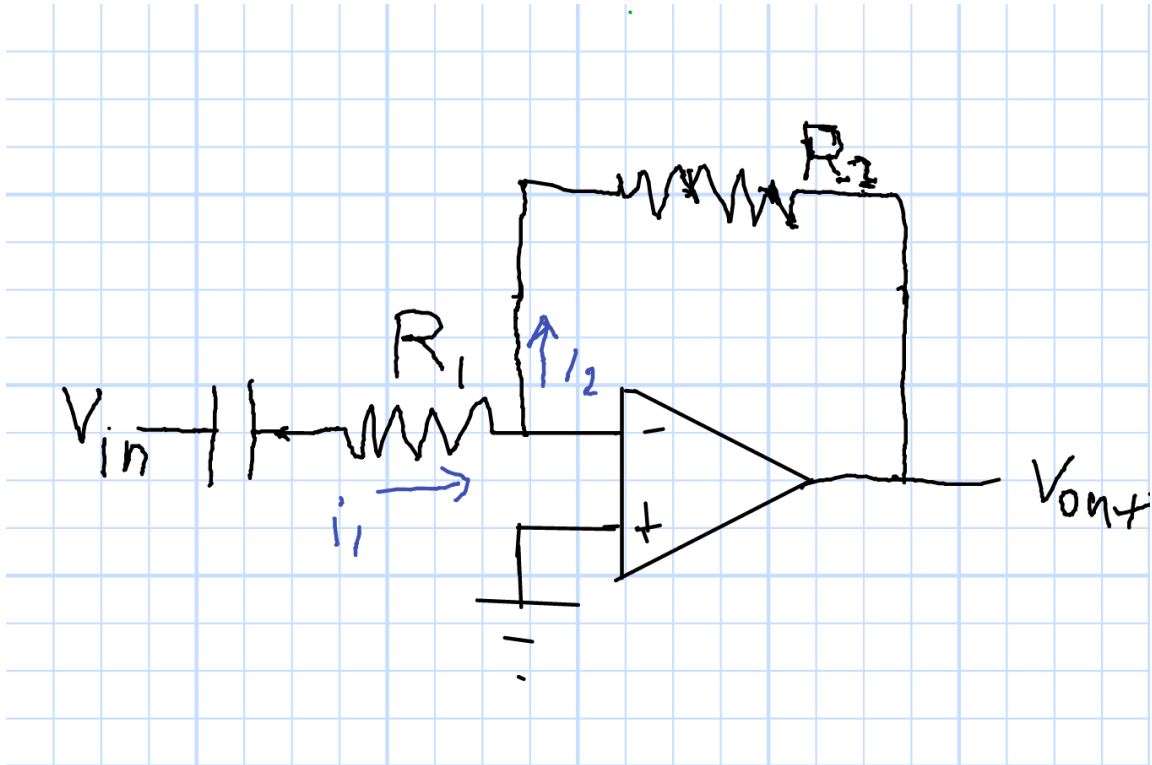

Solutions

1. What type of filter is this?

Low Pass High Pass Band Pass Band Stop

2. What is the value of the capacitor?

$$\omega_c = 2\pi f_c, R_1 C = \tau = 1/\omega_c, C = 400 \text{ nF}$$

3. What is the magnitude of the gain in dB at $f = 60 \text{ Hz}$?

$$Z_1 = \frac{1}{j2\pi fC} + R_1. H(60) = 20 \log_{10} |R_2/Z_1| = 9.2 \text{ dB}$$

4. What is the magnitude of the gain in dB at $f = 1 \text{ kHz}$?

$$H(1000) = 19.8 \text{ dB}$$

5. What is the magnitude of the gain in dB at very high frequencies?

$$H(\infty) = 20 \log_{10} |R_2/R_1| = 20.02 \text{ dB}$$