

Circuits and Signals: Biomedical Applications Week 3

Charles A. DiMarzio
EECE-2150
Northeastern University


Sep 2023

Week 3 Agenda

- Voltage Dividers
- Current Dividers
- Node Analysis
- Mesh Analysis
- Using the Oscilloscope

Voltage Divider

New Concept: Voltage Dividers

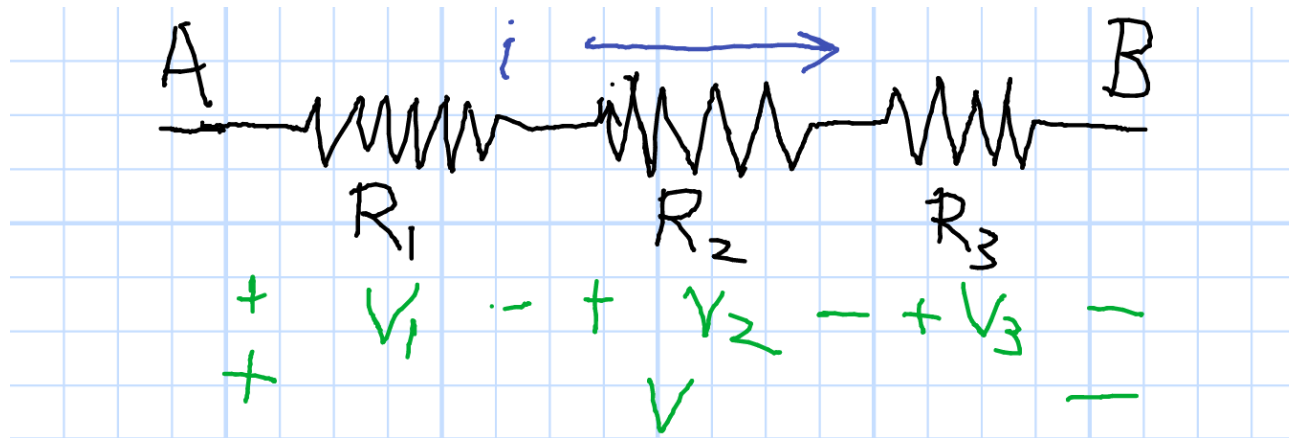


$$v_1 = iR_1 \quad v = iR = i(R_1 + R_2 + R_3)$$

$$v_1 = v \frac{R_1}{R_1 + R_2 + R_3}$$

- Using a Voltmeter
- Understanding Battery Failure

Current Divider

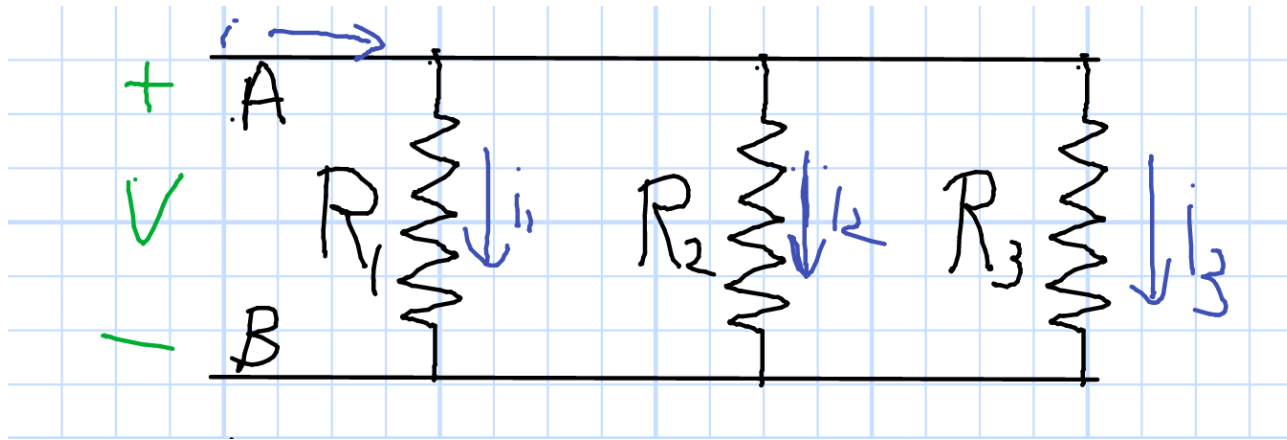

$$v = i_1 R_1 \quad v = iR = i \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$i_1 = i \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


$$i_1 = \frac{G_1}{G_1 + G_2 + G_3}$$

Solve the Circuit



Solve With $v_A = 12V$ $v_B = 0$ All $R_n = 50\Omega$

Solve the Circuit

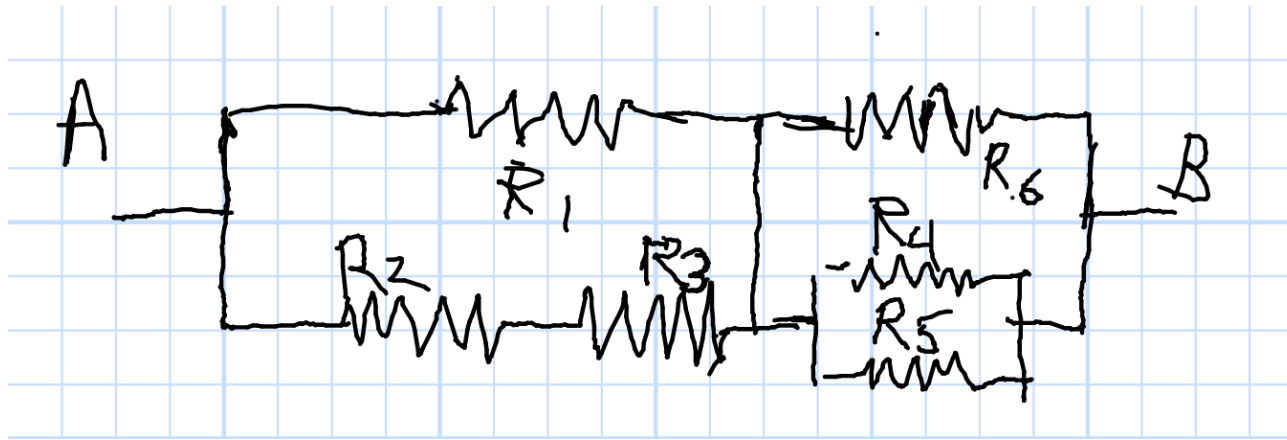


Solve With $v_A = 12V$ $v_B = 0$ All $R_n = 50\Omega$

$$R_1 \parallel (R_2 + R_3) = 33.3\Omega \quad R_6 \parallel R_4 \parallel R_5 = 16.7 \quad \rightarrow \quad R = 50\Omega$$


$$i = \frac{12V}{50\Omega} = 240\text{mA} \quad i_1 = 160\text{mA} \quad i_2 = 80\text{mA}$$

$$i_{4,5,6} = 80\text{mA} \quad v_{crossbar} = 80\text{mA} \times 50\Omega = 4V$$



Volume Control

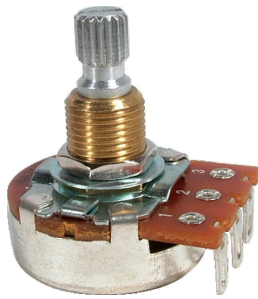

1

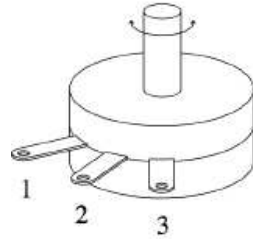


2

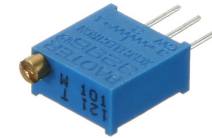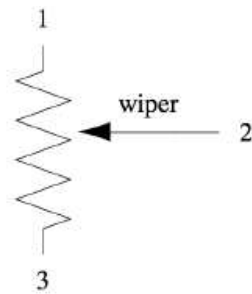

3

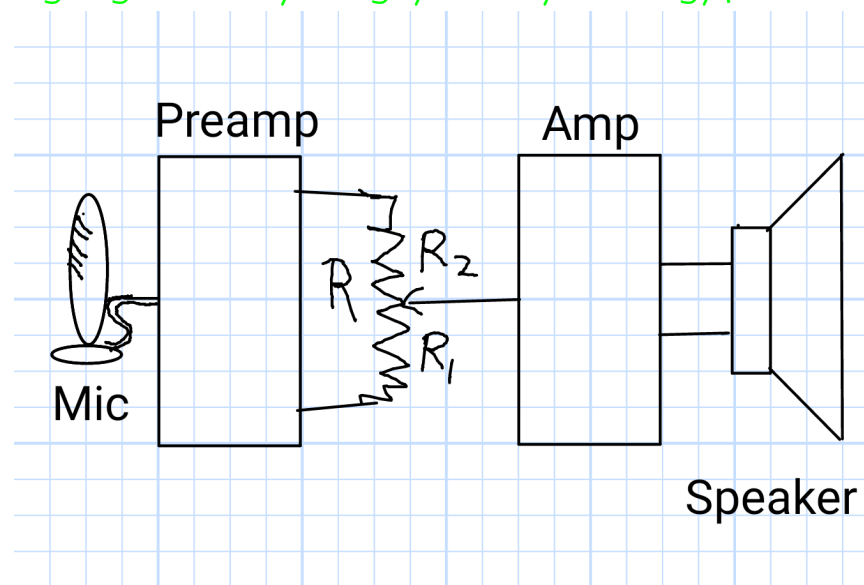1:


https://www.tubesandmore.com/sites/default/files/uc_products/
2: <http://hades.mech.northwestern.edu/images/3/3e/Sensor-potentiometer.png>
3: <https://www.bazaargadgets.com/image/cache/catalog/products/electronics/arduino/>



Would this make a good light dimmer switch?

Current Divider


What Happens if One Burns Out

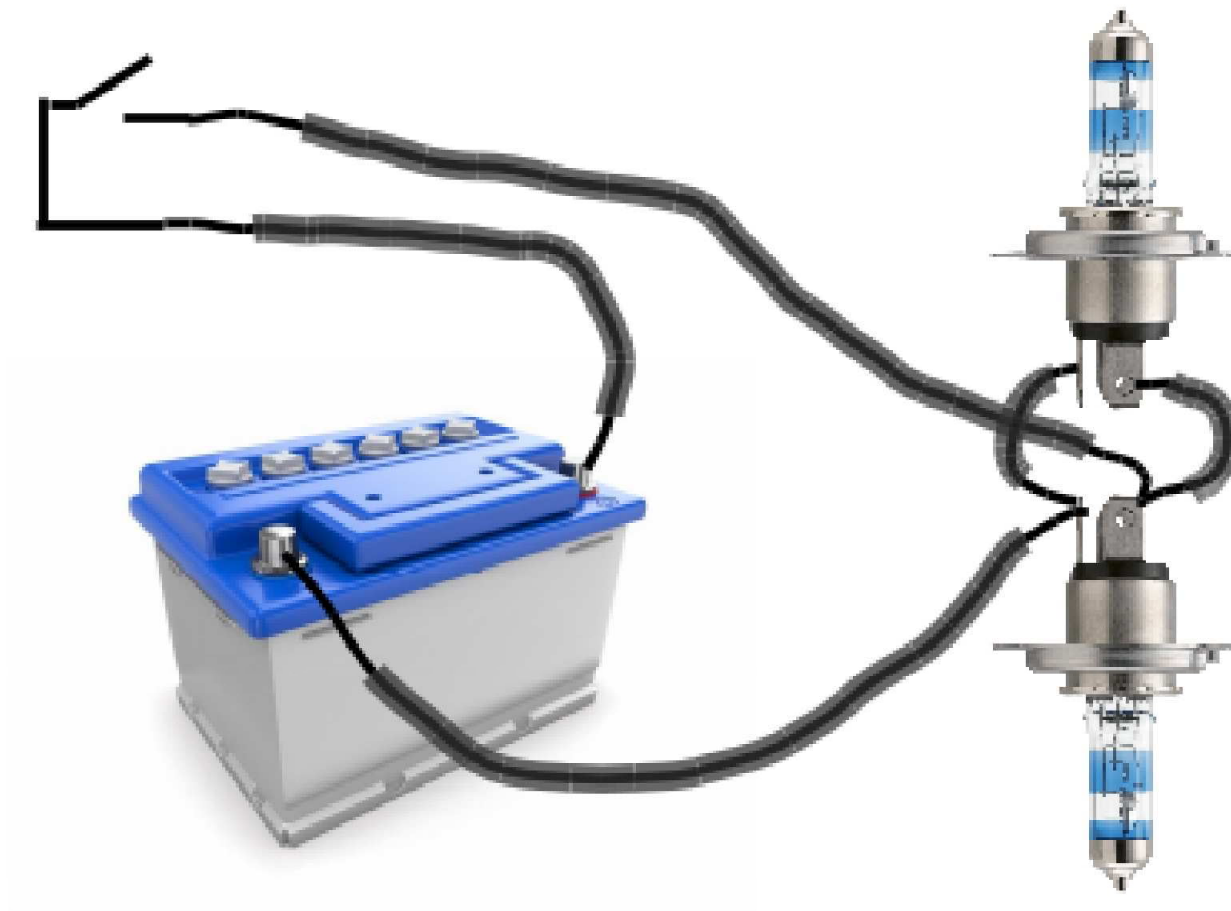

Current Divider

No Big Deal; $R_{1,2} \gg \sum R_w + R_s$

Otherwise Remaining Light Brightens

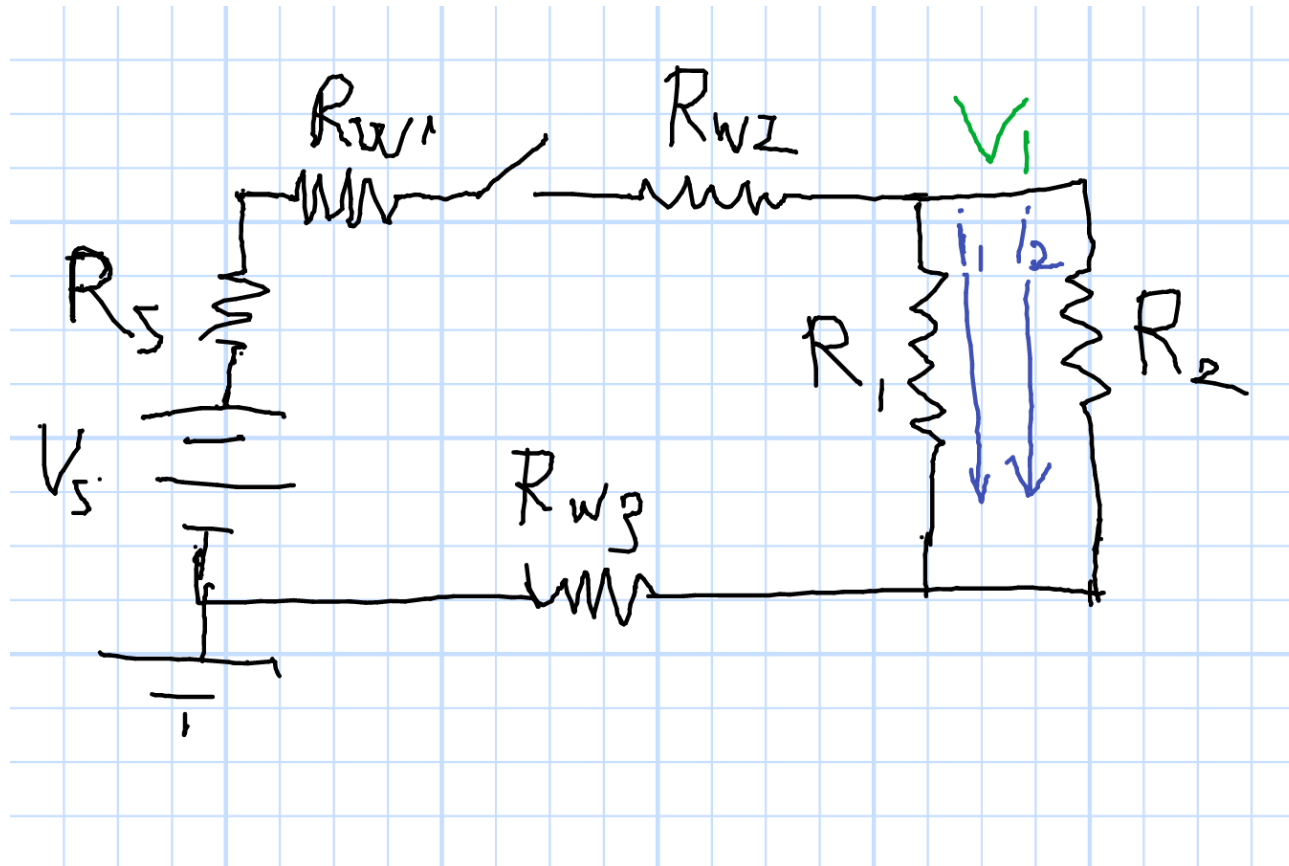


Node Analysis

- We've Learned a Bag of Tricks
 - Simple Circuits
 - Series and Parallel
 - Dividers
- What if None of them Works? Is there Something that Always Works?
 - Node Analysis (KCL and Ohm's Law)
 - Mesh Analysis (KVL and Ohm's Law)

Solve This Circuit
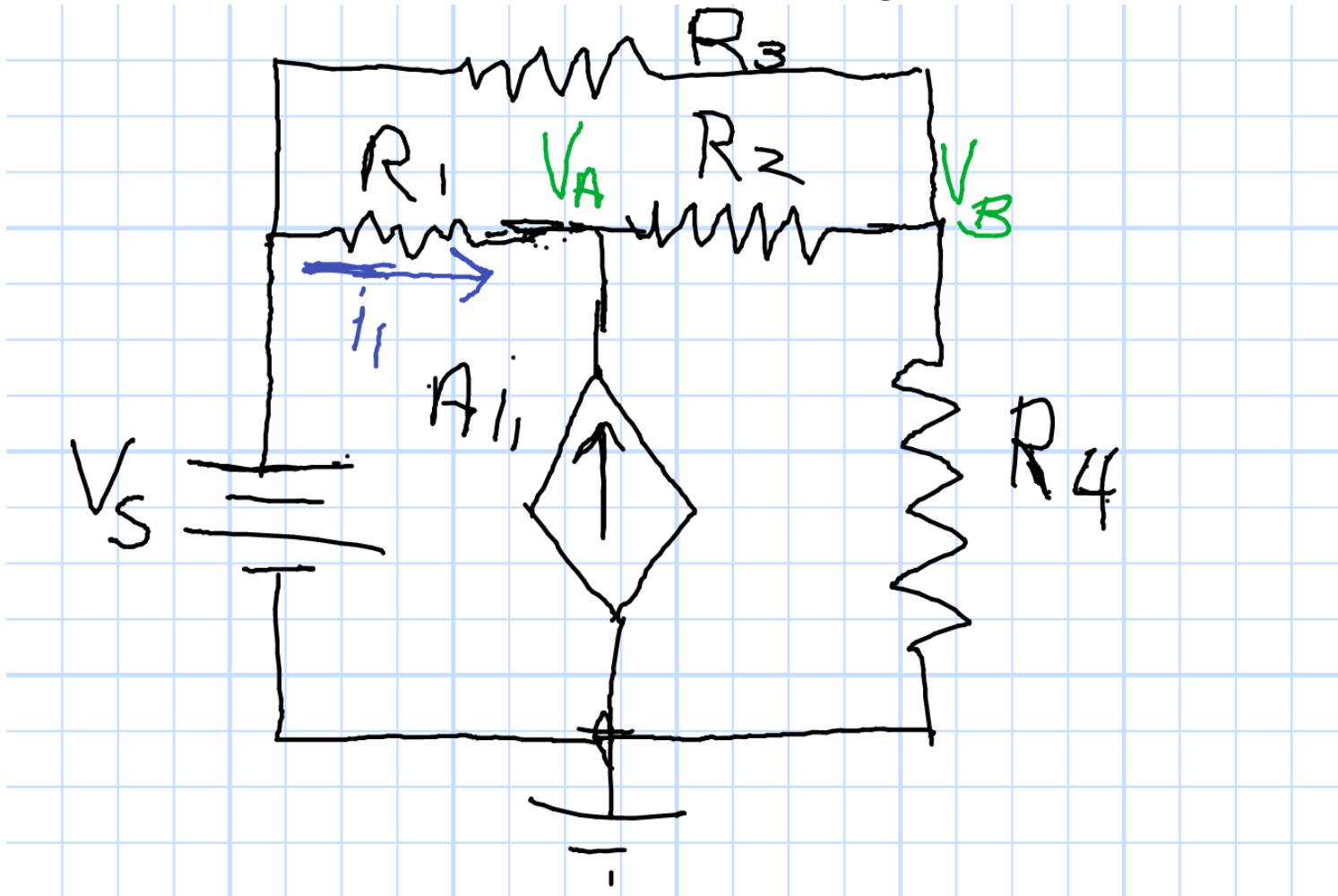
$$V_s = 12\text{V}, A = 3, R_1 = R_2 = 1\text{k}\Omega, R_3 = 5\text{k}\Omega, R_4 = 200\Omega$$



Approach to Solution

Matrix Equation with KCL at Each Node

$$\begin{pmatrix} m_{11} & m_{12} \\ m_{21} & m_{22} \end{pmatrix} \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} y_1 \\ y_2 \end{pmatrix}$$

$$\mathcal{M}\mathbf{x} = \mathbf{y}$$

Circuit Parameters \times Unknowns = Knowns

Solution

$$\mathbf{x} = \mathcal{M}^{-1}\mathbf{y}$$

Do you remember how to find the inverse of a matrix?

Approach to Solution

Matrix Equation with KCL at Each Node

$$\begin{pmatrix} m_{11} & m_{12} \\ m_{21} & m_{22} \end{pmatrix} \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} y_1 \\ y_2 \end{pmatrix}$$

$$\mathcal{M}\mathbf{x} = \mathbf{y}$$

Circuit Parameters \times Unknowns = Knowns

Solution

$$\mathbf{x} = \mathcal{M}^{-1}\mathbf{y}$$

Do you remember how to find the inverse of a matrix?

Use Matlab: `x = inv(M)*y`

KCL at Node A

Inbound Currents at A:

$$\frac{v_s - v_A}{R_1} + \frac{v_B - v_A}{R_2} + Ai_1 = 0$$

$$\frac{v_s - v_A}{R_1} + \frac{v_B - v_A}{R_2} + A \frac{v_s - v_A}{R_1} = 0$$

$$\frac{v_s}{R_1} - \frac{v_A}{R_1} + \frac{v_B}{R_2} - \frac{v_A}{R_2} + A \frac{v_s}{R_1} - A \frac{v_A}{R_1} = 0$$

Constants on the Right

$$-\frac{v_A}{R_1} - \frac{v_A}{R_2} - A \frac{v_A}{R_1} + \frac{v_B}{R_2} = -\frac{v_s}{R_1} - A \frac{v_s}{R_1}$$

$$\left[-\frac{1+A}{R_1} - \frac{1}{R_2} \right] v_A + \frac{1}{R_2} v_B = -\frac{1+A}{R_1} v_s$$


$$V_s = 12V$$

$$A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

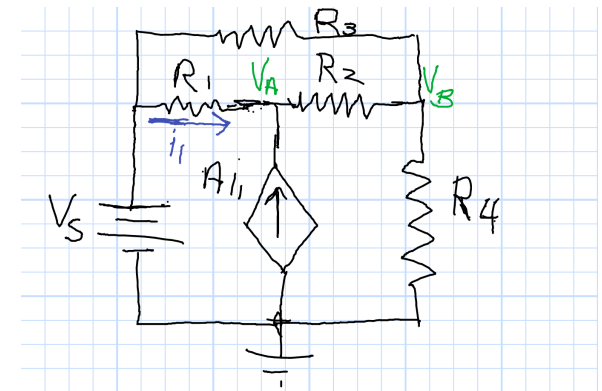

KCL at Node B

Inbound Currents at B:

$$\frac{v_s - v_B}{R_3} + \frac{v_A - v_B}{R_2} + \frac{0 - v_B}{R_4} = 0$$

$$\frac{v_s}{R_3} - \frac{v_B}{R_3} + \frac{v_A}{R_2} - \frac{v_B}{R_2} - \frac{v_B}{R_4} = 0$$

Constants on the Right

$$-\frac{v_B}{R_3} + \frac{v_A}{R_2} - \frac{v_B}{R_2} - \frac{v_B}{R_4} = -\frac{v_s}{R_3}$$

$$\frac{1}{R_2}v_A - \left[\frac{1}{R_3} - \frac{1}{R_2} - \frac{1}{R_4} \right]v_B = -\frac{v_s}{R_3}$$


$$V_s = 12V$$

$$A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

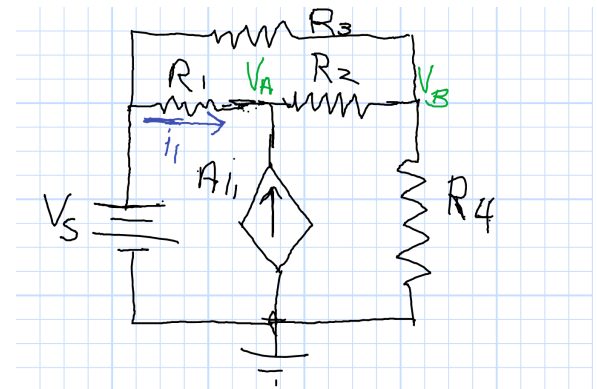

Solve

Inbound Currents at A:

$$\left[-\frac{1+A}{R_1} - \frac{1}{R_2} \right] v_A + \frac{1}{R_2} v_B = -\frac{1+A}{R_1} v_s$$

Inbound Currents at B:

$$\frac{1}{R_2} v_A - \left[\frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} \right] v_B = -\frac{v_s}{R_3}$$

Matrix Equation

$$\begin{pmatrix} \left[-\frac{1+A}{R_1} - \frac{1}{R_2} \right] & \frac{1}{R_2} \\ \frac{1}{R_2} & -\left[\frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} \right] \end{pmatrix} \times \dots$$
$$\dots \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} -\frac{1+A}{R_1} v_s \\ -\frac{v_s}{R_3} \end{pmatrix}$$


$$V_s = 12V$$

$$A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

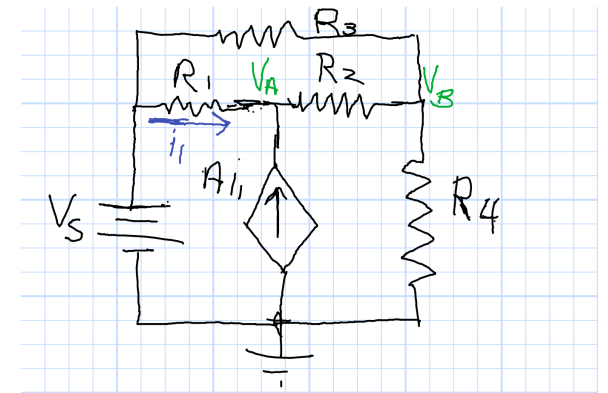

Result

$$\begin{pmatrix} \left[-\frac{1+A}{R_1} - \frac{1}{R_2} \right] & \frac{1}{R_2} \\ \frac{1}{R_2} & -\left[\frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} \right] \end{pmatrix} \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} -\frac{1+A}{R_1} v_s \\ -\frac{v_s}{R_3} \end{pmatrix}$$

From Matlab

$$\begin{pmatrix} -0.0050 & 0.0010 \\ 0.0010 & -0.0062 \end{pmatrix} \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \dots$$

$$\dots \begin{pmatrix} -0.0480 \\ -0.0024 \end{pmatrix}$$

$$\mathbf{y} = \mathcal{M}\mathbf{x} \quad \mathbf{x} = \mathcal{M}^{-1}\mathbf{y}$$


$$\mathbf{x} = \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} 10 \\ 2 \end{pmatrix} \text{Volts}$$

Check Units

$$V_s = 12\text{V} \quad A = 3$$


$$R_1 = R_2 = 1\text{k}\Omega$$
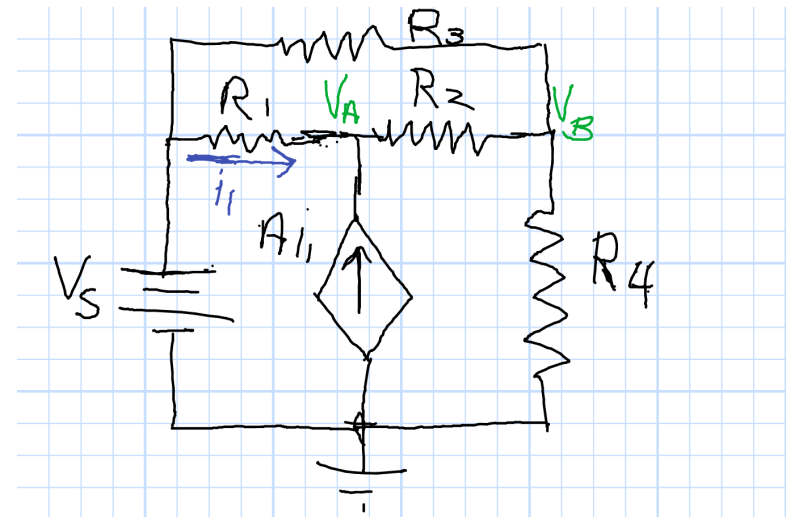
$$R_3 = 5\text{k}\Omega \quad R_4 = 200\Omega$$



Mesh Analysis

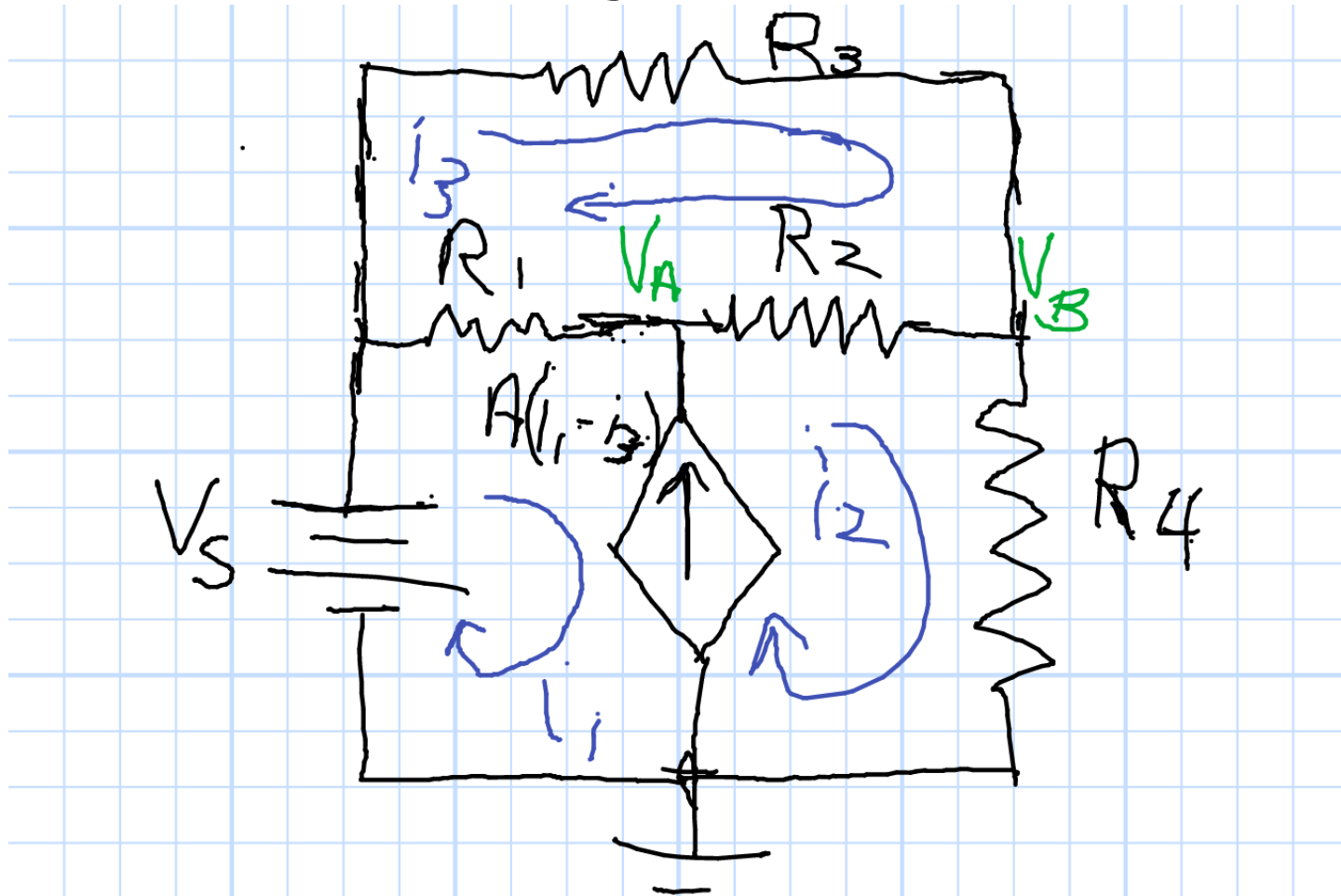Solve Circuits Using KVL Around All Loops




Remember Node Analysis

$$V_s = 12V \quad A = 3$$

$$R_1 = R_2 = 1k\Omega$$


$$R_3 = 5k\Omega \quad R_4 = 200\Omega$$

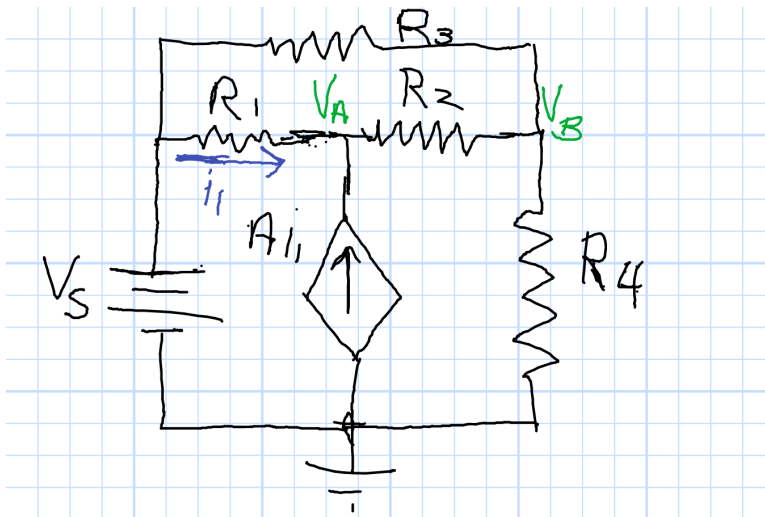

$$\mathbf{x} = \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} 10 \\ 2 \end{pmatrix} \text{Volts}$$

Mesh Analysis

Problem of Dependent Source

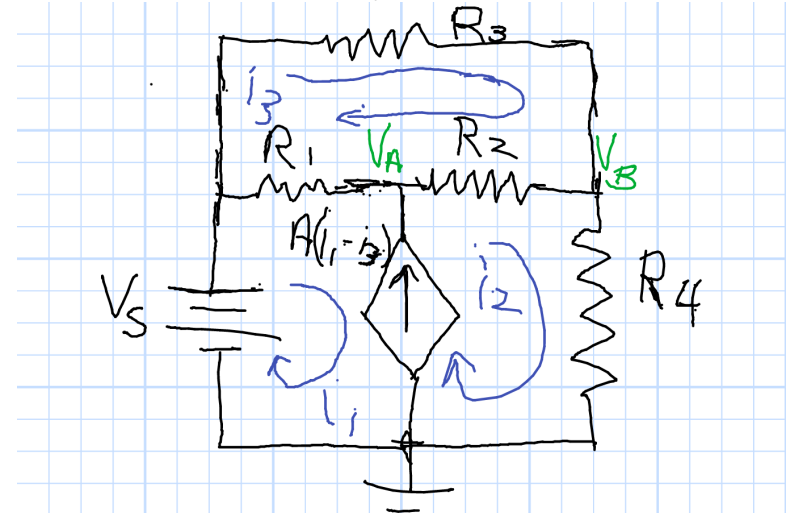

Superloop 1,2

$$v_s - i_1 R_1 + i_3 R_1 - i_2 R_2 + i_3 R_2 - i_2 R_4$$

$$= 0$$

Loop 3

$$i_3 R_3 + (i_3 - i_2) R_2 + (i_3 - i_1) R_1 = 0$$

Example of Mesh Analysis

Dependent Source

$$A(i_1 - i_3) = i_2 - i_1$$

$$(A + 1)i_1 - i_2 - Ai_3 = 0$$

Previous Page

$$v_s - i_1 R_1 + i_3 R_1 - i_2 R_2 + i_3 R_2 - i_2 R_4 = 0$$

$$i_3 R_3 + (i_3 - i_2) R_2 + (i_3 - i_1) R_1 = 0$$

Reorder

$$(A + 1)i_1 - i_2 - Ai_3 = 0$$

$$-R_1 i_1 - (R_2 + R_4) i_2 + (R_1 + R_2) i_3 = -v_s$$


$$-R_1 i_1 - R_2 i_2 + (R_1 + R_2 + R_3) i_3 = 0$$

$$V_s = 12V \quad A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

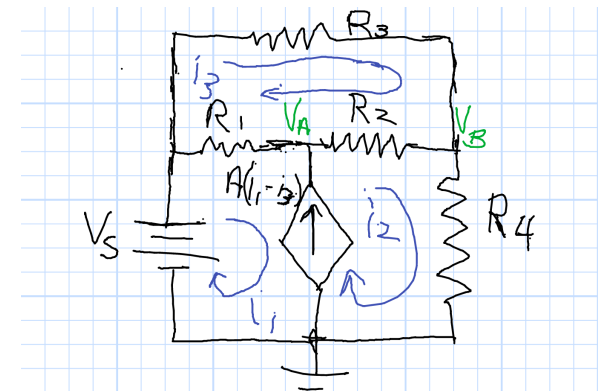

Mesh Analysis Solution

Previous Page

$$(A + 1)i_1 - i_2 - Ai_3 = 0$$

$$-R_1i_1 - (R_2 + R_4)i_2 + (R_1 + R_2)i_3 = -v_s$$

$$-R_1i_1 - R_2i_2 + (R_1 + R_2 + R_3)i_3 = 0$$


$$\mathcal{M} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 0 \\ -v_s \\ 0 \end{pmatrix}$$

$$V_s = 12V \quad A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

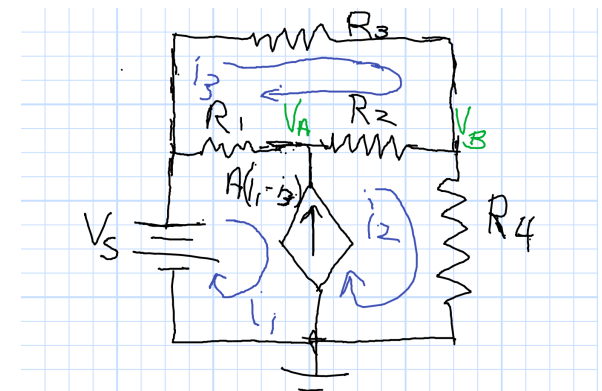

Matlab Mesh Results

```
>> vs=12;A=3;R1=1000;R2=R1;...
R3=5000;R4=200;y=[0;-vs;0];
>> M=[A+1,-1,-A;...
-R1,-(R2+R4),R1+R2;...
-R1,-R2,R1+R2+R3]
```

M =

	4	-1	-3
-1000	-1200	2000	
-1000	-1000	7000	

```
>> x=inv(M)*y
```

x =

0.0040
0.0100
0.0020

```
>> vBcheck=x(2)*R4
```


vBcheck = 2

$$V_s = 12V \quad A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

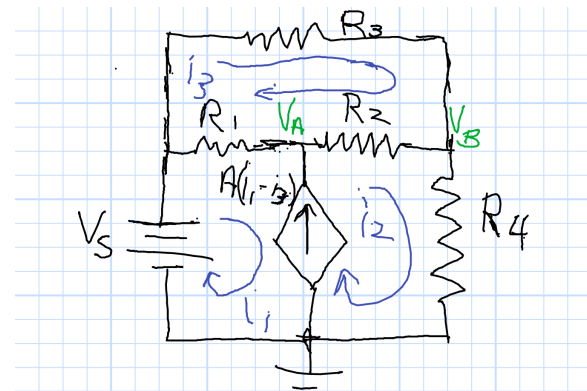


Node Solution

$$\begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} 10 \\ 2 \end{pmatrix} \text{Volts}$$

```
>> vAcheck=vBcheck+x(2)*R2-x(3)*R2
```


vAcheck = 10

Reading an Oscilloscope

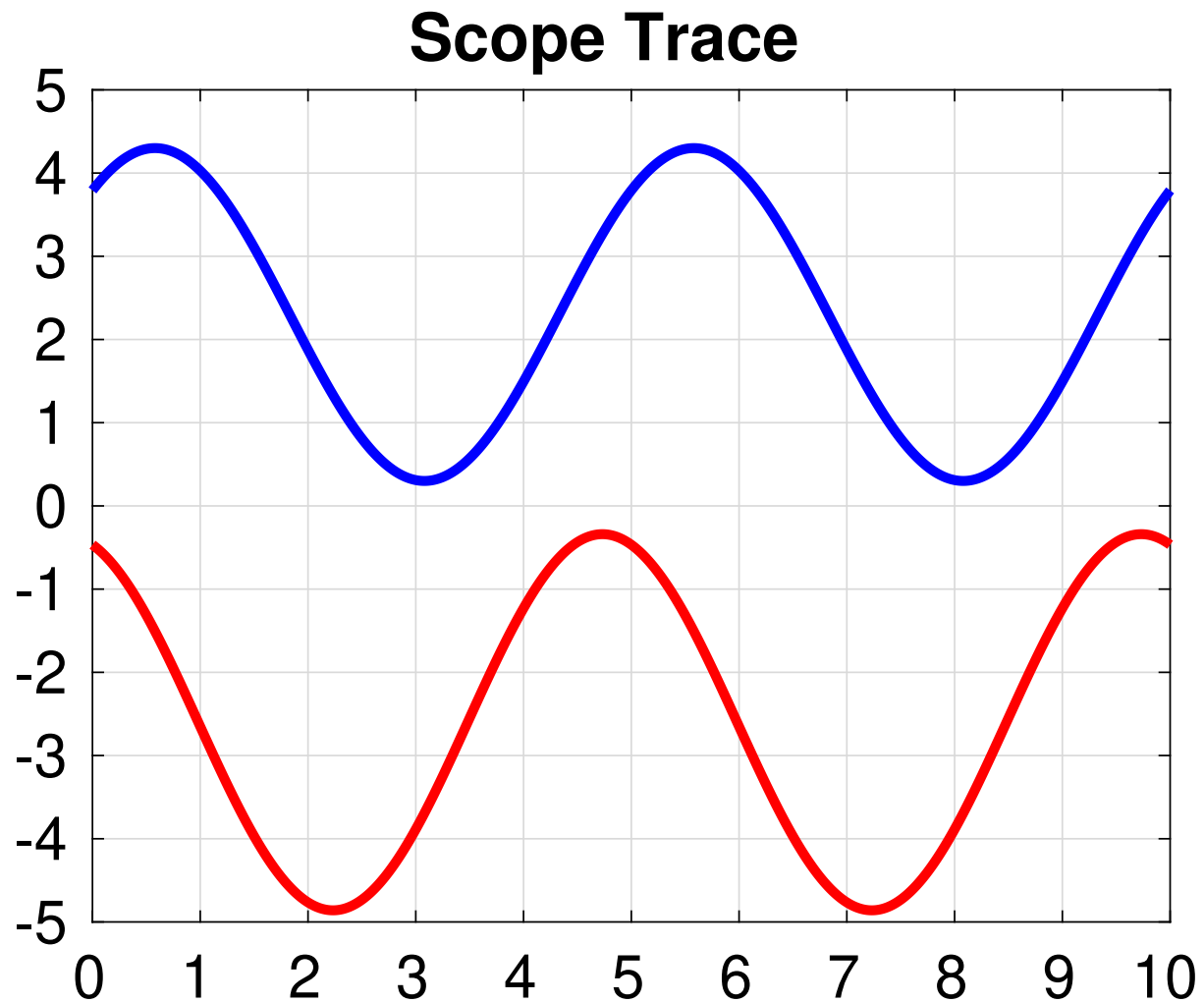


Ch1: V 10V/cm Ch2: V_B , 5V/cm Time base $20\mu\text{s}$

Untriggered Oscilloscope

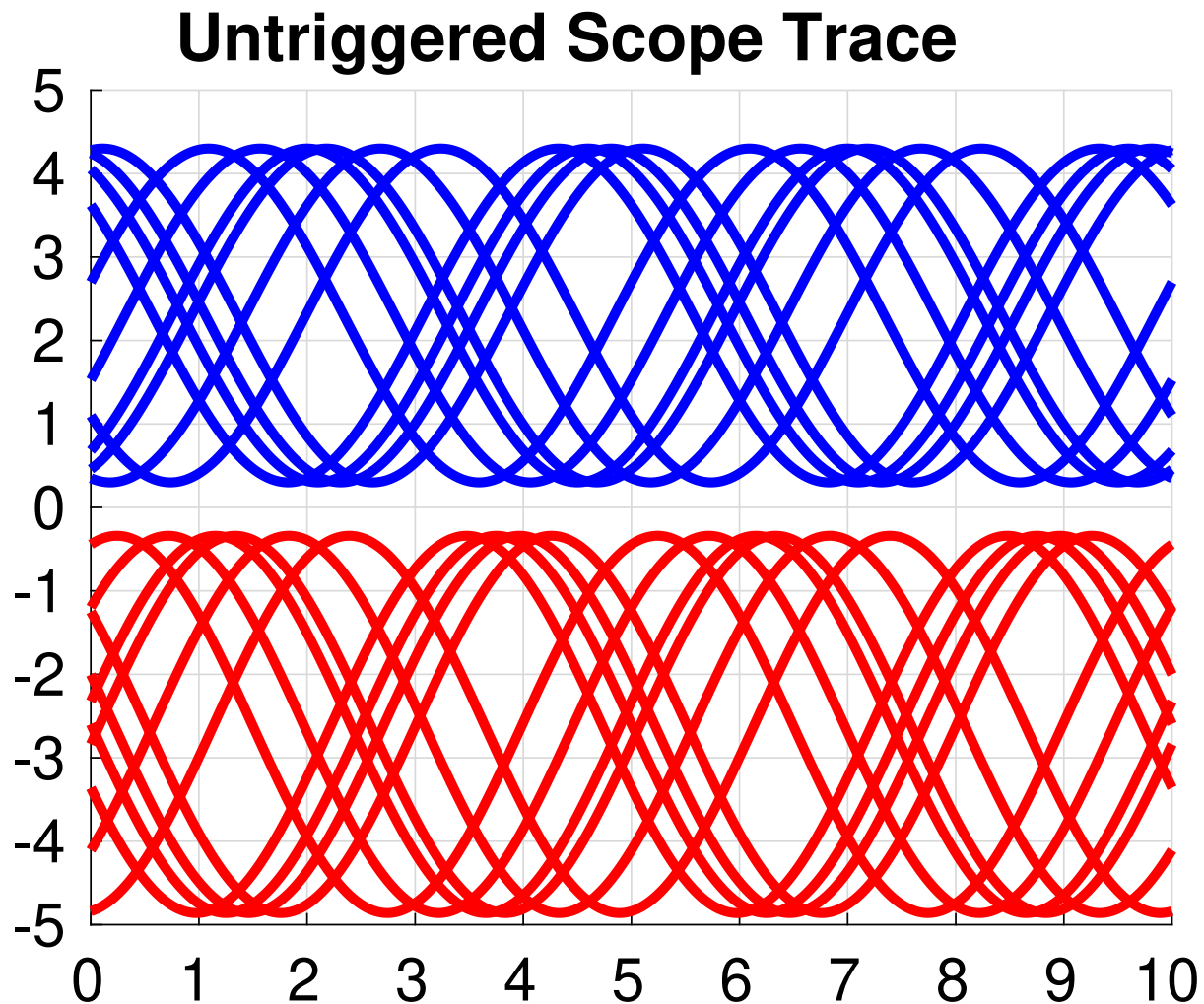


Ch1: V 10V/cm Ch2: V_B , 5V/cm Time base $20\mu\text{s}$
Trigger Mode: Auto

Channel-1 Trigger

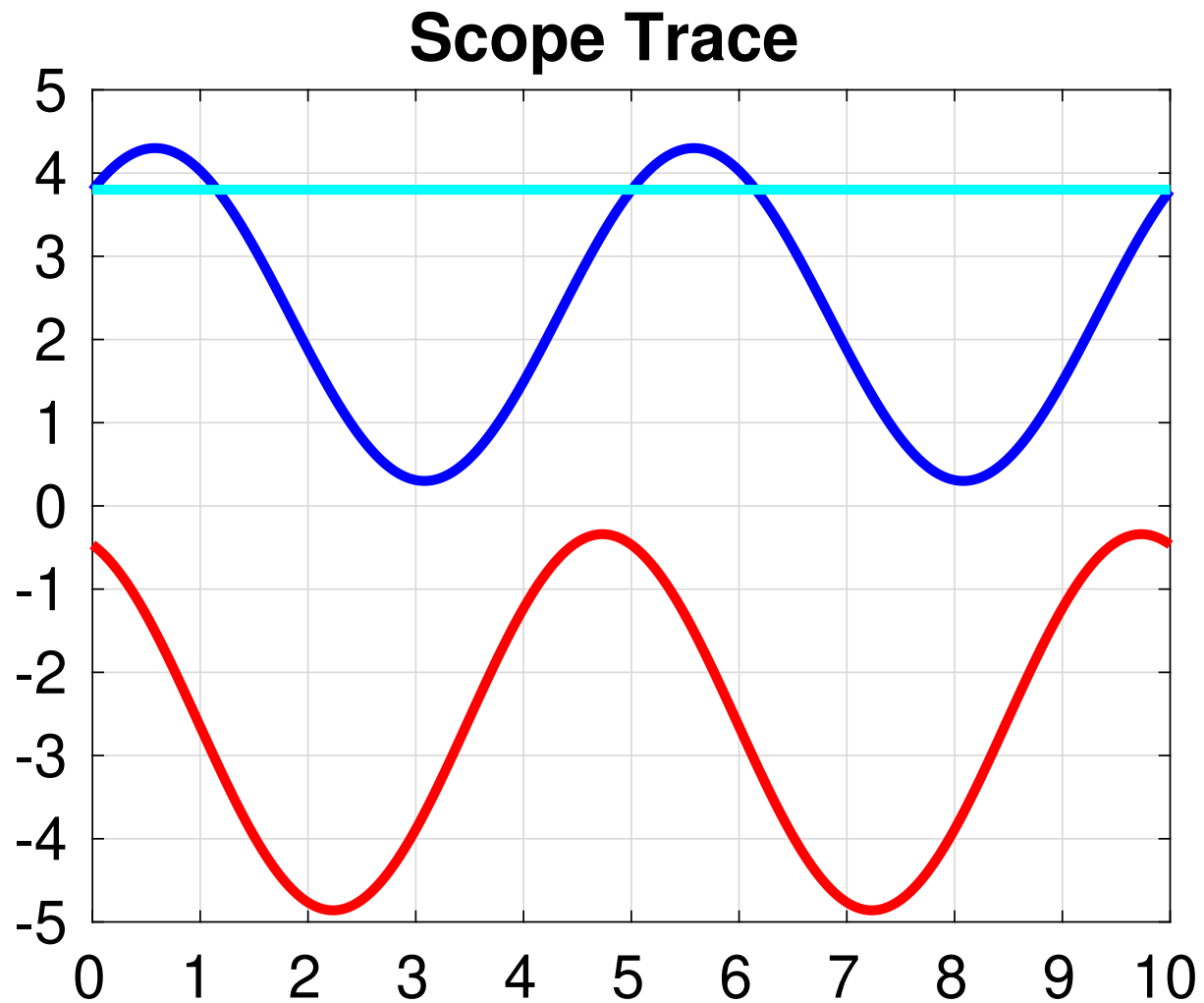


Ch1: V 10V/cm Ch2: V_B , 5V/cm Time base $20\mu\text{s}$
Trigger Ch1, 15V, +slope

Reading the Voltage

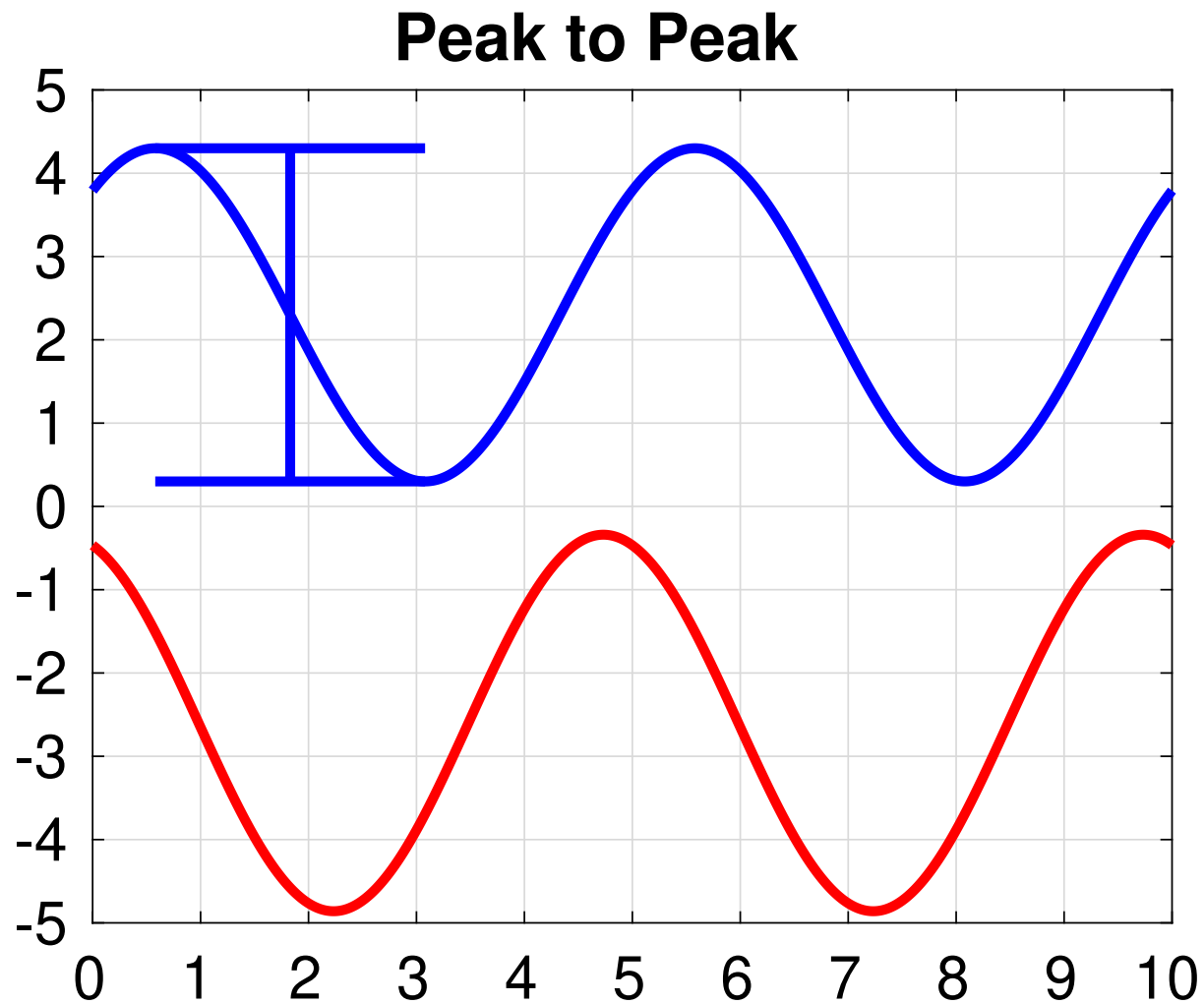


Ch1: V , $40V_{pp}/(10V/cm)$ Ch2: V_B , $22.6V_{pp}/(5V/cm)$

Reading the Period

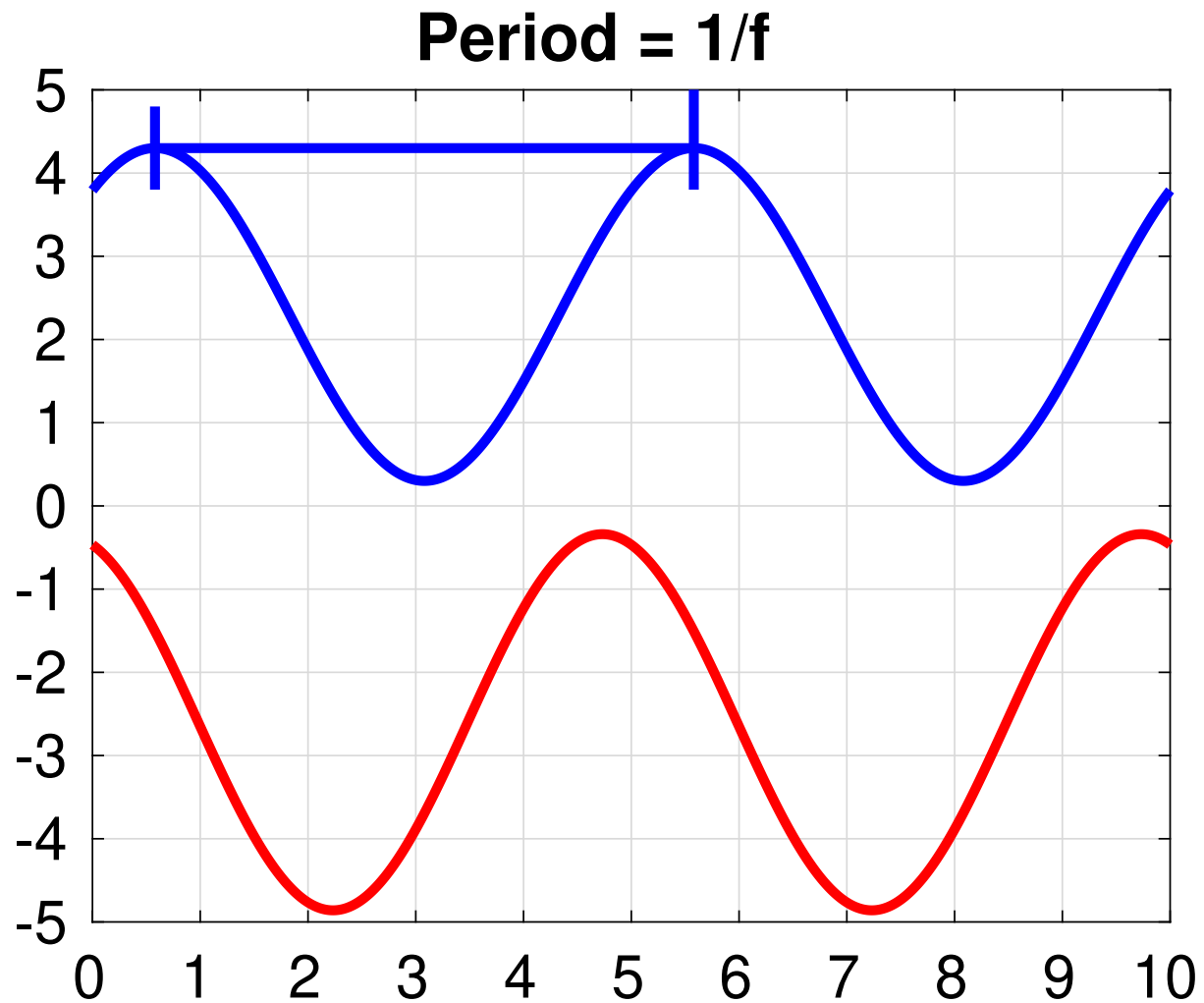

$$T = 1/f; 10\mu\text{s}/2\mu\text{s}/\text{cm}$$

Reading the Phase Difference

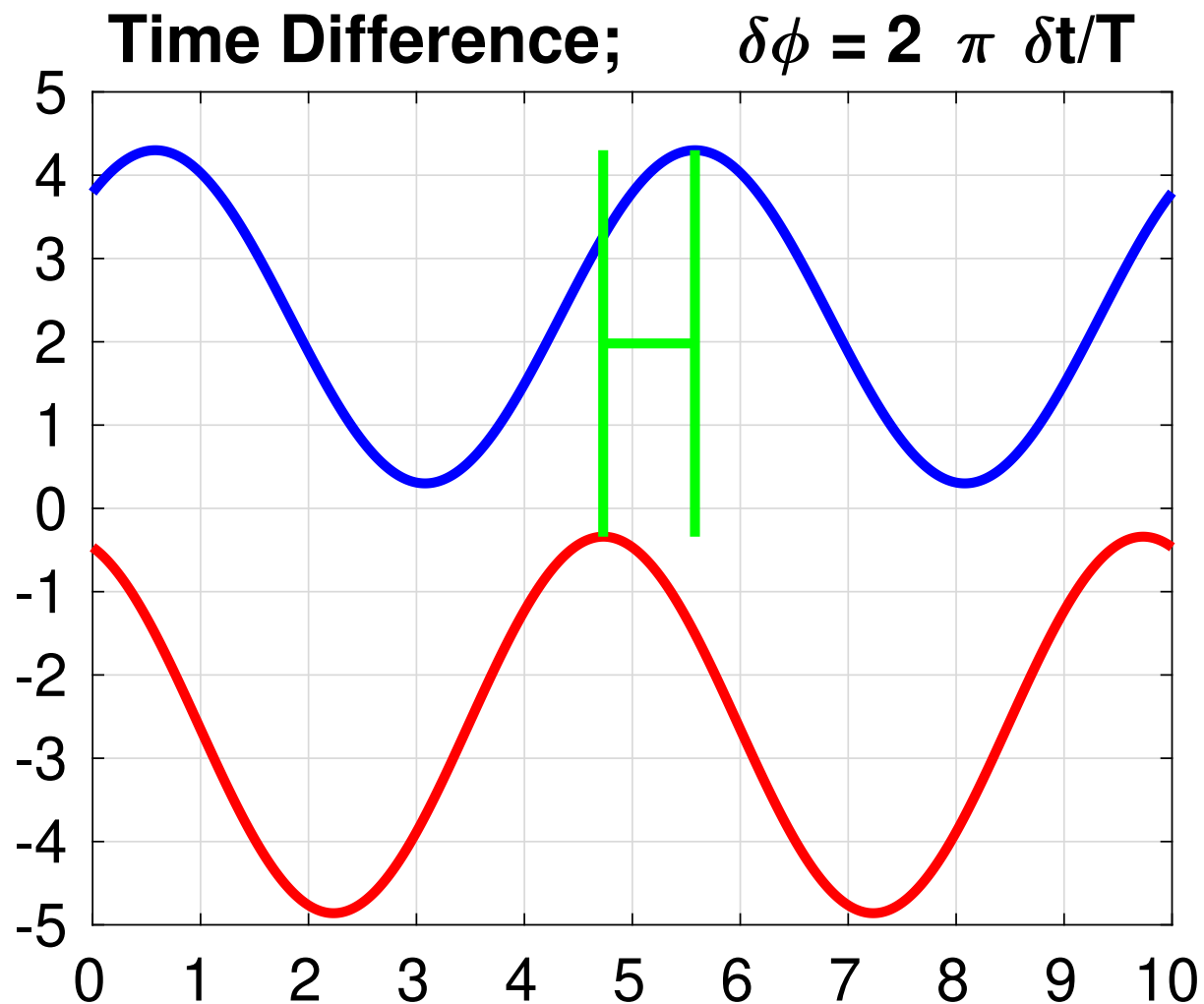

$$\delta t = T \frac{\delta\phi}{2\pi} = T \frac{\delta\phi}{360^\circ}; 1.7 \mu\text{s}/2 \mu\text{s}/\text{cm}$$

Trigger Ch1, 15V, +slope