

EECE 2150 - Electrical Engineering Fall 2021

Quiz 1

Prof. Charles A. DiMarzio

13 September 2021

Student Name: _____

On the next page is a circuit to power some light-emitting diodes, which was part of a laboratory experiment. When I did this experiment, I measured the resistors and found them both to be 480 Ohms and the voltages were;

R_1 and R_2	4.70	V
Yellow <i>LED</i> 1	1.99	V
Red <i>LED</i> 2	2.20	V
“9 Volt Source”	8.95	V


1. Is Kirchoff's Voltage Law closely satisfied? What is the voltage error?

2. The resistors were identified as having a 10% tolerance. Are they within tolerance?

3. What is the current through one of the resistors?

4. What is the power absorbed by each resistor?

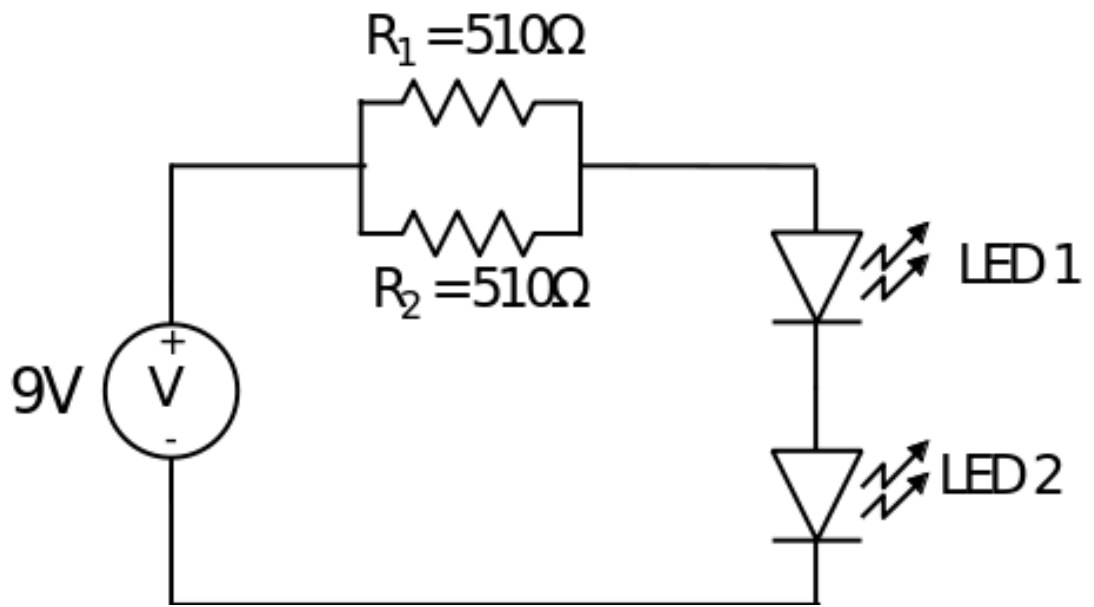5. If the resistors are rated to absorb 1/8 Watt without damage, how much margin of safety is there?



Solution

1. $4.7+1.99+2.20 = 8.89V$. Error is 0.06 V, which is small compared to all voltages in the circuit.

2. Yes. $480/510 = 0.94$ for a 6% error.

3. The current through one resistor is

$$I = \frac{V}{R} = \frac{4.70 \text{ V}}{480 \text{ Ohms}} = 0.0098 \text{ A}$$

so the current is 9.8 mA.

4. The power is $P = IV$ so for one resistor,

$$P = 4.70 \text{ V} \times 0.0098 \text{ A} = 0.046 \text{ W}$$

5. This power is $0.046/(1/8) = 0.37$ of the maximum allowed.