

EECE 2210 - Electrical Engineering

Quiz 11

Prof. Charles A. DiMarzio

22 November 2021

Student Name: _____

The figure shows an amplifier circuit with a feedback impedance that is a combination of a resistor and capacitor. In this circuit, $R_1 = 2\text{ k}\Omega$, $R_2 = 20\text{ k}\Omega$, $C = 100\text{ pF}$. The op-amp is assumed to be an ideal one.

1. If V_{in} is some DC voltage, what is the gain of the amplifier?

Gain = _____ .

2. If V_{in} is a very high-frequency AC voltage, what is the gain? Is this a low-pass or high-pass amplifier?

Gain = _____ . Low-Pass High-Pass

3. Write an equation for the gain as a function of frequency.


$A_V(f) =$ _____ .

4. At what frequency is the gain equal to the maximum (from part 1) divided by $\sqrt{2}$. In other words, what is the cutoff frequency?

Cutoff Frequency = _____ .

5. By what angle is the output voltage different from the input at the cutoff frequency?

Phase = _____ Degrees.

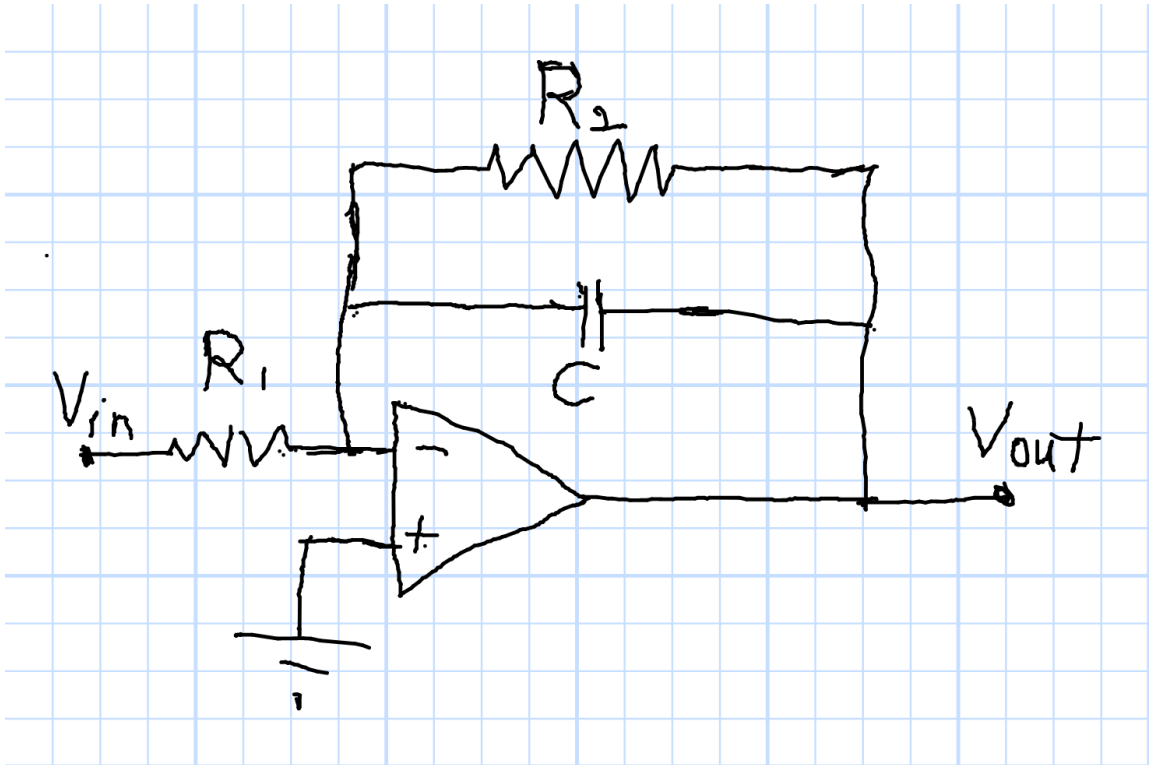

1. If V_{in} is some DC voltage, what is the gain of the amplifier?

$$\text{Gain} = -R_2/R_1 = -10$$

2. If V_{in} is a very high-frequency AC voltage, what is the gain? Is this a low-pass or high-pass amplifier?

$$\text{Gain} = -Z_2/R_1 = 0/R_1 = 0 \quad \text{X Low-Pass} \quad \square \text{ High-Pass}$$

3. Write an equation for the gain as a function of frequency.

$$A_V(f) = \frac{-\left(R_2 \parallel \frac{1}{j2\pi fC}\right)}{R_1}$$

4. At what frequency is the gain equal to the maximum (from part 1) divided by $\sqrt{2}$. In other words, what is the cutoff frequency? $R_2 = \left| \frac{1}{jC2\pi f} \right|$
 $= \frac{1}{2\pi R_2 C}$

$$\text{Cutoff Frequency} = 79.6 \text{ Hz.}$$

5. By what angle is the output voltage different from the input at the cutoff frequency?

$$A_V(f) = \frac{-\left(R_2 \parallel \frac{1}{j2\pi fC}\right)}{R_1} = \frac{-(R_2 \parallel -jR_2)}{R_1}$$

$$\text{Phase} = -45 \text{ Degrees}$$