

EECE 2210 - Electrical Engineering

Quiz 8

Prof. Charles A. DiMarzio

1 November 2021

Student Name: _____

The figure shows a circuit with resistors and capacitors. For this example, $C_1 = 10 \mu\text{F}$, $C_2 = 4.7 \mu\text{F}$, $C_3 = 2 \mu\text{F}$, and $C_4 = 100 \mu\text{F}$. The resistors are all $1 \text{ k}\Omega$.

a. Capacitors C_1 , C_2 , and C_3 can be treated as a single capacitor. What is the value of that single capacitor?

_____ .

b. The voltage source, V_S was turned off for a long time. Now it is turned on to 10 V . Again we wait a long time so that the circuit reaches steady state. What is V_A ?

_____ .

c. In the conditions of part b, what is V_B ?


_____ .

d. In the conditions of part b, what is the charge on C_4 ?

_____ .

e. In part d, how many electrons is that?

_____ .

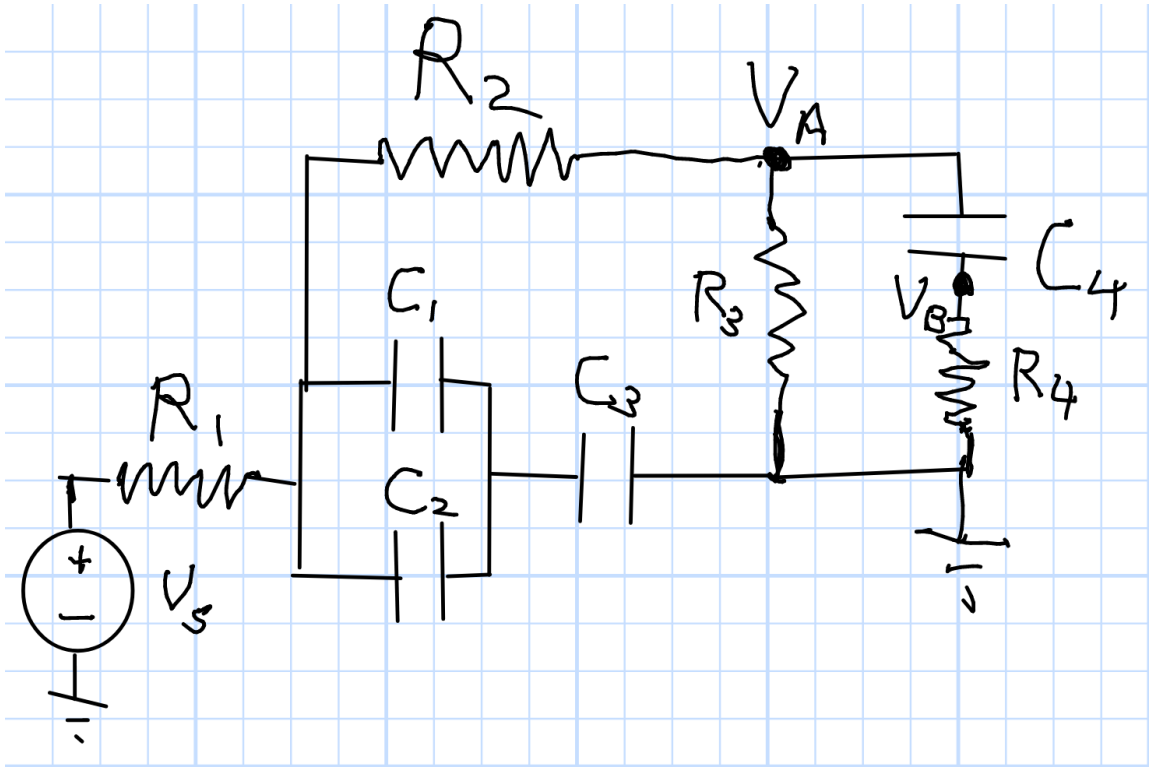

a. Capacitors C_1 , C_2 , and C_3 can be treated as a single capacitor. What is the value of that single capacitor?

$$C_{12} = C_1 + C_2, C_{123} = \frac{1}{\frac{1}{C_{12}} + \frac{1}{C_3}} = 1.76 \mu\text{F}.$$

b. The voltage source, V_S was turned off for a long time. Now it is turned on to 10 V. Again we wait a long time so that the circuit reaches steady state. What is V_A ?

$$V_A = V_S \frac{R_3}{R_1 + R_2 + R_3} = 3.33 \text{ V}$$

c. In the conditions of part b, what is V_B ?

No current in R_4 so $V_B = 0$.

d. In the conditions of part b, what is the charge on C_4 ?

$$Q = C(V_A - V_B) = 333 \mu\text{Coulombs}$$

e. In part d, how many electrons is that?

$$N = Q/e = 2.1 \times 10^{15}$$