

# EECE 2210 - Electrical Engineering

## Quiz 9

Prof. Charles A. DiMarzio

8 November 2021

Student Name: \_\_\_\_\_

The figure shows the de-bounce circuit for a switch as we discussed in class. In this case,  $V_s = 5$  Volts,  $R_1 = 20$  kOhms,  $R_2 = 40$  kOhms, and  $C = 1 \mu\text{F}$ . The switch is a normally-open pushbutton that “bounces” when it is pressed and/or released. The plot in the upper left shows when the switch is opened and closed. The indicated times are  $t_1 = 1$  ms and  $t_2 = 4$  ms.

1. What is the time constant for charging the capacitor when the switch is open?

\_\_\_\_\_ .

2. What is the time constant for discharging the capacitor when the switch is closed?


\_\_\_\_\_ .

3. Up until time  $t_1$  the switch has been changing in some unknown way, but just before  $t_1$ , the voltage on the capacitor is  $v(t_1^-) = 4.5$  Volts. What is the voltage on the capacitor at time  $t_2$ ??

\_\_\_\_\_ .

4. Now suppose instead that the voltage at  $t_1$  is  $v(t_1^-) = 5$  Volts, the maximum possible. I press the button from from  $t_1$  to  $t_2$ , without bouncing, and I want the voltage on the capacitor to fall to 1 Volt. The time  $t_2$  is not sufficient. What must  $t_2$  be for this to work?

\_\_\_\_\_ .

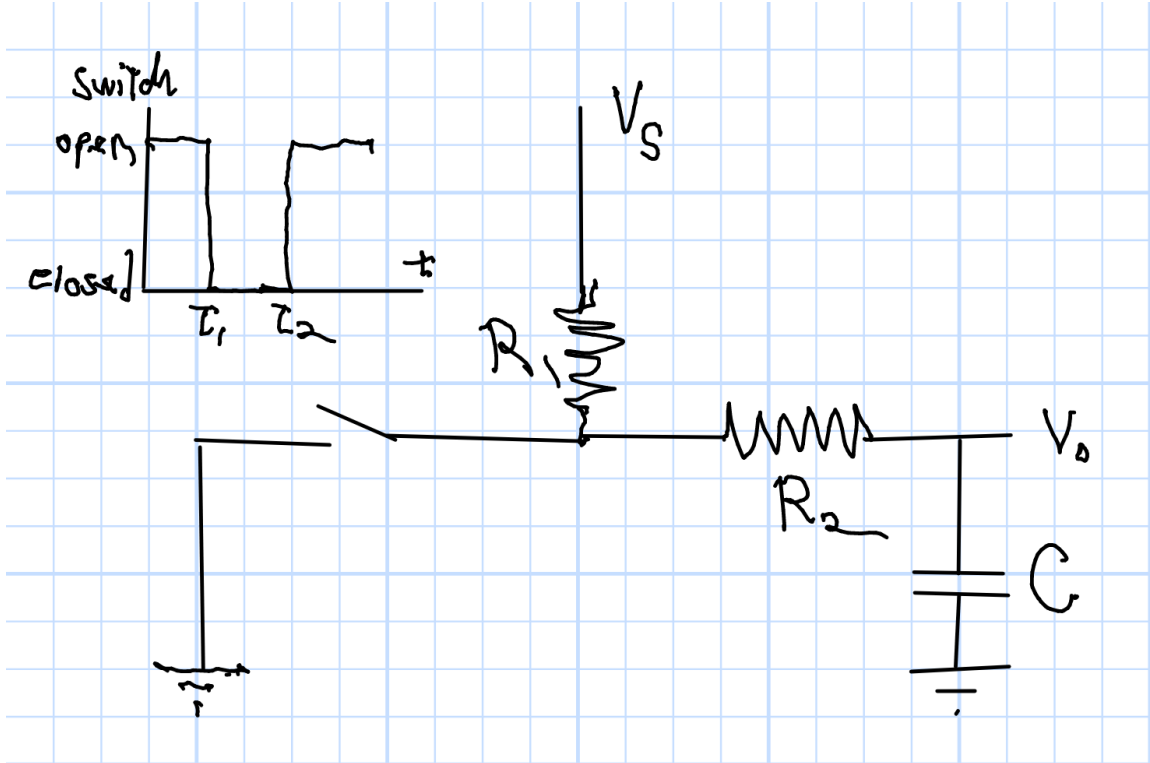

1.  $\tau_{charge} = (R_1 + R_2) C = 60 \text{ ms.}$
2.  $\tau_{discharge} = R_2 C = 40 \text{ ms.}$
3.  $V(t_2) = V(t_1) e^{-(t_2-t_1)\tau_{discharge}} = 4.17 \text{ Volts}$
4.  $t_2 = -\log_e\left(\frac{1}{5}\tau_{discharge}\right) + t_1 = 65 \text{ ms}$