

Electrical Engineering

Week 10


Charles A. DiMarzio
EECE-2210
Northeastern University

Oct 2021


Week 10 Agenda: Second–Order Transients

- Second–Order Equations (LC Circuit)
- Complex Notation
- Series RLC
 - Forced Solution
 - Transient Solution
 - Damping
- Parallel RLC

LC Circuit

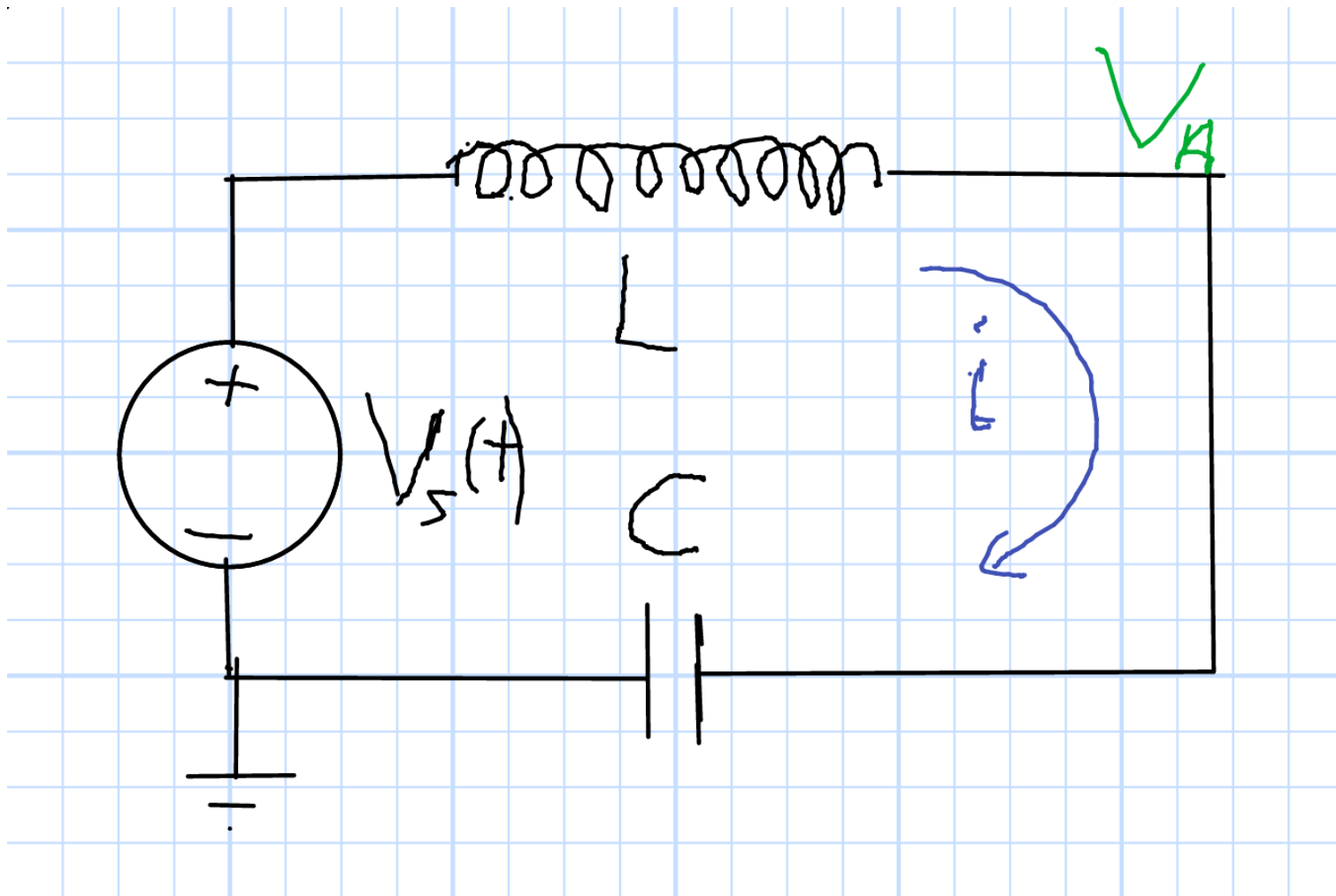

LC Equations

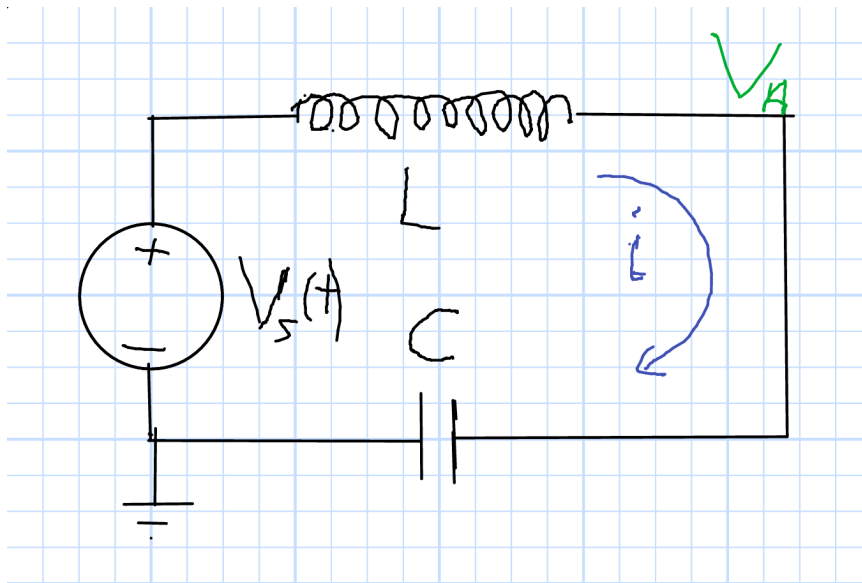

- KVL

$$v_s(t) = L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

- Differentiate All Terms

$$\frac{dv_s(t)}{dt} = L \frac{d^2i(t)}{dt^2} + \frac{1}{C} i(t)$$



- Propose Solution for i

$$i(t) = K e^{st}$$

- Substitute

$$\frac{dv_s(t)}{dt} = L s^2 i(t) + \frac{1}{C} i(t)$$

LC Example

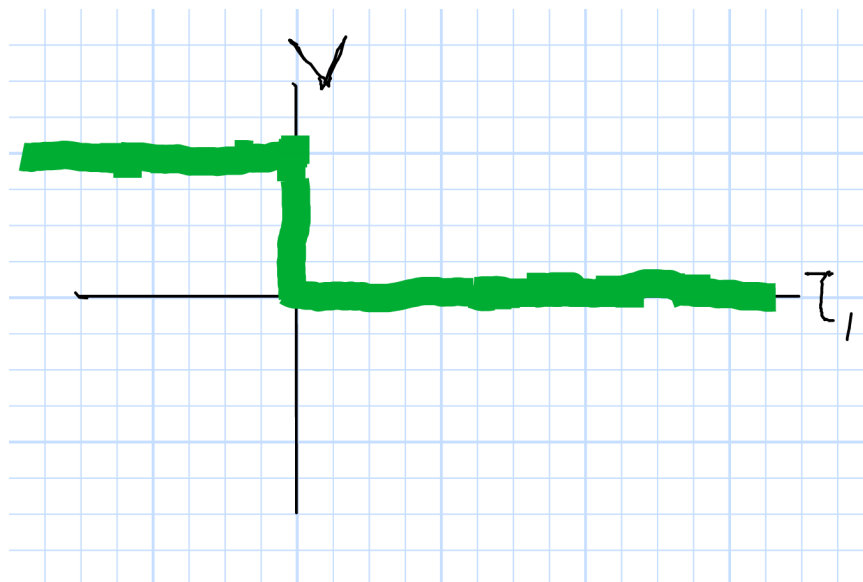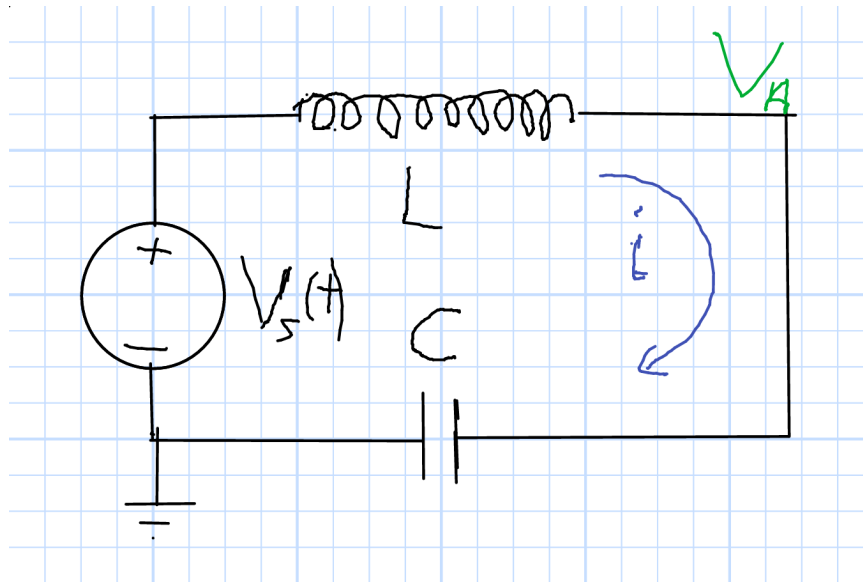

- From Previous Page

$$\frac{dv_s(t)}{dt} = Ls^2i(t) + \frac{1}{C}i(t)$$

- Step Voltage

$$\frac{dv_s(t)}{dt} = -v_s(0^-)\delta(t)$$

- Solution

$$s^2 = -\frac{1}{\sqrt{LC}} \quad s = \pm\sqrt{-\frac{1}{LC}}$$

- Express as Frequency

$$s_1 = \sqrt{-1}\omega_0 \quad s_2 = -\sqrt{-1}\omega_0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Interlude: Complex Representation

- Current vs. Voltage Equations

$$i = C \frac{dV}{dt} \quad v = L \frac{di}{dt}$$

- Exponential Solutions: First Order Transients

$$\frac{de^{st}}{dt} = se^{st}$$

- Sinusoidal Solutions

$$\frac{d \sin \omega t}{dt} = \omega \cos \omega t \quad \frac{d \cos \omega t}{dt} = -\omega \sin \omega t$$

- Almost Nice, but Not Quite

Euler's Formula

- Euler's Formula

$$e^{j\theta} = \cos \theta + j \sin \theta \qquad e^{j\omega t} = \cos \omega t + j \sin \omega t$$

- Cosine and Sine

$$\cos \omega t = \frac{e^{j\omega t}}{2} + \frac{e^{-j\omega t}}{2} \qquad \sin \omega t = \frac{e^{j\omega t}}{2j} - \frac{e^{-j\omega t}}{2j}$$

- Derivatives Are Simple

$$\frac{de^{j\omega t}}{dt} = j\omega e^{j\omega t} \qquad \frac{de^{-j\omega t}}{dt} = -j\omega e^{-j\omega t}$$

$$v = 5V e^{j\omega t} \qquad i = C \frac{dv}{dt} = j\omega C v$$

Two Problems Instead of One

- Cosine Example: Superposition of Two

$$v_+ = 5V e^{j\omega t} \quad i_+ = C \frac{dv}{dt} = j\omega C v$$

$$v_- = 5V e^{-j\omega t} \quad i_- = C \frac{dv}{dt} = -j\omega C v$$

- But It's Almost No Extra Work:

A Linear Function of the Complex Conjugate of something is the Complex Conjugate of the Linear Function

$$v = v_+ + v_- = 10V \cos \omega t$$

$$i = i_+ + i_- = j\omega C v_+ - j\omega C v_-$$

$$= 2\text{Real} [j\omega C v_+] = -C \times 10V \sin \omega t$$

i or j: In EE, it's j

- Imaginary Unit

$$\sqrt{-1} = \pm i$$

- But in EE, i is Current
- We use j

$$\sqrt{-1} = \pm j$$



WPI

- Euler's Formula

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

- Cosine and Sine

$$\cos \omega t = \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

$$\sin \omega t = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

- Why Exponentials?
 - Compact Notation
 - Easy Math

Solving Problems

Real Quantity	Positive Freq.		Negative Freq.	Phasor
$A \cos \omega t$	$\frac{A}{2} e^{j\omega t}$	+	$\frac{A}{2} e^{-j\omega t}$	$A \angle 0$
$A \sin \omega t$	$\frac{-jA}{2} e^{j\omega t}$	+	$\frac{jA}{2} e^{-j\omega t}$	$A \angle 90$
$A \cos(\omega t + \phi)$	$\frac{A e^{j\phi}}{2} e^{j\omega t}$	+	$\frac{A e^{-j\phi}}{2} e^{-j\omega t}$	$A \angle \phi$
$A \cos \phi \cos \omega t - \dots$ $A \sin \phi \sin \omega t =$				
$a \cos \omega t + b \sin \omega t$	$\frac{a+jb}{2} e^{j\omega t}$	+	$\frac{a-jb}{2} e^{-j\omega t}$	$a + jb$

Problem Solution
Unknown = $x + jy$

$$2\text{Re} \left[\frac{x+jy}{2} e^{j\omega t} \right]$$

Pos. Freq. + C.C.

$$\text{Re} \left[(x + jy) e^{j\omega t} \right]$$

Complex Notation (1)

- Phasor A

$$Ae^{j\omega t} = (a + jb) e^{j\omega t}$$

- Include Negative Frequency Part

$$\begin{aligned} \frac{A}{2}e^{j\omega t} + \frac{A^*}{2}e^{-j\omega t} &= \left(\frac{a}{2} + j\frac{b}{2}\right) e^{j\omega t} + \left(\frac{a}{2} - j\frac{b}{2}\right) e^{-j\omega t} = \\ &= \frac{a}{2} (e^{j\omega t} + e^{-j\omega t}) + j\frac{b}{2} (e^{j\omega t} - e^{-j\omega t}) \end{aligned}$$

- From Euler's Formula

$$\cos \omega t = \frac{e^{j\omega t} + e^{-j\omega t}}{2} \quad \sin \omega t = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

- Result

$$\frac{A}{2}e^{j\omega t} + \frac{A^*}{2}e^{-j\omega t} = a \cos \omega t + b \sin \omega t$$

Complex Notation (2)

- Do all the math with $Ae^{j\omega t}$
- Add the negative frequency part at the end
- Don't worry about trigonometric identities ever again
- Phase and Amplitude are in the Phasor

$$|a + jb| = \sqrt{a^2 + b^2} = |A| \quad \phi = \angle A = \arctan \frac{b}{a}$$

- This only works for linear systems
- Some people use A , and some use $A/2$; be careful.

Steady-State Sinusoids (Later)

Resistors

$$v = iR$$

$$\mathbf{V} = \mathbf{I}R$$

Capacitors

$$i = C \frac{dv}{dt}$$

$$\mathbf{I} = j\omega C \mathbf{V}$$

$$\mathbf{V} = \frac{1}{j\omega C} \mathbf{I}$$

Inductors

$$v = L \frac{di}{dt}$$



$$\mathbf{V} = j\omega L \mathbf{I}$$

Easy? . . .

Easy!

Back to the LC Example

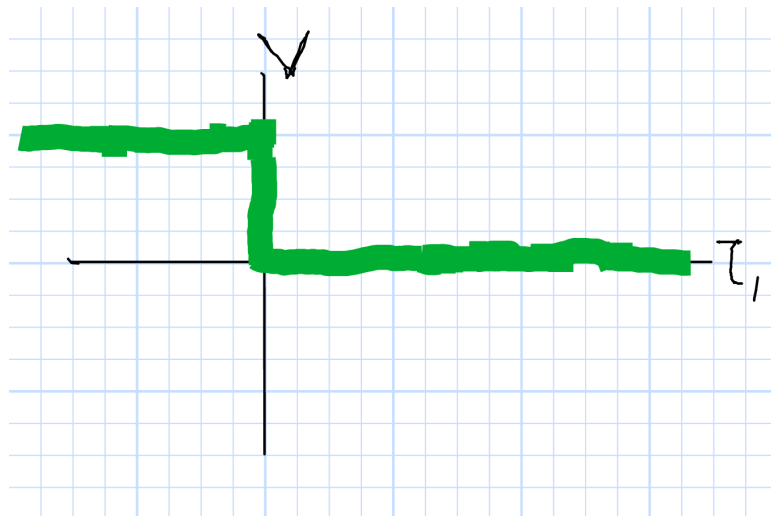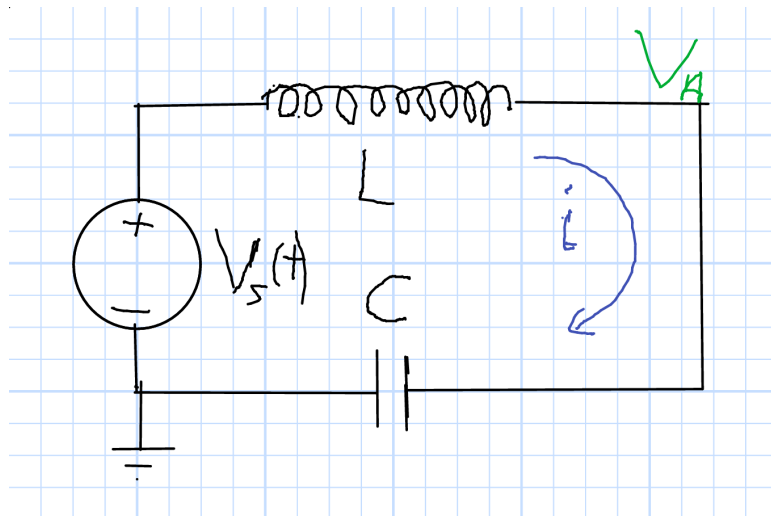Exponential Solutions with Complex Exponents



- Remember

$$i(t) = Ke^{st}$$

$$s_1 = \sqrt{-1}\omega_0 \quad s_2 = -\sqrt{-1}\omega_0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- Solution

$$i(t) = Ke^{j\omega_0 t} + K^*e^{-j\omega_0 t}$$

- Voltage if $v_s = 0$

$$[v_s(t) - v_A(t)] = L \frac{di(t)}{dt}$$

$$v_A(t) = -jK\omega_0 e^{j\omega_0 t} + jK^*\omega_0 e^{-j\omega_0 t}$$

LC Solution

- From Previous Page


$$v_A(t) = -jK\omega_0 e^{j\omega_0 t} + jK^*\omega_0 e^{-j\omega_0 t}$$

- 2 Unknowns, Real and Imaginary Parts of K
- v Continuous Across Capacitor (V_A)
- i Continuous Through Inductor (and Capacitor)


$$v_A(0^+) = v_s(0^-) \quad \left. \frac{dv_A}{dt} \right|_{0^+} = 0$$

$$v_A(t+) = v_s(0^-) \cos \omega_0 t$$

LC Result

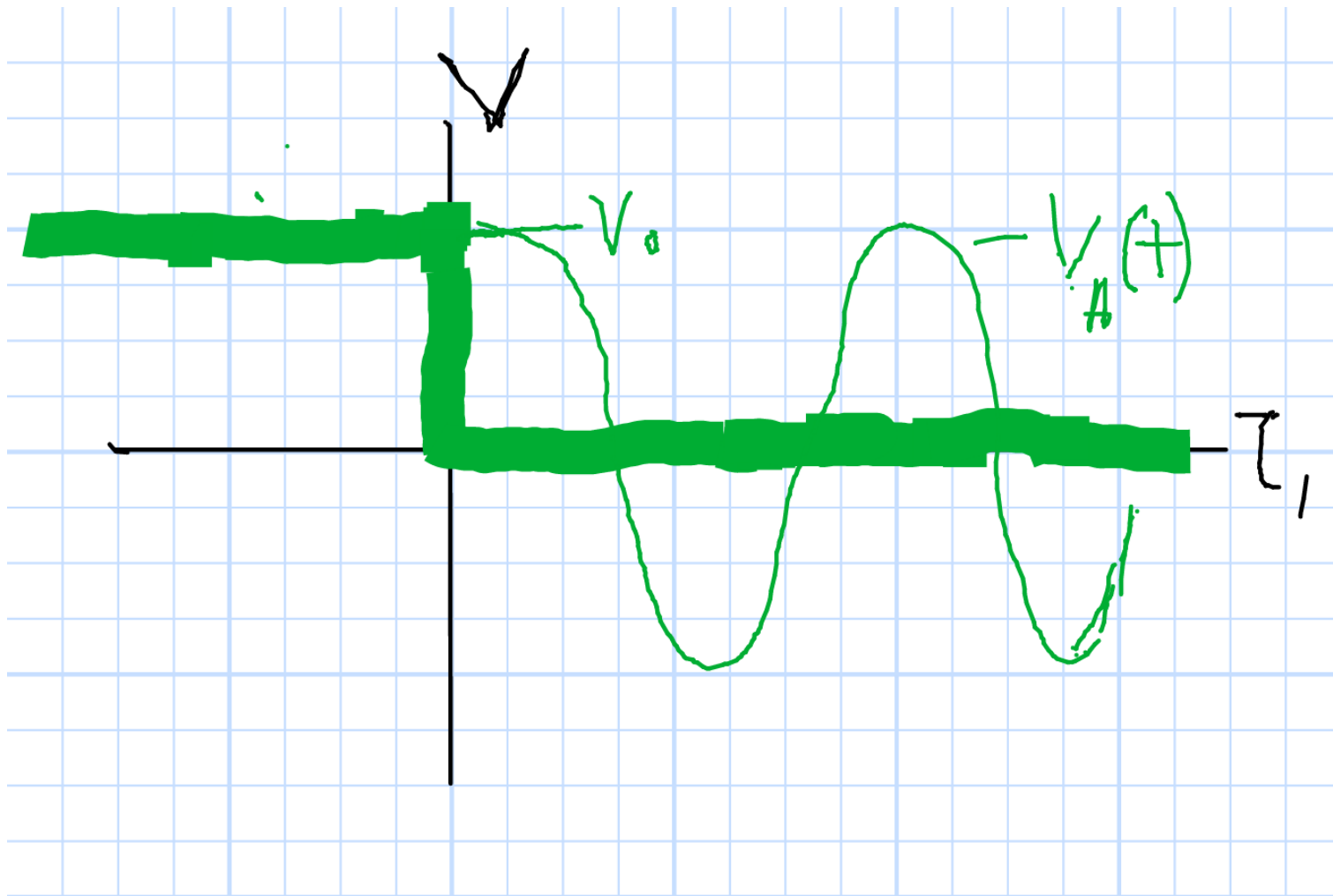


RLC Series Circuit

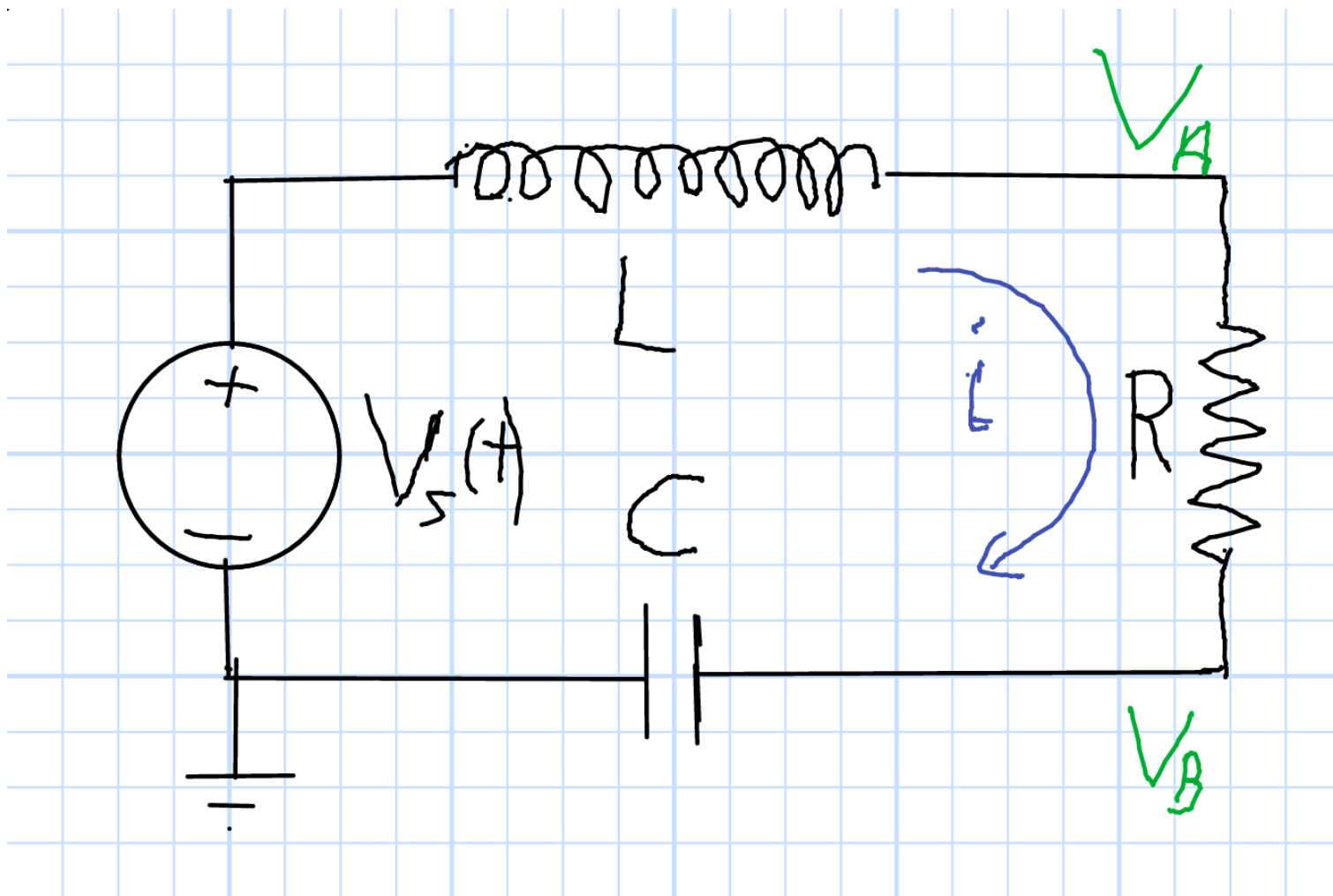

RLC Series Circuit Analysis

- KVL
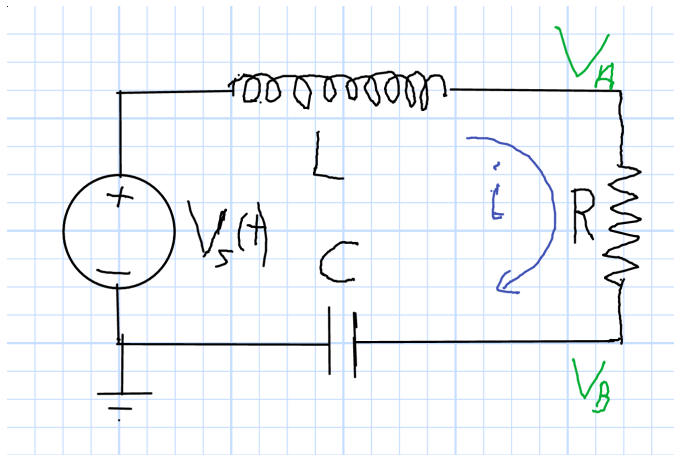
$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int i(t) dt = v_s(t)$$



- Undamped Resonant Frequency

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- Damping Coefficient

$$\alpha = \frac{R}{2L}$$

- Differentiate

$$L \frac{d^2i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = \frac{dv_s(t)}{dt}$$

- Divide by L

$$\frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$$

- Use Definitions, ω_0 and α

$$\frac{d^2i(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$$

General Second–Order DE

- From Previous Page

$$\frac{d^2i(t)}{dt^2} + 2\alpha\frac{di(t)}{dt} + \omega_0^2i(t) = \frac{1}{L}\frac{dv_s(t)}{dt}$$

- Define Forcing Function, $f = \frac{dv_s}{dt}\frac{1}{L}$

$$\frac{d^2i(t)}{dt^2} + 2\alpha\frac{di(t)}{dt} + \omega_0^2i(t) = f(t)$$

- Particular (Forced) and Complementary Solutions
- DC: Forced Solution is Steady–State Solution, i_p
- Transient Solution, i_c for

$$\frac{d^2i(t)}{dt^2} + 2\alpha\frac{di(t)}{dt} + \omega_0^2i(t) = 0$$

Damping

- Transient Equation From Previous Page

$$\frac{d^2i(t)}{dt^2} + 2\alpha\frac{di(t)}{dt} + \omega_0^2i(t) = 0 \quad i(t) = ke^{st}$$

- Characteristic Equation

$$s^2i + 2\alpha si + \omega_0^2i = 0 \quad s^2 + 2\alpha s + \omega_0^2 = 0$$


- Solutions

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

- Define Damping Ratio

“zeta” $\zeta = \frac{\alpha}{\omega_0}$

Damping in the Complex Plane

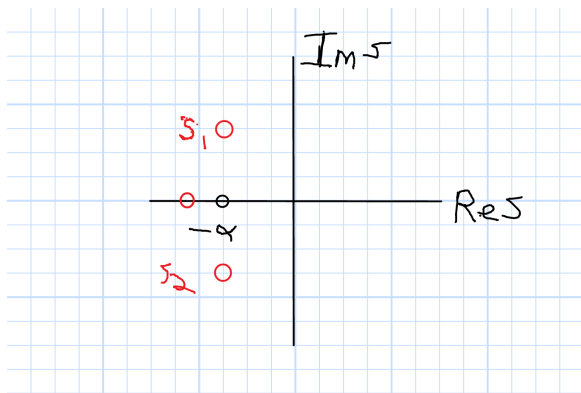

Underdamped

$$\zeta < 1$$

$$\alpha < \omega_0$$


$$\Re s < 0$$

$\Im s$ Symmetric

Solutions:

Damped Sinusoids

Frequency Shifted

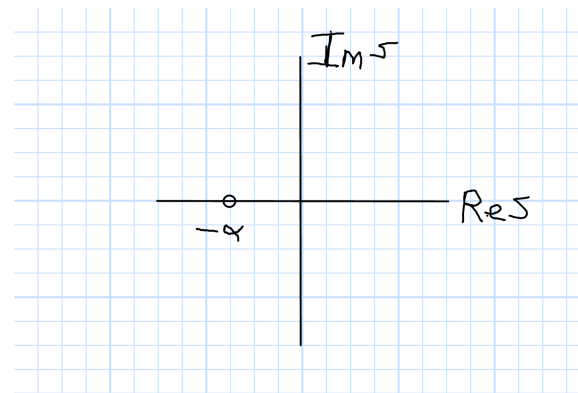

Critically Damped

$$\zeta = 1$$

$$\alpha = \omega_0$$


$$\Re s < 0$$

$$\Im s = 0$$

Degenerate

Exponential

$$+e^{-t/\tau}$$

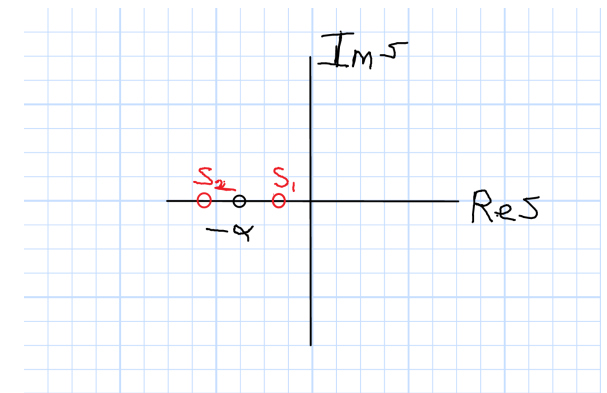

Overdamped

$$\zeta > 1$$

$$\alpha > \omega_0$$

$$\Re s < 0$$

$$\Im s = 0$$

Exponentials

Underdamped (1)

- Solutions for s

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \alpha < \omega_0$$

- Solution Contains $\sqrt{\text{Negative}}$

$$s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \quad s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$$

- Natural Frequency

$$\omega_n = \sqrt{\omega_0^2 - \alpha^2}$$

$$s_1 = -\alpha + j\omega_n \quad s_2 = -\alpha - j\omega_n$$

- Solution

$$i(t) = Ke^{-\alpha + j\omega_n t} + K^*e^{-\alpha - j\omega_n t}$$

Underdamped (2)

- Previous Page (K Complex)


$$i(t) = Ke^{-\alpha+j\omega_n t} + K^*e^{-\alpha-j\omega_n t}$$

- Alternative Form (K_1, K_2 Real)

$$i(t) = K_1e^{-\alpha t} \cos \omega_n t + K_2e^{-\alpha t} \sin \omega_n t$$

- Add **Particular Solution**
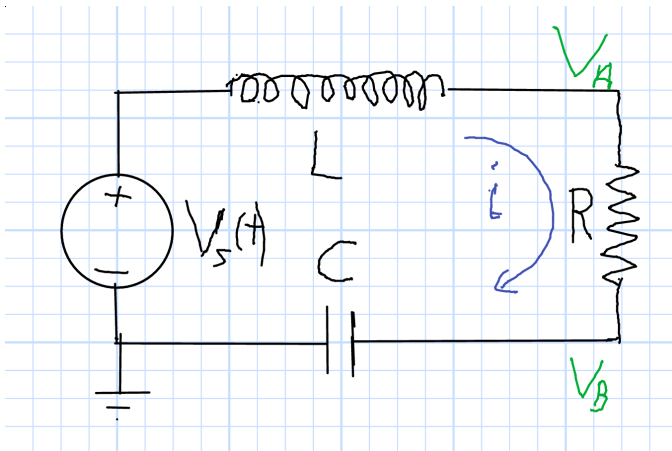
$$i(t) = K_1e^{-\alpha t} \cos \omega_n t + K_2e^{-\alpha t} \sin \omega_n t + 0$$



- Initial Conditions $i(0^+) = 0$

$$i(t) = K_2e^{-\alpha t} \sin \omega_n t$$

$$K_2 = \frac{v_S(0^+)}{\omega_n L}$$

Example

- Let's Make $\omega_0 = 2\pi \times 5\text{kHz}$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad L = \frac{1}{\sqrt{\omega_0^2 C}}$$

$$C = 1\mu\text{F} \quad \rightarrow \quad L = 1\text{mH}$$

- Choose Underdamped $\zeta = 0.1$


$$\alpha = \omega\zeta \quad \alpha = \frac{R}{2L}$$

$$R = 2\alpha L = 6.4\Omega$$


- Parameters

$$\frac{\omega_n}{2\pi} = 4975\text{Hz}$$

Underdamped Current

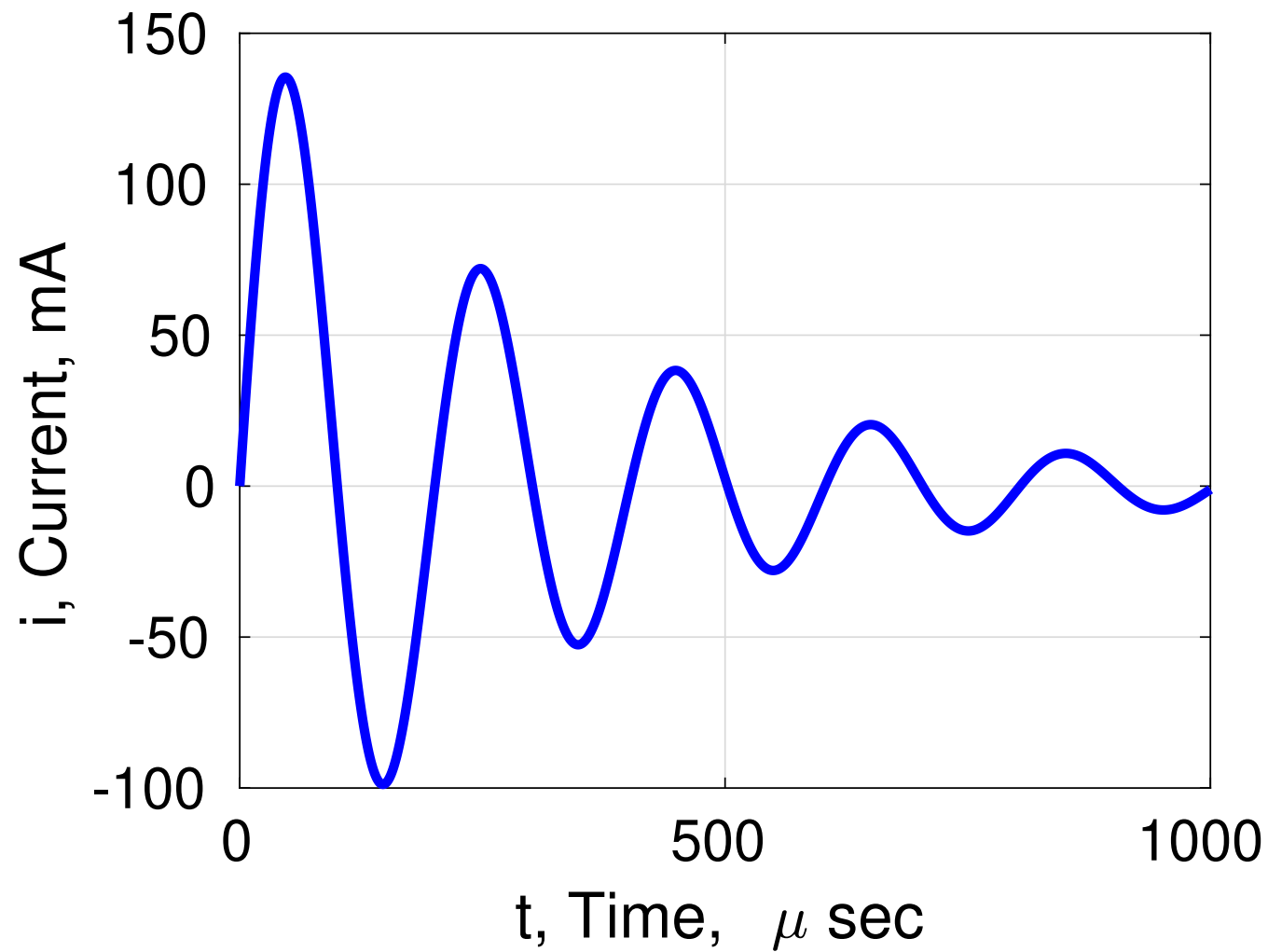

Overdamped Current

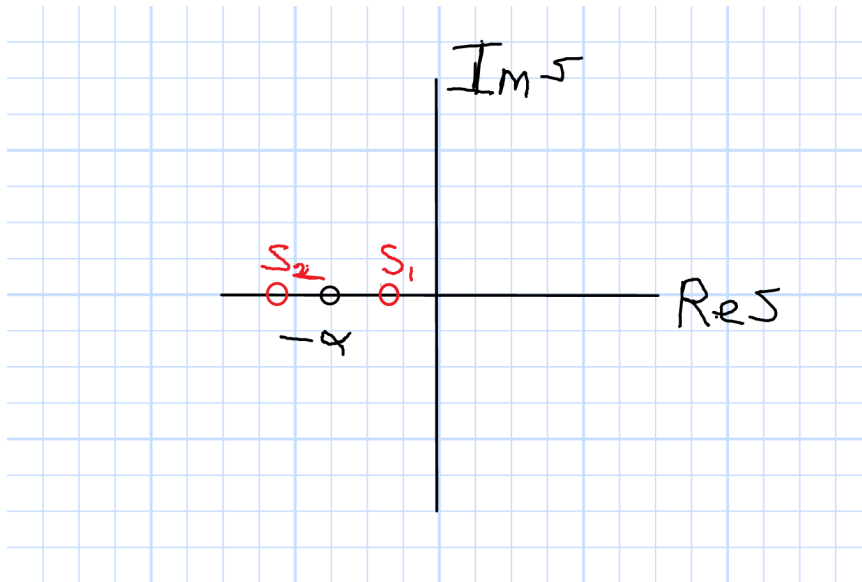

- Solutions for s

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\omega_0 < \alpha$$

- Solution Contains $\sqrt{\text{Positive}}$


$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


$$i(t) = K_1 e^{-\alpha + \sqrt{\alpha^2 - \omega_0^2} t} + K_2 e^{-\alpha - \sqrt{\alpha^2 - \omega_0^2} t}$$

$$i(t) = K_1 e^{(-1 + 0.87) \times 6.2 \times 10^4 t} + K_2 e^{(-1 - 0.87) \times 6.2 \times 10^4 t}$$

Overdamped Example

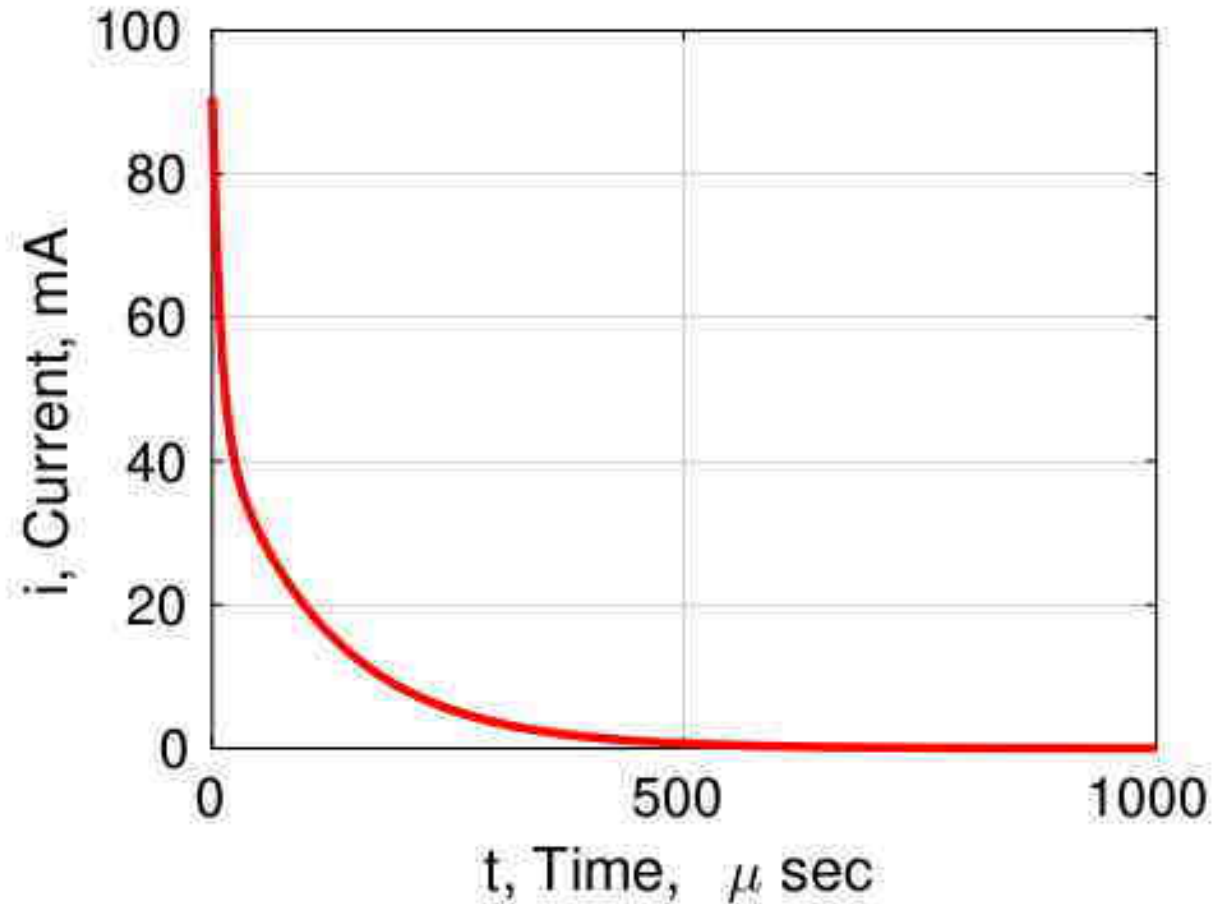

Critically Damped Example

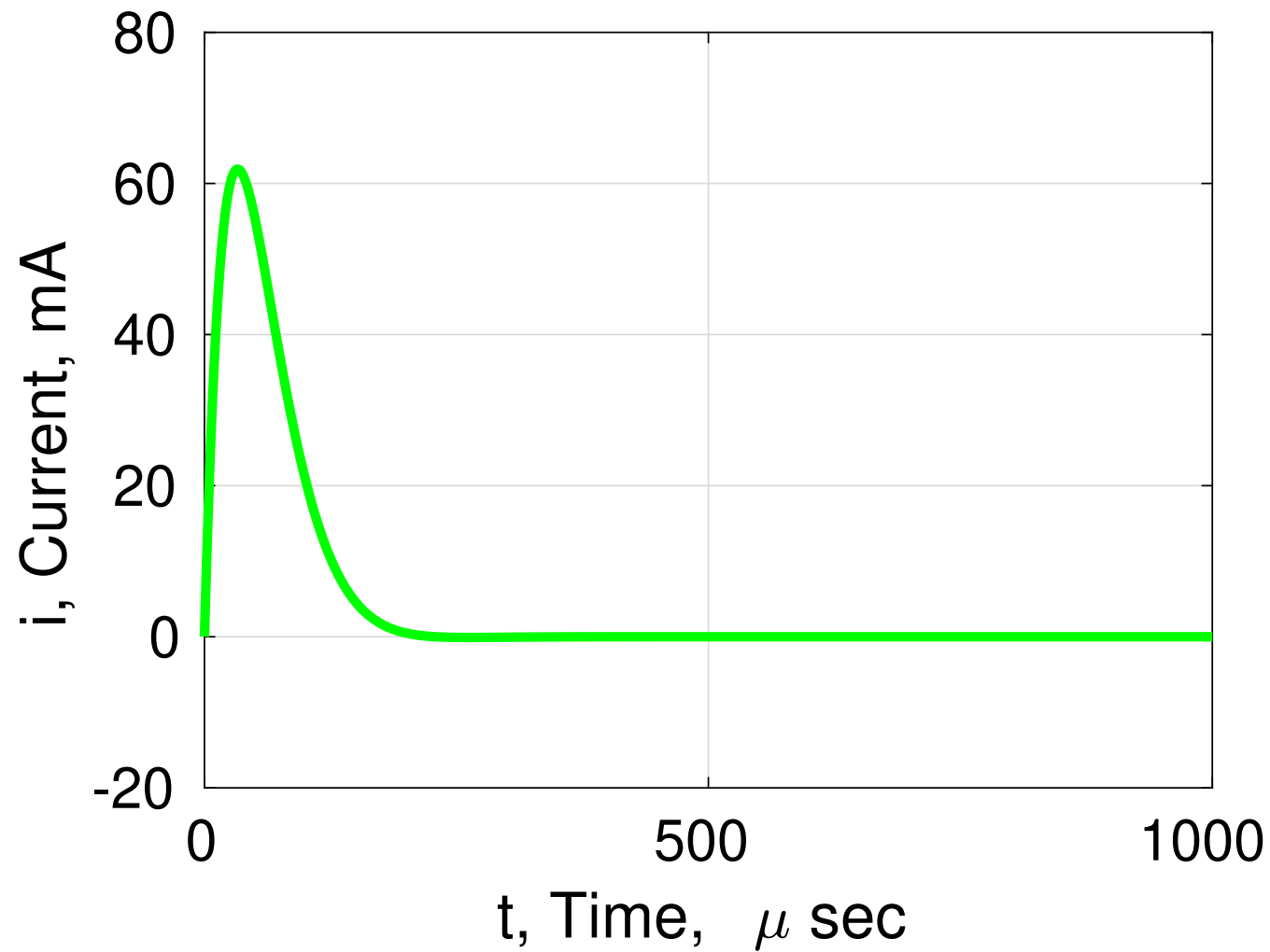

Application

- Scanning Lidar
- Rapid Scan from Left to Right
 - Move the Laser Beam 10 Meters
 - Sample 1000 Times for 1 centimeter steps
- Quick Return From Right to Left
 - Time Constant τ


$$10\text{m} \times e^{-t/\tau} < 10^{-2}\text{m}$$

$$t > \tau \log_e \frac{10\text{m}}{10^{-2}\text{m}} \approx 7\tau = \frac{7}{\alpha}$$


- Critical Damping

$$\zeta = 1 \quad \rightarrow \quad \alpha = \omega_0 \quad t > \frac{7}{\omega_0}$$

Three Damping Examples

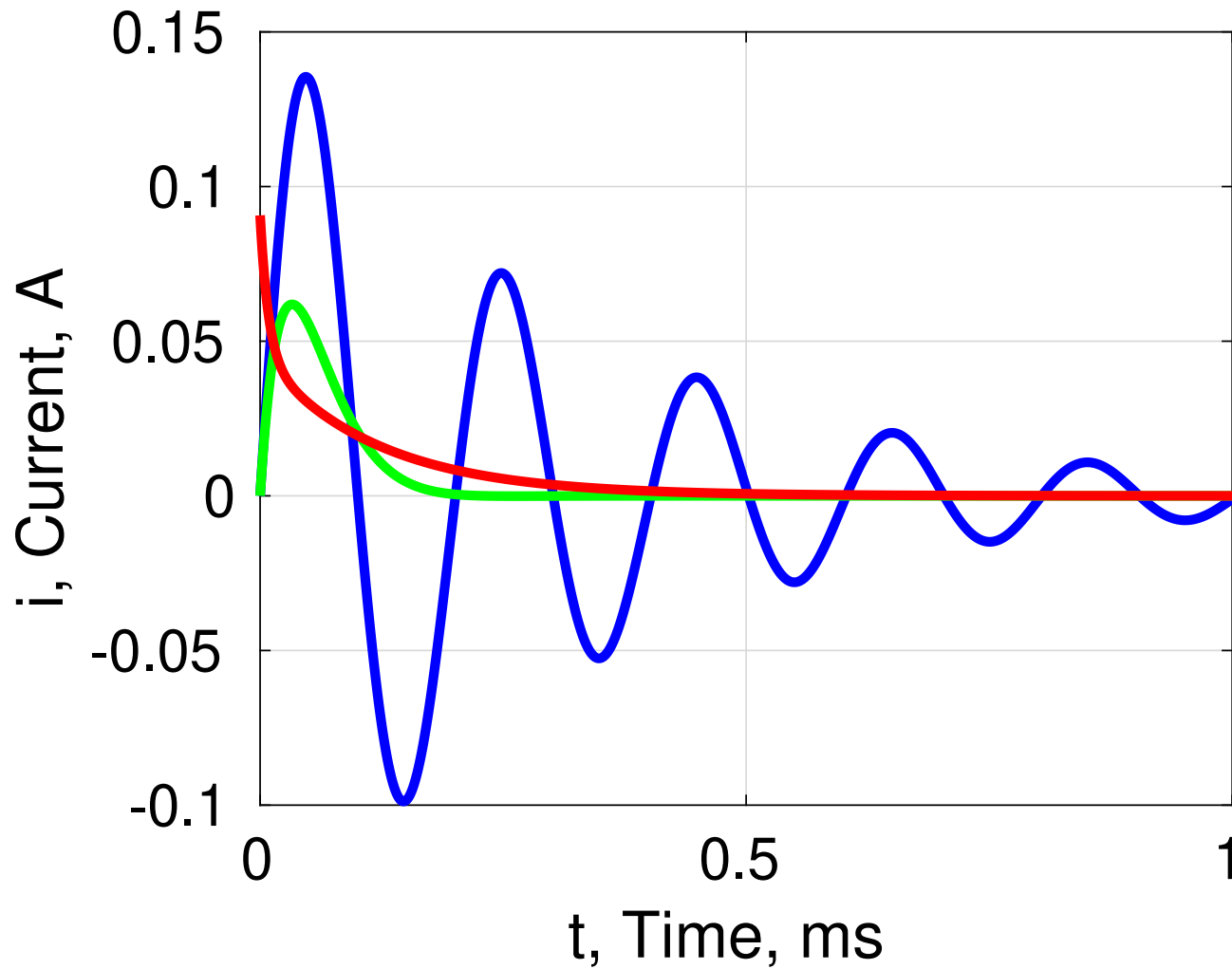

RLC Parallel Circuit

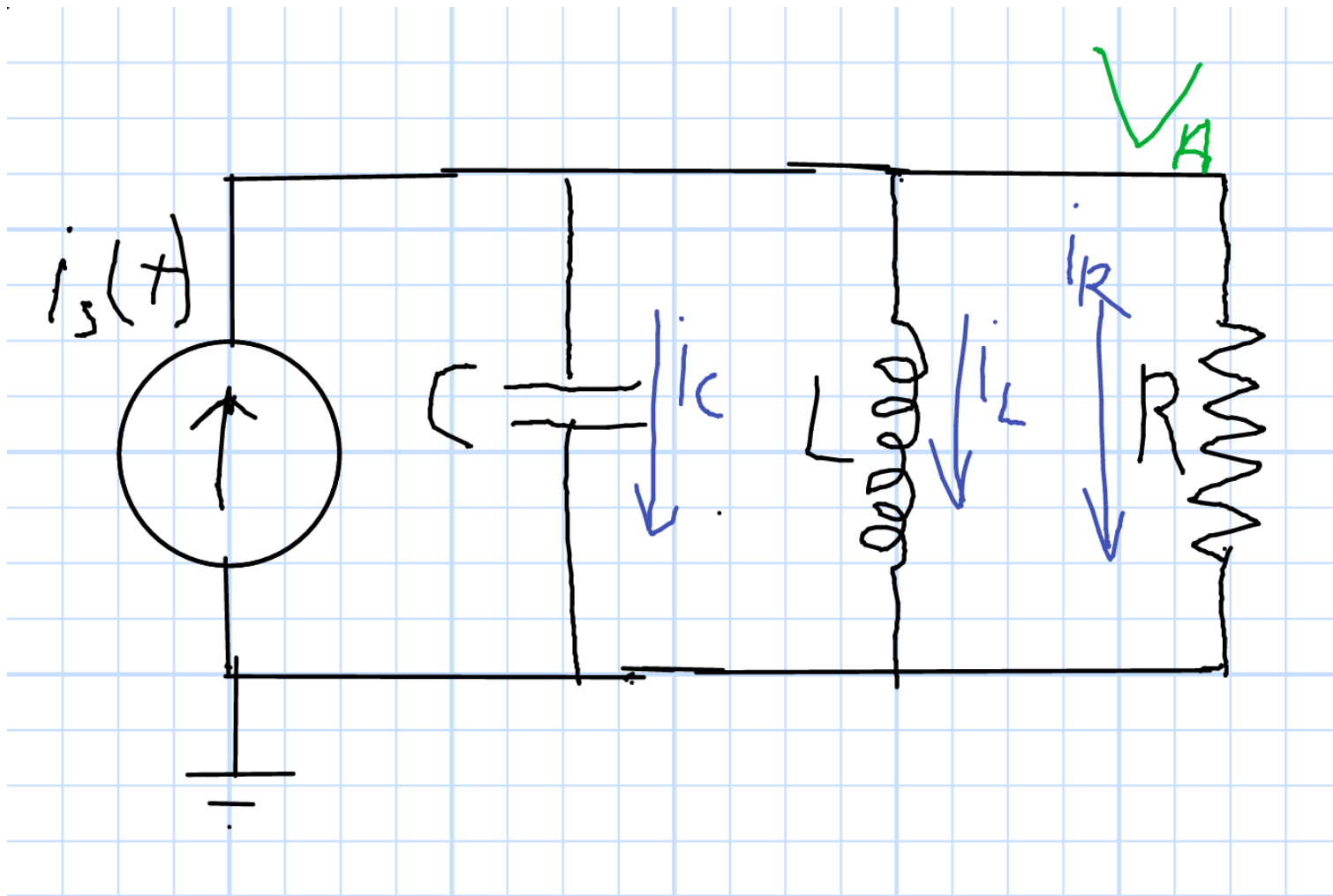

$$C \frac{dv(t)}{dt} + \frac{1}{L} \int v(t) dt + \frac{1}{R} v(t) = i_s(t)$$

Equation for i_L

- From Previous Page

$$C \frac{dv(t)}{dt} + \frac{1}{L} \int v(t) dt + \frac{1}{R} v(t) = i_s(t)$$

- Inductor Equation

$$v(t) = L \frac{di_L(t)}{dt}$$

- Substitute


$$LC \frac{d^2 i_L(t)}{dt^2} + i_L(t) + \frac{L}{R} \frac{di_L(t)}{dt} = i_s(t)$$

- Divide by LC , Reorder

$$\frac{d^2 i_L(t)}{dt^2} + \frac{1}{RC} \frac{di_L(t)}{dt} + \frac{1}{LC} i_L(t) = i_s(t)$$

- Define ω_0 , α
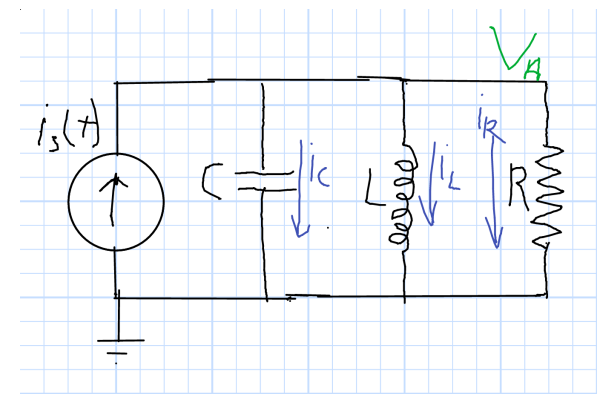
$$\frac{d^2 i_L(t)}{dt^2} + 2\alpha \frac{di_L(t)}{dt} + \omega_0^2 i_L(t) = i_s(t)$$



$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{\alpha}{\omega_0}$$

Solutions (1)

- From Previous Page

$$\frac{d^2 i_L(t)}{dt^2} + 2\alpha \frac{di_L(t)}{dt} + \omega_0^2 i_L(t) = i_s(t)$$

- Step Current ($i_s(0^-) = 0$, $i_s(0^+) = 100\text{mA}$)

- Particular Solution (Steady State)

$$i_L(t) = i_s(0^+)$$

- Complementary Solution (Transient) $i_L(t) = Ke^{st}$

$$s^2 i_L(t) + 2\alpha s i_L(t) + \omega_0^2 i_L(t) = 0$$

Solutions (2)

- Complementary Solution From Previous Page

$$s^2 i_L(t) + 2\alpha s i_L(t) + \omega_0^2 i_L(t) + i_s(0) = 0$$

- Overdamped Solutions (Add Forced Solution)

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


$$i_L(t) = K_1 e^{-s_1 t} + K_2 e^{-s_2 t} + i_s(0+)$$

- Underdamped Solutions $\omega_n = \sqrt{\omega_0^2 - \alpha^2}$

$$s_1 = -\alpha + j\omega_n \quad s_2 = -\alpha - j\omega_n$$

$$i(t) = K_1 e^{-\alpha t} \cos \omega_n t + K_2 e^{-\alpha t} \sin \omega_n t + i_s(0+)$$

Initial Conditions

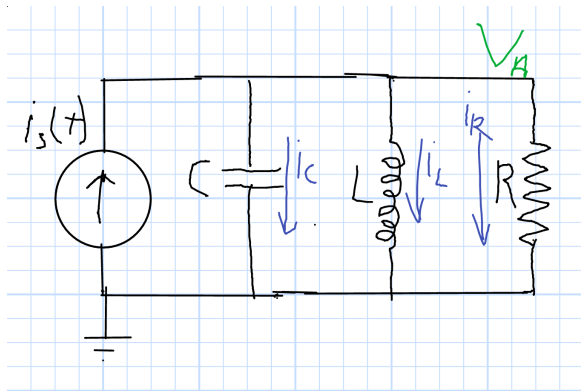

- Inductor Requires

$$i_L(0^+) = i_L(0^-) = 0$$

- Capacitor Requires v_A Continuous

$$\frac{di_L}{dt} = 0 \text{ at } t = 0^+$$

- Underdamped Equation from Previous Page

$$i(t) = K_1 e^{-\alpha t} \cos \omega_n t + K_2 e^{-\alpha t} \sin \omega_n t + i_s(0^+)$$

- Initial Current

$$i(0) = K_1 + i_s(0^+) = 0$$

- $di_L/dt = 0$ at $t = 0$ (d/dt by Product Rule)

$$-\alpha K_1 + \omega_n K_2 = 0$$

Plots


$$\omega_0 = 2\pi \times 5\text{kHz}$$

$$C = 1\mu\text{F}$$

$$L = 1\text{mH}$$


$$\alpha = \omega_0\zeta \quad \alpha = \frac{1}{2RC}$$

$\zeta = 0$	$R \rightarrow \infty$
$\zeta = 0.3$	$R = 53.0\Omega$
$\zeta = 1$	$R = 15.9\Omega$
$\zeta = 3$	$R = 5.3\Omega$

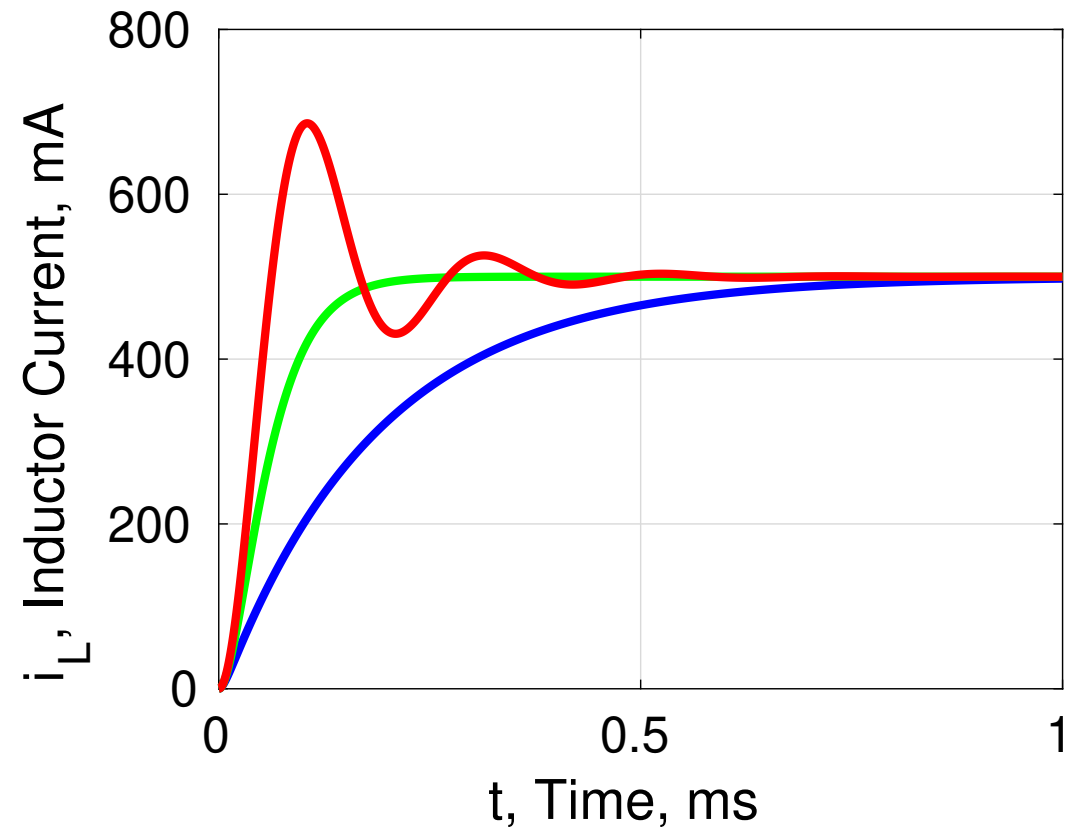

Application: Magnet

Source and Magnet Coil

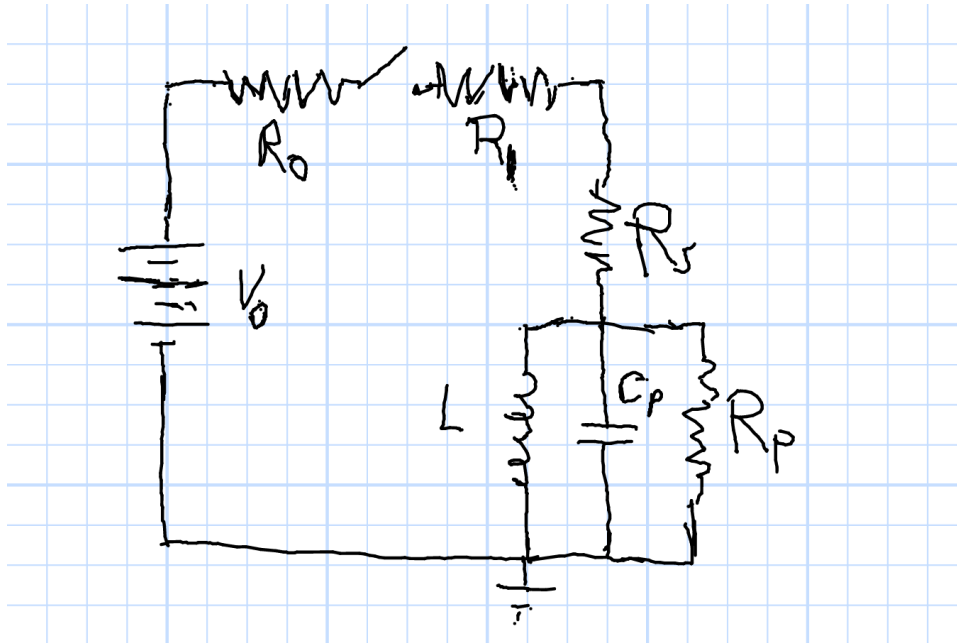

Norton Equivalent

