

# Electrical Engineering

## Week 11

Charles A. DiMarzio  
EECE-2210  
Northeastern University

Nov 2021

# Week 11 Agenda: Circuits and Sine/Cosine Waves

- Complex Arithmetic
- C, L, Reactance and Impedance
- Eli the Ice Man
- Series and Parallel
- Voltage and Current Dividers
- Power, RMS, Peak-to-Peak, Oscilloscopes and Meters
- Resistive and Reactive Power, Power Factor
- One More Op-Amp Circuit

# Complex Notation

- Voltage

$$v_x(t) = V_x \cos(\omega t + \phi)$$

- From Euler

$$v_x(t) = \frac{V_x}{2} e^{j(\omega t + \phi)} + \frac{V_x}{2} e^{-j(\omega t + \phi)}$$

$$v_x(t) = \frac{V_x e^{j\phi}}{2} e^{j\omega t} + \frac{V_x e^{-j\phi}}{2} e^{-j\omega t}$$

$$v_x(t) = \frac{V_x}{2} e^{j\omega t} + \frac{V_x^*}{2} e^{-j\omega t}$$

- Phasor

$$\mathbf{V}_x = V_x \angle \phi = V_x e^{j\phi}$$

$$v_x(t) = \text{Re} \left[ \mathbf{V}_x e^{j\omega t} \right]$$

- Example Cosine

$$v(t) = 5V \times \cos \omega t$$

$$\mathbf{V} = 5V$$

- Example Sine

$$v(t) = 5V \times \sin \omega t$$

$$\mathbf{V} = j5V = 5V \angle 90^\circ$$


- Example with Phase

$$v(t) = 5V \times \cos(\omega t + 30^\circ)$$

$$\mathbf{V} = 5V \angle 30^\circ = 5V e^{j30^\circ \frac{\pi}{180^\circ}}$$

$$\mathbf{V} = 4.33 + 2.5j$$

# Phasor Graphical Representation

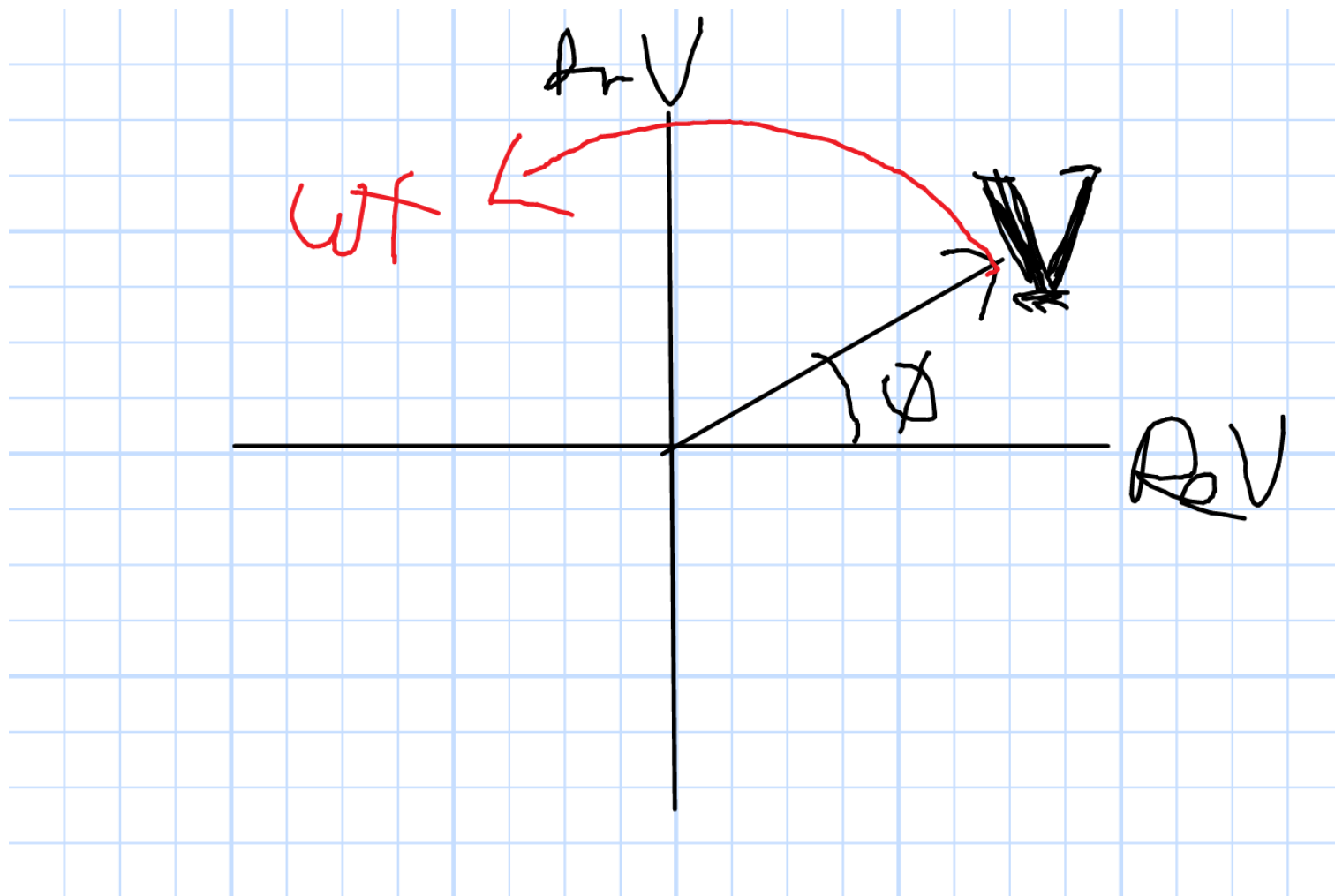

# Complex Arithmetic

- Addition/Subtraction

$$z_1 = x_1 + jy_1 \quad z_2 = x_2 + jy_2$$

$$z = z_1 + z_2$$

$$x = x_1 + x_2 \quad y = y_1 + y_2$$

- Multiplication/Division

$$z = z_1 z_2 = (x_1 + jy_1)(x_2 + jy_2)$$

$$z = x_1 x_2 - y_1 y_2 + jx_1 y_2 + jy_1 x_2$$

- Easier

$$z_1 z_2 : \quad V \angle \phi = V_1 V_2 \angle (\phi_1 + \phi_2)$$

$$\frac{z_1}{z_2} : \quad \frac{V_1}{V_2} \angle (\phi_1 - \phi_2)$$

- Conjugate

$$z = x + jy \quad z^* = x - jy$$

$$(V \angle \phi)^* = V \angle -\phi$$

$$(V e^{j\phi})^* = V e^{-j\phi}$$

- Example

$$\frac{5 \angle 30^\circ + 7}{2 \angle -45^\circ}$$

```
>> moose=...
```

```
(5*exp(1j*30*pi/180)+7)...
```

```
/2*exp(-1j*45*pi/180)
```

```
moose =
```

```
4.8897 - 3.1219i
```

```
>>
```

# Capacitor (1)

- Capacitor Equation

$$i = C \frac{dv}{dt}$$

- Voltage Equation

$$v = V e^{j\omega t}$$

- Current

$$i = C j\omega V e^{j\omega t}$$

$$i = I e^{j\omega t} = C j\omega V e^{j\omega t}$$

$$I = j\omega C V$$

- Impedance

$$Z = \frac{V}{I} = \frac{1}{j\omega C}$$

- Example  $C = 1\mu\text{F}$

$$Z = \frac{1}{j\omega C} \quad \omega = 2\pi f$$

$$V = 10\text{V at } f$$

- Current

$$I = \frac{V}{Z} \quad i = I e^{j\omega t}$$

```
>> C=1e-6;V=10;f=50;
```

```
>> Z=1/(1j*2*pi*f*C)
```

```
Z =
```

```
0.0000e+00 - 3.1831e+03i
```

```
>> I=V/Z
```

```
I =
```


```
0.0000 + 0.0031i
```

$$I = 3.1\text{mA} \angle 90^\circ$$

# Capacitor (2); Current Leads

$$C = 1\mu\text{F} \quad V = 10\text{V at } f$$

$f$	$Z$	$ I $
50Hz	$-j3200\Omega$	3.1mA
500Hz	$-j320\Omega$	31mA
5kHz	$-j32\Omega$	310mA
50kHz	$-j3.2\Omega$	3.1A

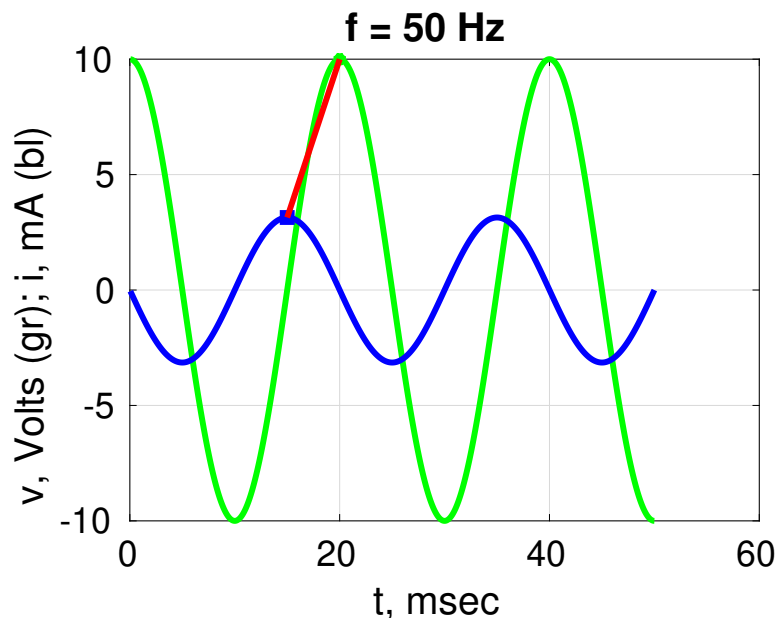

```
t=[0.001:0.001:1]*0.05;
C=1e-6;V=10;f=50;omega=2*pi*f;
Z=1/(1j*omega*C);I=V/Z;
vc=real(V*exp(1j*omega*t));
ic=real(I*exp(1j*omega*t));
fv=find(vc==max(vc),1);
fi=find(ic==max(ic),1);
figure;plot(t*1e3,vc,'g',...
    t*1e3,ic*1e3,'b',...
    t(fv)*1e3,vc(fv),'g*',...
    t(fi)*1e3,ic(fi)*1e3,'bs',...
    [t(fv),t(fi)]*1e3,...
    [vc(fv),ic(fi)*1e3],'r');
grid on;xlabel('t, msec');
ylabel('v, Volts (gr); i, mA (bl)');
title('f = 50 Hz');
```

# Inductor: Current Lags

- Inductor Equation

$$v = L \frac{di}{dt}$$

- Current Equation

$$i = \mathbf{I}e^{j\omega t}$$

- Voltage

$$v = Lj\omega \mathbf{I}e^{j\omega t}$$

$$v = \mathbf{V}e^{j\omega t} = Lj\omega \mathbf{I}e^{j\omega t}$$

$$\mathbf{V} = j\omega L \mathbf{I}$$

- Impedance

$$Z = \frac{\mathbf{V}}{\mathbf{I}} = j\omega L$$

- Example  $L = 5\text{H}$

$$Z = j\omega L$$

- Current

$$I = \frac{V}{Z} \quad i = Ie^{j\omega t}$$

```
>> L=5;V=10;f=50;omega=2*pi*f;
```

```
>> Z=1j*omega*L
```

```
Z =
```

```
0.0000e+00 + 1.5708e+03i
```

```
>> I=V/Z
```

```
I =
```


```
0.0000 - 0.0064i
```

$$Z = 1600\Omega \angle 90^\circ$$


$$I = 6.4\text{mA} \angle -90^\circ$$




# R, L, and C

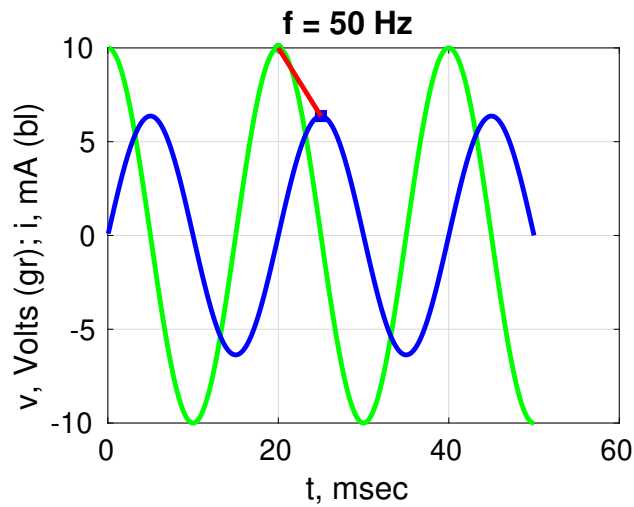

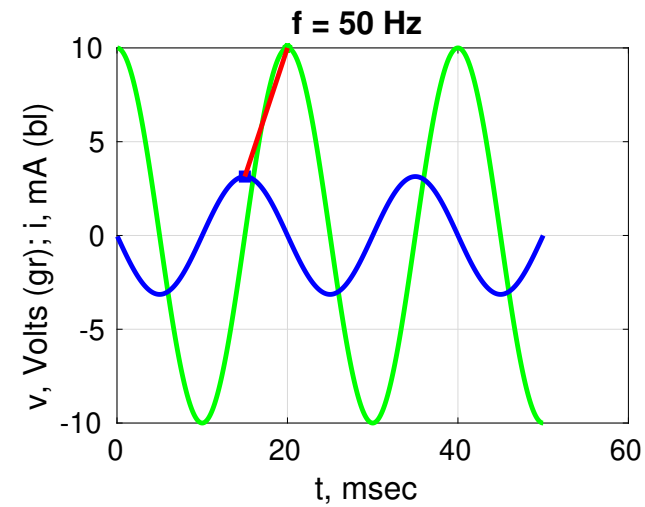$L = 500\text{mH}$  (Peak  $v$  before  $i$ )



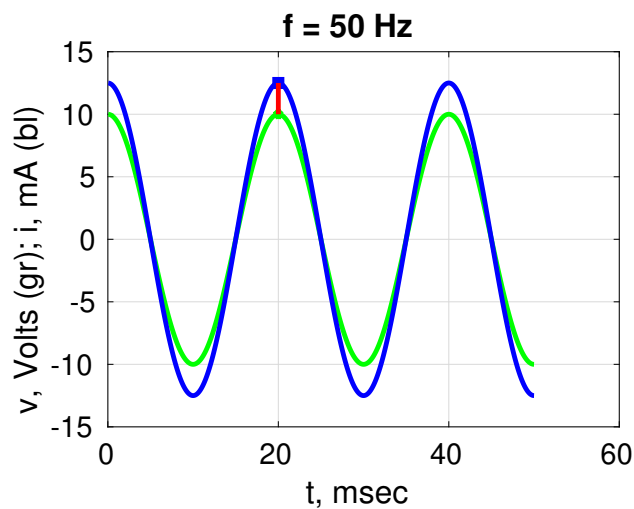$C = 1\mu\text{F}$  (Peak  $v$  after  $i$ )



$500\Omega$  Resistor


Nov 2021

$$Z_C = 3200\Omega \angle -90^\circ$$


$$Z_L = 1600\Omega \angle +90^\circ$$

$$Z_R = 500\Omega \angle 0^\circ$$

# Eli the Ice Man

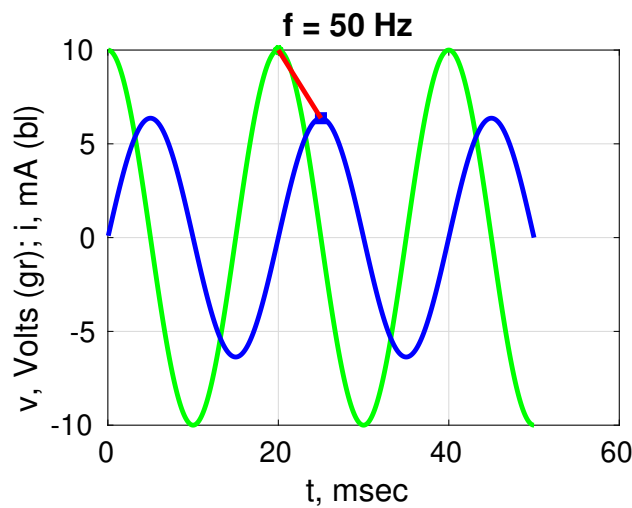

500mH Inductor

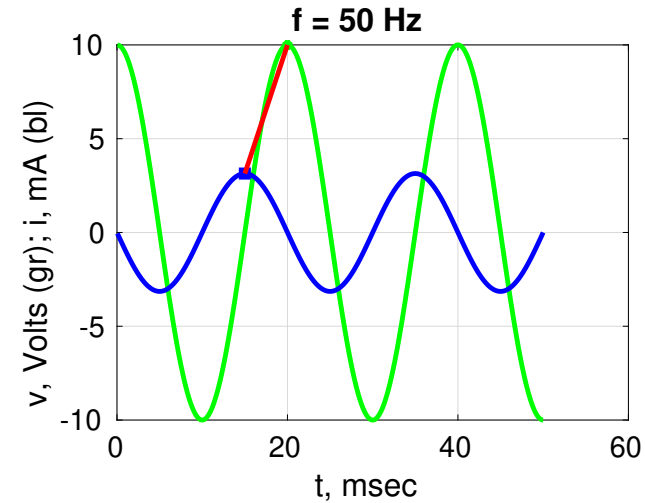

$1\mu\text{F}$  Capacitor

- E for Electromotive Force (Voltage)
- Inductor (ELI)  
E (Voltage) Leads I (Current):  
Peak of Voltage (Green) Before Current (Blue)
- Capacitor (ICE)  
I (Current) Leads E (Voltage):  
Peak of Current (Blue) Before Voltage (Green)

# Resistance, Reactance, Impedance

- Resistance

$$Z_R = R \quad \mathbf{V} = \mathbf{I}R$$

- Reactance

$$Z = jX \quad \mathbf{V} = \mathbf{I}jX$$

- Examples

$$Z_C = X_C = \frac{1}{j\omega C} = \frac{-j}{\omega C} \quad Z_L = X_L = j\omega L$$

- Impedance

$$Z = R + jX \quad \mathbf{V} = \mathbf{I}Z$$

# AC Circuits & Steady–State Sinusoids

- Voltage Sources, Current Sources, Resistors

$$v = iR$$

- Voltage Sources, Current Sources, Impedances

$$\mathbf{V} = \mathbf{IZ} = \mathbf{IR} + j\mathbf{IX}$$

- Everything We Learned Before Works
  - Series and Parallel Circuits
  - Voltage and Current Dividers
  - Node and Mesh Analysis
  - Even Op–Amps

- Just Remember the Numbers are Complex

$$i = \operatorname{Re} \left( \mathbf{I}e^{j\omega t} \right) \quad v = \operatorname{Re} \left( \mathbf{V}e^{j\omega t} \right)$$

# Series and Parallel

- Resistors in Series

$$R = R_1 + R_2$$

- Resistors in Parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

- Inductors in Series

$$j\omega L = j\omega L_1 + j\omega L_2$$

- Inductors in Parallel

$$\frac{1}{j\omega L} = \frac{1}{j\omega L_1} + \frac{1}{j\omega L_2}$$

- Capacitors in Series

$$\frac{1}{j\omega C} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}$$

- Capacitors in Parallel

$$\frac{1}{1/j\omega C} = \frac{1}{1/j\omega C_1} + \frac{1}{1/j\omega C_2}$$


- Impedances in Series

$$Z = Z_1 + Z_2$$

- Impedances in Parallel


$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

# Voltage Divider

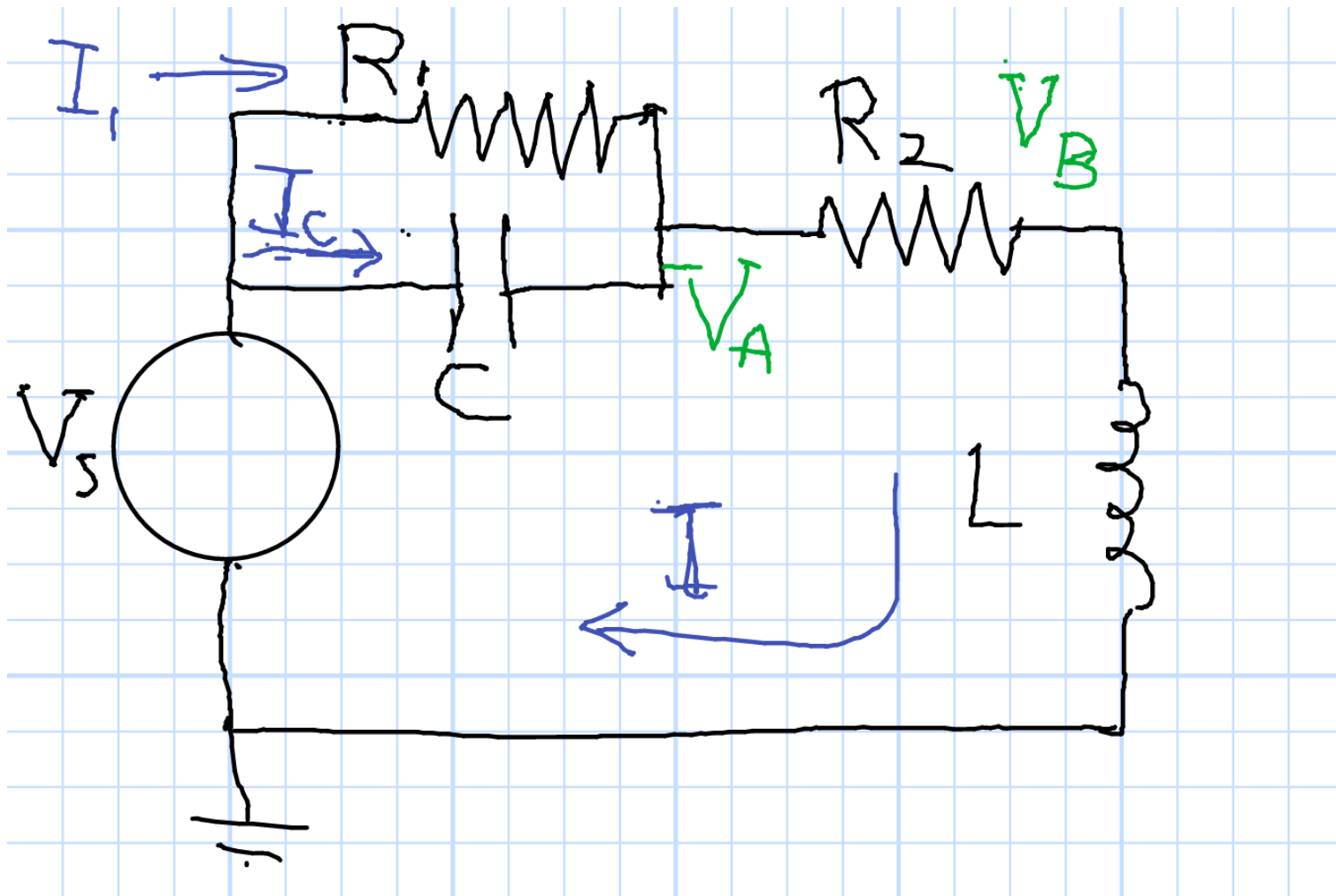

$$R_1 = 1\text{k}\Omega, R_2 = 2\text{k}\Omega, C = 470\text{pF}, L = 3\text{mH}, V = 20\text{V},$$
$$f = 100\text{kHz}$$

# Overall Impedance

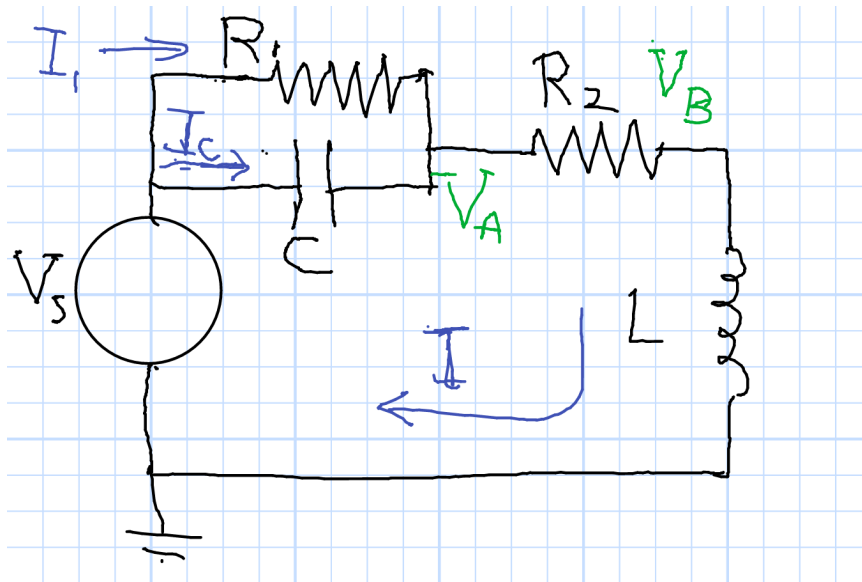

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V = 20\text{V at } f = 100\text{kHz}$$

$$Z = \left( R_1 \parallel \frac{1}{j\omega C} \right) + R_2 + j\omega L$$

$$Z_C = 1 / (1j * \omega * C);$$

$$Z_L = 1j * \omega * L;$$

$$Z_{1C} = 1 / (1/R_1 + 1/Z_C);$$

$$\gg Z = Z_{1C} + R_2 + Z_L$$

$$Z =$$

$$2.9198\text{e}+03 + 1.6133\text{e}+03i$$

$$\gg \text{abs}(Z)$$

$$\text{ans} =$$

$$3.3359\text{e}+03$$


$$\gg \text{angle}(Z) * 180 / \pi$$

$$\text{ans} =$$

$$28.9229$$

$$Z = 3.3\text{k}\Omega \angle 29^\circ$$

# Current

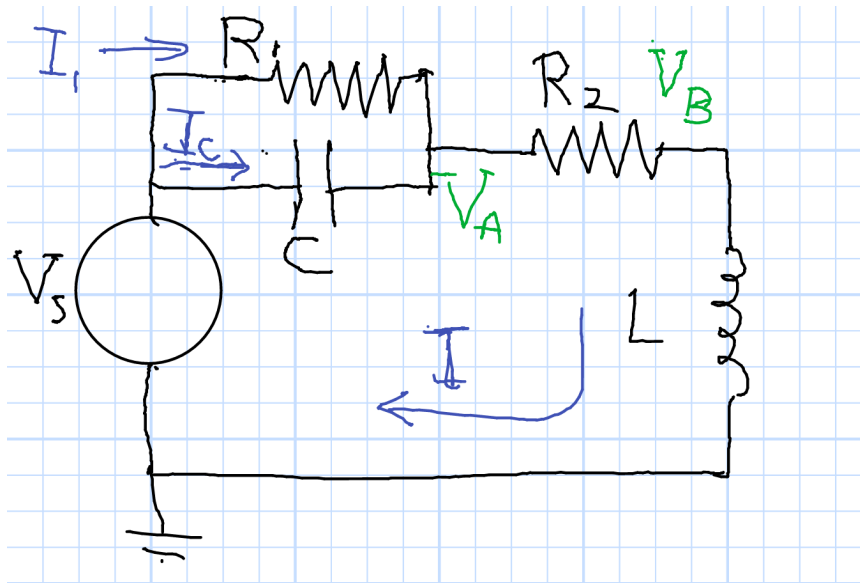

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V = 20\text{V at } f = 100\text{kHz}$$

$$I = \frac{V}{Z} = \frac{20\text{V}}{Z}$$

>> I=V/Z

I =

$$0.0052 - 0.0029i$$

>> abs(I)

ans =

$$0.0060$$

>> angle(I)\*180/pi


ans =

$$-28.9229$$

$$I = 6\text{mA} \angle -29^\circ$$



# Current Divider

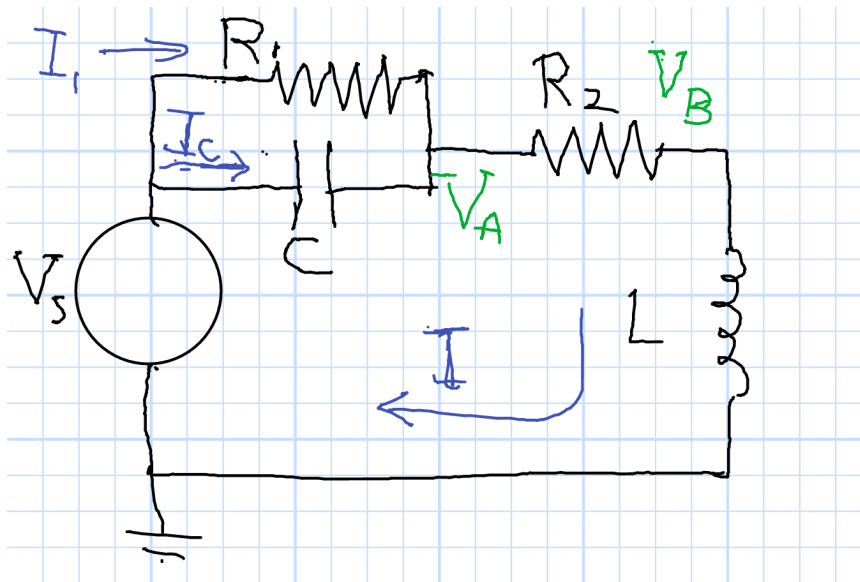

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V = 20\text{V at } f = 100\text{kHz}$$

$$I_C = I \frac{R_2}{R_1 + Z_C}$$

$$I_1 = I \frac{Z_C}{R_1 + Z_C}$$

$$I_C = I * R_2 / (R_1 + Z_C)$$

$$I_C =$$

$$0.0012 + 0.0012i$$

$$I_1 = I * Z_C / (R_1 + Z_C)$$

$$I_1 =$$

$$0.0040 - 0.0041i$$

$$I_{\text{check}} = I_C + I_1, \quad I$$


$$I_{\text{check}} =$$

$$0.0052 - 0.0029i$$

$$I =$$

$$0.0052 - 0.0029i$$

# Voltage Divider

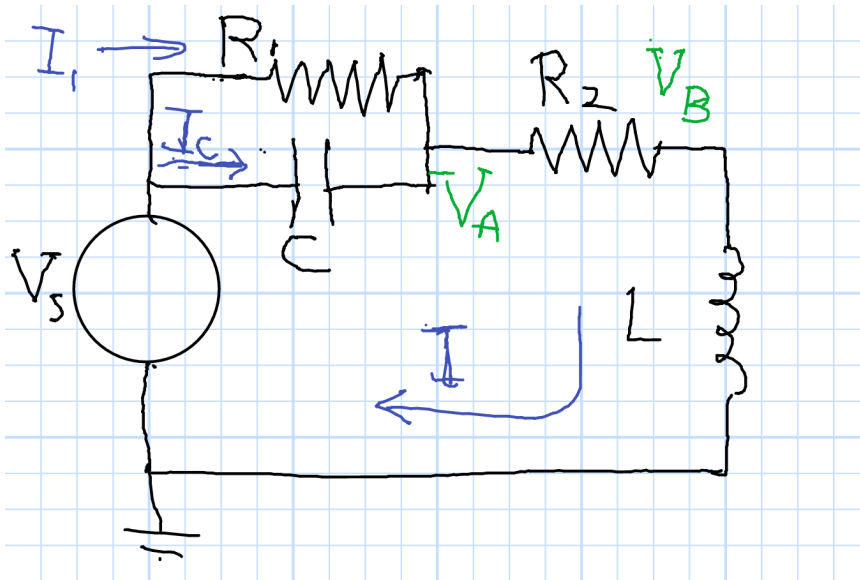

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V = 20\text{V} \text{ at } f = 100\text{kHz}$$

$$V_A = V \frac{R_2 + j\omega L}{Z}$$

$$\gg V_A = V * (R_2 + Z_L) / Z$$

$$V_A =$$

$$15.9609 + 4.0924i$$

$$\gg \text{abs}(V_A), \text{angle}(V_A) * 180 / \pi$$

$$\text{ans} =$$

$$16.4772$$

$$\text{ans} =$$


$$14.3809$$

$$V_A = 16.4\text{V} \angle 14^\circ$$

$$V_B = V \frac{j\omega L}{Z}$$

$$= 11.3\text{V} \angle 61^\circ$$

# Power

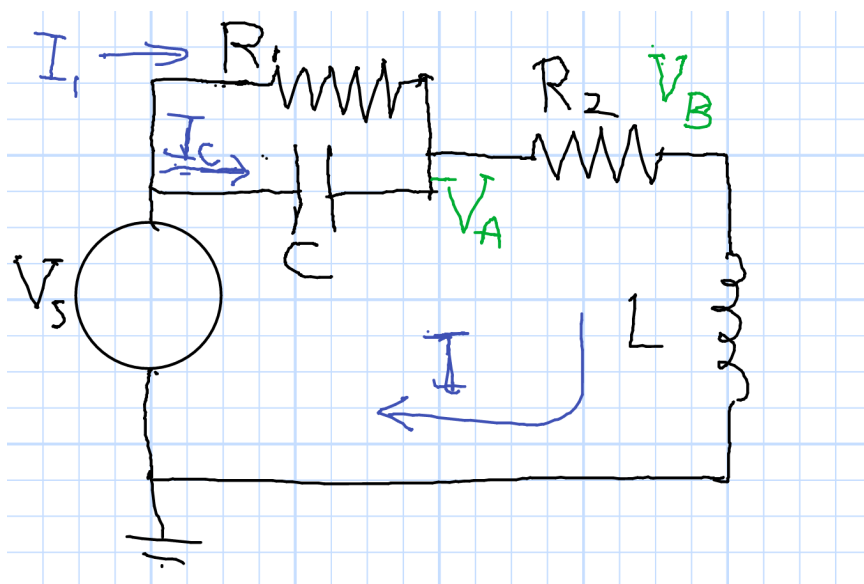

$$R_1 = 1\text{k}\Omega \quad R_2 = 2\text{k}\Omega$$

$$C = 470\text{pF} \quad L = 3\text{mH}$$

$$V = 20\text{V} \text{ at } f = 100\text{kHz}$$

Capacitor:  $V_C = V_S - V_A$





$$v_c = \text{Re } V_C e^{j\omega t} \quad i_c = \text{Re } I_C e^{j\omega t}$$

$$p_c = v_c i_c$$

```
>> t=[0:0.001:1]*2/f;
>> vc=real(VC*exp(1j*omega*t));
ic=real(IC*exp(1j*omega*t));
pc=vc.*ic;
figure;plot(t*1e6,vc,'g',...
t*1e6,ic*1e3,'b',...
t*1e6,pc*1e3,'r',...
t([1,end])*1e6,...
real(VC*conj(IC))/2*[1,1]*1e3,...
'r');
```

grid on;

# Power Summary

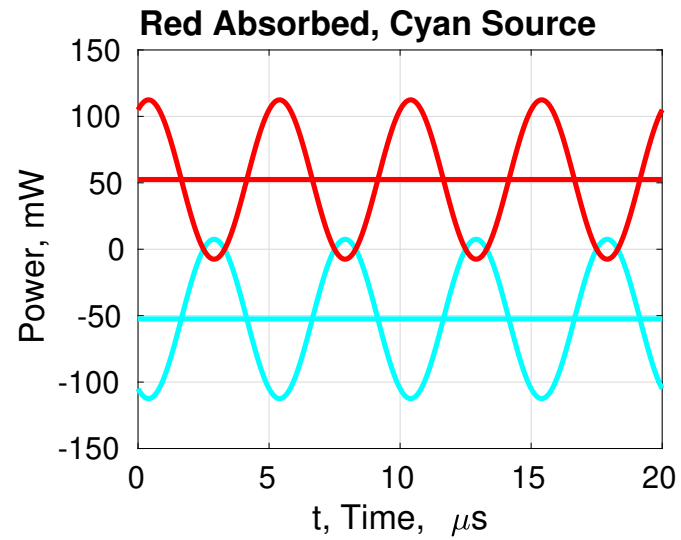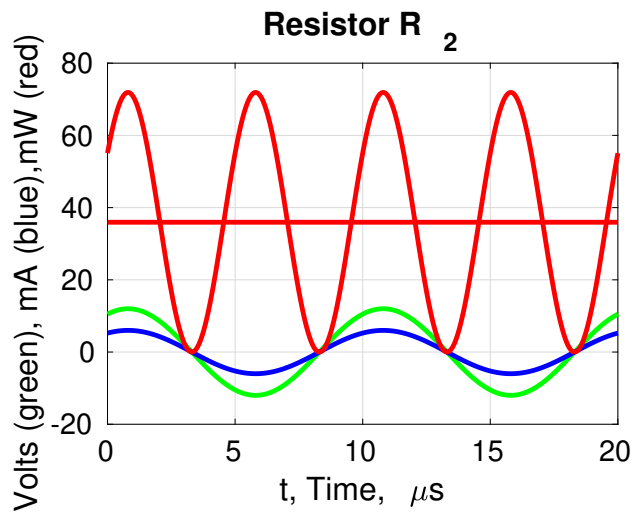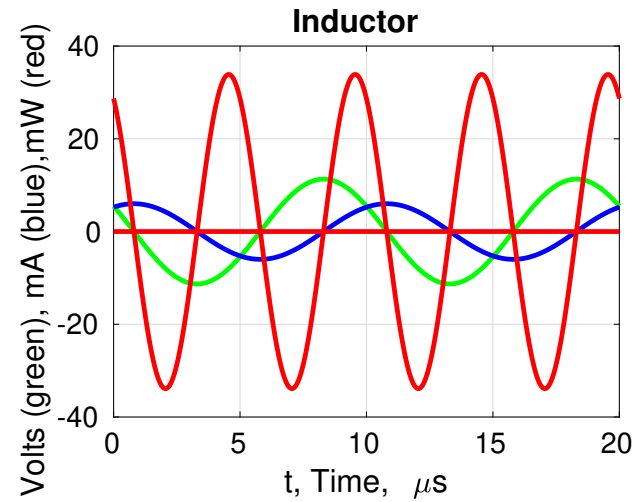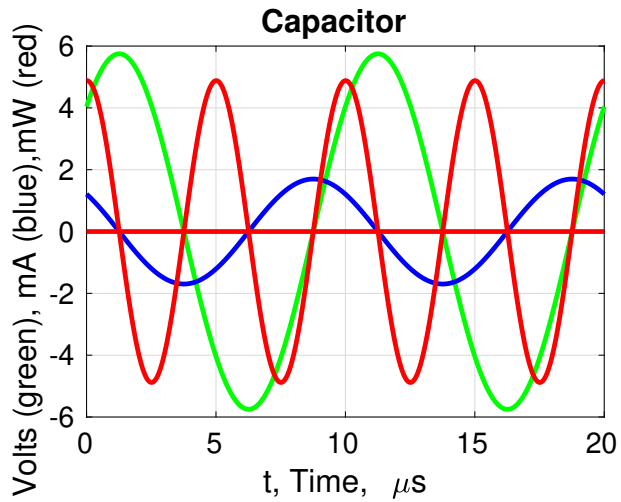

Note That Source Absorbs Power at Times.

# Resistive and Reactive Power

- Power Equations

$$v = \operatorname{Re} \left( V e^{j\omega t} \right) \quad i = \operatorname{Re} \left( I e^{j\omega t} \right) \quad p = vi$$

- Complex Notation

$$v = \frac{V}{2} e^{j\omega t} + \frac{V^*}{2} e^{-j\omega t} \quad i = \frac{I}{2} e^{j\omega t} + \frac{I^*}{2} e^{-j\omega t}$$

$$p = \frac{VI^*}{4} + \frac{V^*I}{4} + \frac{VI}{4} e^{j2\omega t} + \frac{V^*I^*}{4} e^{-j2\omega t}$$

$$p = \operatorname{Re} \left( \frac{VI^*}{2} \right) + \frac{|VI|}{2} \cos(2\omega t + \phi)$$

$$\phi = \operatorname{Angle} \left( \frac{VI}{2} \right)$$

# Average Power

- Previous Page

$$p = \operatorname{Re} \left( \frac{VI^*}{2} \right) + \frac{|VI|}{2} \cos(2\omega t + \phi)$$

$$\phi = \operatorname{Angle} \left( \frac{VI}{2} \right)$$

- Time Average (over whole number of cycles)

$$\bar{p} = \operatorname{Re} \left( \frac{VI^*}{2} \right) = \frac{|VI|}{2} \cos \phi$$

- RMS Voltage and Current

$$\bar{p} = \frac{|V|}{\sqrt{2}} \frac{|I|}{\sqrt{2}} \cos \phi = V_{RMS} I_{RMS} \cos \phi$$

# Resistive and Reactive Power

- Previous Page

$$p = \operatorname{Re} \left( \frac{VI^*}{2} \right) + \frac{|VI|}{2} \cos(2\omega t + \phi) \quad \bar{p} = \operatorname{Re} \left( \frac{VI^*}{2} \right)$$

- Complex Power

$$\mathbf{S} = \frac{\mathbf{V}\mathbf{I}^*}{2}$$


- Resistive Power

$$P = \operatorname{Re} \mathbf{S}$$

- Reactive Power

$$Q = \operatorname{Im} \mathbf{S}$$

# Power Factor

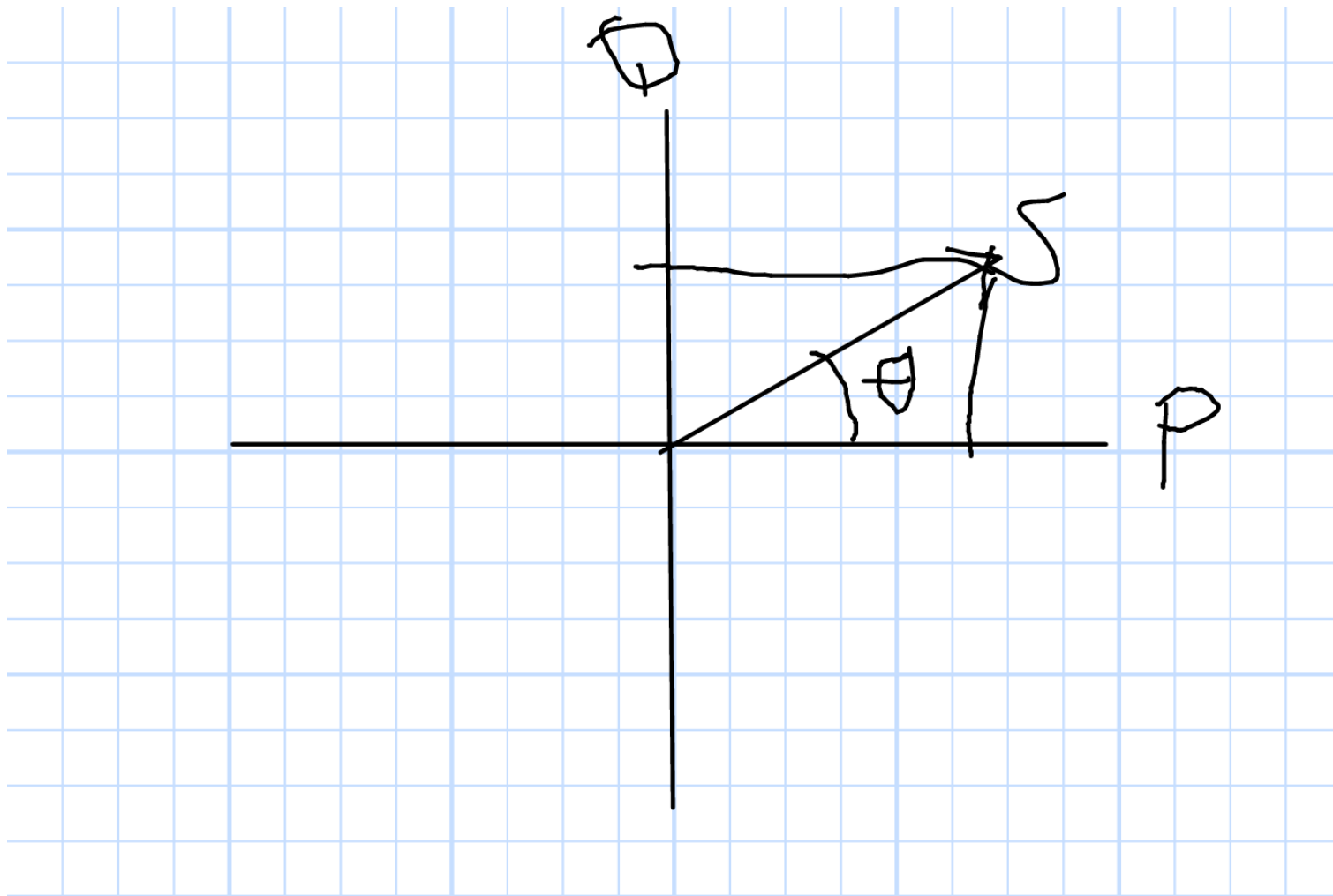

$S = P + jQ$ . Power Factor:  $\cos \theta$

$P$  Watts,  $S$  Volt-Amps = VA,  $Q$ , Volt-Amps-Reactive = VAR



# Generators



150 kVA ([exmod.uk](http://exmod.uk))



600 MVA ([nuclearstreet.com](http://nuclearstreet.com))






1KVA Portable Petrol Generator

1 kVA [indiamart.com](http://indiamart.com)



1177MVA ([transformer-technology.com](http://transformer-technology.com))

# Power Summary

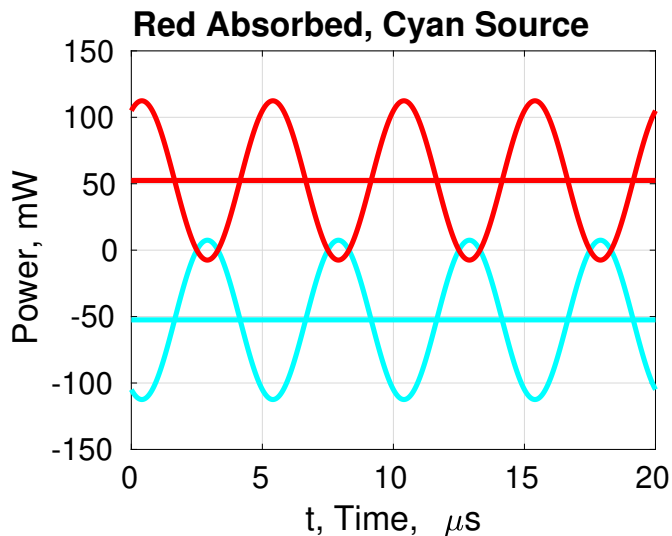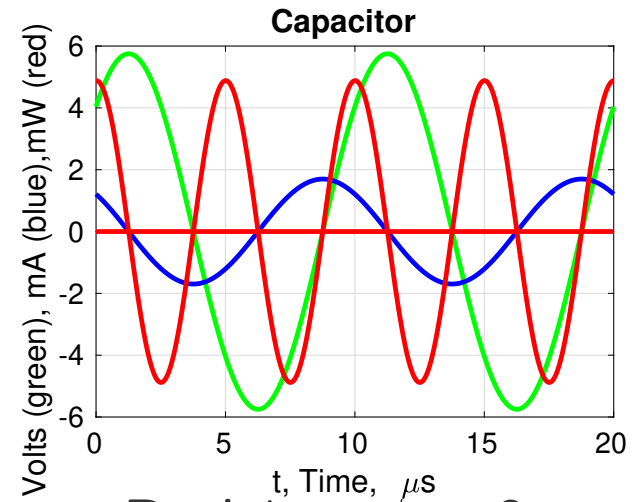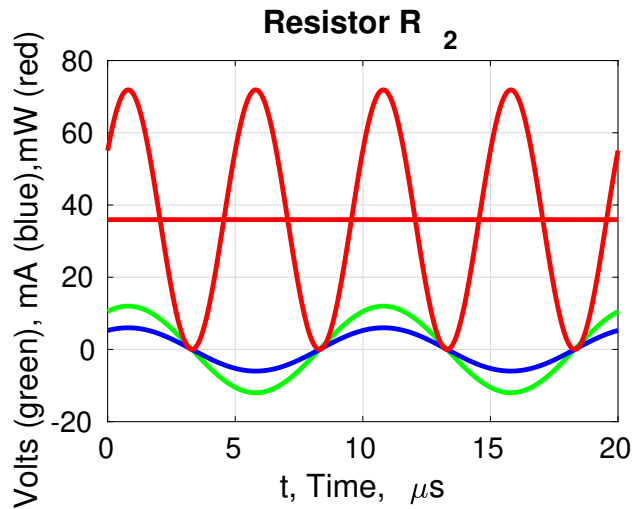

- Resistor;  $\phi = 0$

$$\bar{p} = v_{rms}i_{rms} = \frac{v_{rms}^2}{R}$$

- Cap/Inductor;  $\phi = \pm 90^\circ$

$$\bar{p} = 0$$


- General Sinusoids

$$\bar{p} = v_{rms}i_{rms} \cos \phi$$
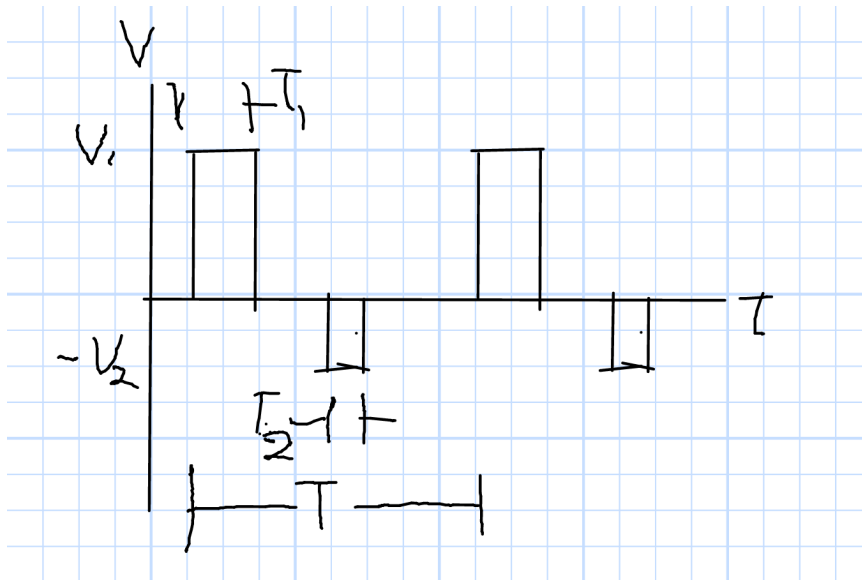
# RMS More Generally

$$p = \frac{v^2}{R} \quad \bar{p} = \frac{v_{rms}^2}{R} \quad \bar{p} = \frac{w(t : t + T)}{T}$$

$$\bar{p} = \frac{1}{T} \int_t^{t+T} \frac{v^2}{R} dt$$



$$\bar{p} = \frac{1}{RT} (v_1^2 t_1 - v_2^2 t_2)$$

$$\bar{p} = \frac{v_{rms}^2}{R}$$

$$v_{rms}^2 = \frac{v_1^2 t_1 - v_2^2 t_2}{T}$$

# Voltage Readings

- Equations

$$v = \operatorname{Re} \left( V e^{j\omega t} \right) = 20V \cos \omega t$$

$$v_{max} = |V| \quad v_{min} = -|V|$$


- Volt Meter Measures RMS

$$v_{rms} = \frac{|V|}{\sqrt{2}} = 14V$$

- Oscilloscope Measures Peak-to-Peak

$$v_{pp} = 2|V| = 40V$$


# Reading an Oscilloscope

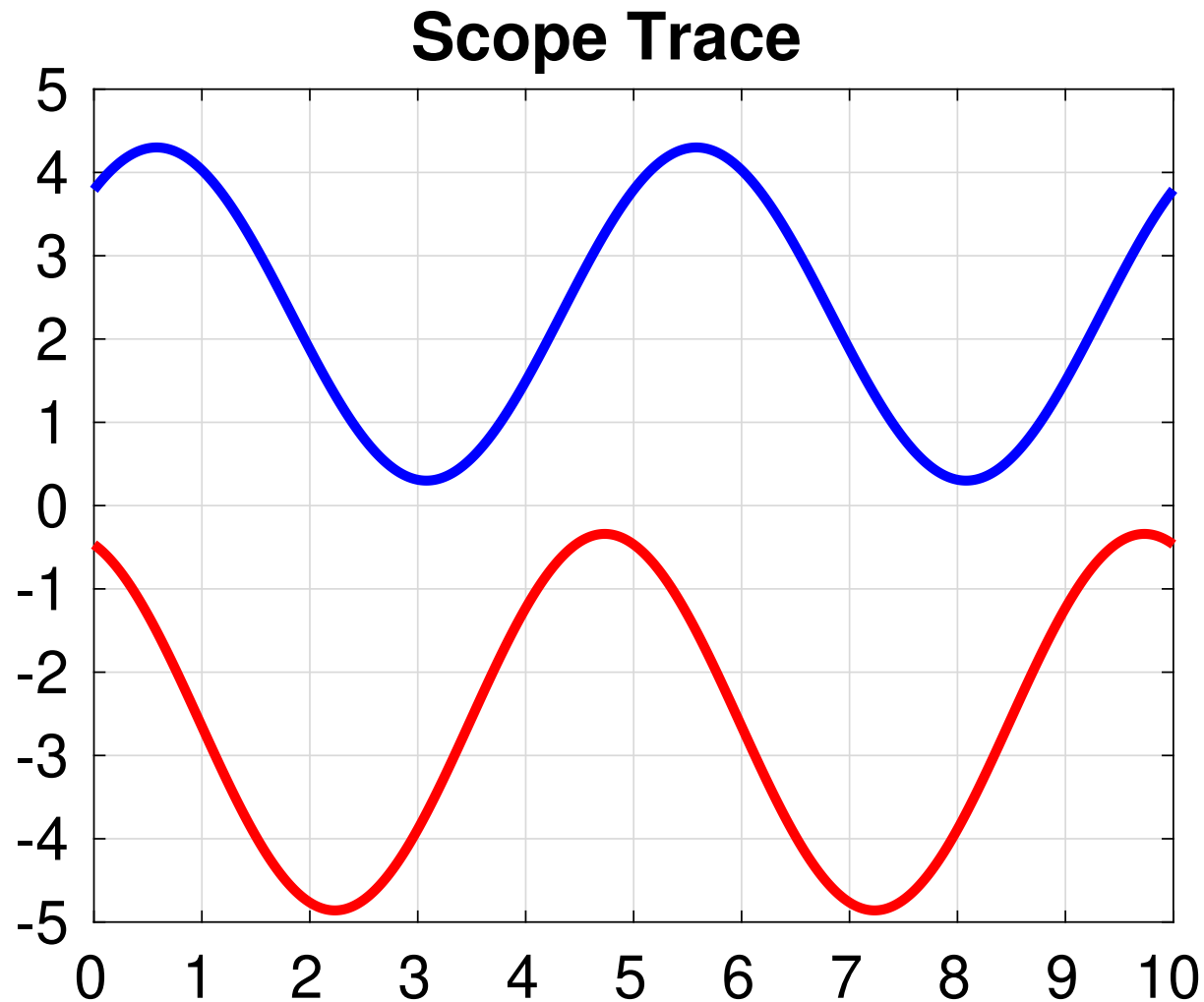

Ch1:  $V$  10V/cm   Ch2:  $V_B$ , 5V/cm   Time base  $20\mu\text{s}$


# Untriggered Oscilloscope

## Untriggered Scope Trace

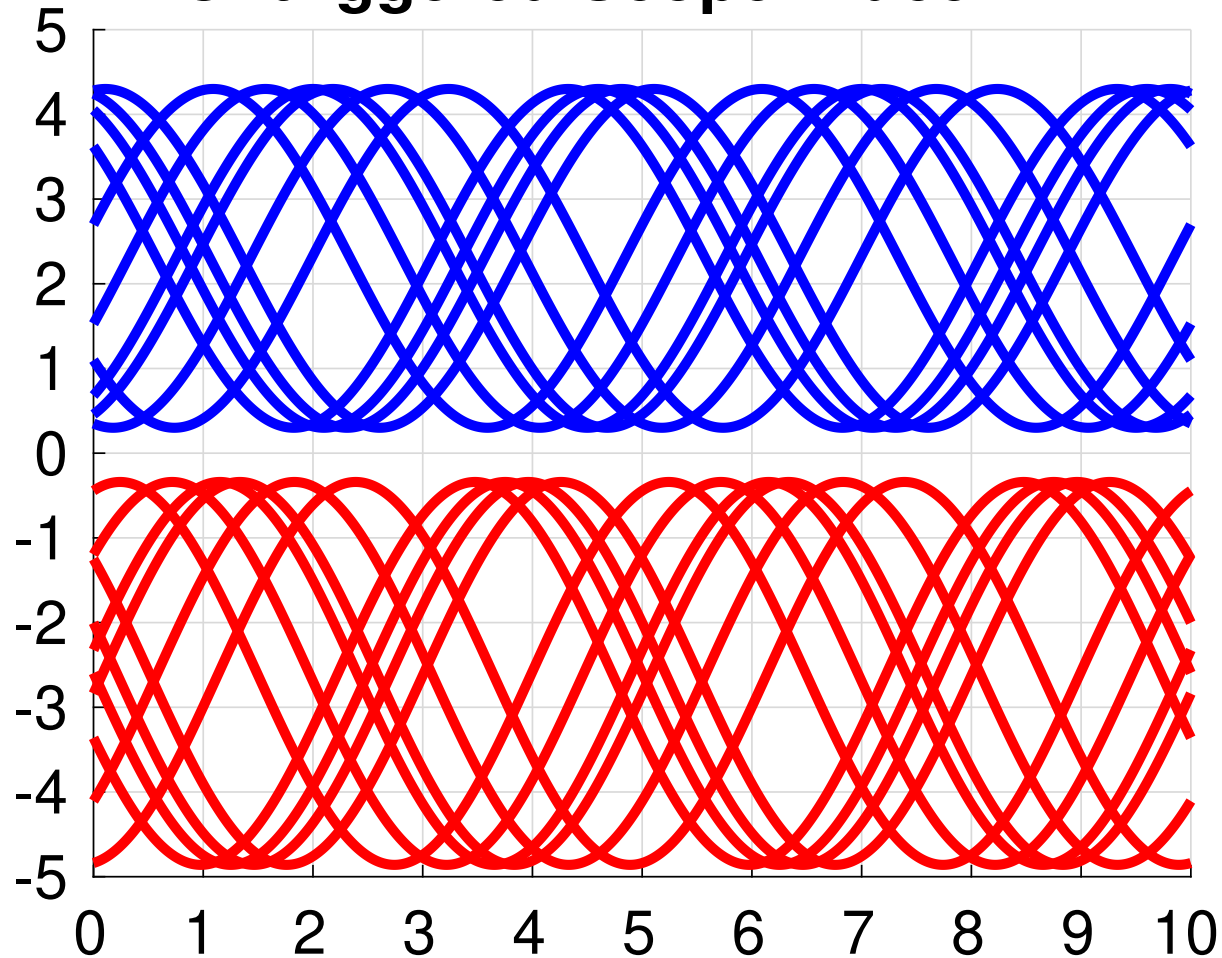


Ch1:  $V$  10V/cm Ch2:  $V_B$ , 5V/cm Time base  $20\mu\text{s}$   
Trigger Mode: Auto

# Channel-1 Trigger

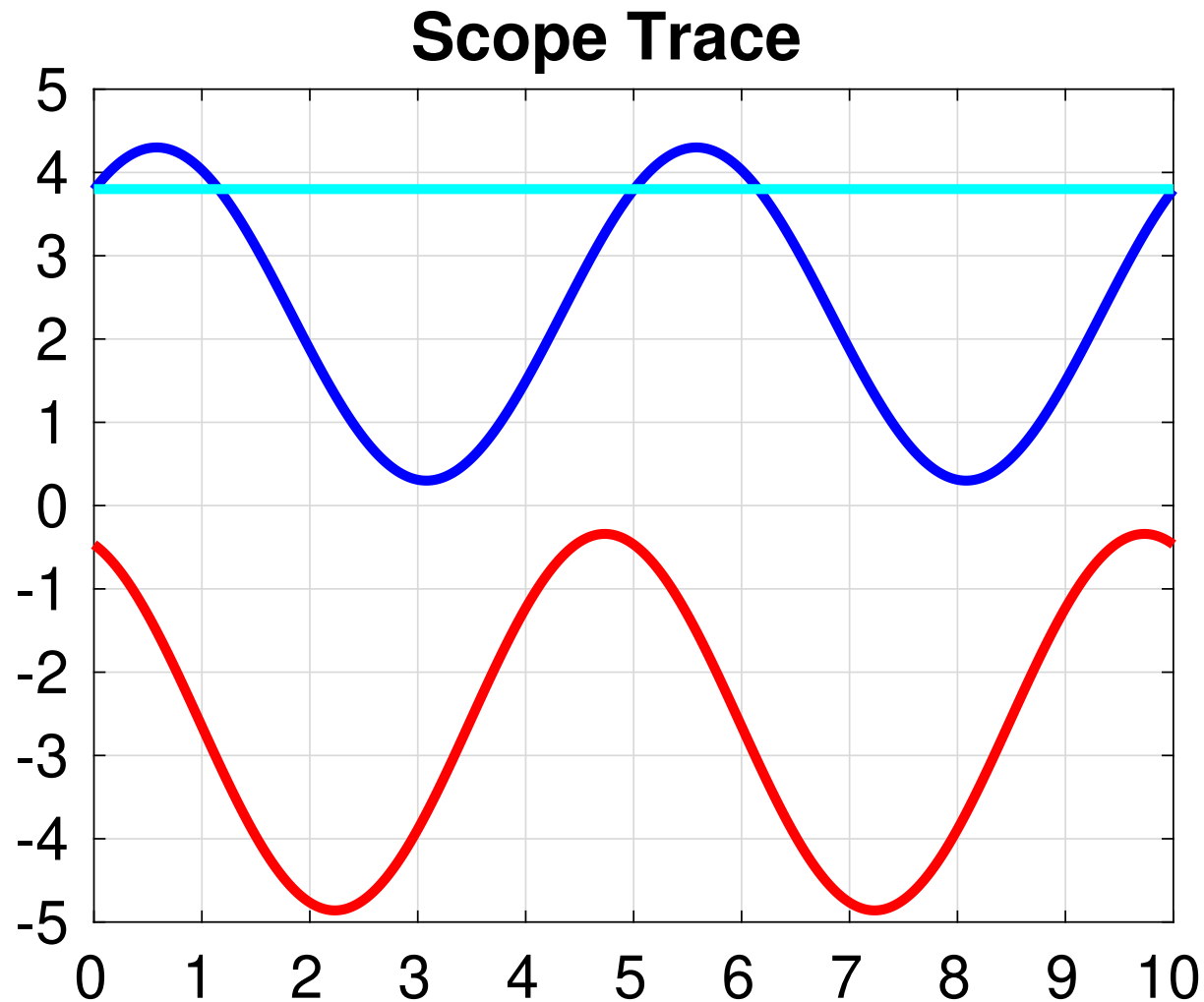

Ch1:  $V$  10V/cm Ch2:  $V_B$ , 5V/cm Time base  $20\mu\text{s}$   
Trigger Ch1, 15V, +slope


# Reading the Voltage

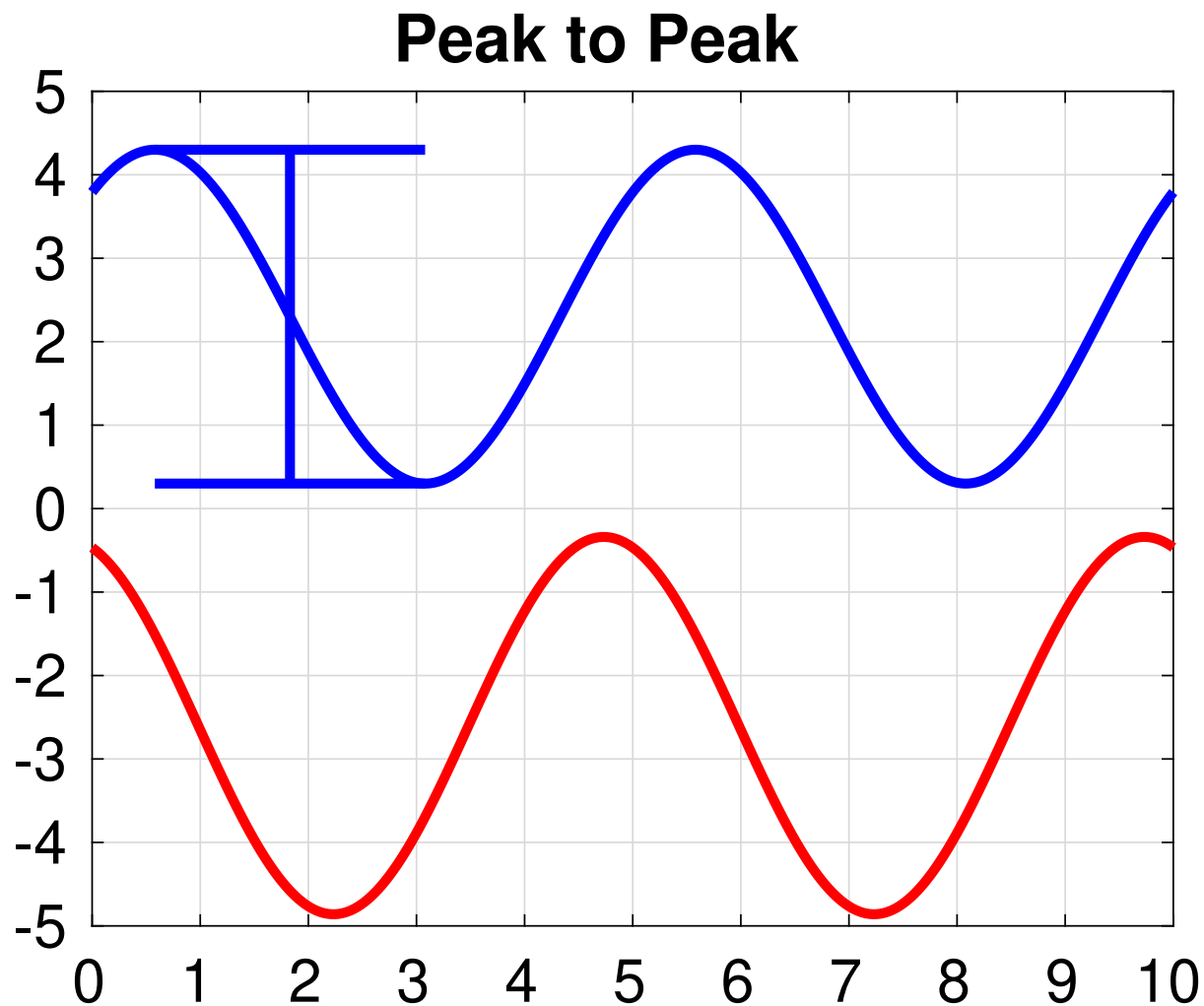

Ch1:  $V$ ,  $40V_{pp}/(10V/cm)$  Ch2:  $V_B$ ,  $22.6V_{pp}/(5V/cm)$




# Reading the Period

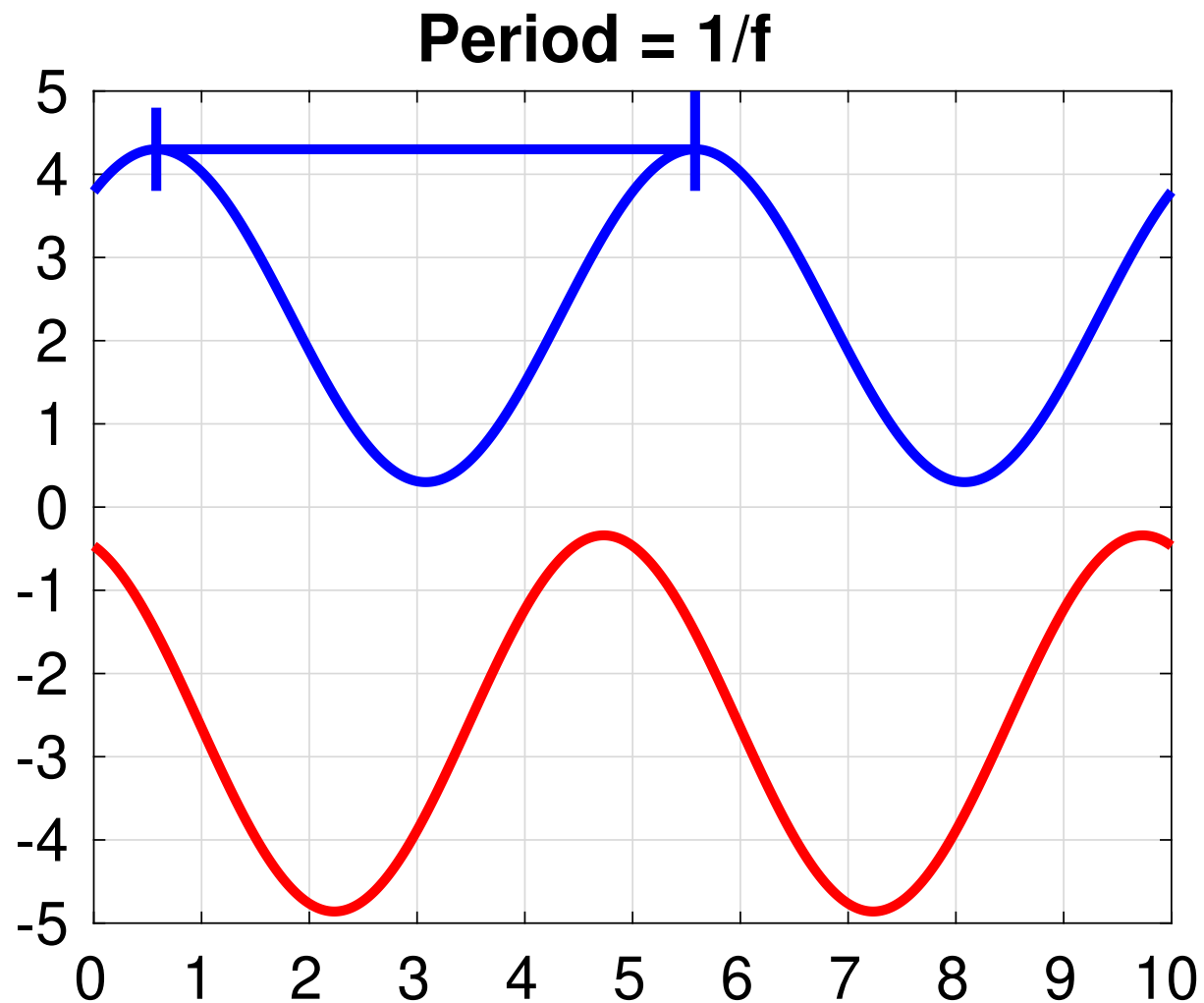

$$T = 1/f; 10\mu\text{s}/2\mu\text{s}/\text{cm}$$

# Reading the Phase Difference

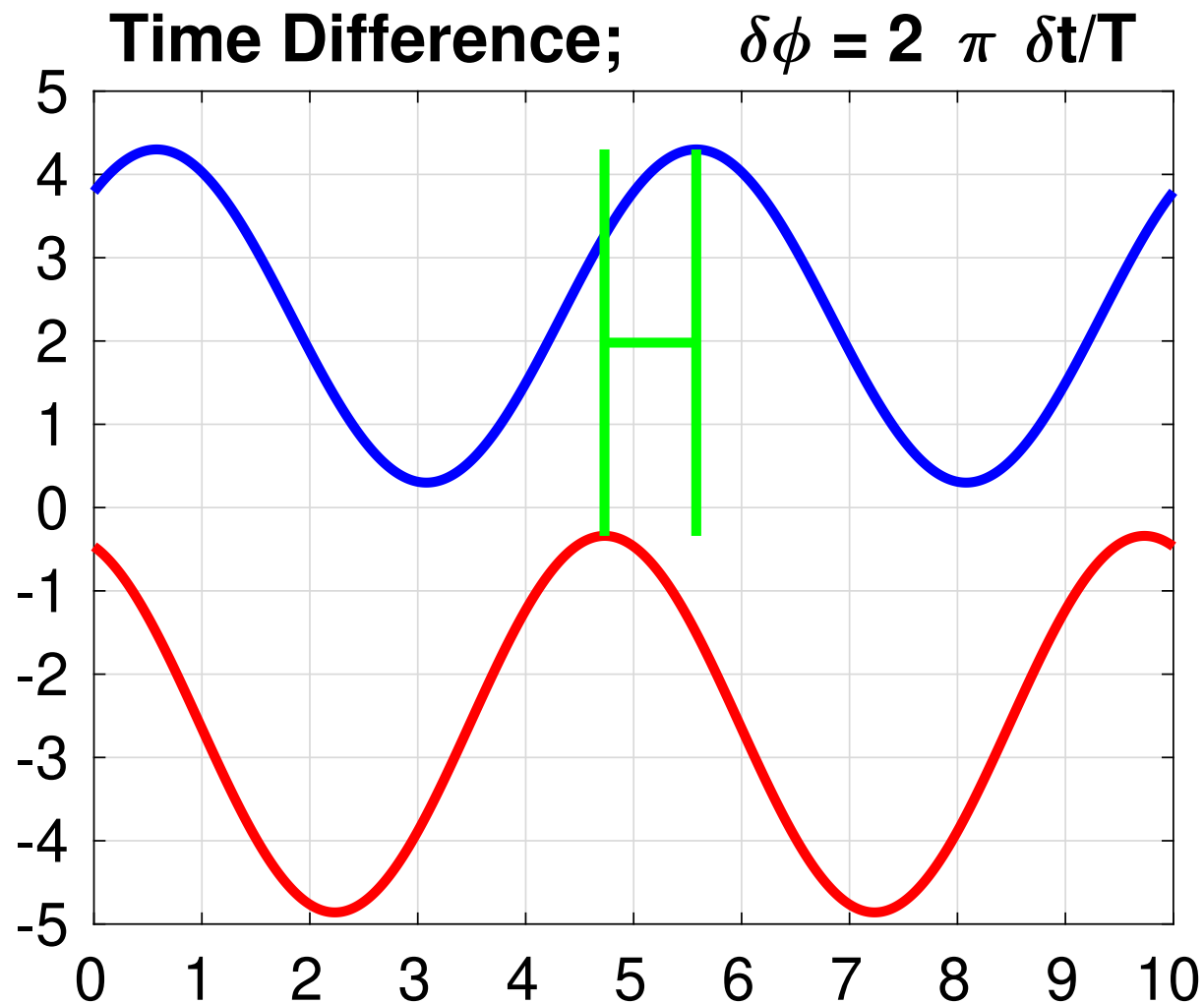


$$\delta t = T \frac{\delta\phi}{2\pi} = T \frac{\delta\phi}{360^\circ}; 1.7\mu\text{s}/2\mu\text{s}/\text{cm}$$

Trigger Ch1, 15V, +slope

# Questions


How much does all of this change in the current circuit if the input to the oscilloscope is  $1\text{M}\Omega$ ?

How about if it is  $50\Omega$ ?

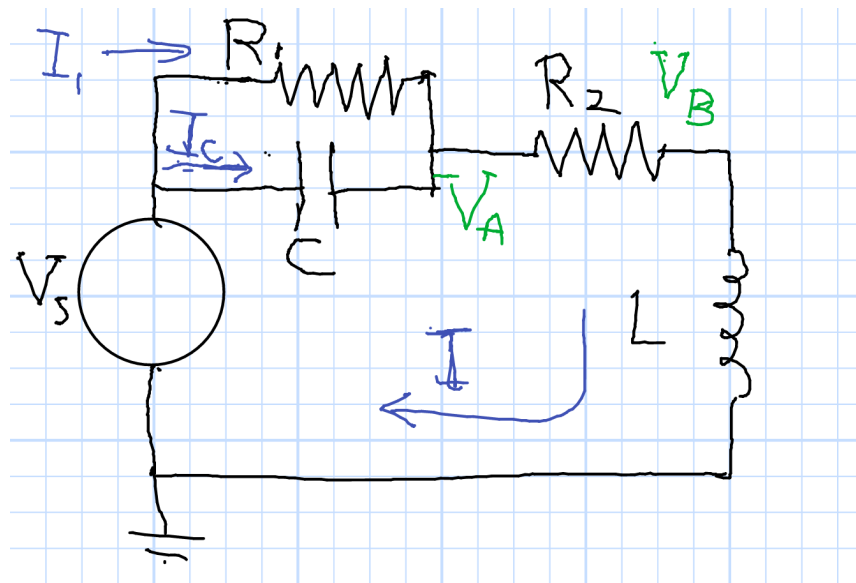


$$R_1 = 1\text{k}\Omega, R_2 = 2\text{k}\Omega, Z_C = -j3.4\text{k}\Omega, Z_L = j1.9\text{k}\Omega, \\ V = 20\text{V}, f = 100\text{kHz}$$

# AC-Coupled Op-Amp Circuit

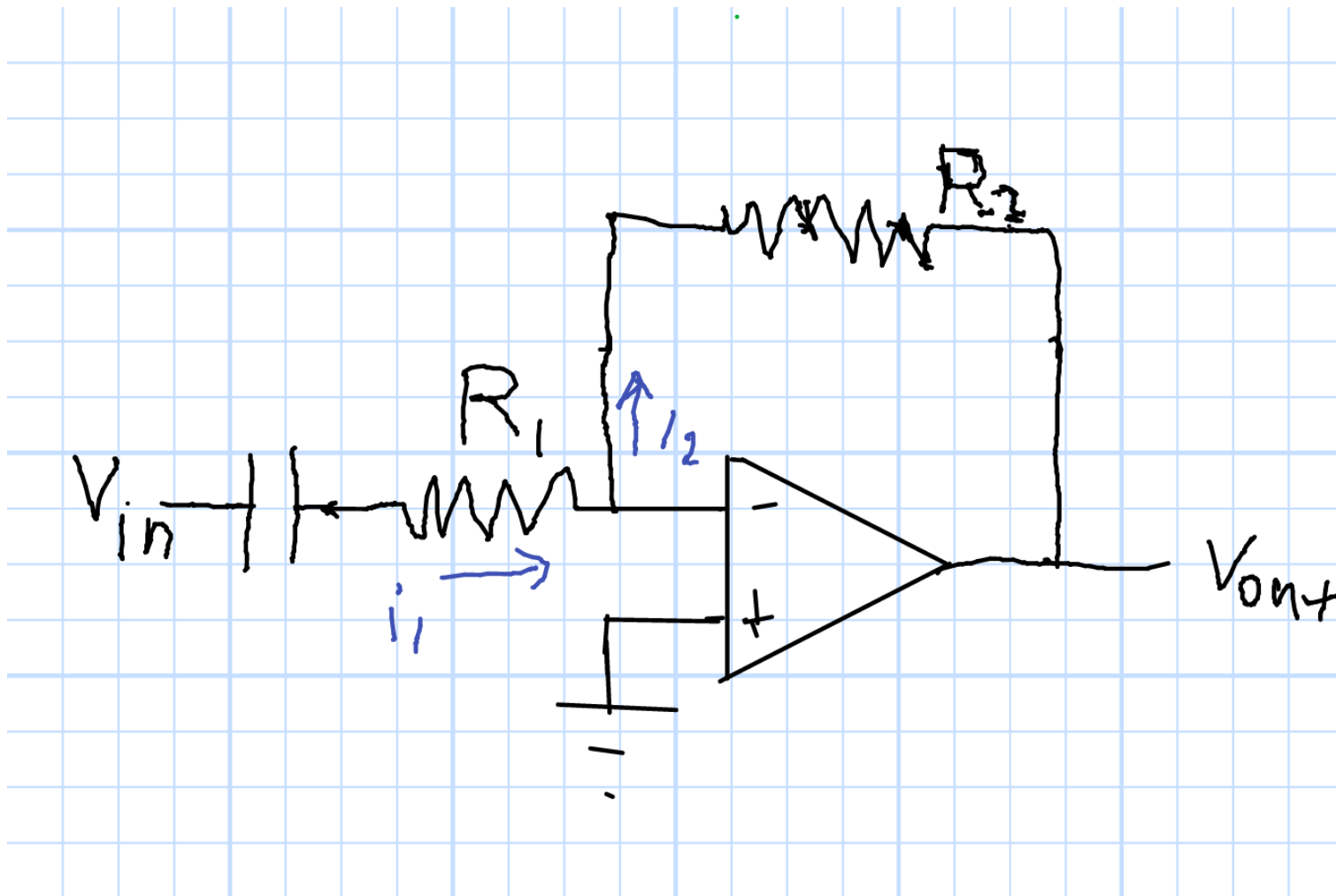

# AC-Coupled Amplifier Solution

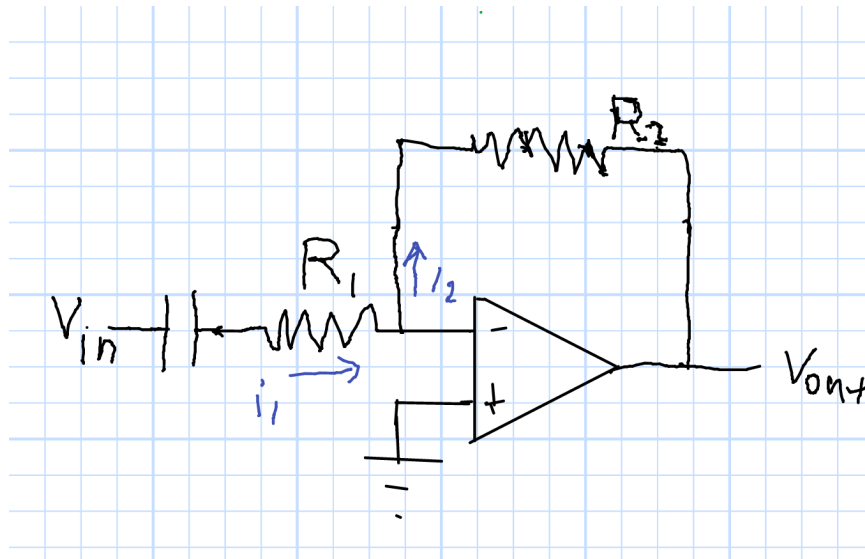


$$A_v = -\frac{R_2}{R_1 + \frac{1}{j\omega C}}$$

$$R_1 = 1\text{k}\Omega \quad R_2 = 10\text{k}\Omega$$

$$C = 1\mu\text{F} \quad X_C = \frac{1}{j2\pi f C}$$

$$X_C = -160\text{k}\Omega \text{ at } 1\text{Hz}$$
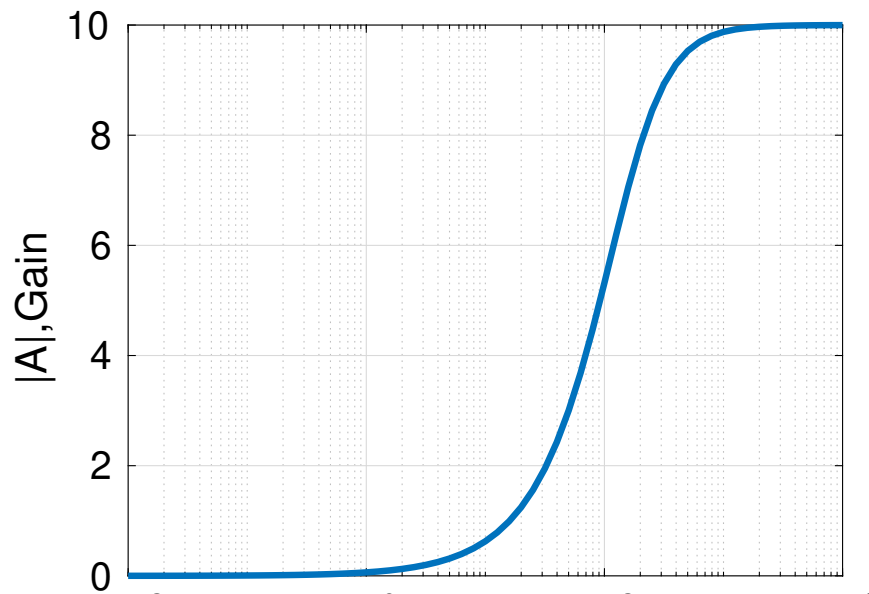
$$X_C = -160\Omega \text{ at } 1\text{kHz}$$



```
>> f=10.^[-2:0.1:4];
>> R1=1000;R2=10e3;C=1e-6;
>> A=-R2./(R1+1./(1j*2*pi*f*C));
>> figure;semilogx(f,abs(A));
grid on;
>> xlabel('f, Hz');
```