

# Electrical Engineering

## Week 12


Charles A. DiMarzio  
EECE-2210  
Northeastern University

Nov 2021

# Week 12 Agenda: Equivalent Circuits Again


- Thévenin Equivalent
- Norton Equivalent
- Power Transfer

# Some AC Circuit

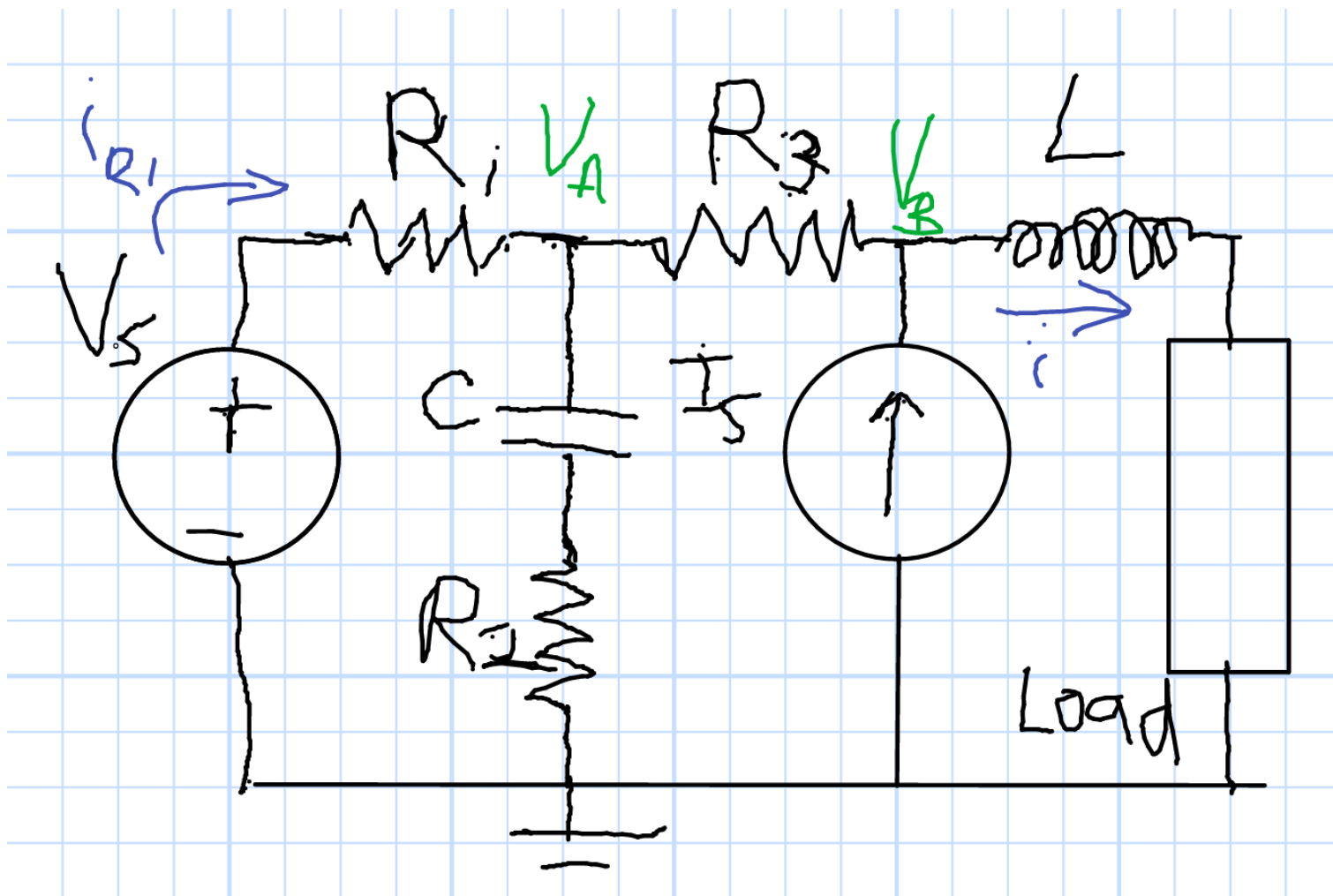

$$R_1 = 1\text{k}\Omega, R_2 = 3\text{k}\Omega, R_3 = 2\text{k}\Omega, C = 10\text{nF}, L = 80\text{mH}, \\ f = 10\text{kHz}, V_S = 5\text{V}, I_S = 10\text{mA}$$

# Open-Circuit Voltage (1)

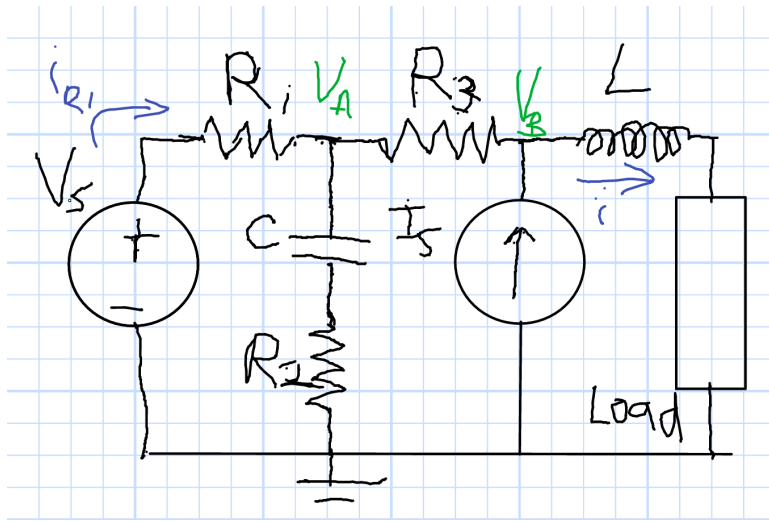

$$R_1 = 1\text{k}\Omega, R_2 = 3\text{k}\Omega,$$

$$R_3 = 2\text{k}\Omega, C = 10\text{nF},$$

$$L = 80\text{mH},$$

$$f = 10\text{kHz}$$

$$V_S = 5\text{V}, I_S = 10\text{mA}$$

- Open Circuit

$$Z_{load} \rightarrow \infty$$

- No Current in  $L$
- Inbound Current at One Node

$$\frac{V_S - V_A}{R_1} + I_S - \frac{V_A}{R_2 + \frac{1}{j\omega C}} = 0$$

$$V_A \left( \frac{1}{R_2 + \frac{1}{j\omega C}} + \frac{1}{R_1} \right) = \frac{V_S}{R_1} + I_S$$


- Result

$$V_A = 11.7625 + 1.2881j$$

- Check Inbound Current

$$\approx -2 \times 10^{-18} + 2 \times 10^{-18}j$$

# Open-Circuit Voltage (2)

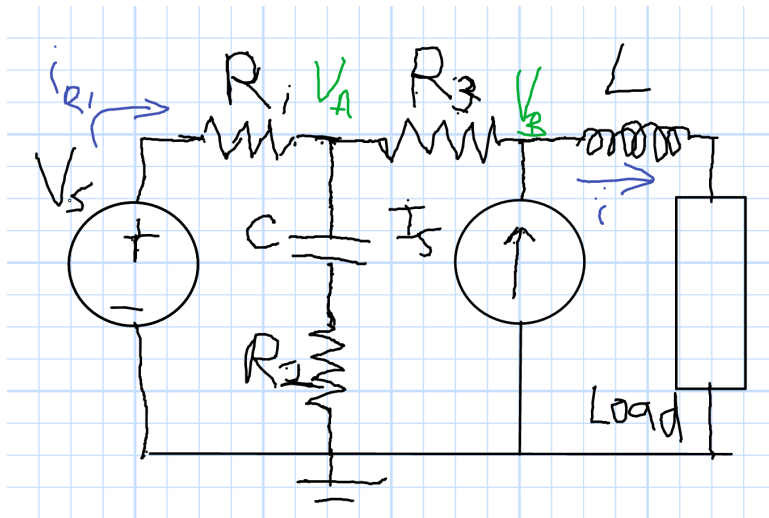

$R_1 = 1\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$ ,  
 $R_3 = 2\text{k}\Omega$ ,  $C = 10\text{nF}$ ,  
 $L = 80\text{mH}$ ,  
 $f = 10\text{kHz}$   
 $V_S = 5\text{V}$ ,  $I_S = 10\text{mA}$

- Open Circuit

$$Z_{load} \rightarrow \infty$$

- Previous Page


$$V_A = 11.7625 + 1.2881j$$

$$11.83\text{V} \angle -6.25^\circ$$

$$V_{OC} = V_A + I_S R_3 = 31.8 - 1.29j$$

$$= 31.8\text{V} \angle -2.3^\circ$$

# Short-Circuit Current

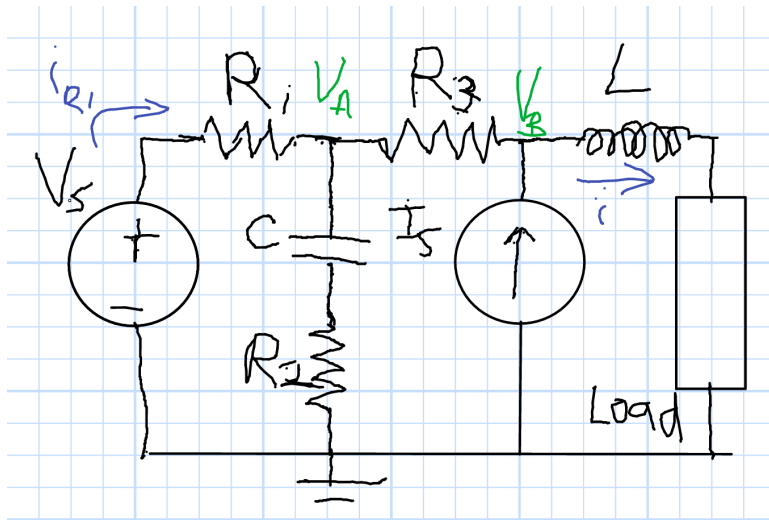


$R_1 = 1\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$ ,  
 $R_3 = 2\text{k}\Omega$ ,  $C = 10\text{nF}$ ,  
 $L = 80\text{mH}$ ,  
 $f = 10\text{kHz}$   
 $V_S = 5\text{V}$ ,  $I_S = 10\text{mA}$

- Short Circuit

$$Z_{load} = 0$$

- Two Nodes (Oh No!)
- Try Superposition

# Short the Voltage Source

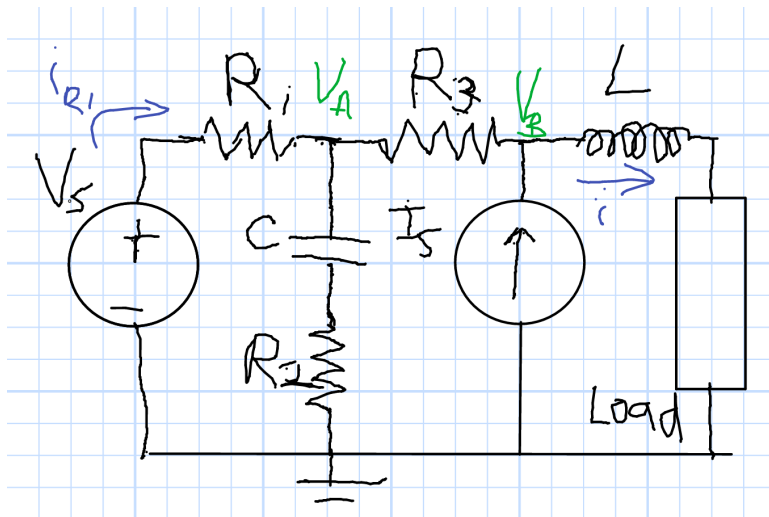

$R_1 = 1\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$ ,  
 $R_3 = 2\text{k}\Omega$ ,  $C = 10\text{nF}$ ,  
 $L = 80\text{mH}$ ,  
 $f = 10\text{kHz}$   
 $V_S = 5\text{V}$ ,  $I_S = 10\text{mA}$

- Short Circuit

$$V_S = 0$$

- Current Source Sees  $Z_1$

$$Z_1 = L \parallel \{R_3 + [R_1 \parallel (R_2 + Z_C)]\}$$

- Voltage


$$V_B = I_S Z_1$$

- Current Contribution

$$I_{1sc} = \frac{V_B}{Z_L}$$

$$I_{1sc} = 2.3\text{mA} - 4.4j\text{mA}$$

# Open the Current Source

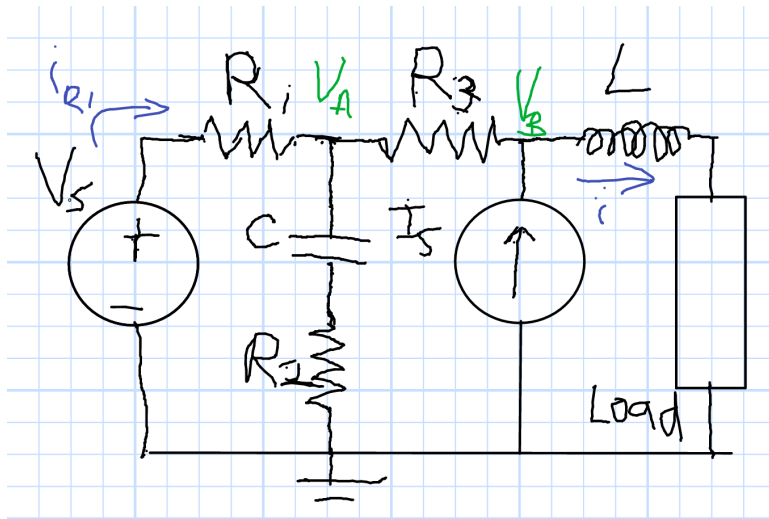

$R_1 = 1\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$ ,  
 $R_3 = 2\text{k}\Omega$ ,  $C = 10\text{nF}$ ,  
 $L = 80\text{mH}$ ,  
 $f = 10\text{kHz}$   
 $V_S = 5\text{V}$ ,  $I_S = 10\text{mA}$

- Open Circuit

$$I_S = 0$$

- Voltage Source Sees  $Z_2$

$$Z_2 = R_1 + (Z_C + R_2) \parallel (R_3 + Z_L)$$

$$I_{R1} = \frac{V_S}{Z_2}$$


- Current Contribution (Divider)

$$I_{2sc} = I_{R1} \frac{Z_C + R_2}{(Z_C + R_2)(R_3 + Z_L)}$$

$$I_{2sc} = 270\mu\text{A} + 640j\mu\text{A}$$



# Superposition Result for $I_{sc}$

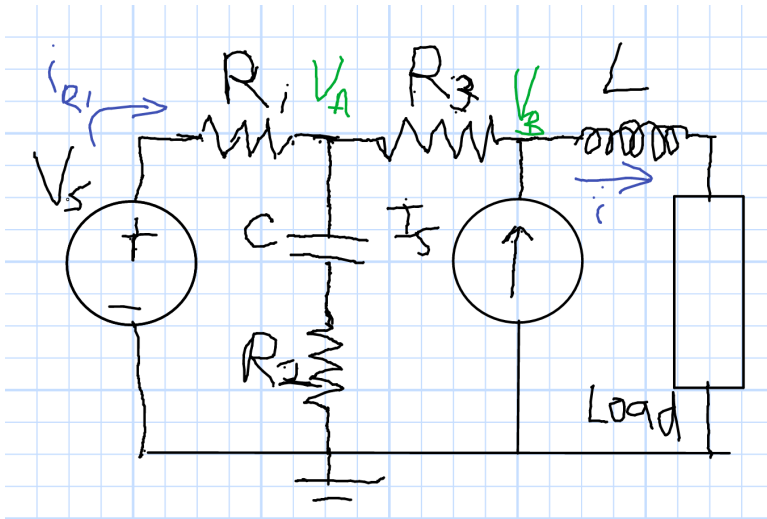

$R_1 = 1\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$ ,  
 $R_3 = 2\text{k}\Omega$ ,  $C = 10\text{nF}$ ,  
 $L = 80\text{mH}$ ,  
 $f = 10\text{kHz}$   
 $V_S = 5\text{V}$ ,  $I_S = 10\text{mA}$

- Current Source Alone

$$I_{1sc} = 2.3\text{mA} - 4.4j\text{mA}$$

- Voltage Source Alone

$$I_{2sc} = 270\mu\text{A} + 640j\mu\text{A}$$


- Superposition

$$I_{sc} = I_{1sc} + I_{2sc}$$

$$I_{sc} = 2.6\text{mA} - 5.0j\text{mA}$$

$$I_{sc} = 5.6\text{mA} \angle -63^\circ$$

# Impedance

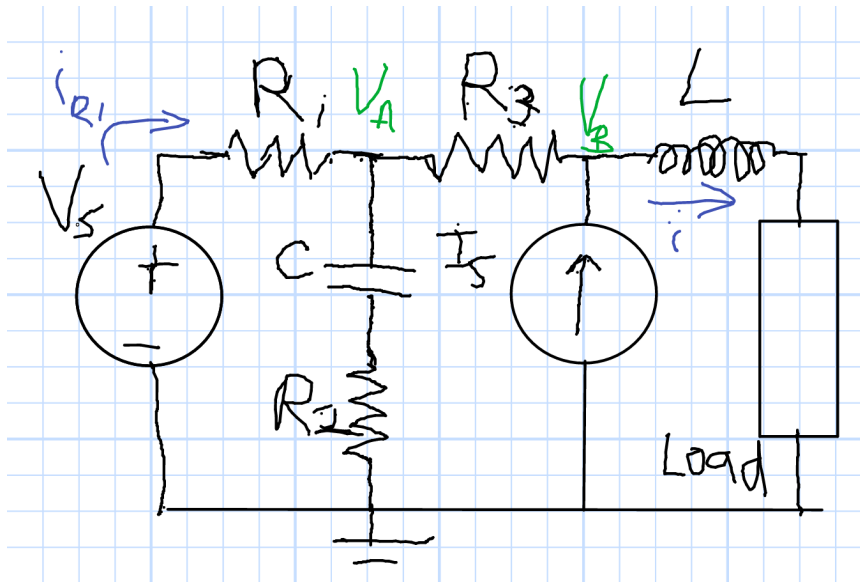

$R_1 = 1\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$ ,  
 $R_3 = 2\text{k}\Omega$ ,  $C = 10\text{nF}$ ,  
 $L = 80\text{mH}$ ,  
 $f = 10\text{kHz}$   
 $V_S = 5\text{V}$ ,  $I_S = 10\text{mA}$

- $V_S = 0$  (Short)
- $I_S = 0$  (Open)
- Load Sees  $Z_T = Z_N$


$$Z_T = Z_L + R_3 + [R_1 \parallel (Z_C + R_2)]$$

$$Z_T = 2.8\text{k}\Omega + 4.9j\text{k}\Omega$$


$$= 5.7\text{k}\Omega \angle -61^\circ$$

- Trust but Verify  
 >> `check=ISC*Z_T-VOC`  
`check =`  
 $-7.1054\text{e-}15 + 1.3323\text{e-}15i$

# Thévenin Equivalent

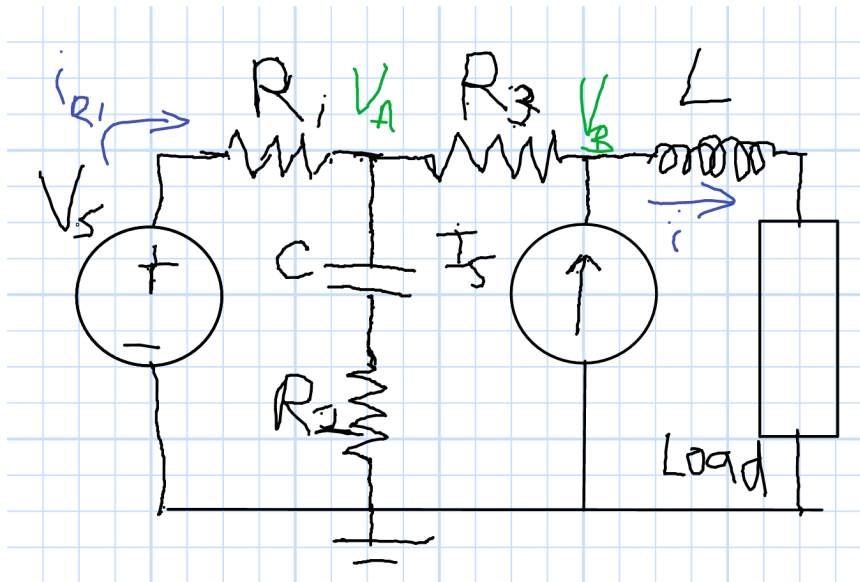

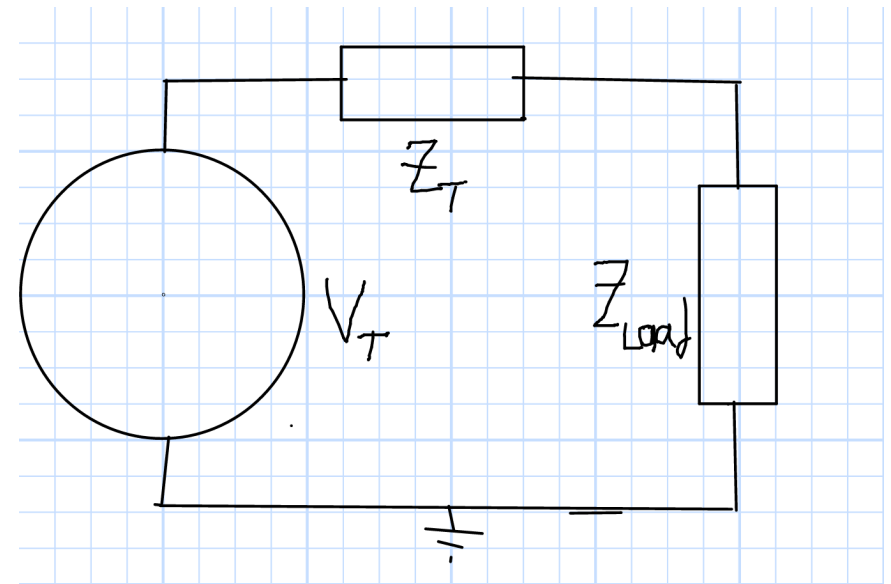
$R_1 = 1\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$ ,  
 $R_3 = 2\text{k}\Omega$ ,  $C = 10\text{nF}$ ,  
 $L = 80\text{mH}$ ,  
 $f = 10\text{kHz}$   
 $V_S = 5\text{V}$ ,  $I_S = 10\text{mA}$




$$V_T = V_{oc} = 31.8\text{V} \angle -2.3^\circ$$

$$Z_T = 5.7\text{k}\Omega \angle -61^\circ$$

# Norton Equivalent

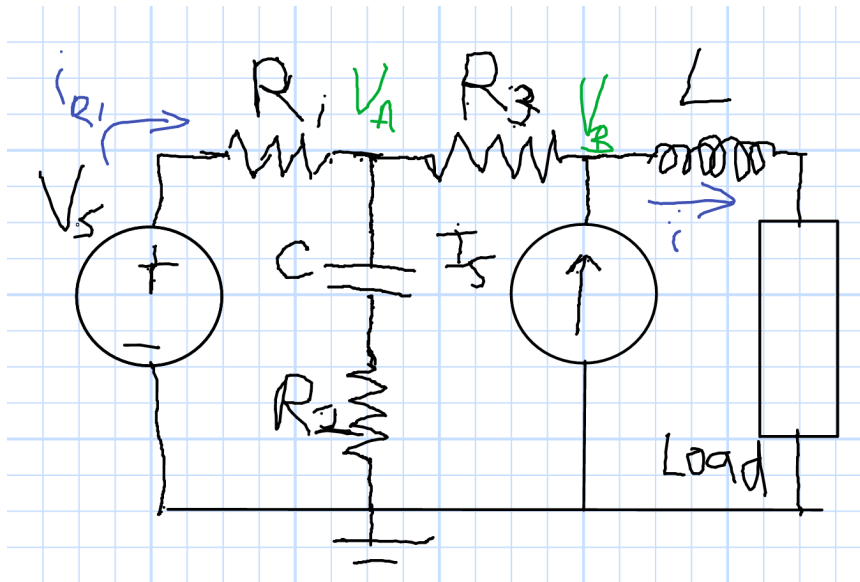

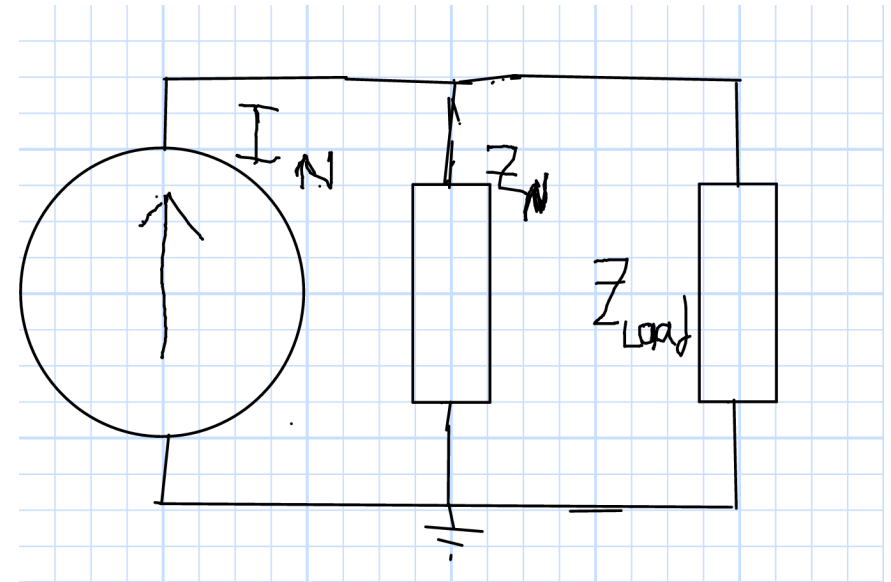$R_1 = 1\text{k}\Omega$ ,  $R_2 = 3\text{k}\Omega$ ,  
 $R_3 = 2\text{k}\Omega$ ,  $C = 10\text{nF}$ ,  
 $L = 80\text{mH}$ ,  
 $f = 10\text{kHz}$   
 $V_S = 5\text{V}$ ,  $I_S = 10\text{mA}$



$$I_N = I_{sc} = 5.6\text{mA} \angle -63^\circ$$

$$Z_N = Z_T = 5.7\text{k}\Omega \angle -61^\circ$$

# Happy Thanksgiving

