

# Electrical Engineering

## Week 13


Charles A. DiMarzio  
EECE-2210  
Northeastern University

Nov 2021

# Week 13 Agenda: Fourier Analysis

- Motivation: Diffusive Optical Tomography
- Fourier Series
- Transfer Function
- Bels and deciBels
- High- and Low-Pass Filters
- Low-Pass Example
- Bode Plots
- Notch Filter

# Diffusive Optical Imaging

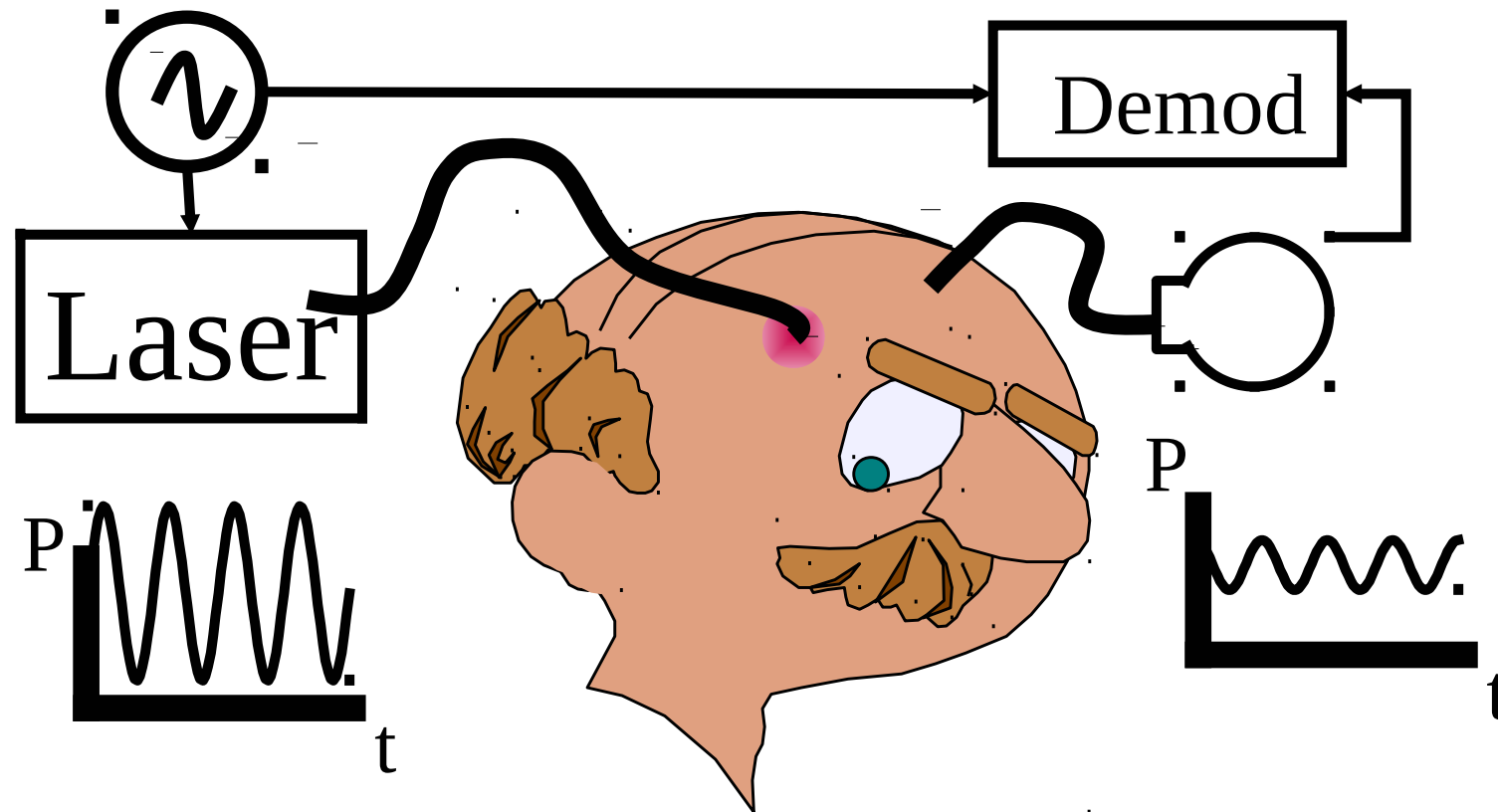

Light Source can be DC, Sinusoidal, or Pulsed

# Fourier Series

- Sinusoids From Last Week

$$v(t) = \operatorname{Re} \left( \mathbf{V} e^{j\omega t} \right) = \frac{\mathbf{V}}{2} e^{j\omega t} + \frac{\mathbf{V}^*}{2} e^{-j\omega t}$$

- General Periodic Function


$$v(t) = \sum_{n=-\infty}^{\infty} \left( \frac{\mathbf{V}_n}{2} e^{jn\omega t} \right)$$

- Constraint for Real Functions of Time


$$\mathbf{V}_{-n} = \mathbf{V}_{+n}^*$$

- Given a Periodic  $v(t)$ , We Can Find  $\mathbf{V}_n$  for All  $n$ .

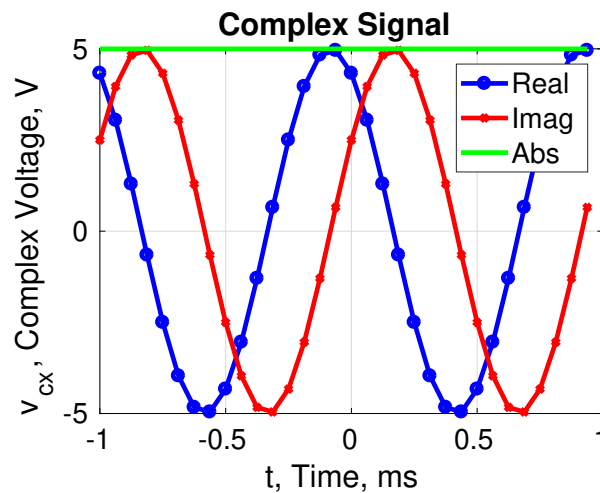
# Fourier Series of Complex and Real Signals




$$V e^{j30\pi/180} e^{j\omega t}$$

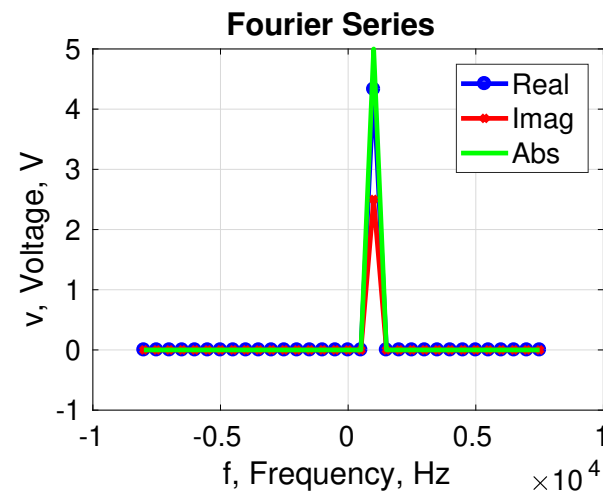

$$V(-f) = 0$$

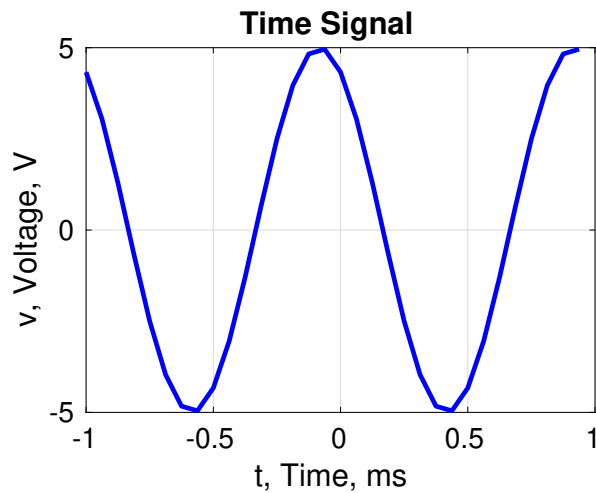


$$\cos(\omega t + 30^\circ)$$

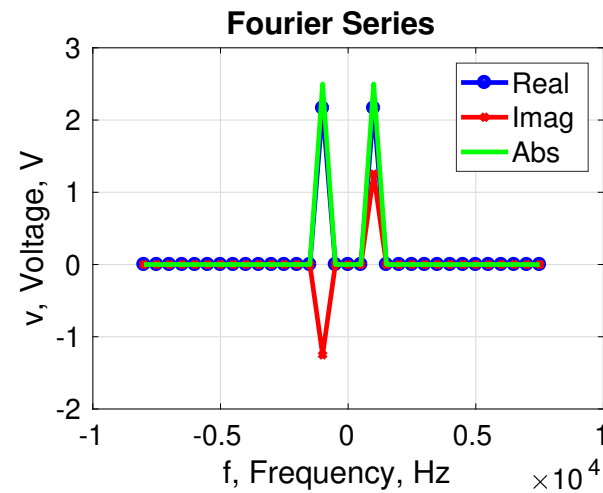


$$V(-f) = V^*(f)$$


# Square Wave

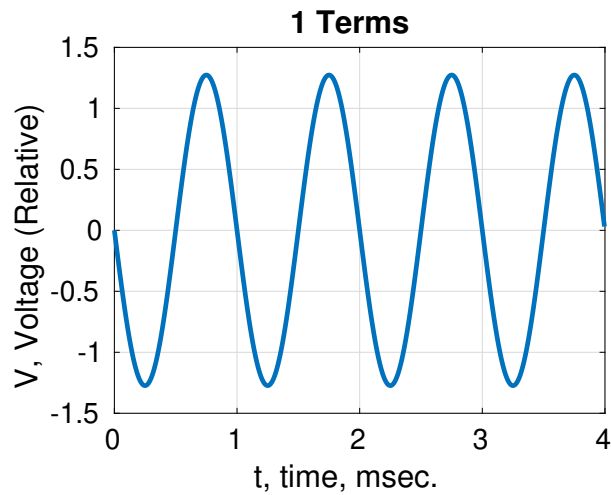


$$\frac{4}{\pi} \sin \omega t$$

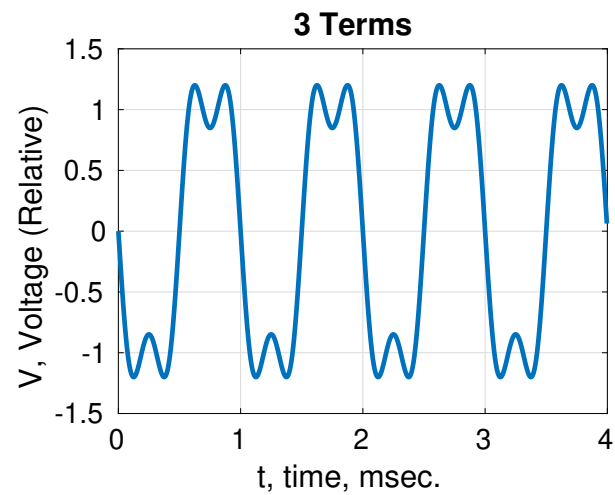

$$+ \frac{4}{2\pi} \sin 3\omega t$$

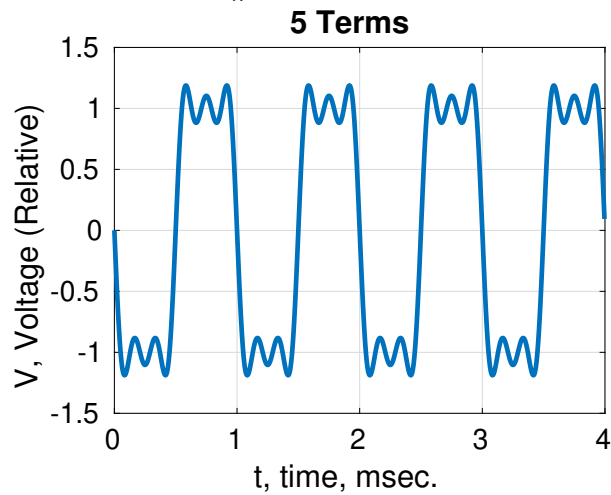


$$+ \frac{4}{5\pi} \sin 5\omega t$$

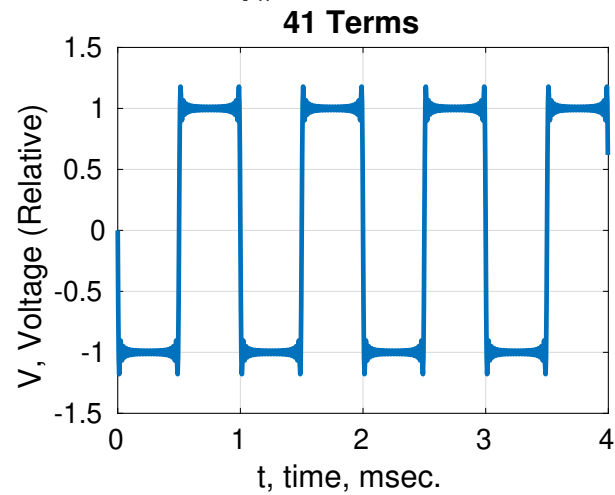


$$+ \dots + \frac{4}{41\pi} \sin 41\omega t$$

# Harmonics Added

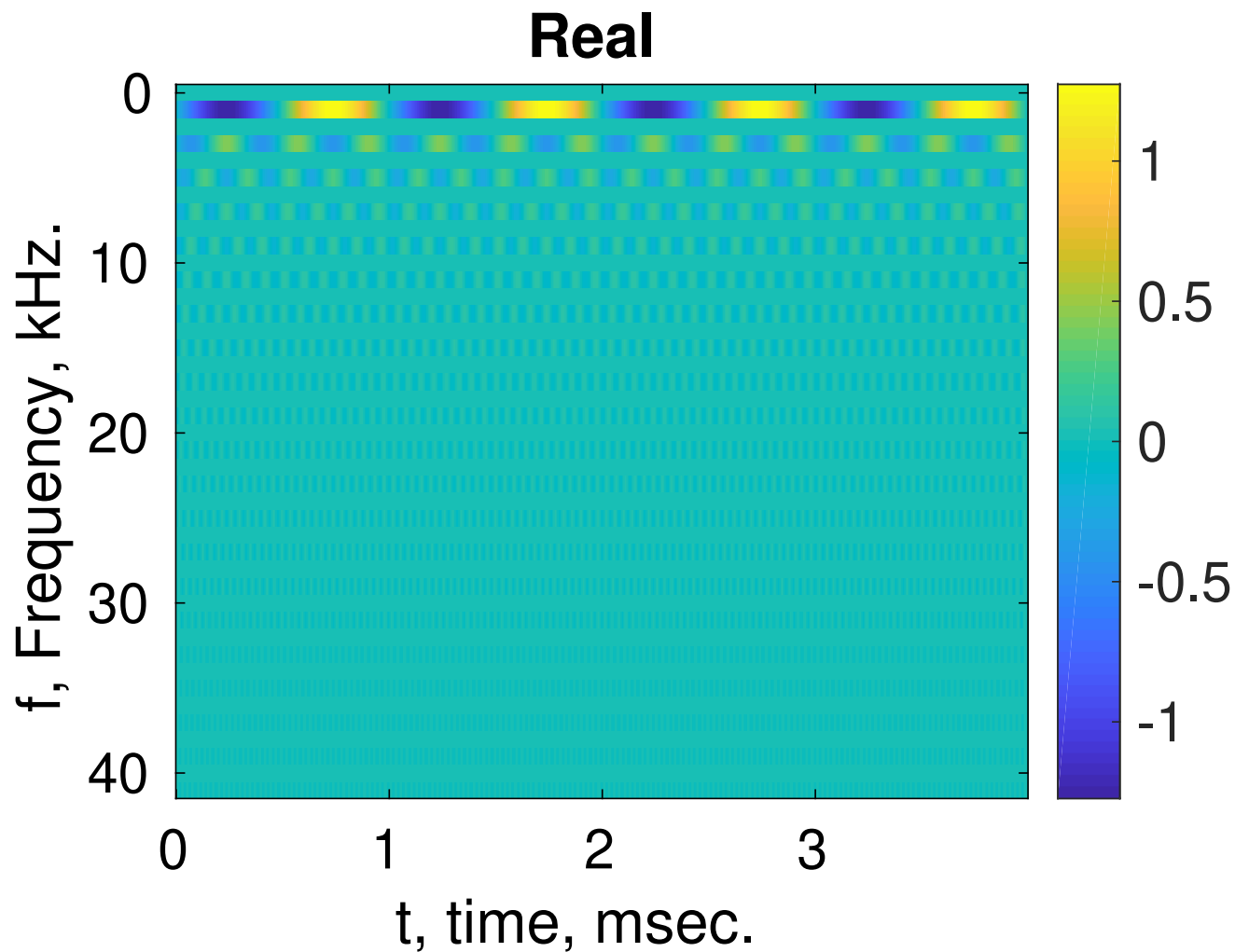

No Even Harmonics, Higher Harmonics Contribute Little


# Square Wave Approximation

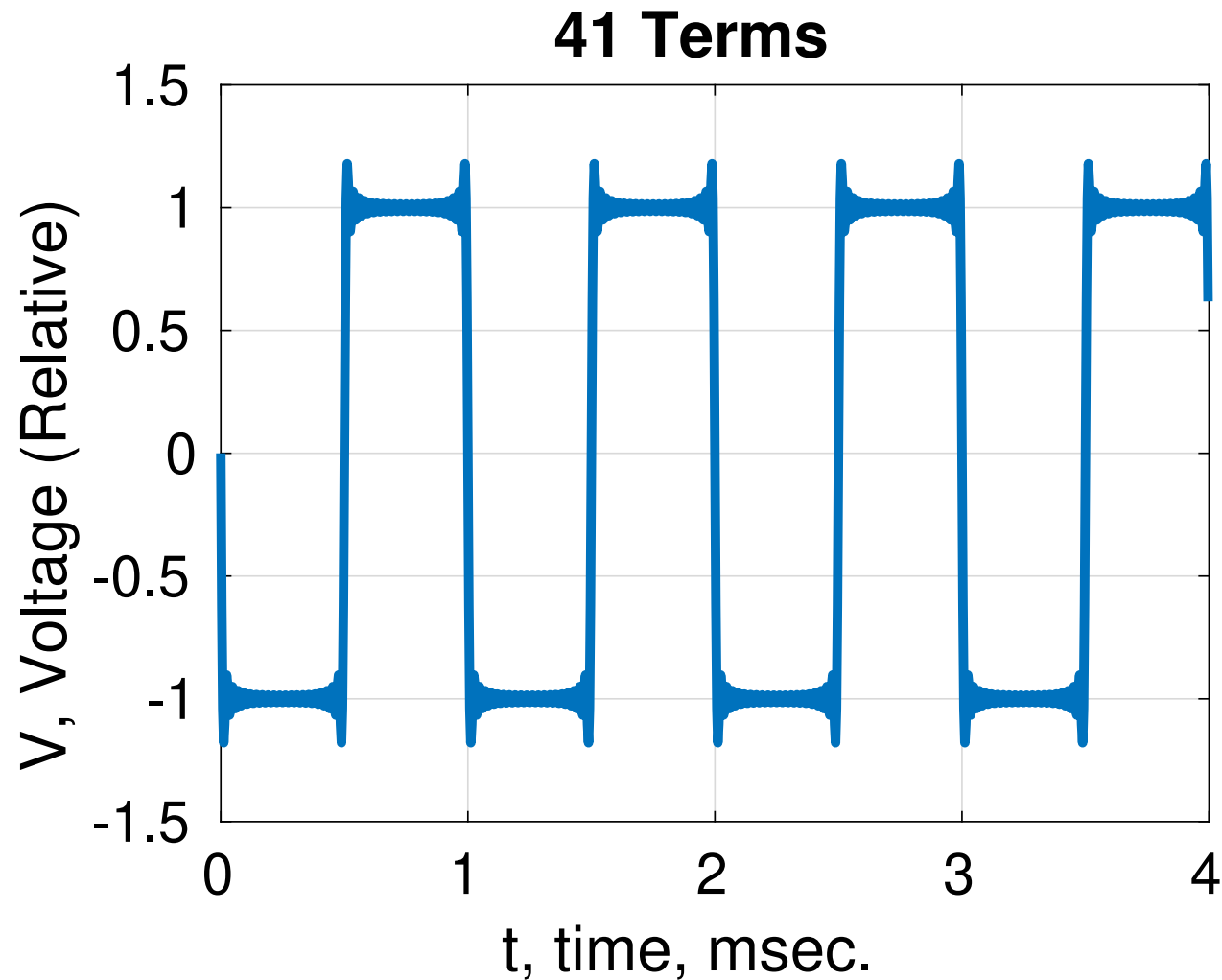

More Harmonics Would Reduce the Ringing (Gibbs Phenomenon)







# Transfer Function Concept

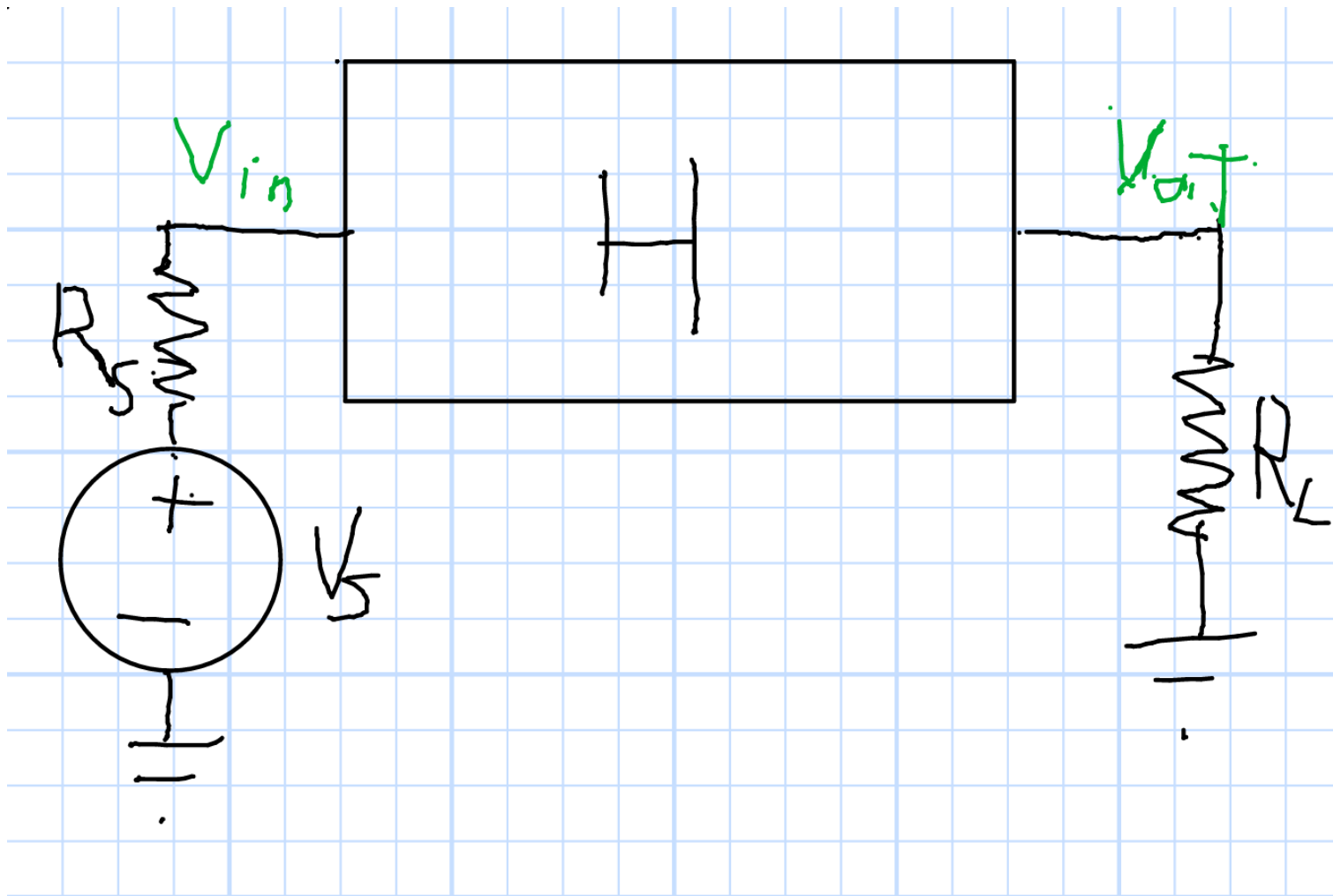

$$V_{out}(\omega) = H(\omega) V_{in}(\omega) \text{ and No Coupling}$$





# High-Pass Filter/Amplifier

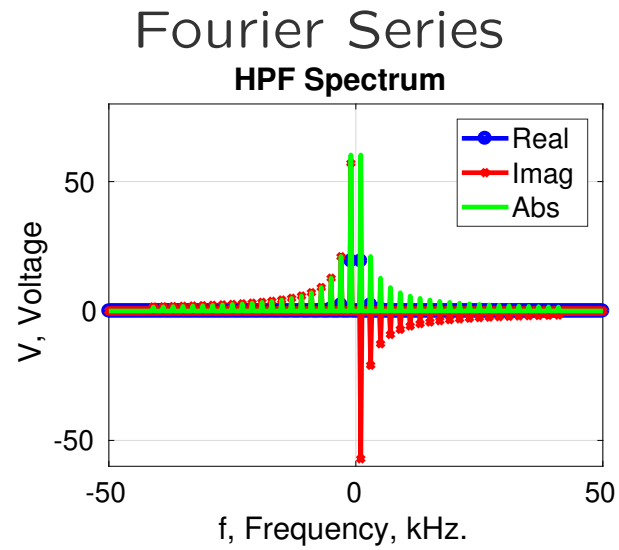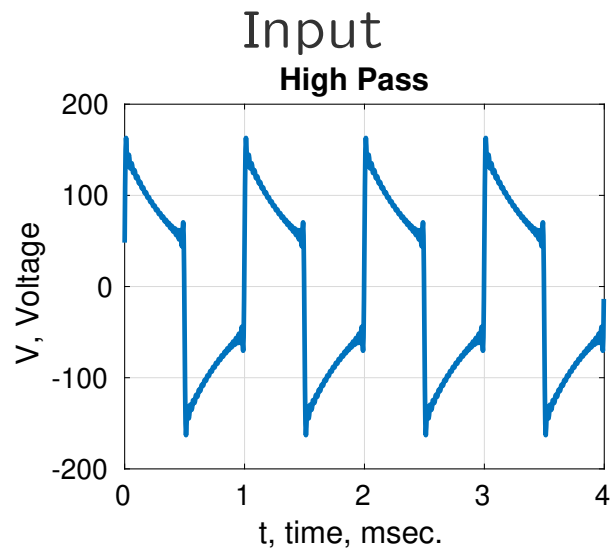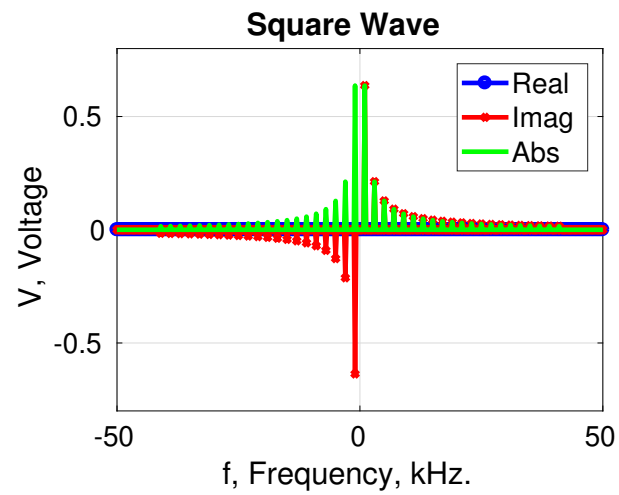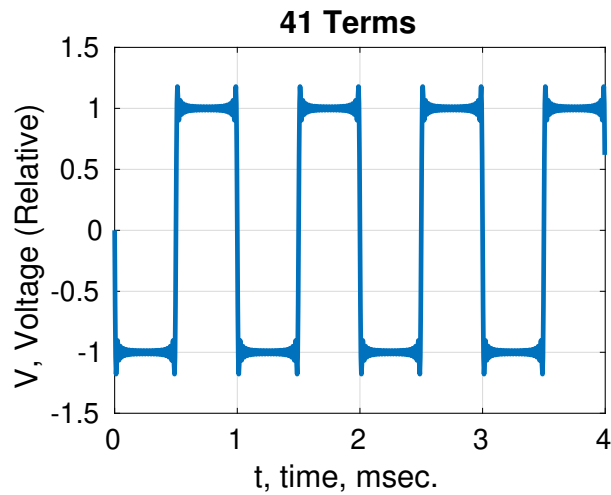

HPF Output

Fourier Series


# High-Pass and Low Pass

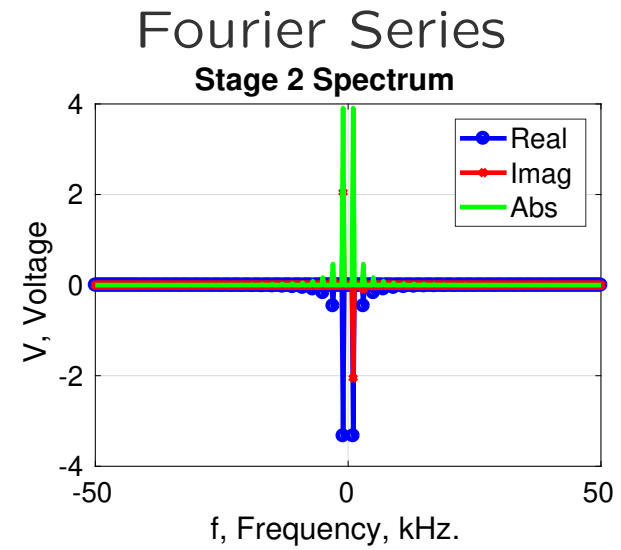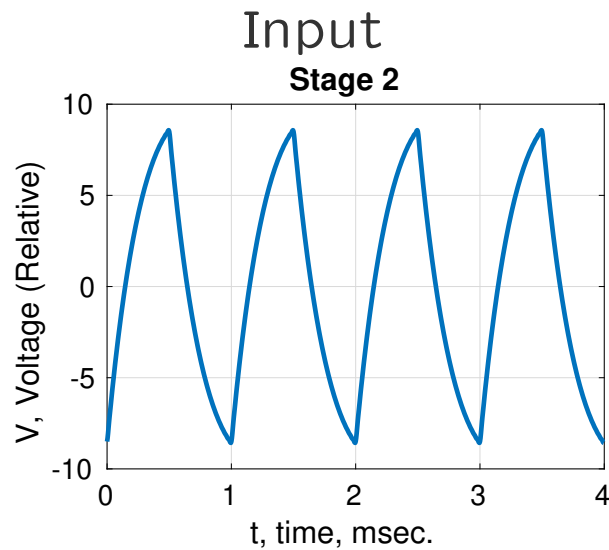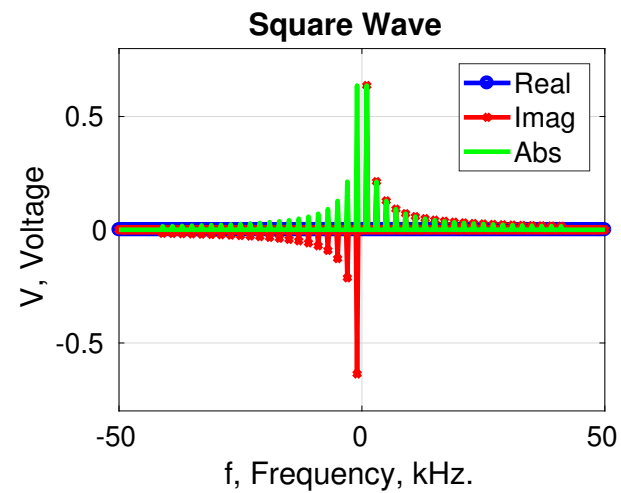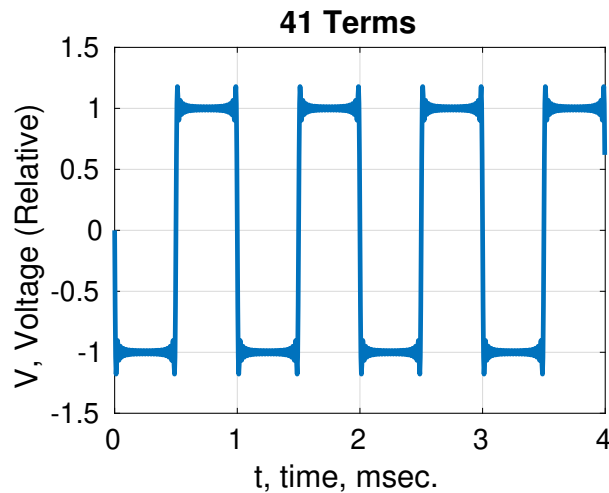


2-Filter Output

Fourier Series

# Transfer Function Concept

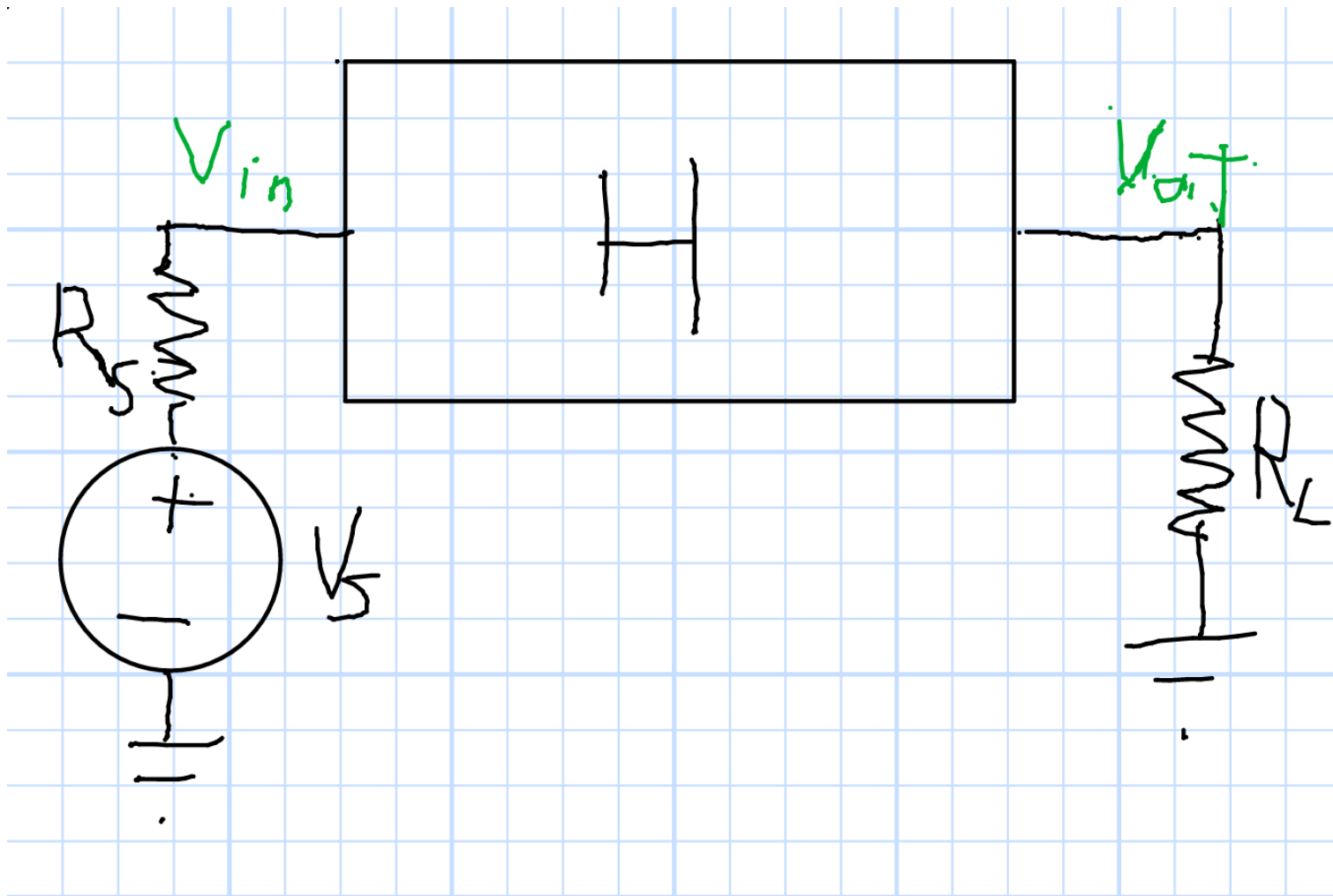

# Transfer Function Concept

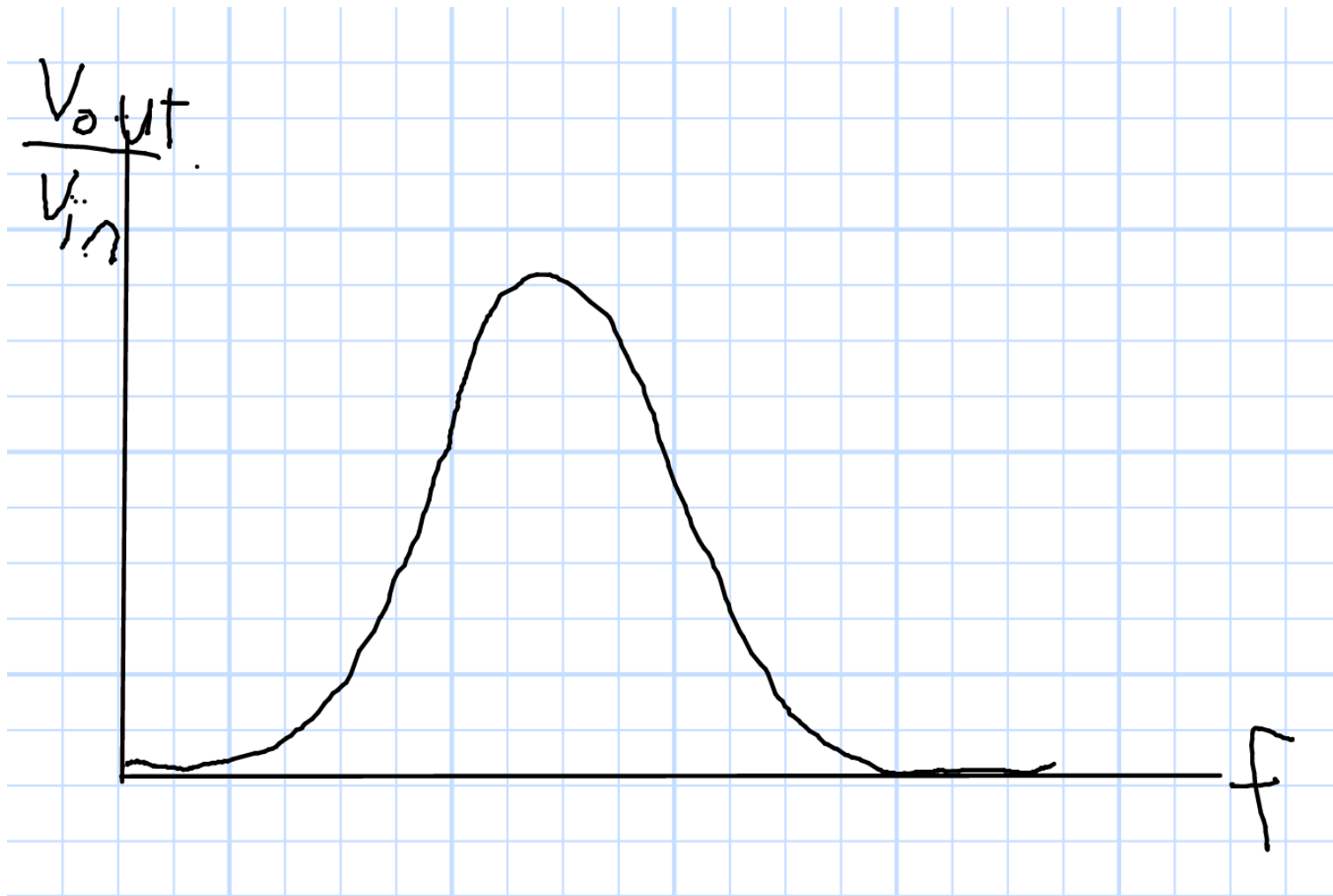


# But It's Complex




Plot Amplitude and Phase

# And It's Nice to Talk About Power

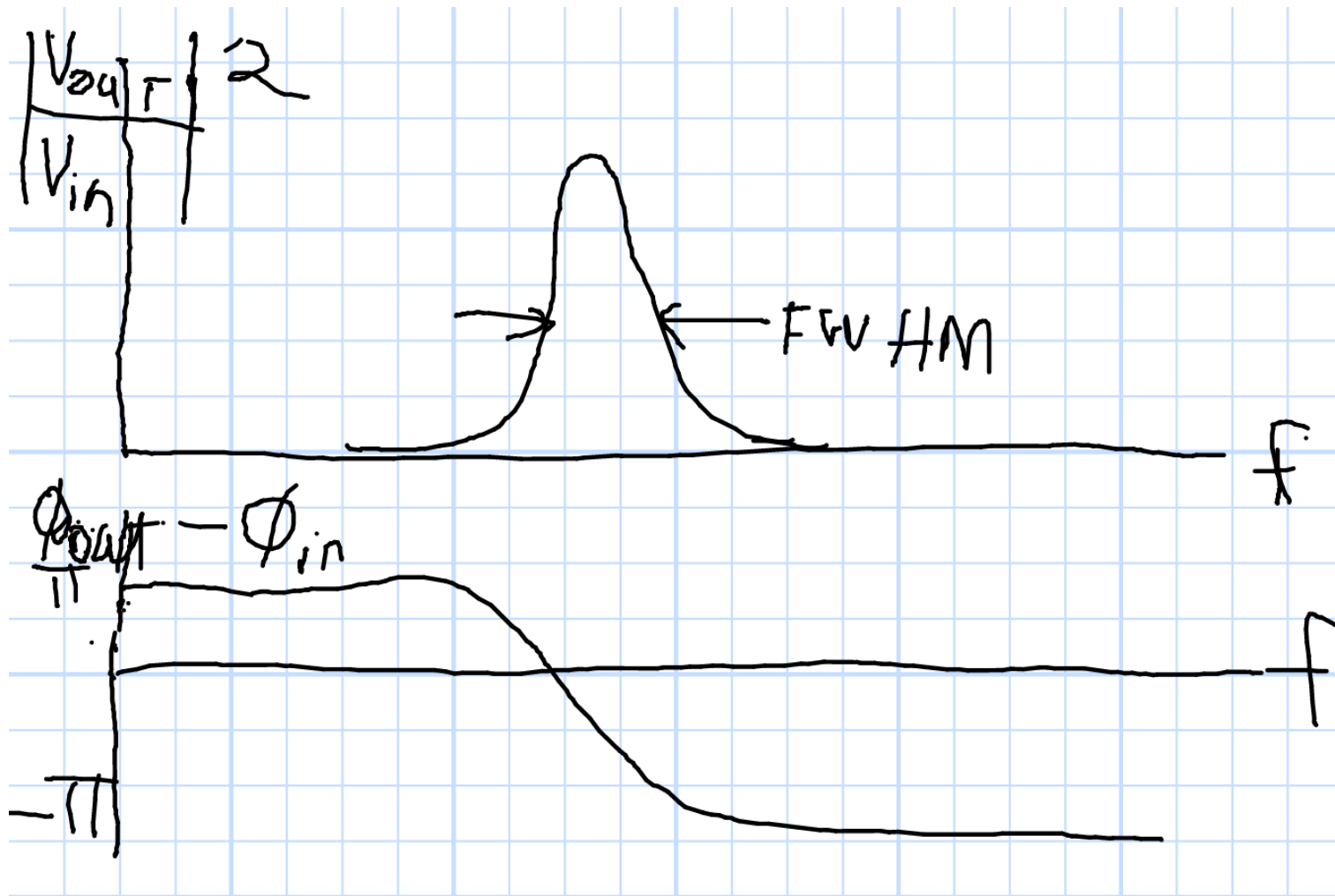

Square the Amplitude.

# And Sometimes We Want a Log Scale

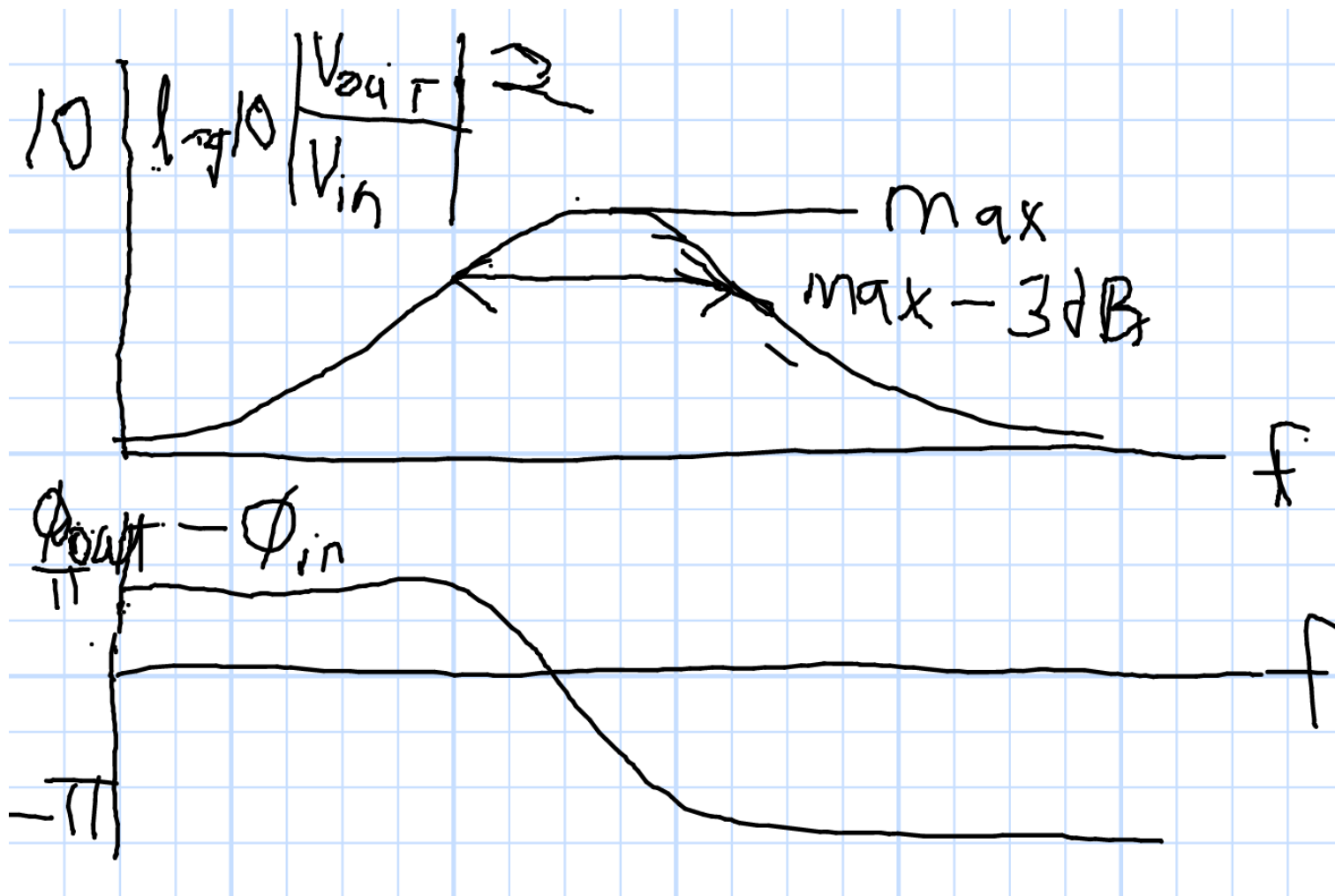

Use Decibels



# DeciBels, dB

- Always Refers to a Ratio

$$\frac{|V_{out}|}{|V_{in}|} \quad \text{Or} \quad \frac{P_{out}}{P_{in}} = ? \left| \frac{V_{out}}{V_{in}} \right|^2$$

- Log Base 10

$$\log_{10} \frac{P_{out}}{P_{in}}$$

- But That's too Coarse; Multiply by 10

$$R_{dB} = 10 \log_{10} \frac{P_{out}}{P_{in}} = 20 \log_{10} \frac{|V_{out}|}{|V_{in}|} \quad \frac{|V_{out}|}{|V_{in}|} = 10^{R_{dB}/20}$$

- lower case d, Capital B (Named for Alexander Graham Bell)

# Some Ratios in dB

dB	Power Ratio	Voltage Ratio
-40	0.0001	0.01
-30	0.001	$\sqrt{0.001} \approx 0.032$
-20	0.01	0.1
-10	0.1	$\sqrt{0.1} \approx 0.32$
-6	0.25	0.5
-3	0.5	$\sqrt{0.5} \approx 0.71$
0	1	1
3	2	$\sqrt{2} \approx 1.4$
6	4	2
10	10	$\sqrt{10} \approx 3.2$
20	100	10
30	1000	$\sqrt{1000} \approx 32$
40	10000	100

The cool thing is that they add.

# Some Special References

- Electronics and Optics  $dBm$

$$10 \log_{10} \frac{P}{1\text{mW}}$$

- Sometimes Used for Voltage, Assuming 50 Ohms

$$10 \log_{10} \frac{|V|^2}{50\Omega \times 1\text{mW}}$$

- Example:  $1V_{RMS} \rightarrow 13\text{dBm}$
- Radar Meteorology  $dBZ$  (One 1mm raindrop per  $\text{m}^3$ )
- Acoustics  $dBu$  and more

# Comment on Digitization

- Eight–Bit Digitizer

- Smallest Step = 1, Max Error = 0.5

- Largest Value  $2^8 - 1 = 255$

- Ratio


$$20 \log_{10} \frac{255}{1} = 48\text{dB}$$

- In General, for  $n$ –bit Digitizer


$$20 \log_{10} \frac{2^n - 1}{1} \approx 20 \log_{10} 2^n = 20n \log_{10} 2$$

Dynamic Range in dB  $\approx 6n$

# Generic Amplifier

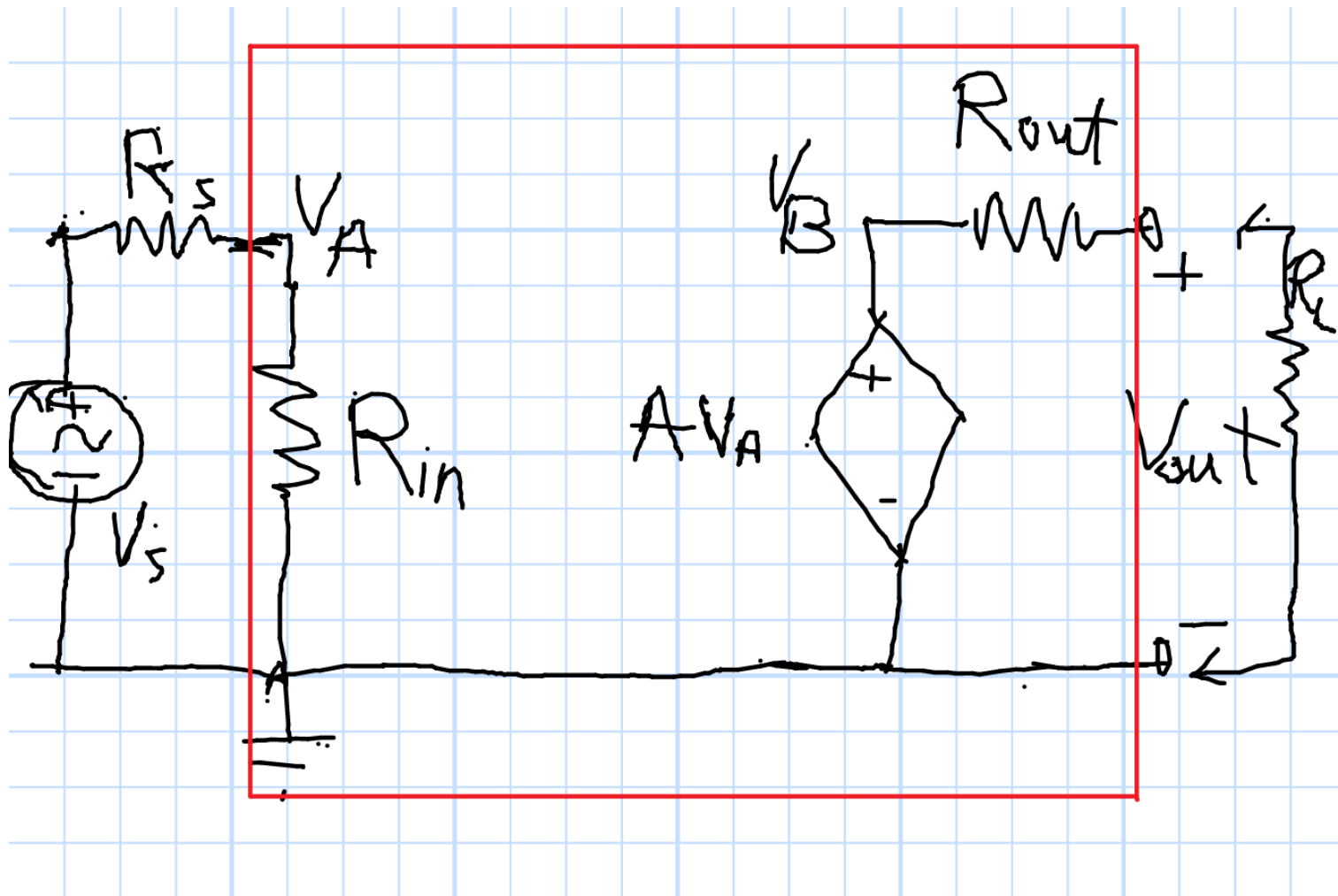

# Amplifier Specifications

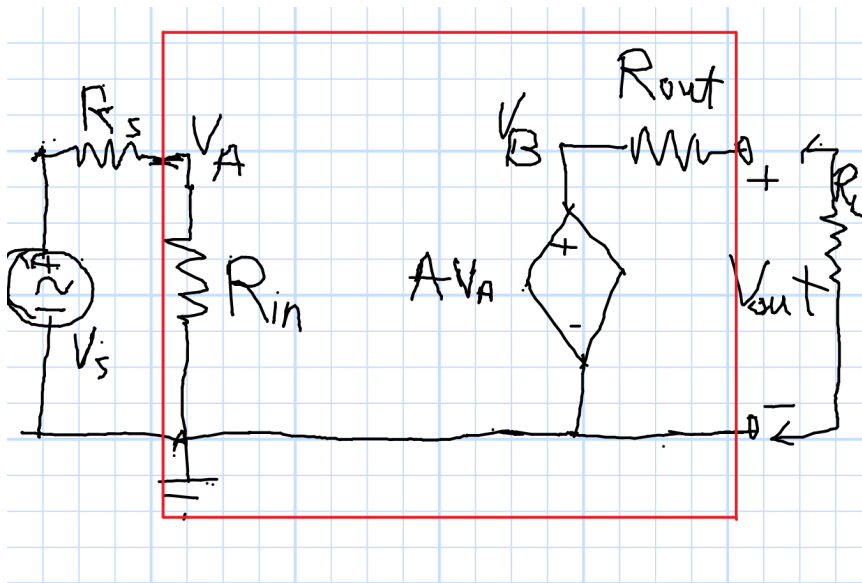


- Gain & Bandwidth Examples
  - $30\text{dB} \pm 1\text{dB}$   
from 30Hz to 16kHz
  - 60dB at 70MHz and  
< 30dB at 80MHz
- Impedances
  - High  $R_{in}$ , Low  $R_{out}$  for  
Maximum Voltage Gain
  - Matched for Maximum  
Power Gain
  - Often 50 Ohms
- Maximum Outputs
- Noise at Input
- Other

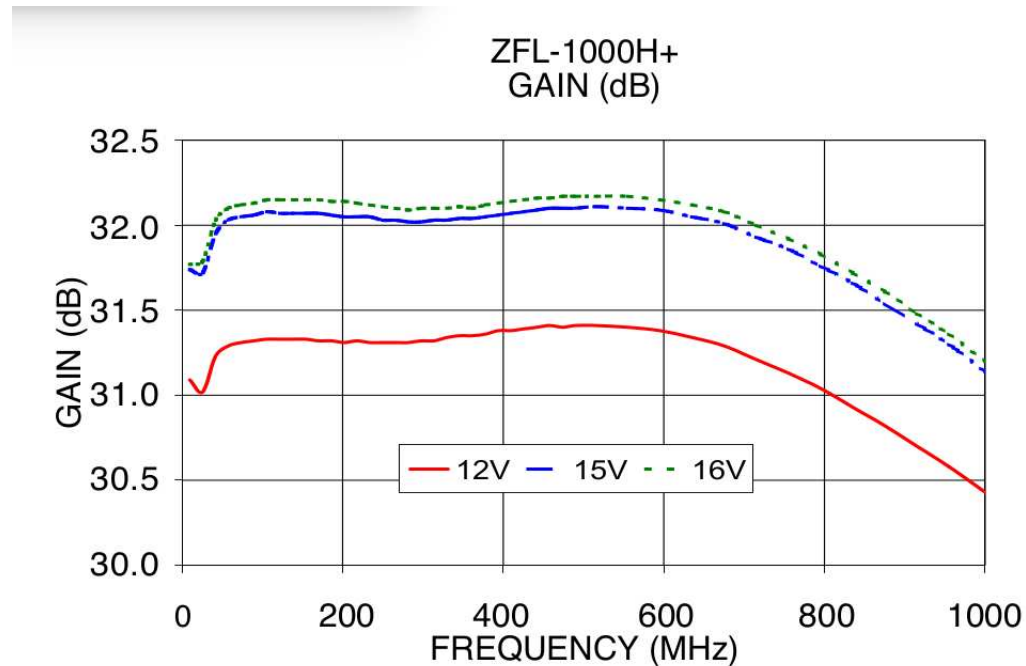
# Amplifier Example



30dB Gain,  $50\Omega$  in and out, SMA Connectors  
+15V Supply, Max Output 20dBm  
10 to 1000MHz, Power +15V, from Minicircuits.



# Amplifier Measurements

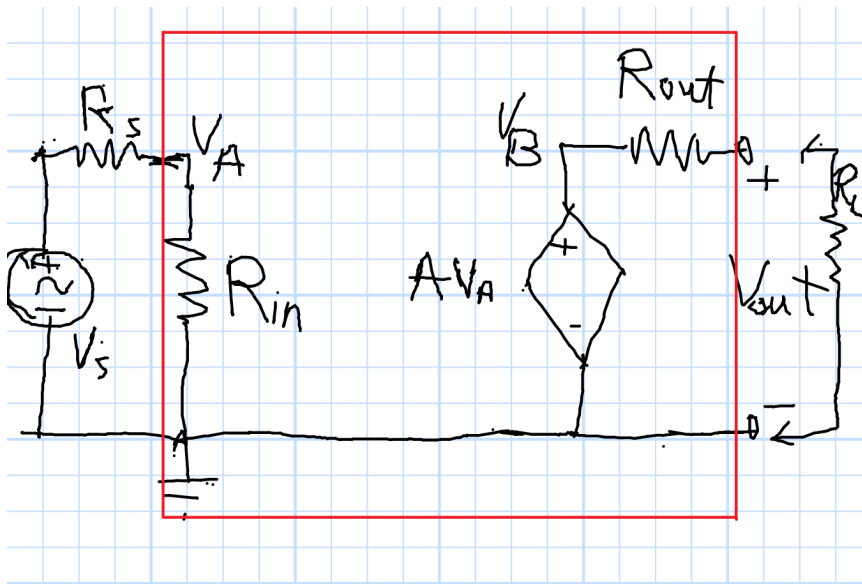

- Example: 50Ω Amplifier
- Input Measured Correctly

$$V_A = \frac{V_S}{2}$$

- Source without Load

$$V_A = V_S$$

- Output Measured Correctly

$$V_{OUT} = \frac{V_B}{2}$$


- Output without Load

$$V_{OUT} = V_B$$


- Watch P-P vs. RMS





# Low-Pass Filter

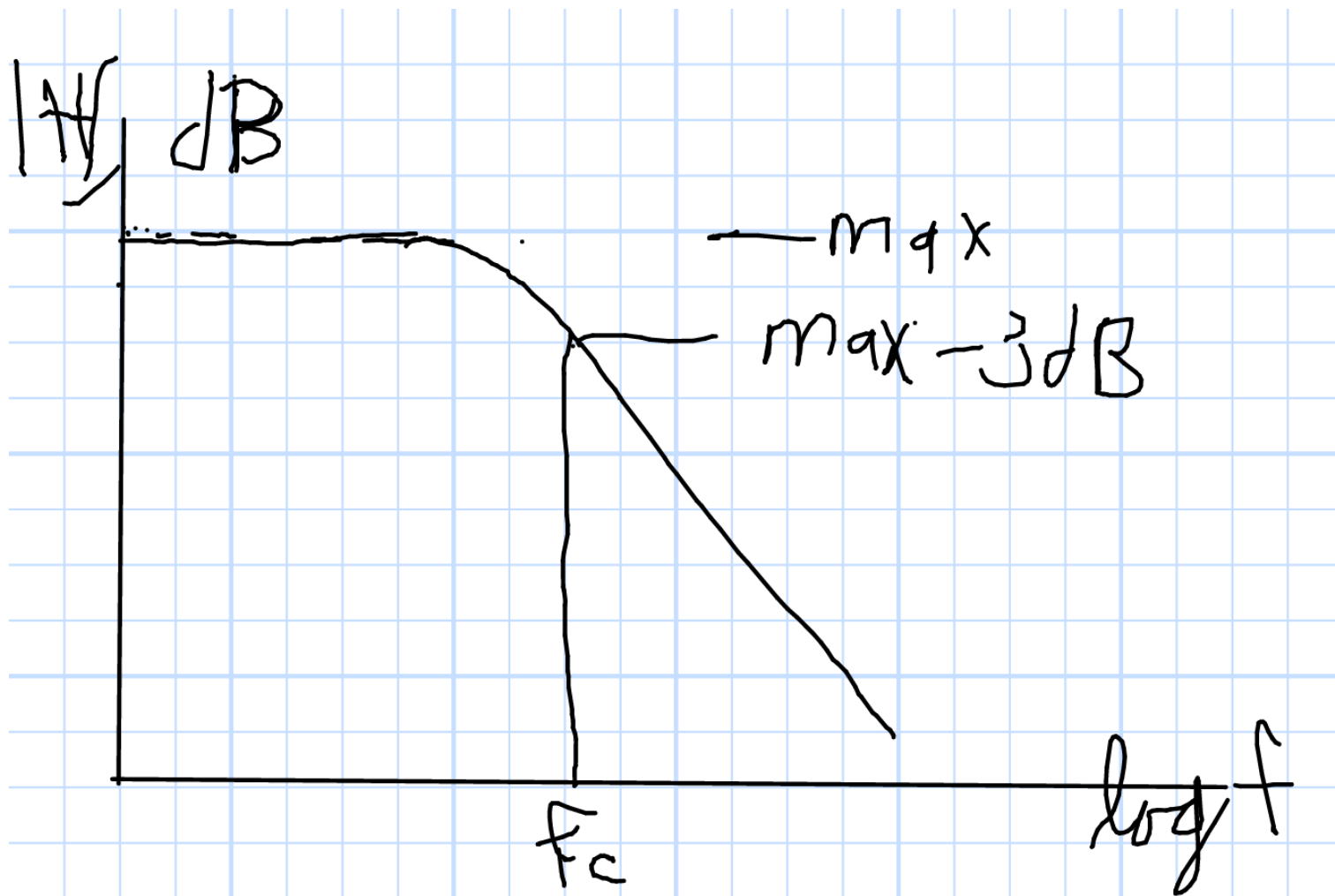

# High-Pass Filter

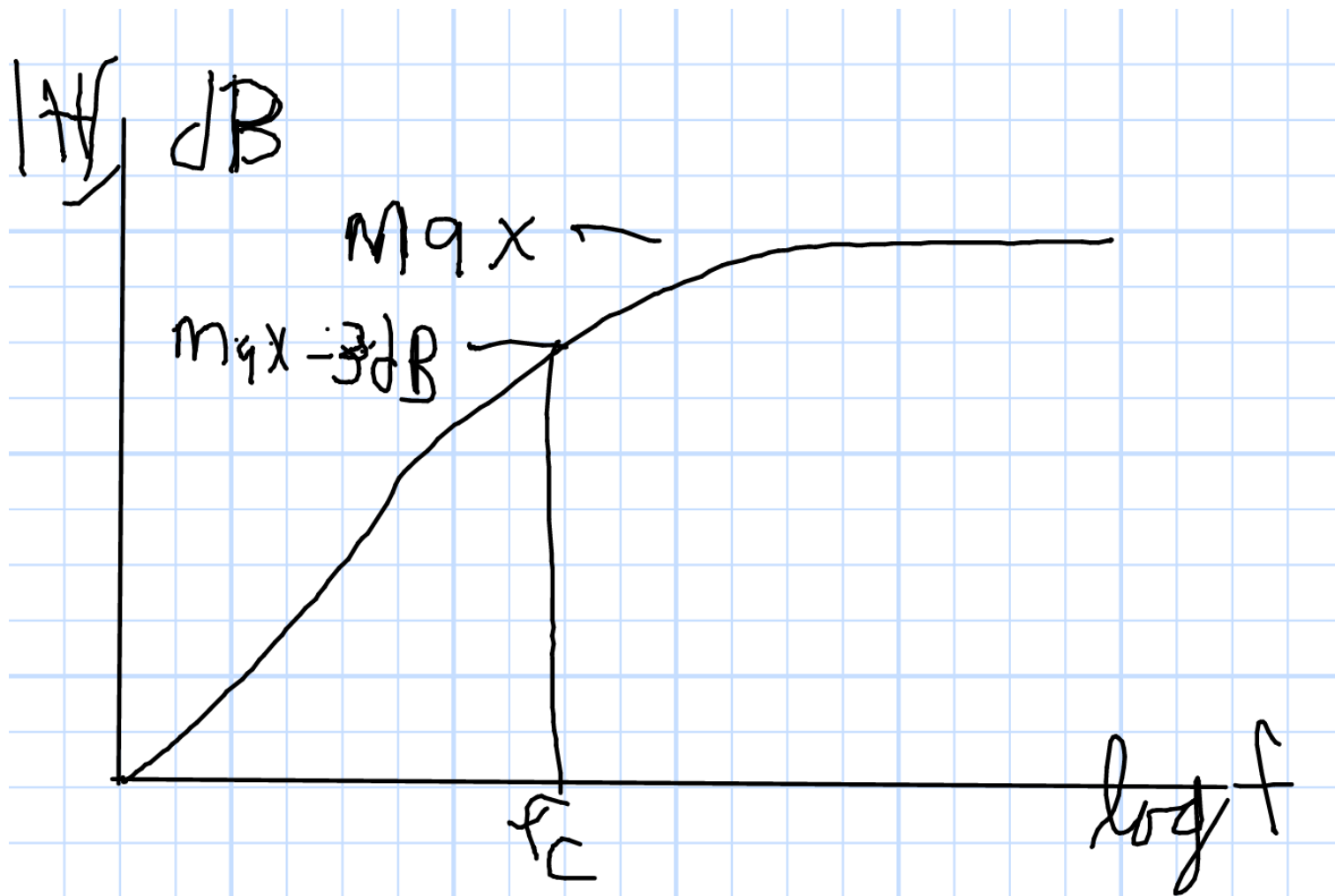

# Half-Power Point

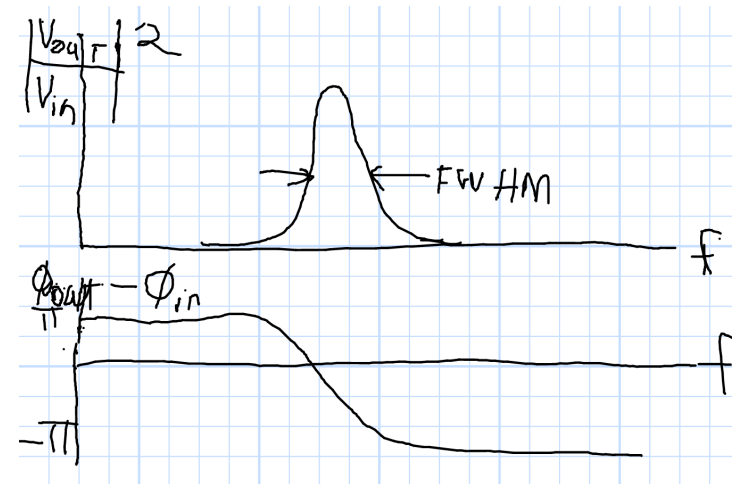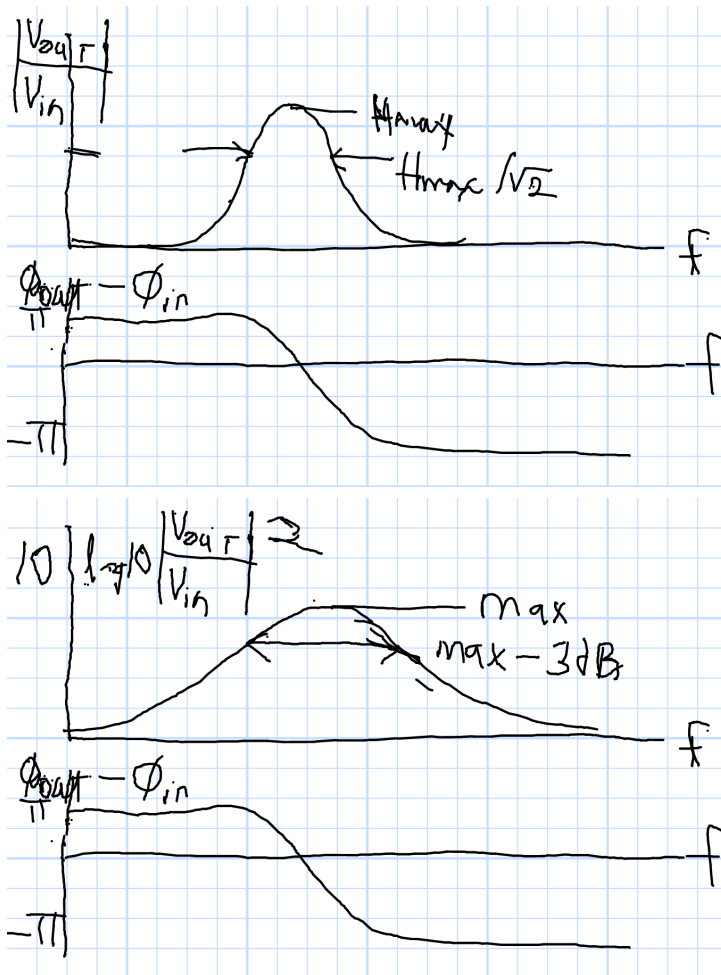


- Power Gain is Voltage Gain Squared

$$A_P = |A_V|^2 = \left| \frac{V_{out}}{V_{in}} \right|^2$$


- in deciBels

$$10 \log_{10} A_P = 20 \log_{10} |A_V|$$

# Example Circuit

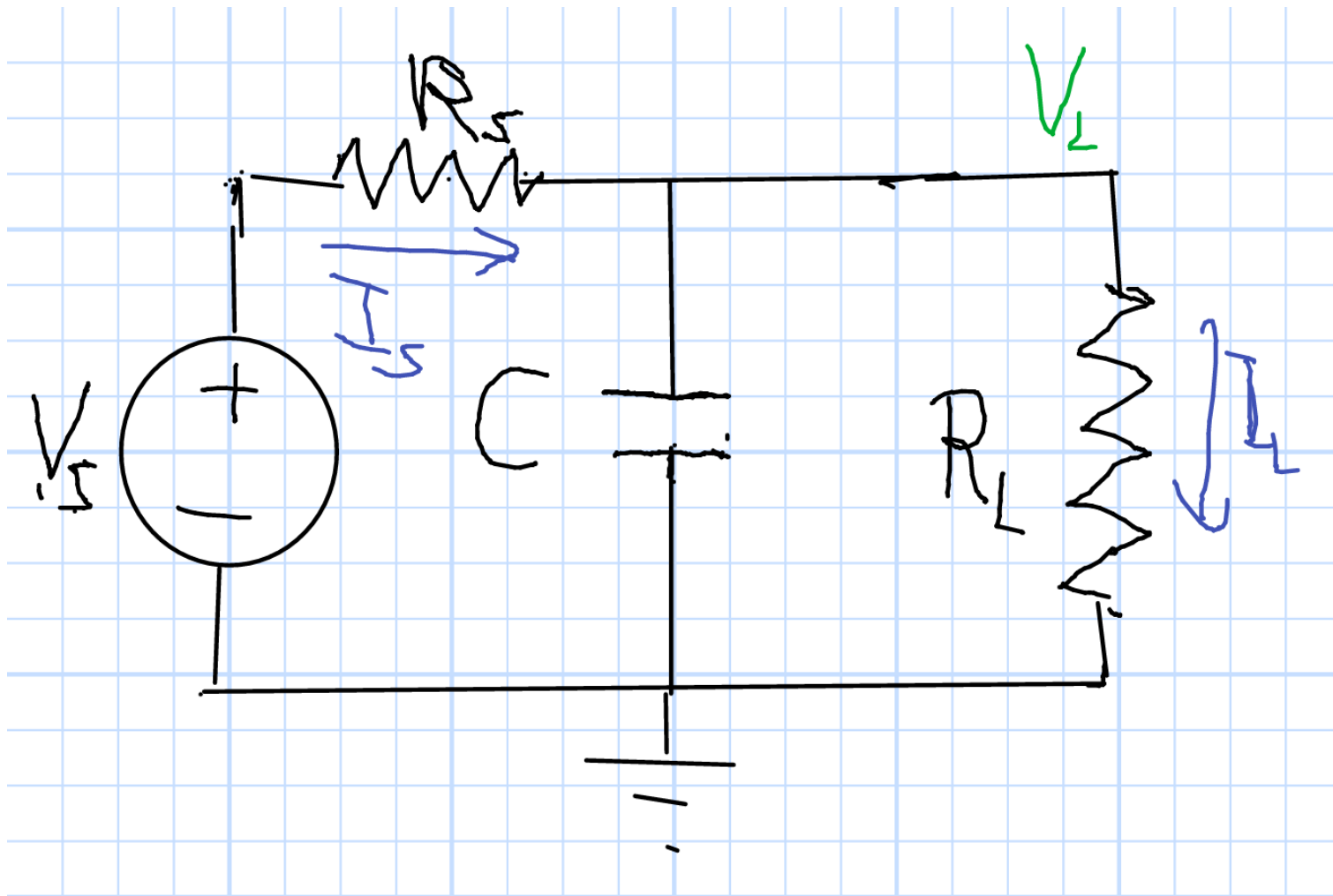

# Solution

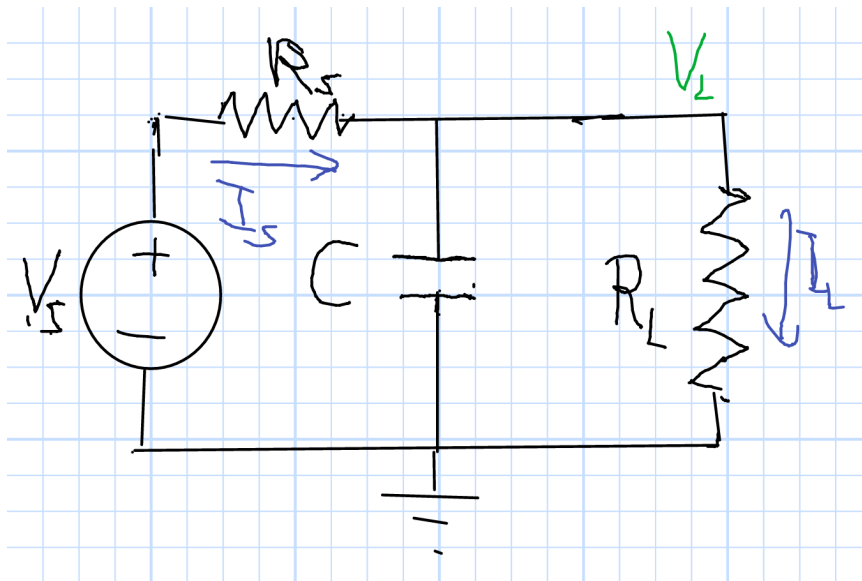

$$R_S = 1\text{k}\Omega \quad R_L = 500\Omega$$

$$C = 68\text{nF}$$


- Voltage Divider

$$\frac{V_L}{V_S} = H = \frac{R_L \parallel \frac{1}{j\omega C}}{R_S + (R_L \parallel \frac{1}{j\omega C})}$$

- Simplify

$$\begin{aligned} H &= \frac{1}{\frac{R_S}{R_L \parallel \frac{1}{j\omega C}} + 1} \\ &= \frac{1}{\frac{R_S \left( R_L + \frac{1}{j\omega C} \right)}{\frac{R_L}{j\omega C}} + 1} \\ &= \frac{R_L}{R_S R_L j\omega C + R_S + R_L} \end{aligned}$$

# Transfer Function Values

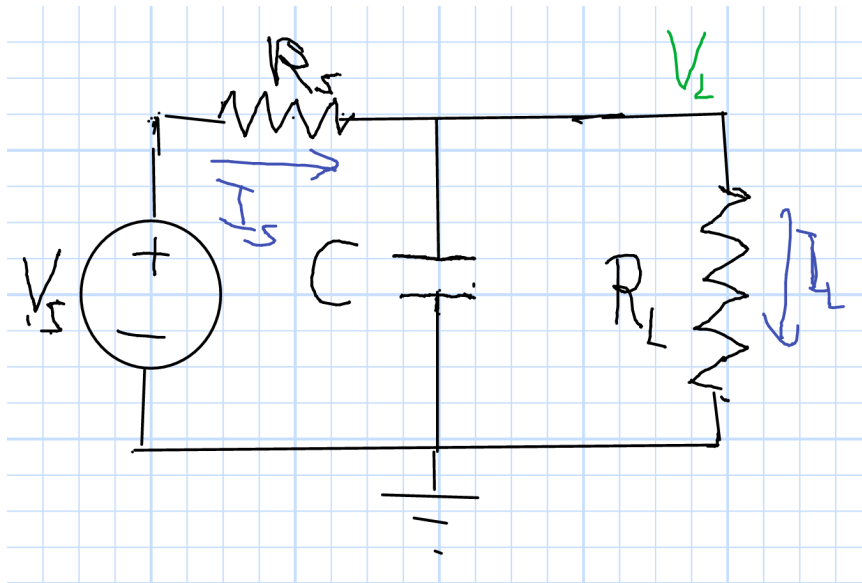

$$R_S = 1\text{k}\Omega \quad R_L = 500\Omega$$

$$C = 68\text{nF}$$

- Previous Page

$$H = \frac{R_L}{R_S R_L j\omega C + R_S + R_L}$$

- Simplify a Bit More

$$H = \frac{1/R_S}{j\omega C + \frac{1}{R_S \parallel R_L}}$$

- Max at  $f = 0$  (Cap Open)


$$\frac{R_S \parallel R_L}{R_S} = \frac{R_L}{R_S + R_L} = \frac{1}{3}$$

- Cutoff

$$\frac{1}{\omega C} = R_S \parallel R_L$$

$$f_C = \frac{1}{2\pi (R_S \parallel R_L) C} = \frac{1}{2\pi\tau}$$

# Transfer Function

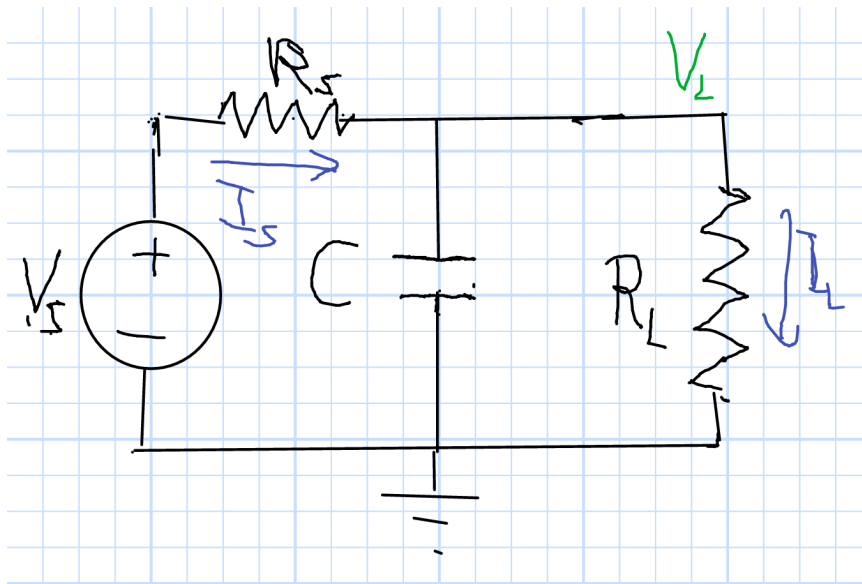

$$R_S = 1\text{k}\Omega \quad R_L = 500\Omega$$

$$C = 68\text{nF}$$

- Previous Page

$$H_{max} = 1/3$$

$$\frac{1}{\omega C} = R_S \parallel R_L$$

$$f_C = \frac{1}{2\pi (R_S \parallel R_L) C} \approx 7\text{kHz}$$

- Cutoff Significance

$$H = \frac{H_{max}}{\sqrt{2}} \times 1 \angle -45^\circ$$

- Half-Power Point
- Half Phase Shift
- Equation

$$H = \frac{H_{max}}{1 + jf/f_c}$$

# Approximations

- Previous Page

$$H = \frac{H_{max}}{1 + jf/f_c}$$



- Low Frequency

$$H \approx H_{max}$$

- High Frequency





$$|H| = \frac{|H|_{max} f_c}{f}$$

- 20 dB per Decade
- 6 dB per Octave

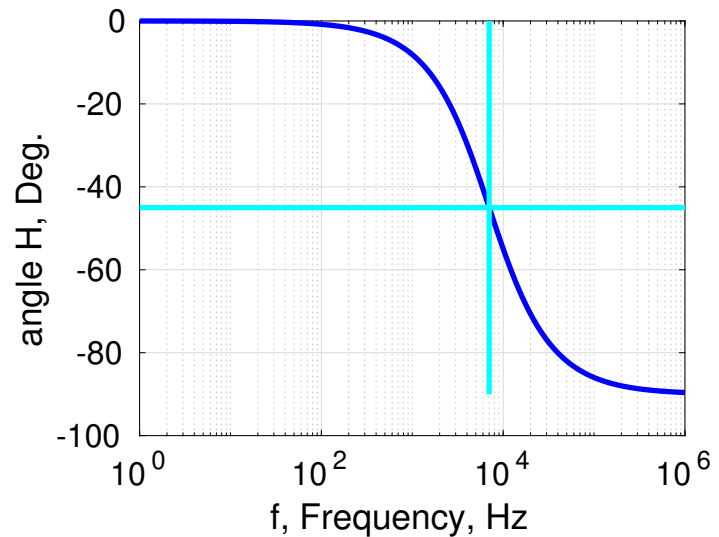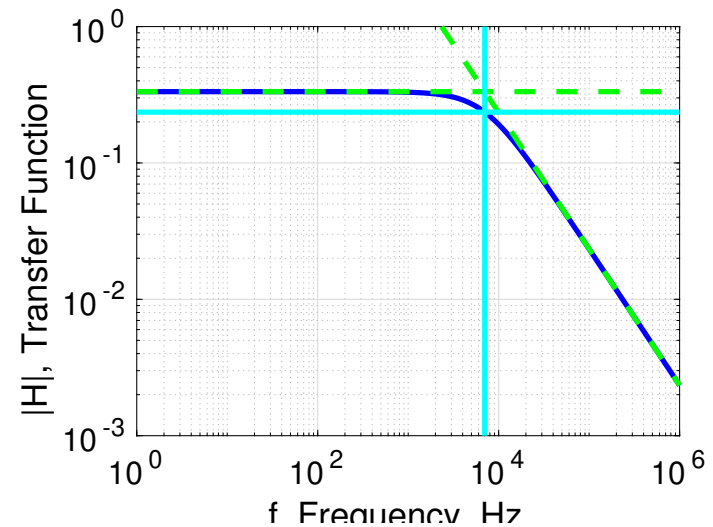




# Plots

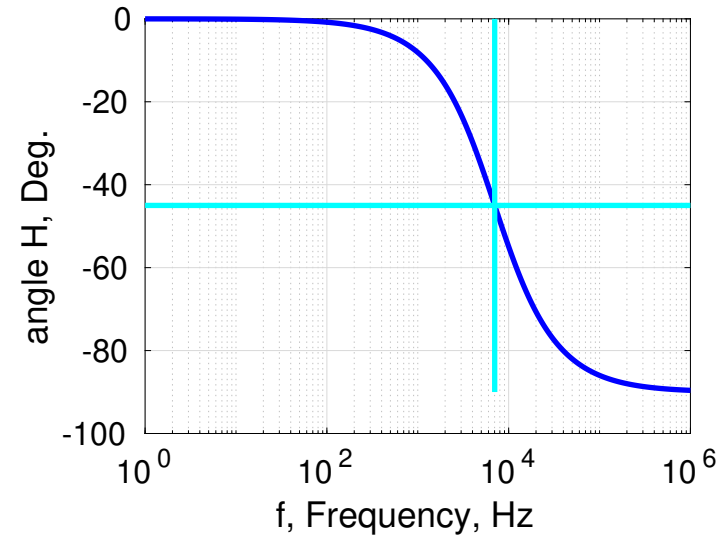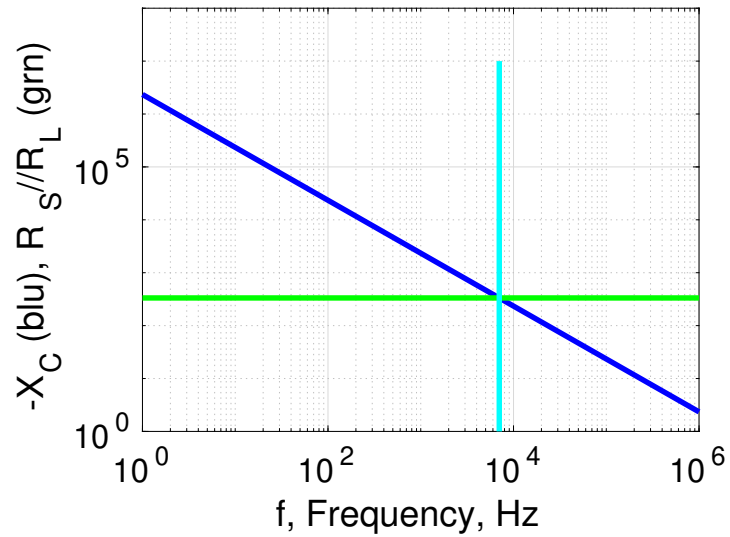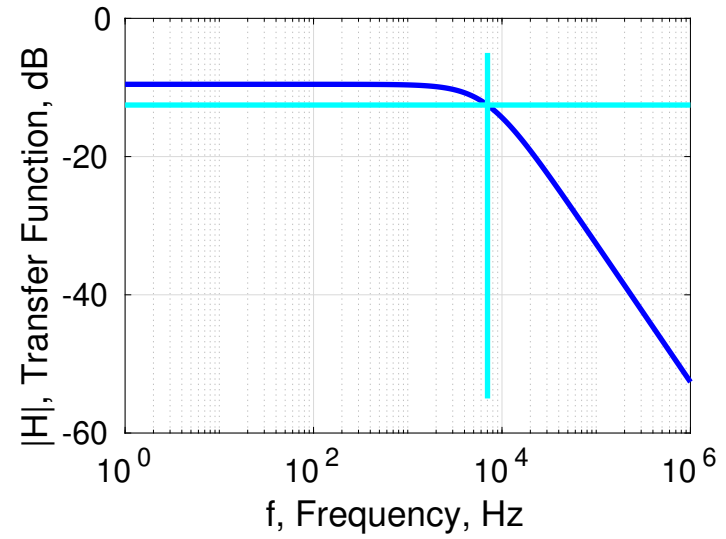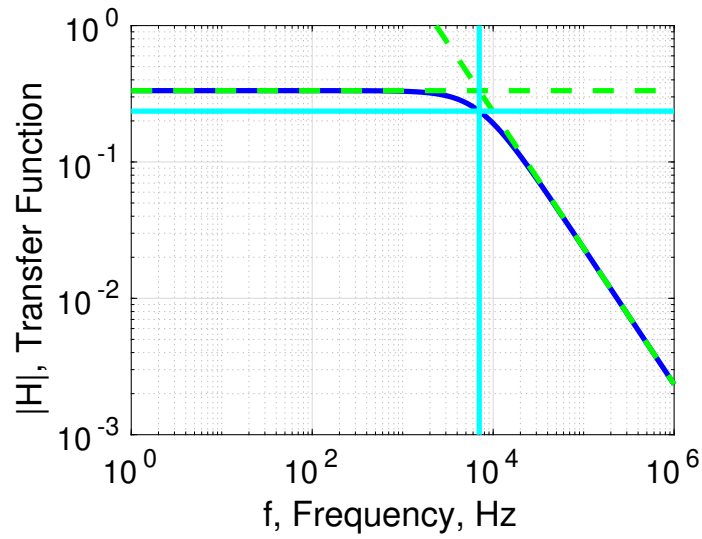


# Example Circuit: Active Notch Filter

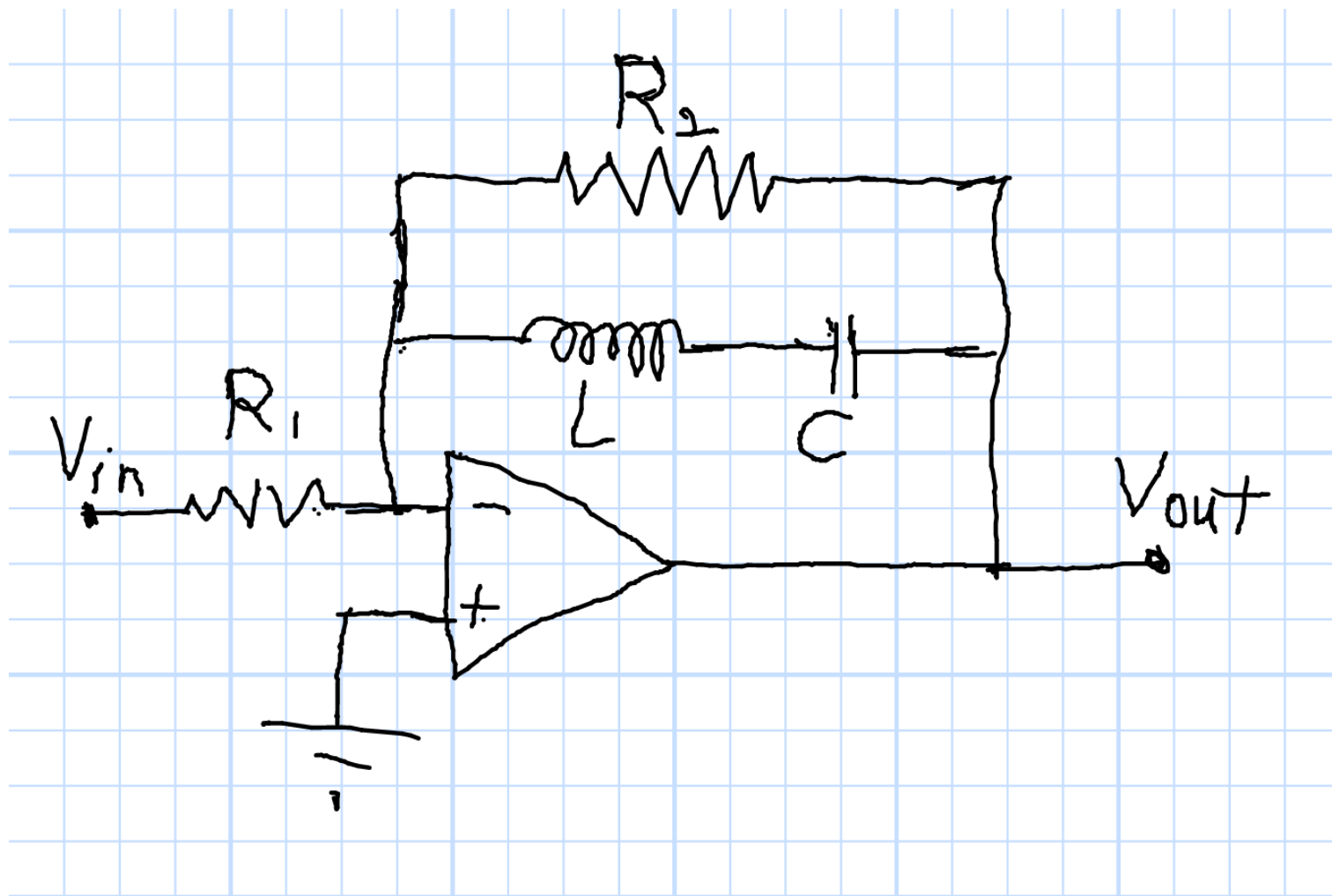

$$A_v = \frac{-Z_2}{Z_1}; \quad f \approx 0, Z_C \approx \infty \text{ or } f \rightarrow \infty, Z_L \approx \infty; \quad A_v = \frac{-R_2}{R_1}$$

# Notch Filter Solution

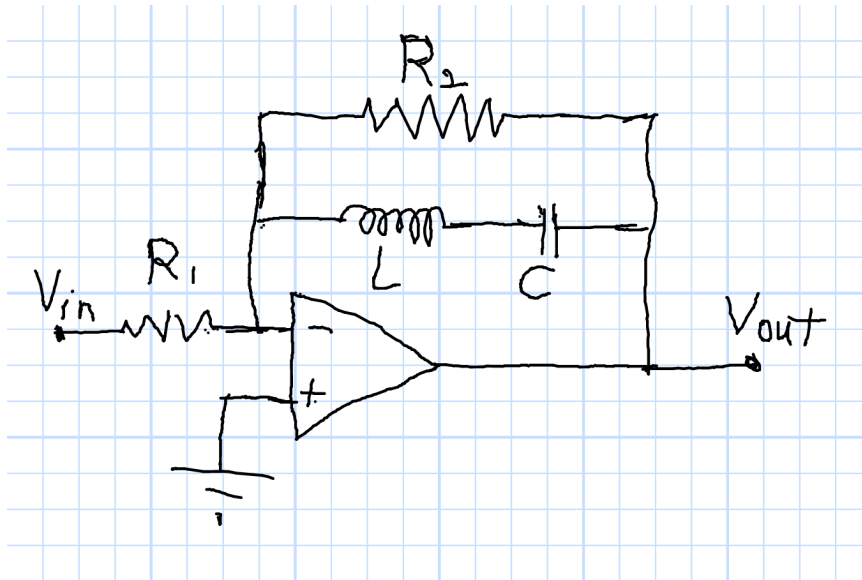

Design Frequency  $f_0 = 70\text{MHz}$ ,  
 $C = 2.3\text{nF}$ ,  $L = 1/\omega_0^2/C$   
 $R_1 = 50\Omega$ ,  $R_2 = 50\Omega$

Non-Ideal Components

$R_{CP} = 1\text{G}\Omega$ ,  $R_{LS}$  Various

- Ideal Solution

$$Z_1 = R_1$$

$$Z_2 = R_2 \parallel \left( j\omega L + \frac{1}{j\omega C} \right)$$

$$A_V = -\frac{Z_2}{Z_1}$$


$$\text{Max } |A_V| = \frac{R_2}{R_1}$$

- Actual with Series  $R_{LS}$  and Parallel  $R_{CP}$


$$Z_2 = R_2 \parallel$$

$$\left[ j\omega L + R_{LS} + \left( R_{CP} \parallel \frac{1}{j\omega C} \right) \right]$$

# Reactance Tradeoff

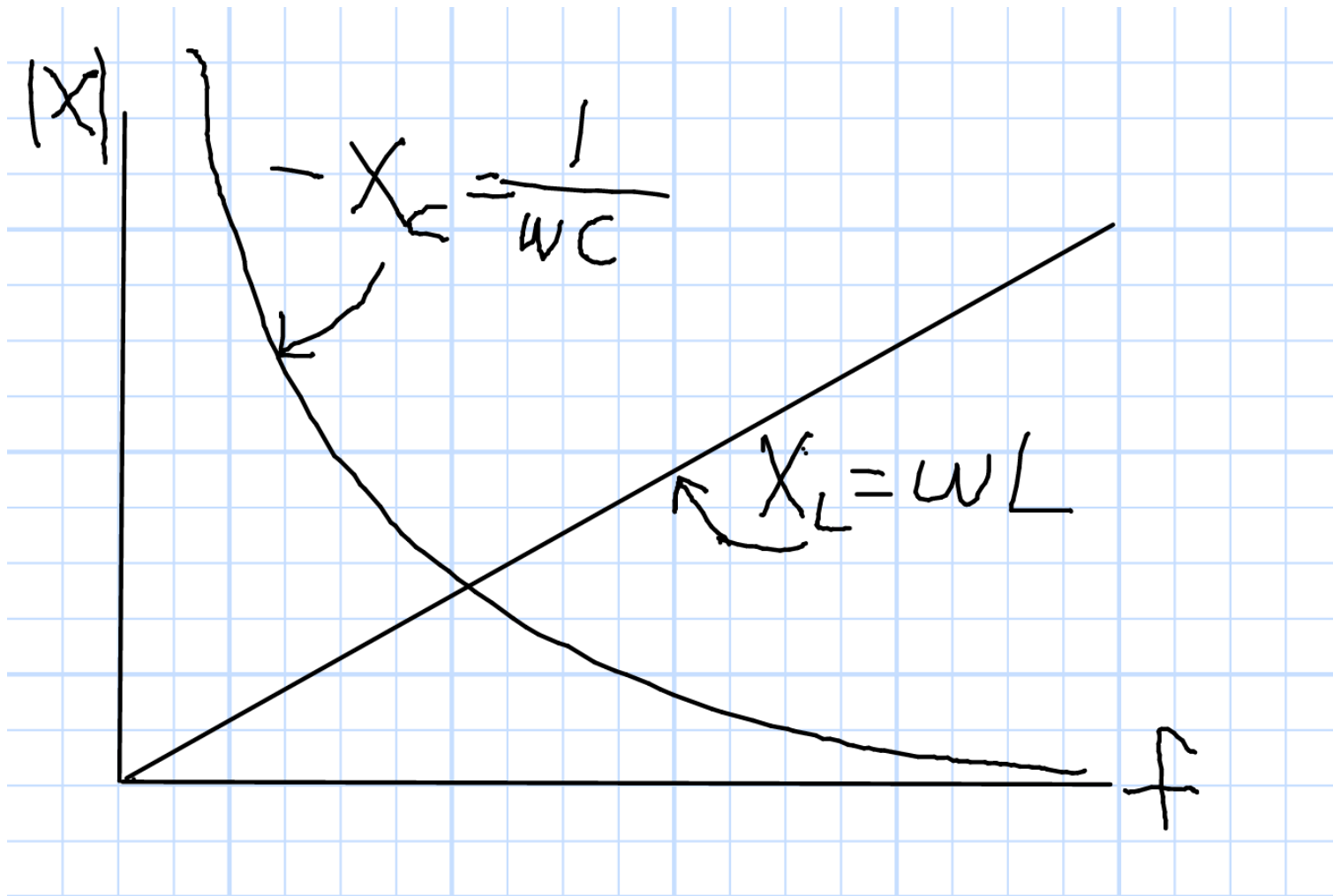


# Notch Transfer Function

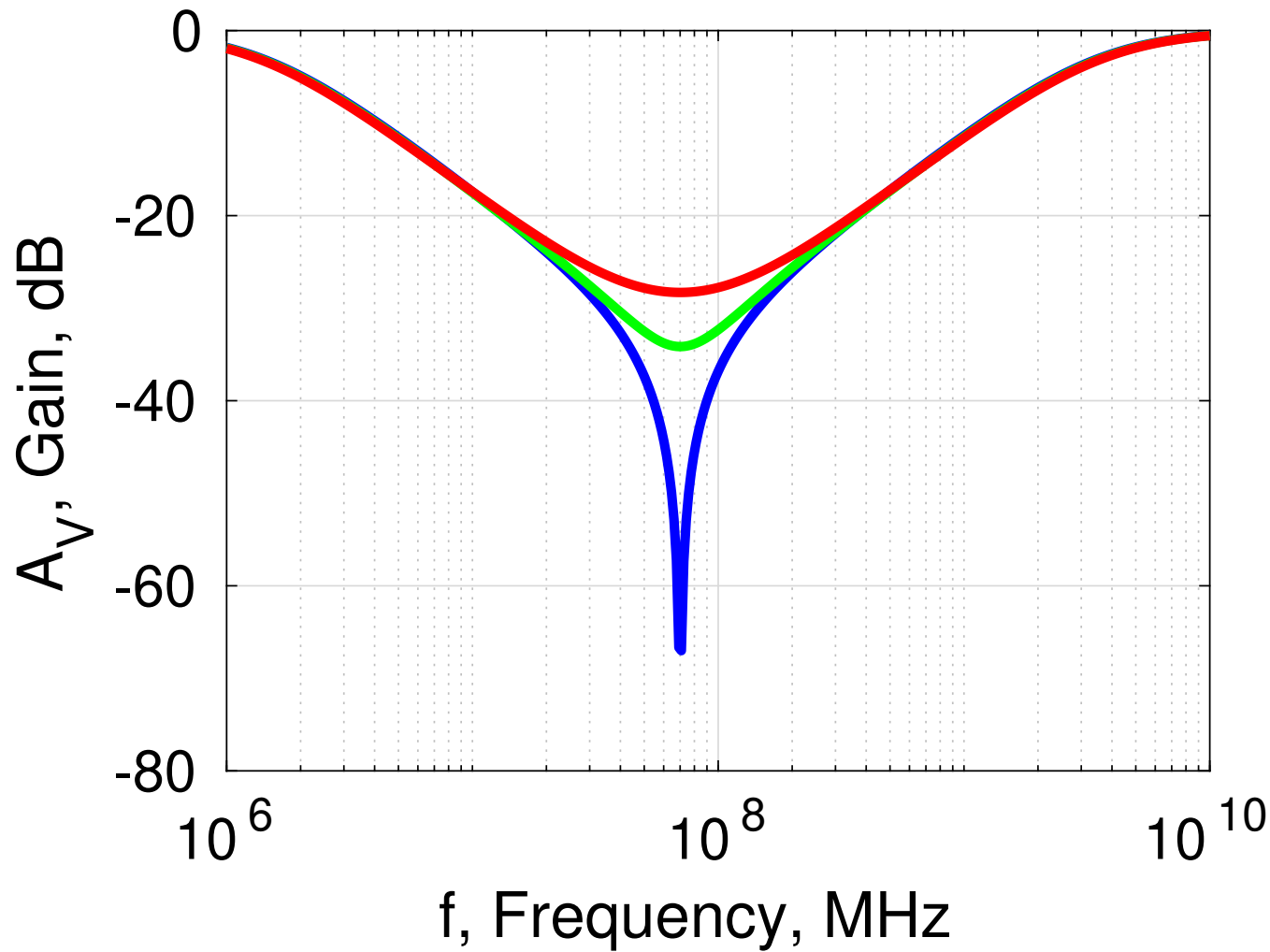

$R_{LS} = 0$  (Blue),  $1\Omega$  (Green),  $2\Omega$  (Red)

# Cascade Transfer Function

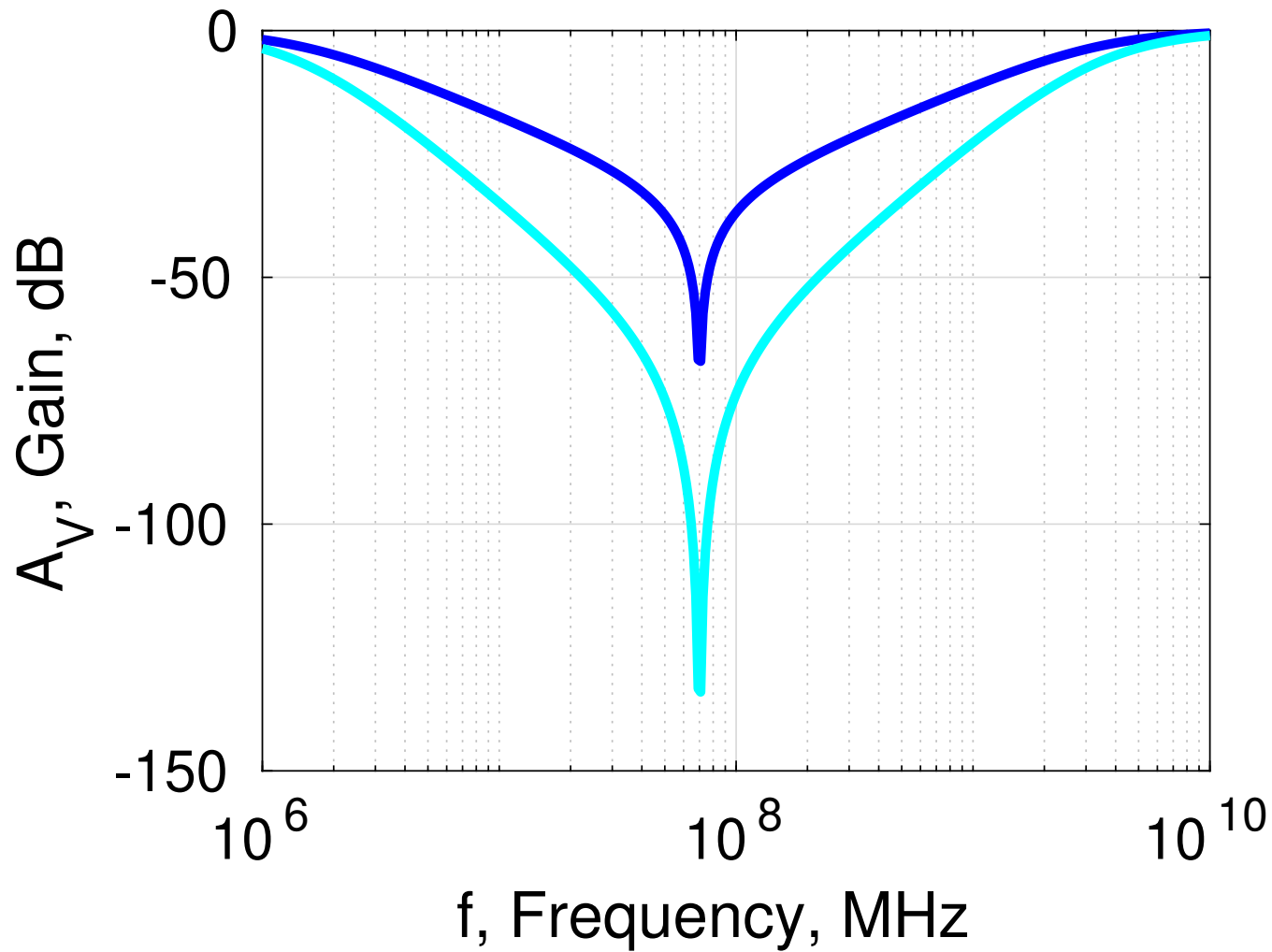


$R_{LS} = 0$  (Blue), 2 Cascaded Notches (Cyan)

# Cascaded Circuits

- General Rule:  $A = A_1 \times A_2 \dots$  (Add dB)
- Gain  $|A| > 1$  (0dB): Gain Increases with Cascaded Circuits
- Loss  $|A| < 1$  (0dB): Gain Decreases with Cascaded Circuits
- Slopes Increase with Cascaded Circuits
- Bandwidths Decrease

# First-Order Circuit

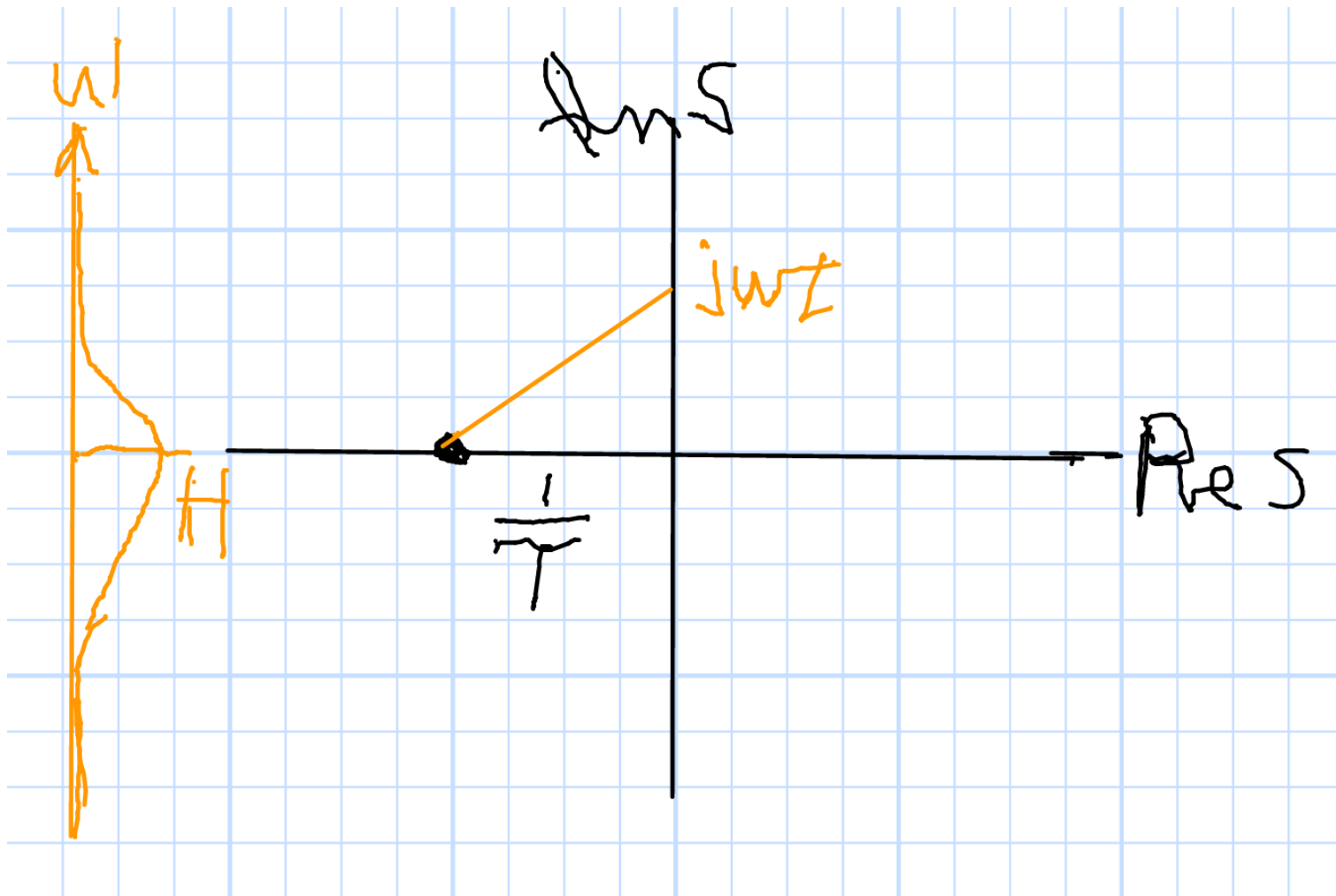



# Second-Order Circuit

