

Electrical Engineering

Week 4

Charles A. DiMarzio
EECE-2210
Northeastern University


Sep 2022

Week 4 Agenda

- Mesh Analysis
- Thévenin Equivalent Circuits
- Norton Equivalent Circuits
- Solutions Using Superposition
- Wheatstone Bridge

Mesh Analysis

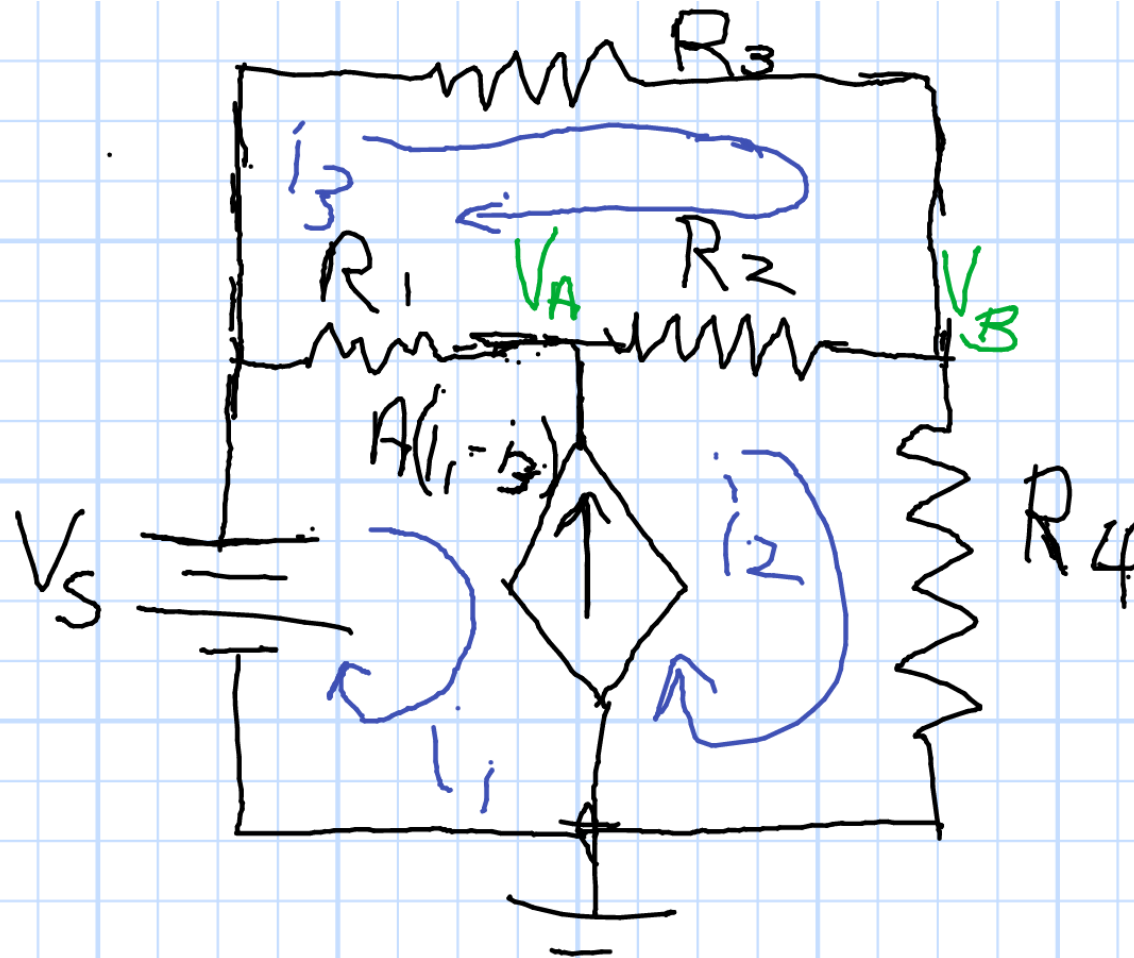Solve Circuits Using KVL Around All Loops




Remember Node Analysis

$$V_s = 12V \quad A = 3$$

$$R_1 = R_2 = 1k\Omega$$


$$R_3 = 5k\Omega \quad R_4 = 200\Omega$$

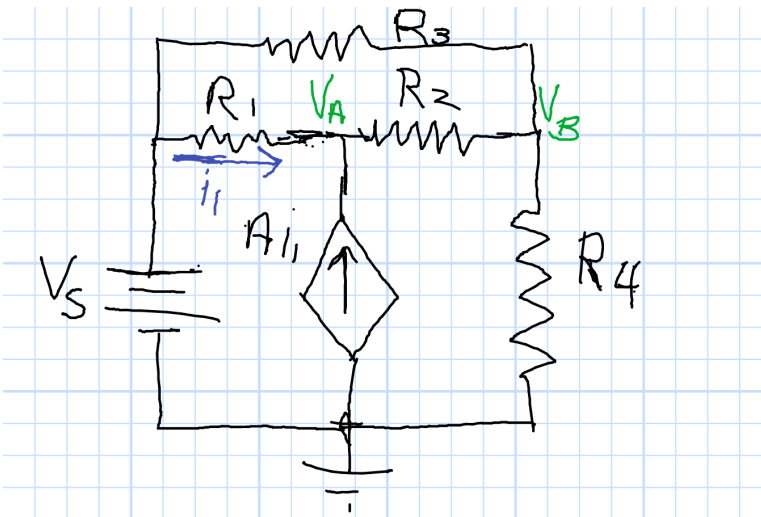

$$\mathbf{x} = \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} 10 \\ 2 \end{pmatrix} \text{ Volts}$$

Mesh Analysis

Problem of Dependent Source

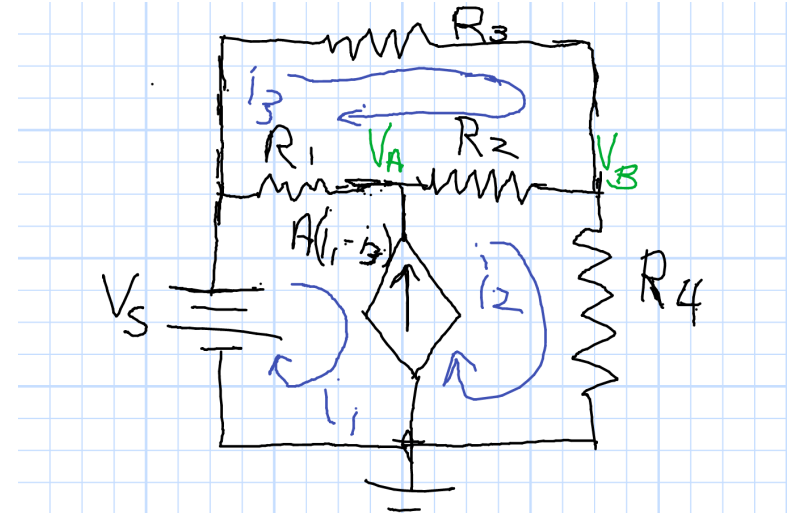

Superloop 1,2

$$v_s - i_1 R_1 + i_3 R_1 - i_2 R_2 + i_3 R_2 - i_2 R_4 = 0$$

Loop 3

$$i_3 R_3 + (i_3 - i_2) R_2 + (i_3 - i_1) R_1 = 0$$

Example of Mesh Analysis

Dependent Source

$$A(i_1 - i_3) = i_2 - i_1$$

$$(A + 1)i_1 - i_2 - Ai_3 = 0$$

Previous Page

$$v_s - i_1R_1 + i_3R_1 - i_2R_2 + i_3R_2 - i_2R_4 = 0$$

$$i_3R_3 + (i_3 - i_2)R_2 + (i_3 - i_1)R_1 = 0$$

Reorder

$$(A + 1)i_1 - i_2 - Ai_3 = 0$$

$$-R_1i_1 - (R_2 + R_4)i_2 + (R_1 + R_2)i_3 = -v_s$$


$$-R_1i_1 - R_2i_2 + (R_1 + R_2 + R_3)i_3 = 0$$

$$V_s = 12V \quad A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

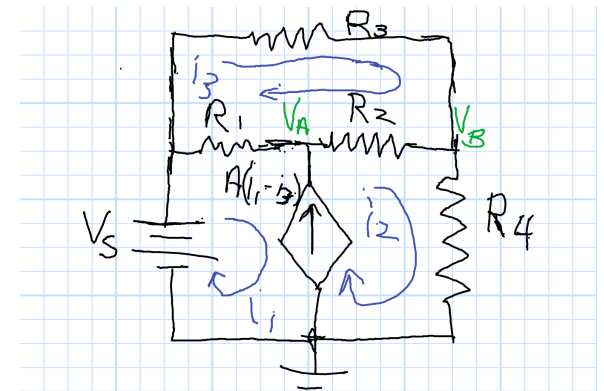

Mesh Analysis Solution

Previous Page

$$(A + 1)i_1 - i_2 - Ai_3 = 0$$

$$-R_1i_1 - (R_2 + R_4)i_2 + (R_1 + R_2)i_3 = -v_s$$

$$-R_1i_1 - R_2i_2 + (R_1 + R_2 + R_3)i_3 = 0$$


$$\mathcal{M} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 0 \\ -v_s \\ 0 \end{pmatrix}$$

$$V_s = 12V \quad A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

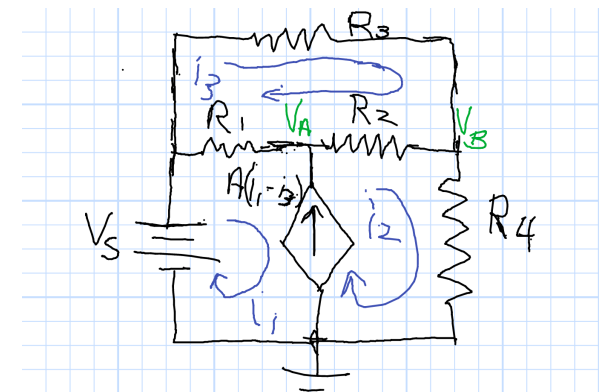

Matlab Mesh Results

```
>> vs=12;A=3;R1=1000;R2=R1;...
R3=5000;R4=200;y=[0;-vs;0];
>> M=[A+1,-1,-A;...
-R1,-(R2+R4),R1+R2;...
-R1,-R2,R1+R2+R3]
```

M =

```
     4     -1     -3
-1000  -1200  2000
-1000  -1000  7000
```

```
>> x=inv(M)*y
```

x =

```
 0.0040
 0.0100
 0.0020
```

```
>> vBcheck=x(2)*R4
```


```
vBcheck =    2
```

$$V_s = 12V \quad A = 3$$

$$R_1 = R_2 = 1k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 200\Omega$$

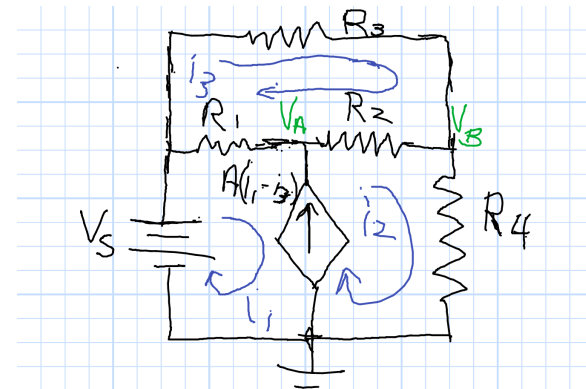



Node Solution

$$\begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} 10 \\ 2 \end{pmatrix} \text{Volts}$$

```
>> vAcheck=vBcheck+x(2)*R2-x(3)*R2
```

```
vAcheck =    10
```

Thévenin Equivalent Circuit

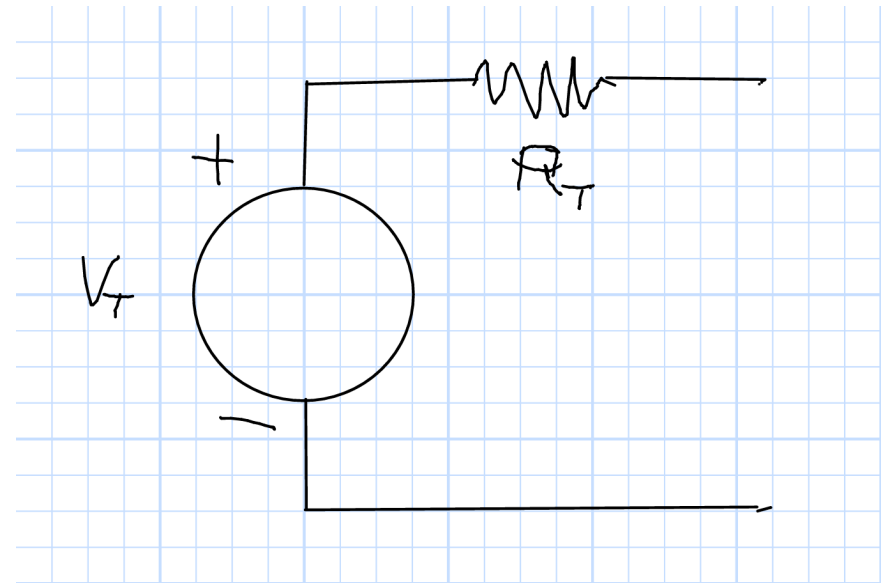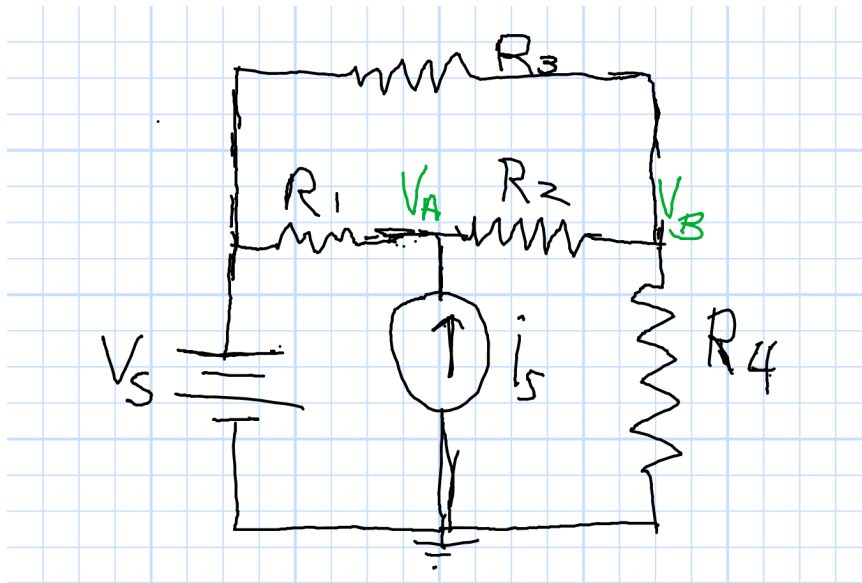

R_4 is the Load: Draw a circuit for everything else.

Linear Circuits: i vs. v is a straight line.

We need two points to determine the line.


$i = 0$: Open Circuit Voltage. $v = 0$: Short-Circuit Current

Load Resistor: $i = \frac{v}{R_4}$

Solution: Voltage Divider

Everything Else: $i = \frac{v_T - v}{R_T}$


Thévenin Concept

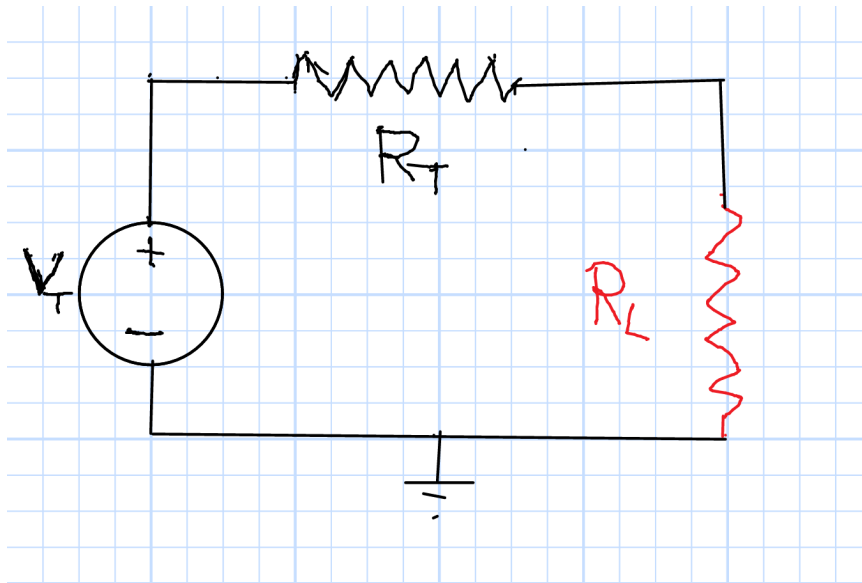

Circuit Equation

$$i = \frac{v_T - v}{R_T}$$

Load Line



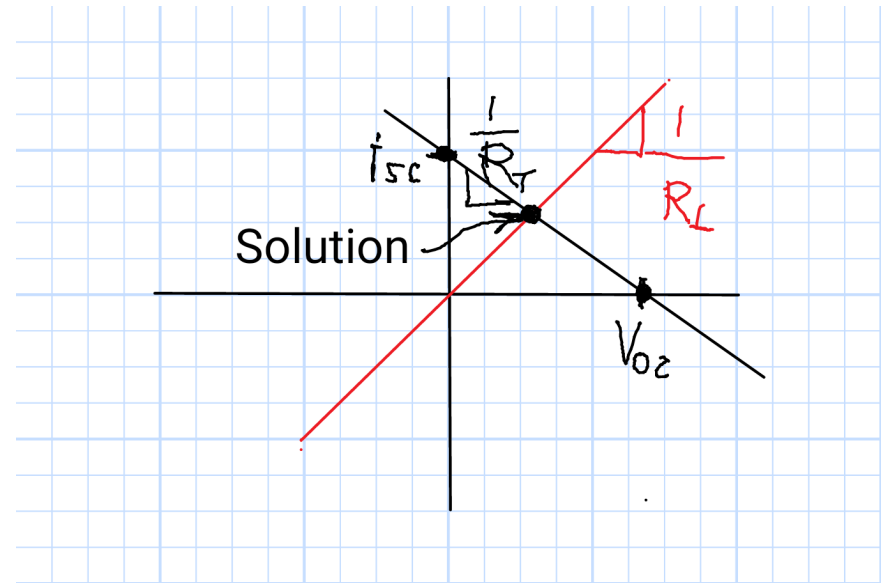


Load Equation

$$i = \frac{v}{R}$$



Solution is at the intersection.

Thévenin Calculation

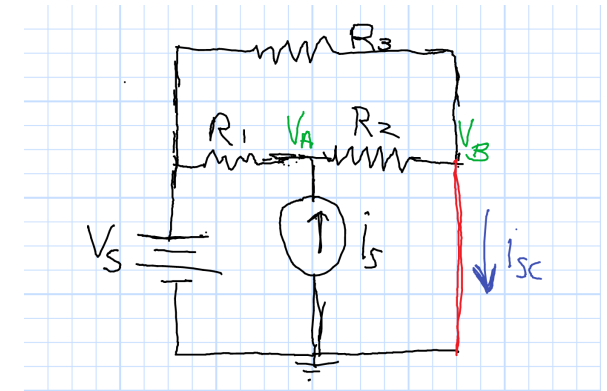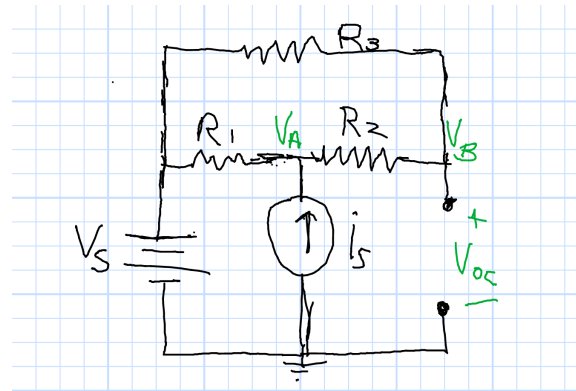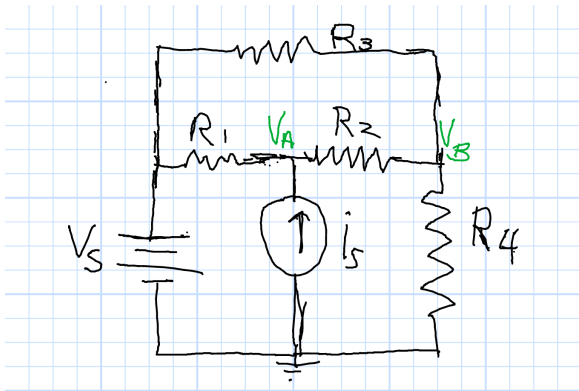

- Calculate Open–Circuit Voltage, v_{oc} .
- Calculate Short–Circuit Current, i_{sc} .
- Find Equivalent Circuit, $v_T = v_{oc}$ and $R_T = \frac{v_{oc}}{i_{sc}}$.

Zeroing All Sources

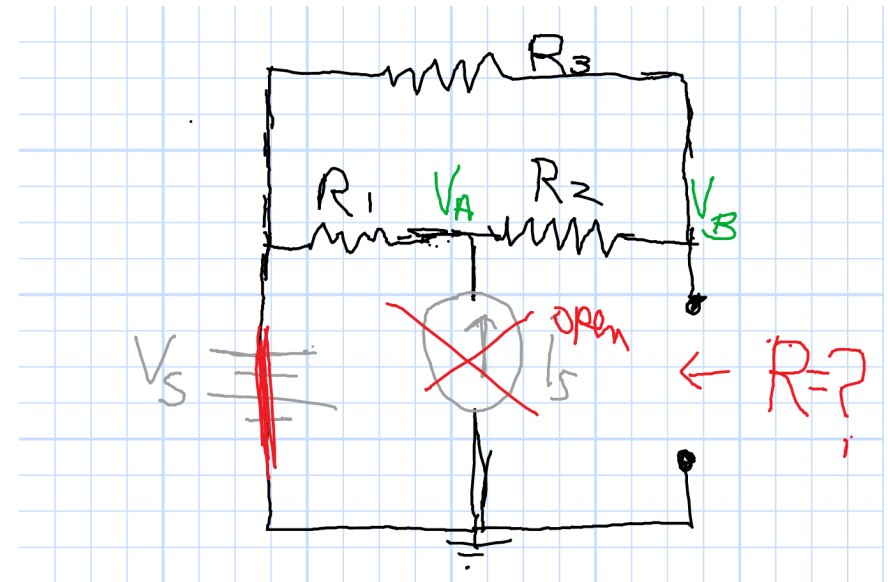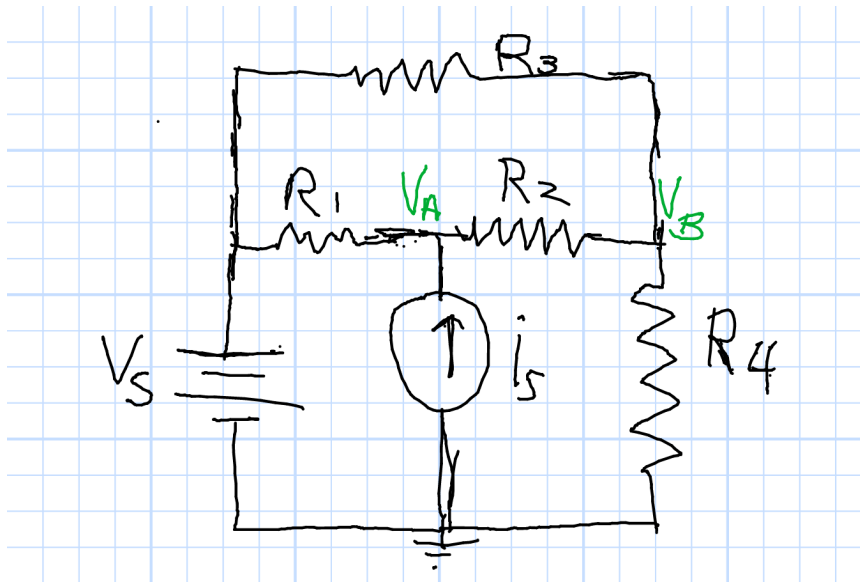

Alternative to Compute R_T

Voltage Sources Shorted ($v = 0$)


Current Sources Opened ($i = 0$)

Use Series and Parallel Combinations

Do This if v_{oc} or i_{sc} Looks Messy.


In This Example, $R_T = (R_1 + R_2) \parallel R_3 = 1430\text{Ohms}$

Thévenin Example: Parallel Batteries

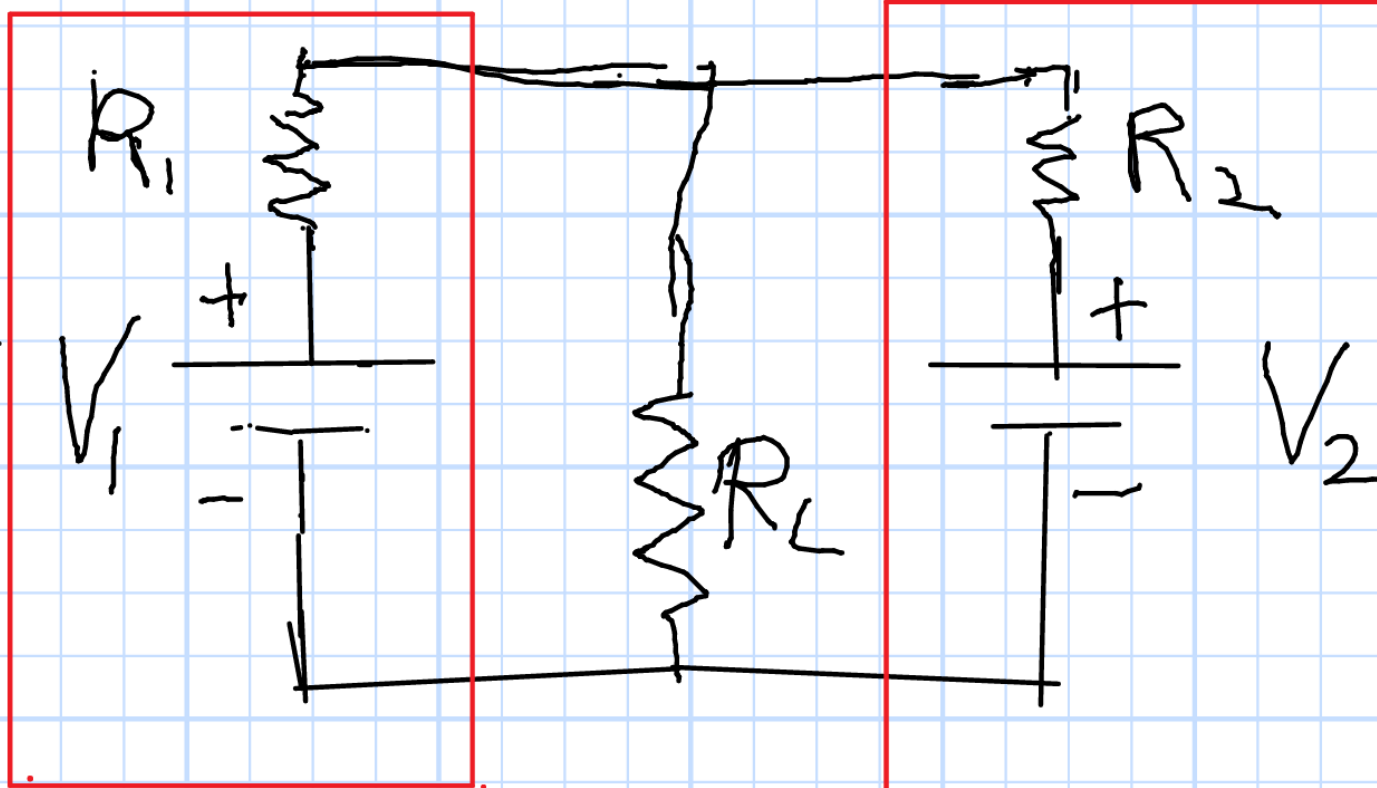


Parallel Batteries Solution
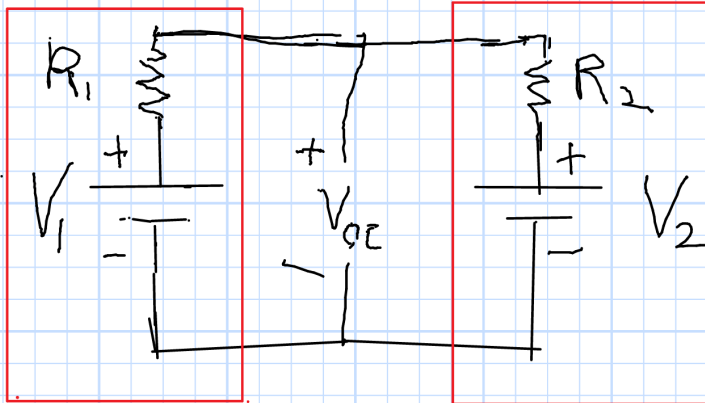
$$V_1 = 12\text{V}, R_1 = 1\Omega, V_2 = 11.9\text{V}, R_2 = 3\Omega$$



Voltage Divider
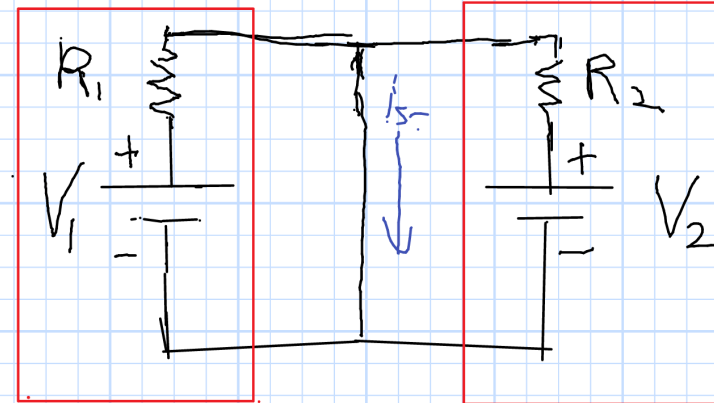
$$\begin{aligned} v_{oc} &= v_1 - (v_1 - v_2) \frac{R_1}{R_1 + R_2} \\ &= v_1 \frac{R_2}{R_1 + R_2} + v_2 \frac{R_1}{R_1 + R_2} \\ &= \frac{v_1 R_2 + V_2 R_1}{R_1 + R_2} \\ &= 11.97\text{V} \end{aligned}$$





KCL

$$i_{sc} = \frac{v_1}{R_1} + \frac{v_2}{R_2} = \frac{v_1 R_2 + v_2 R_1}{R_1 R_2}$$

Thévenin Resistor

$$R_T = \frac{v_{oc}}{i_{sc}} = 0.75\Omega$$

Norton Equivalent Circuit

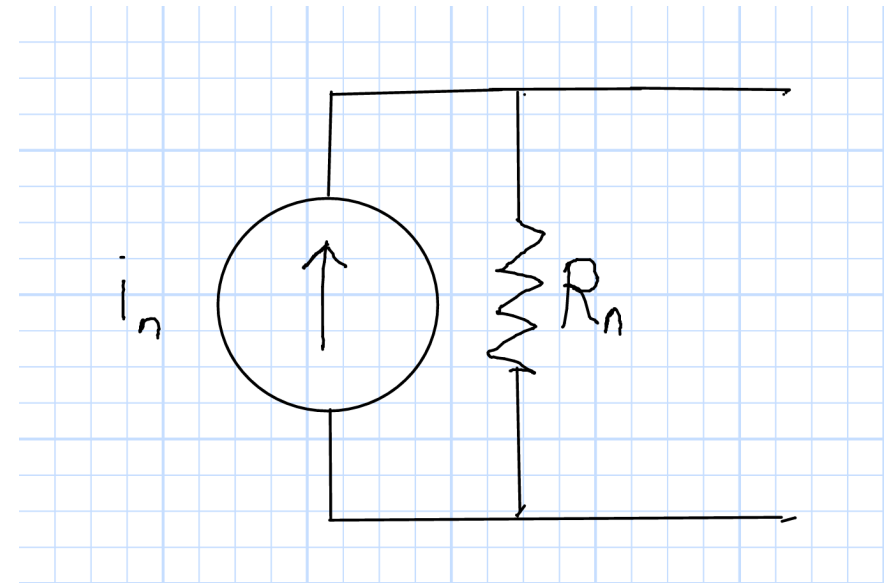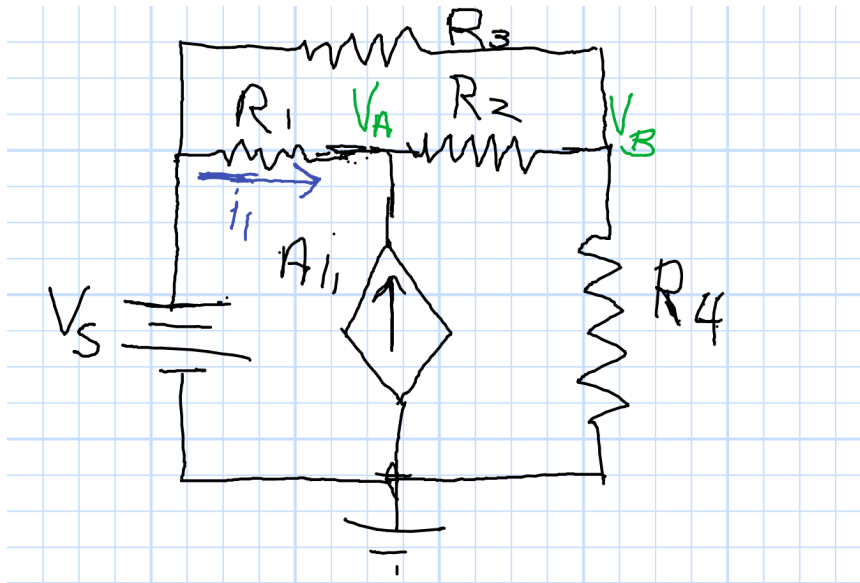

R_4 is the Load: Draw a circuit for everything else.

Linear Circuits: i vs. v is a straight line.

We need two points to determine the line.


$i = 0$: Open Circuit Voltage. $v = 0$: Short-Circuit Current

Load Resistor: $i = \frac{v}{R_4}$

Solution: Current Divider

Everything Else: $i = i_N - \frac{v}{R_N}$

Norton Example

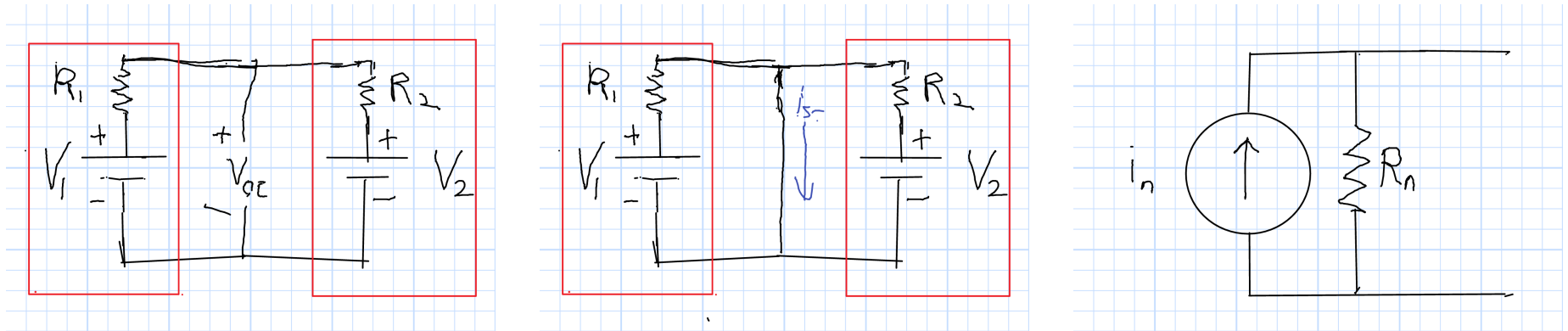

From Thévenin Equivalent


$$v_{oc} = 11.97\text{V} \quad R_T = 0.75\Omega$$

$$i_{sc} = \frac{v_1}{R_1} + \frac{v_2}{R_2} = \frac{v_1 R_2 + v_2 R_1}{R_1 R_2} = 15.96\text{A}$$


Norton Equivalent

$$i_N = i_{sc} = 15.96\text{A} \quad R_N = R_T = 0.75\Omega$$


Superposition Example

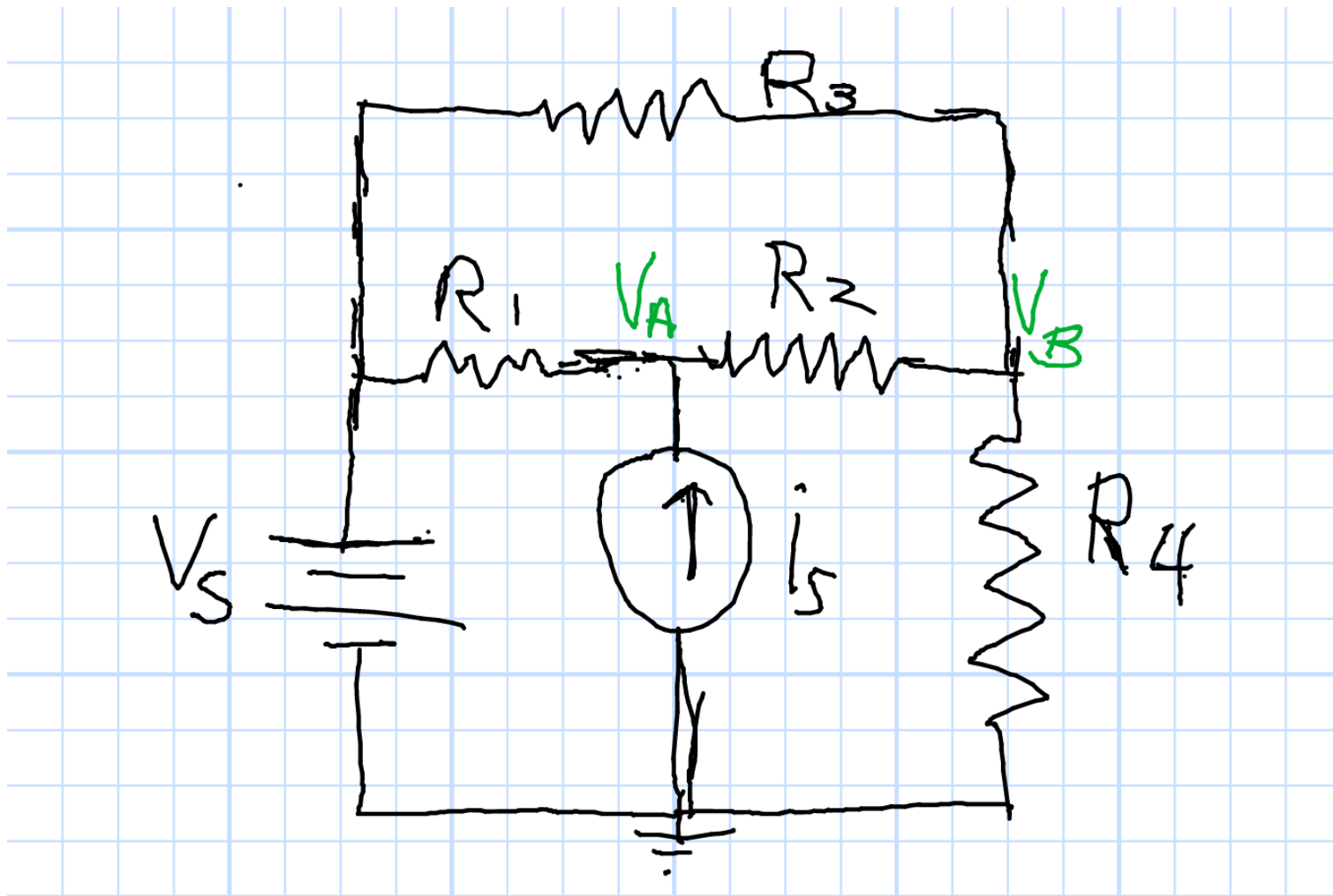


Zeroing Sources

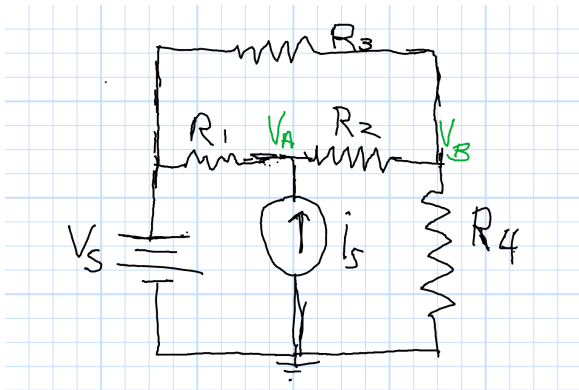

Original

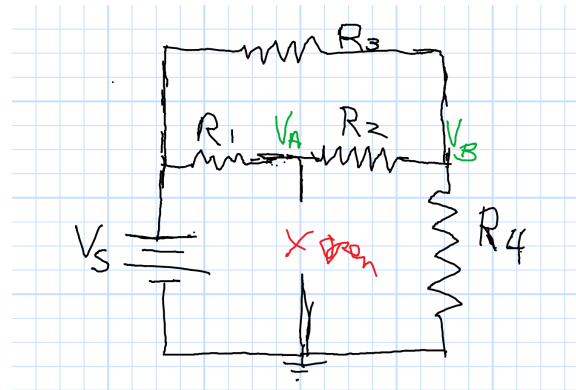


Zero Current Source
Open

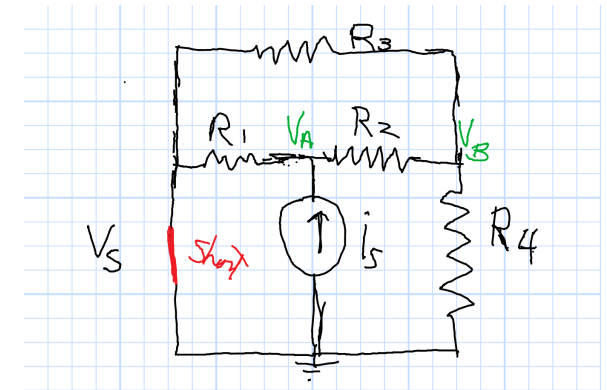

Zero Voltage Source
Short

- Zero the Sources One at a Time
- Solve the Circuit for All Unknowns in Each Case
- Sum the Results

Superposition Solution

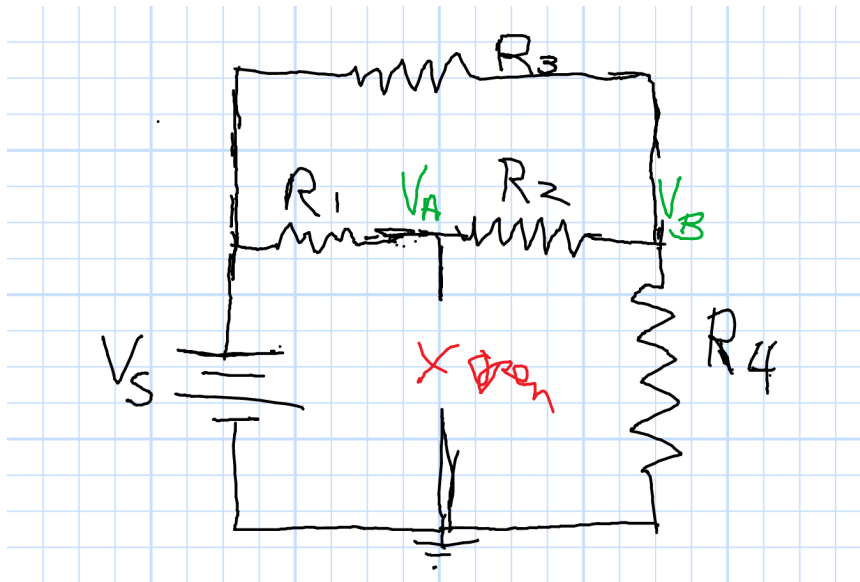


Series-Parallel Solution

$$i = v_s / [(R_1 + R_2) \parallel R_3] + R_4$$

$$v_B = iR_4$$

Voltage Divider
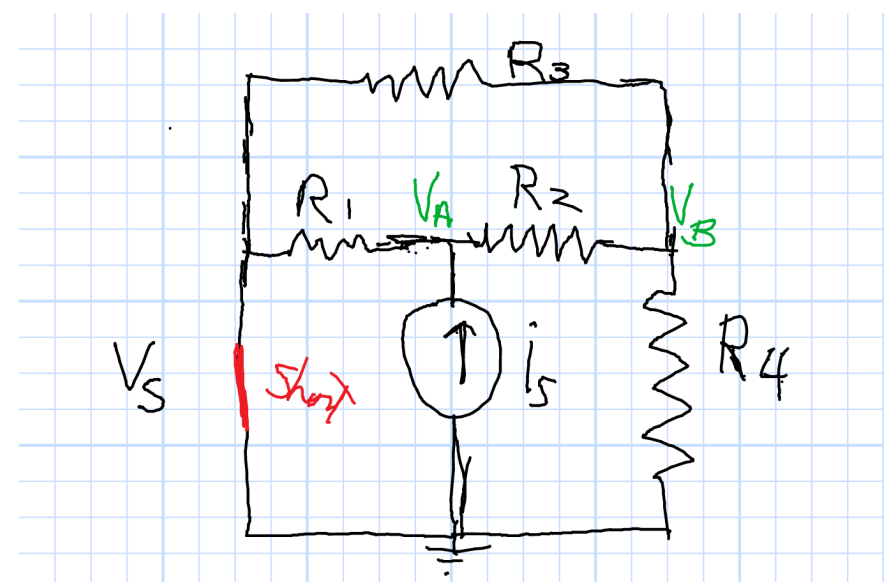
$$v_A = v_s + (v_B - v_s) \frac{R_1}{R_1 + R_2}$$



Series-Parallel Solution

$$v_A = i_s \{R_1 \parallel [R_2 + (R_3 \parallel R_4)]\}$$




Current Divider (i_2 to the right)

$$i_2 = i_s \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)}$$

$$v_B = i_2 (R_3 \parallel R_4)$$

Conclusion
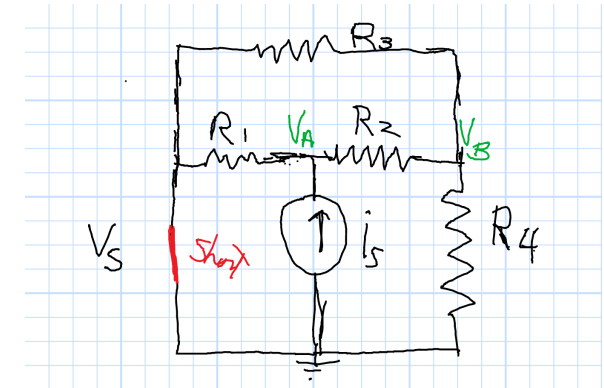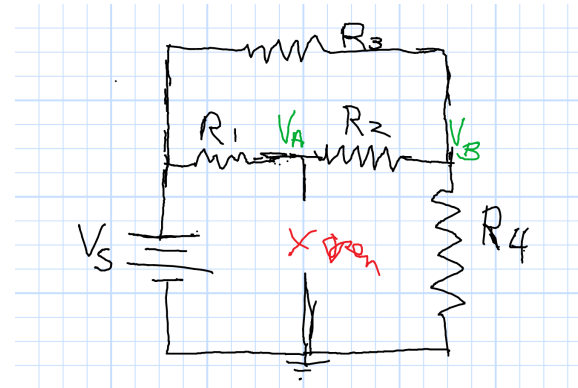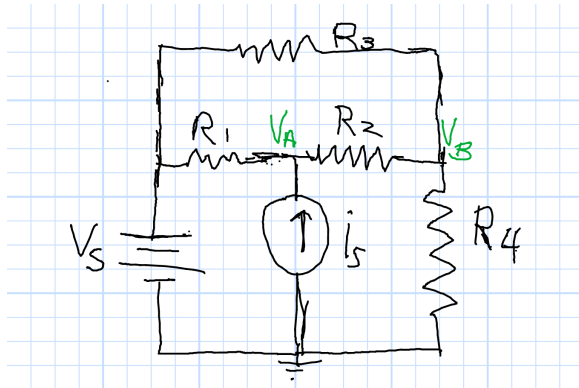
$$V_s = 12V, i_s = 6mA, R_1 = R_2 = 1k\Omega, R_3 = 5k\Omega, R_4 = 200\Omega$$



V_{total}

=

v_1

+

v_2

$$v_A = 6.74V$$

$$v_B = 1.47V$$

$$v_A = 3.26V$$

$$v_B = 0.53V$$


$$V_A = 10.0V$$

$$V_B = 2.0V$$

Same Result We Had Before.

Parallel Batteries: Superposition
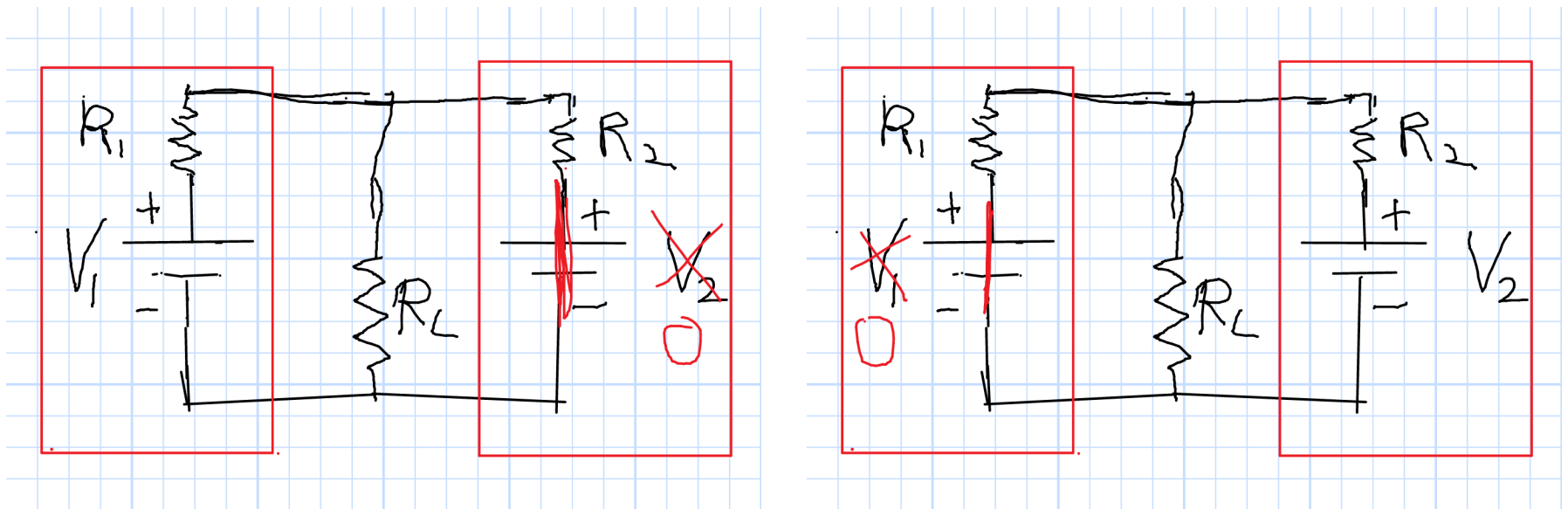
$$V_1 = 12\text{V}, R_1 = 1\Omega, V_2 = 11.9\text{V}, R_2 = 3\Omega$$




$$v_L = v_1 \frac{R_L \parallel R_2}{R_1 + (R_L \parallel R_2)} = 7.83\text{V}$$

$$v_L = v_2 \frac{R_L \parallel R_1}{R_2 + (R_L \parallel R_1)} = 2.59\text{V}$$


$$v_L = 7.83\text{V} + 2.59\text{V} = 10.4\text{V}$$

Balancing the Load

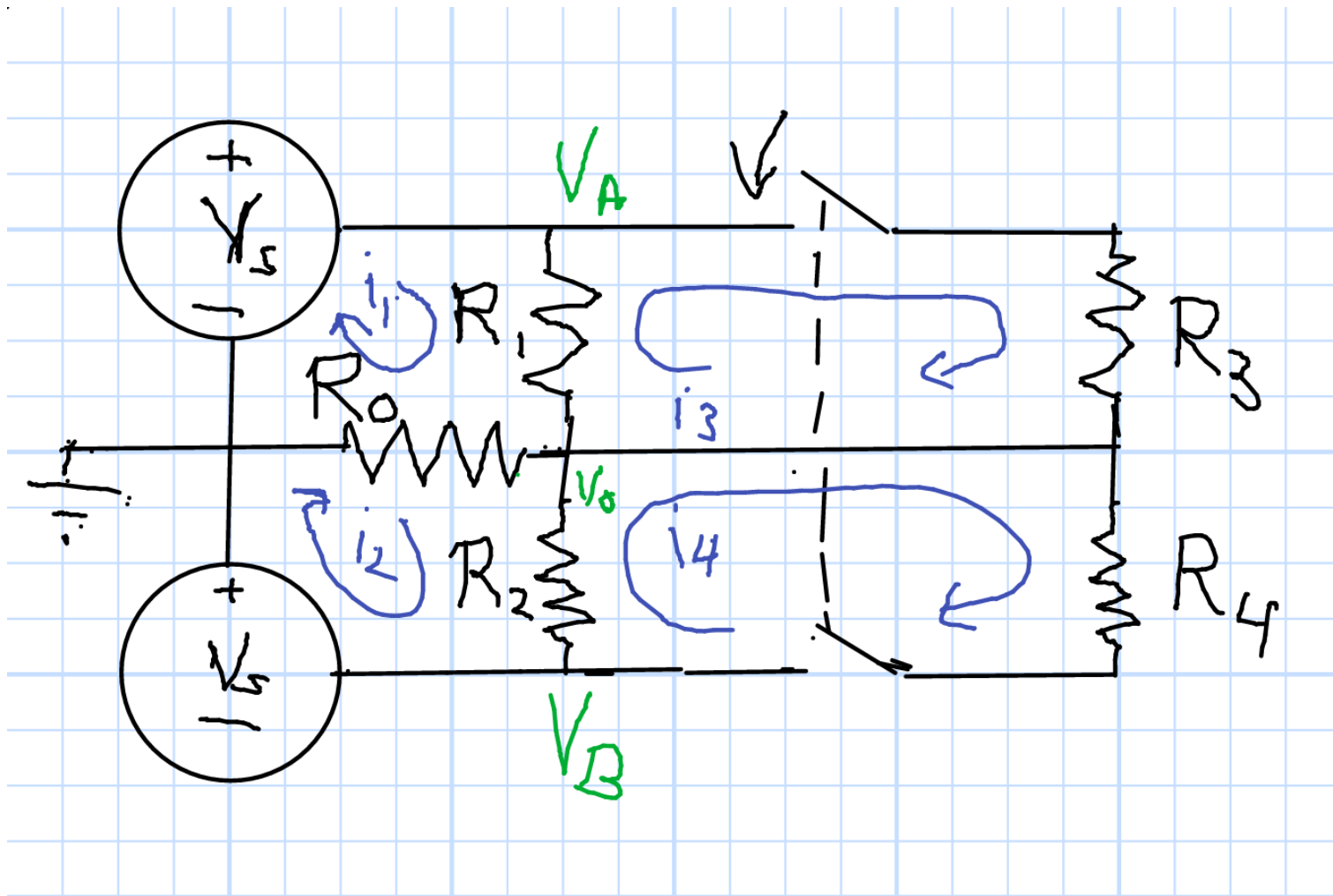

Source: $v_s = 120\text{V RMS}$. Bad Ground: $R_0 = 20\Omega$
 Lights: $R_1 = 14.4\Omega$, $R_2 = 144\Omega$. Stove: $R_3 = R_4 = 7.2\Omega$.

Stove Off

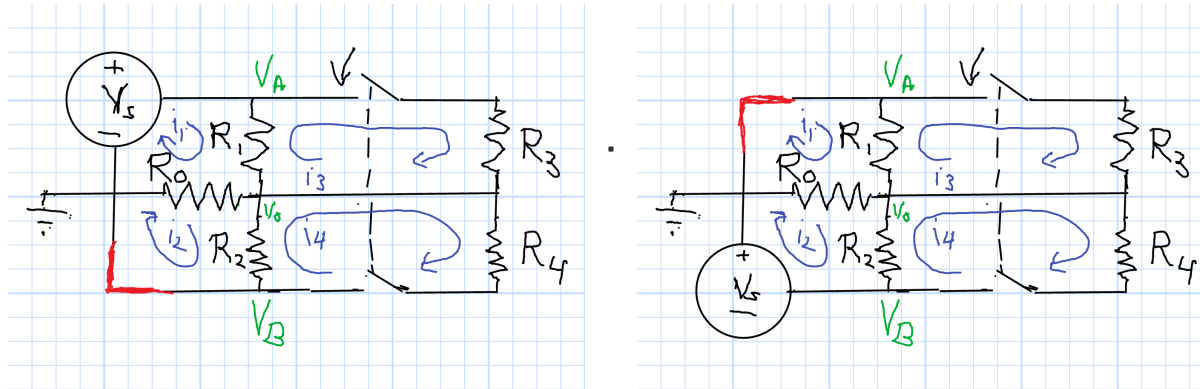

Voltage Divider with Top Source: Zero Bottom so $R_2 \parallel R_0$

$$v_1 = v_s \frac{R_1}{R_1 + (R_0 \parallel R_2)}$$

$$v_2 = v_s \frac{R_0 \parallel R_2}{R_1 + (R_0 \parallel R_2)}$$

Bottom Source: Zero Top so $R_1 \parallel R_0$

$$v_1 = -v_s \frac{R_1 \parallel R_0}{R_2 + (R_0 \parallel R_1)}$$

$$v_2 = -v_s \frac{R_2}{R_2 + (R_0 \parallel R_1)}$$

Total

$$v_1 = 60.7\text{V}$$

$$v_2 = 179.3\text{V}$$

$$\text{Check } v_1 + v_2 = 240\text{V}$$

$$v_A = 120\text{V}$$

$$v_B = -120\text{V}$$

$$v_0 = v_A - v_1 = 59.3\text{V}$$

Stove On: Balance Load

Same as Previous Page, but with $R_1 \parallel R_3$ and $R_2 \parallel R_4$

Top Source

$$v_1 = v_s \frac{R_1 \parallel R_3}{(R_1 \parallel R_3) + (R_0 \parallel R_2 \parallel R_4)}$$

$$v_2 = v_s \frac{R_0 \parallel R_2 \parallel R_4}{(R_1 \parallel R_3) + (R_0 \parallel R_2 \parallel R_4)}$$

Bottom Source

$$v_1 = -v_s \frac{R_1 \parallel R_3 \parallel R_0}{(R_2 \parallel R_4) + (R_0 \parallel R_1 \parallel R_3)}$$

$$v_2 = -v_s \frac{R_2 \parallel R_4}{(R_2 \parallel R_4) + (R_0 \parallel R_1 \parallel R_3)}$$

Total

$$v_1 = 101.4\text{V}$$

$$v_2 = 138.6\text{V}$$

$$\text{Check } v_1 + v_2 = 240\text{V}$$

$$v_A = 120\text{V}$$

$$v_B = -120\text{V}$$

$$v_0 = v_A - v_1 = 18.6\text{V}$$

Comparison

Stove Off

$$v_1 = 60.7\text{V} \quad v_2 = 179.3\text{V}$$

$$v_A = 120\text{V} \quad v_B = -120\text{V} \quad v_0 = v_A - v_1 = 59.3\text{V}$$

Lights Represented by R_1 Are Dim

Lights Represented by R_2 Are Too Bright

Stove On

$$v_1 = 101.4\text{V} \quad v_2 = 138.6\text{V}$$

$$v_A = 120\text{V} \quad v_B = -120\text{V} \quad v_0 = v_A - v_1 = 18.6\text{V}$$


Lights Represented by R_1 Become Brighter

Lights Represented by R_2 Become Dimmer

Better Balance

“Ground” Voltage, v_0 , Closer to Zero

Wheatstone Bridge

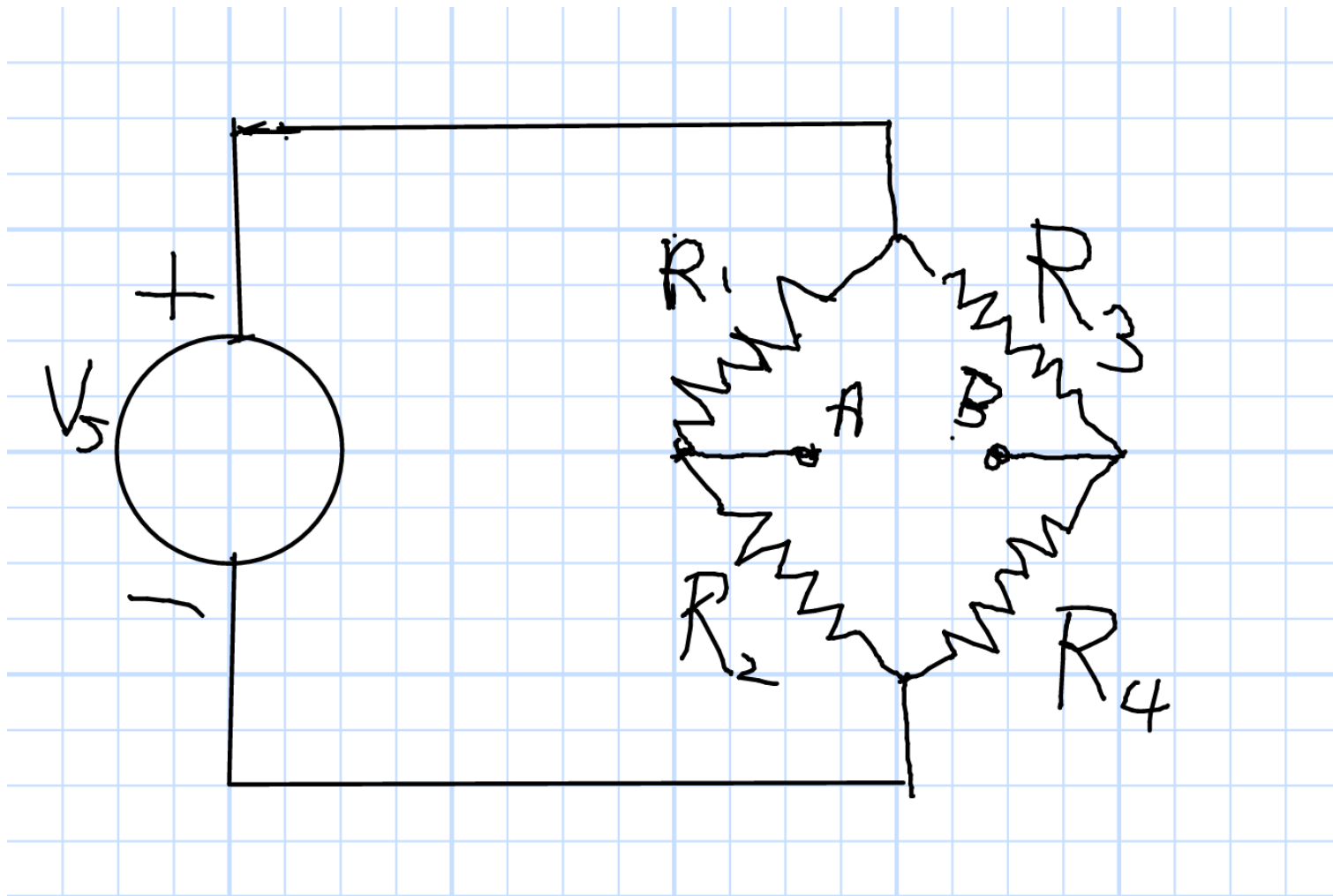

Balancing the Bridge


$$v_A = v_s \frac{R_2}{R_1 + R_2}$$

$$v_B = v_s \frac{R_3}{R_3 + R_4}$$

$$v_{BA} = v_s \left(\frac{R_2}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$

Application:

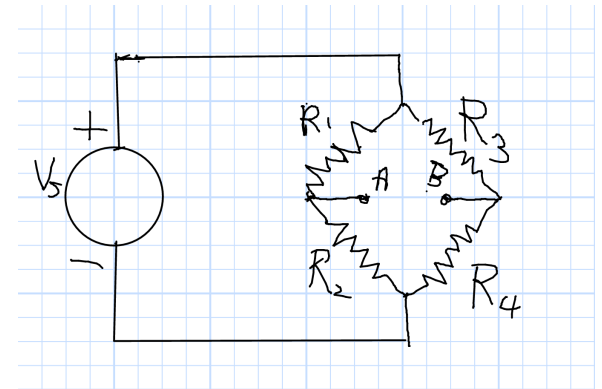- R_4 is Unknown
- R_2 is Variable and Calibrated
- R_1 and R_3 are Precision Resistors
- Adjust for $V_{BA} = 0$
- Solve for R_4



Strain Gauge


- R_4 is a Strain Gauge
- $R_4 = R_0 + \Delta R$
- $R_{1:3} = R_0$ Precision Resistors
- Calculate v_{AB}

$$v_{BA} = v_s \left(\frac{R_0}{2R_0} - \frac{R_0 + \Delta R}{2R_0 + \Delta R} \right)$$

$$v_{BA} = v_s \left(\frac{1}{2} - \frac{R_0 + \Delta R}{2R_0 + \Delta R} \right)$$

$$v_{BA} \approx v_s \left(\frac{1}{2} - \frac{R_0 + \Delta R}{2R_0} \right)$$
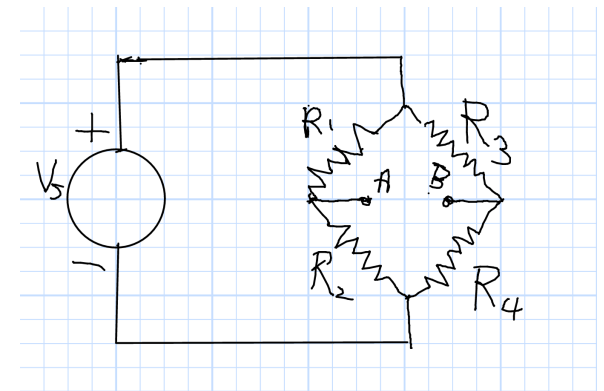
$$v_{BA} \approx -v_s \frac{\Delta R}{2R_0}$$




4 Balanced Strain Gauges

- $R_1 = R_4 = R_0 + \Delta R$ Are Strain Gauge
- $R_2 = R_3 = R_0 - \Delta R$ Measure Opposite Strain
- Calculate v_{AB}

$$v_{BA} = v_s \left(\frac{R_0 + \Delta R}{2R_0} - \frac{R_0 - \Delta R}{2R_0} \right)$$

$$v_{BA} = v_s \frac{2\Delta R}{2R_0}$$

$$v_{BA} = v_s \frac{\Delta R}{R_0}$$

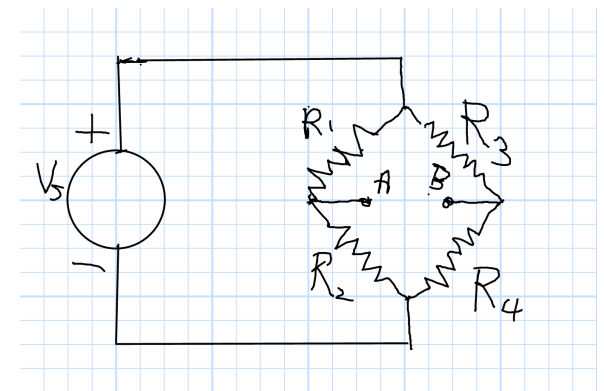

May Need a Variable to Get a Good Null