

Electrical Engineering




Week 5

Charles A. DiMarzio
EECE-2210
Northeastern University

Sep 2022

Week 5 Agenda: Operational Amplifiers

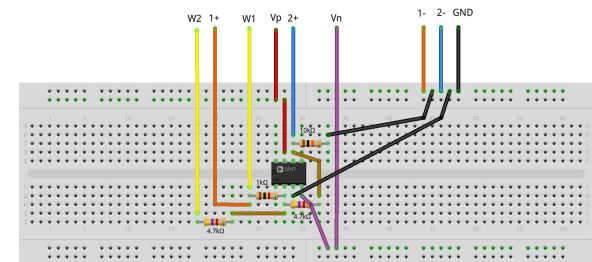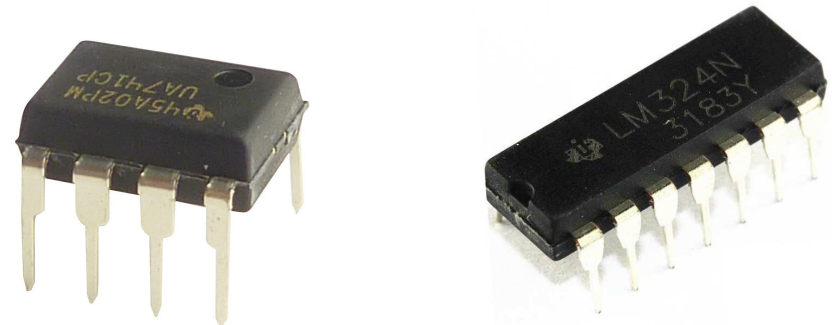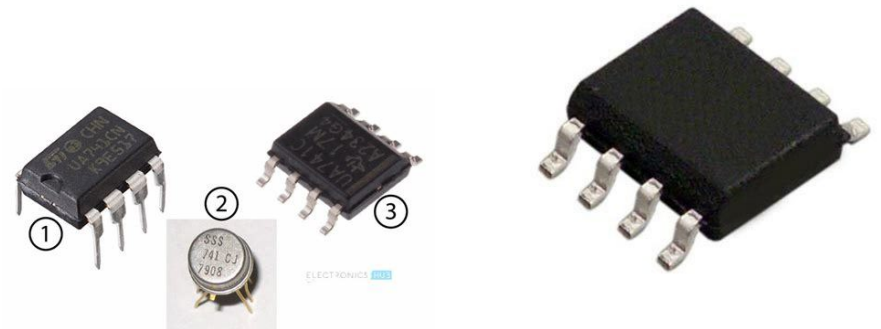
- Amplifiers
- The Basic Op Amp
- Circuit Equations
- Virtual Short,
Virtual Ground
- Negative Feedback
- Inverting Amplifier
- High Gain Amplifier
- Summing Junction
- Positive Feedback Briefly
- Non-Inverting Amplifier
- Other Amplifiers



Why?


- Why Amplifiers?
 - Increase Voltage
 - Increase Current
 - Control Impedance
- Why Now?
 - Prepare for Lab
 - Nice Fit with Equivalent Circuits
- Back to Capacitors and Inductors in 2 Weeks

An Amplifier Model

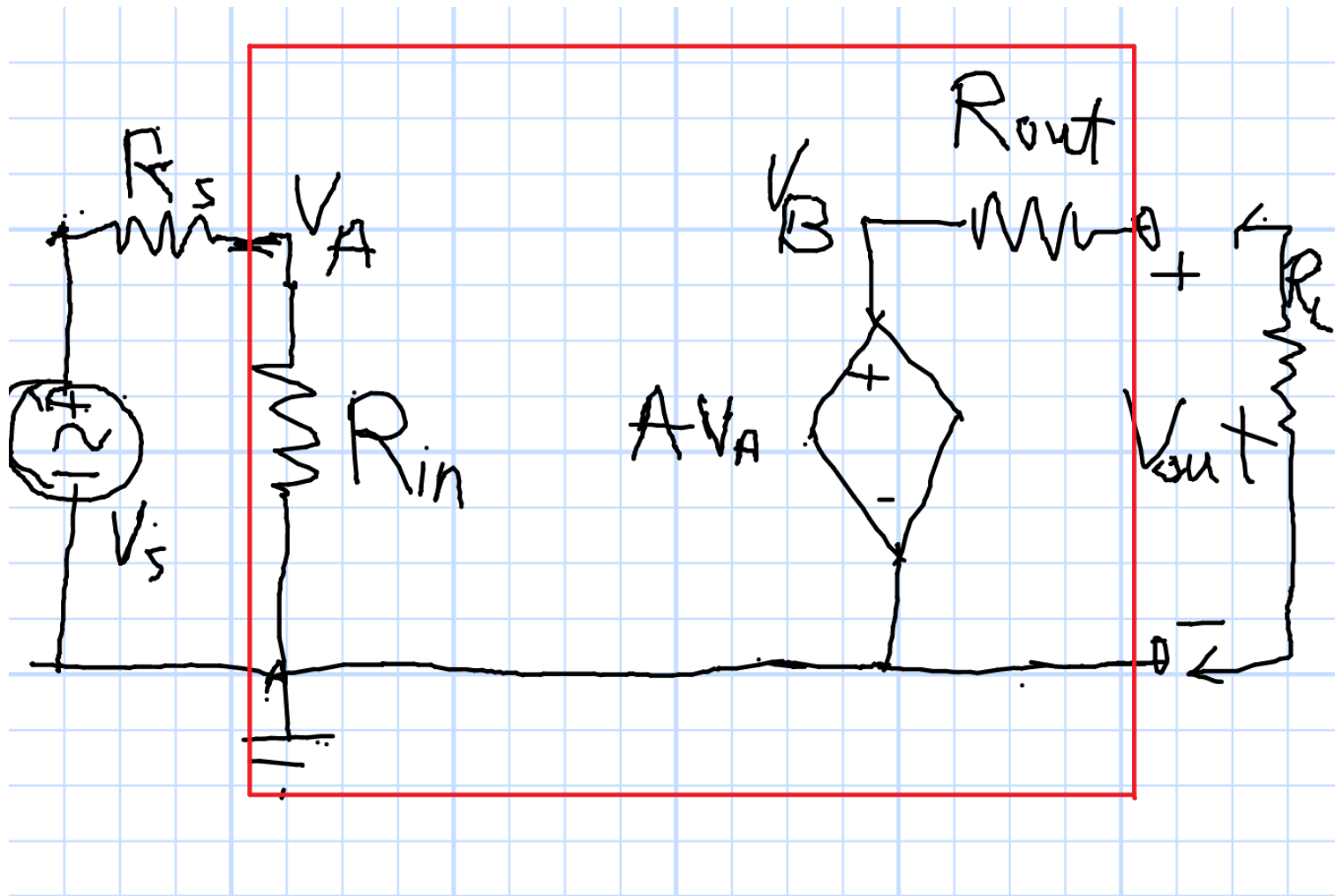

We want to Choose A , R_{in} , and R_{out}

Impedance Choices

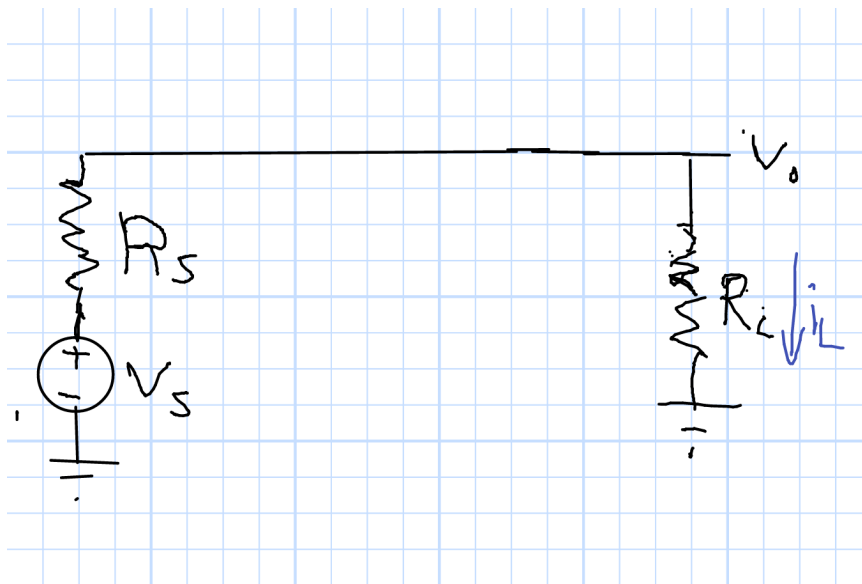

Voltage Divider

Maximum Voltage to Load

$$R_L \gg R_s$$

$$R_L \rightarrow \infty \text{ or } R_s \rightarrow 0$$

Maximum Power to Load


$$i_L = i = \frac{v_s}{R_s + R_L}$$

$$v_L = v_s \frac{R_L}{R_s + R_L}$$

$$p_L = v_s^2 \frac{R_L}{(R_s + R_L)^2}$$

$$R_L = R_s \quad P_L = \frac{v_s^2}{4R_L}$$

Input and Output Impedance

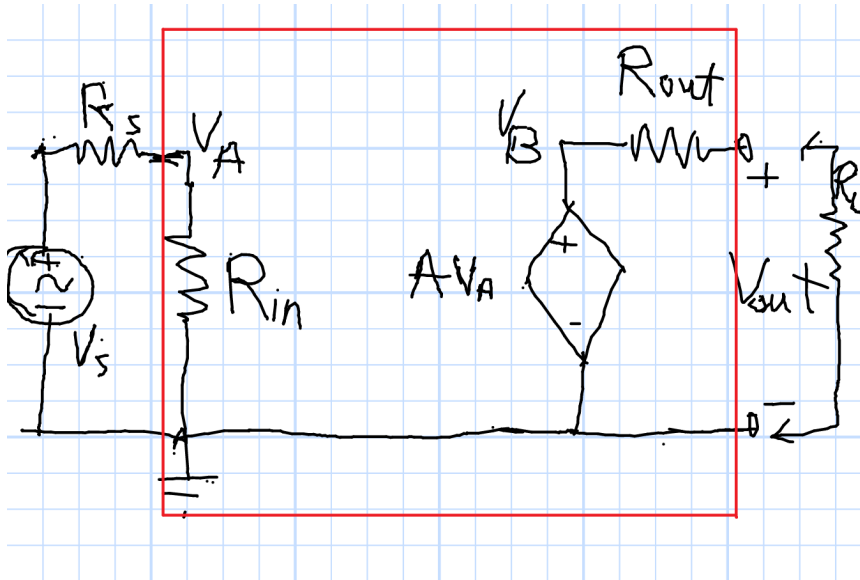

- Mix Input and Output Choices as Needed
- Maximum Power to Load for Minimum Reflected Power

Maximum Voltage

$$R_{in} \rightarrow \infty$$

$$R_{out} = 0$$

Maximum Power

$$R_{in} = R_s$$


$$R_{out} = R_L$$

Maximum Current

$$R_{in} = 0$$

$$R_{out} \rightarrow \infty$$


The Operational Amplifier

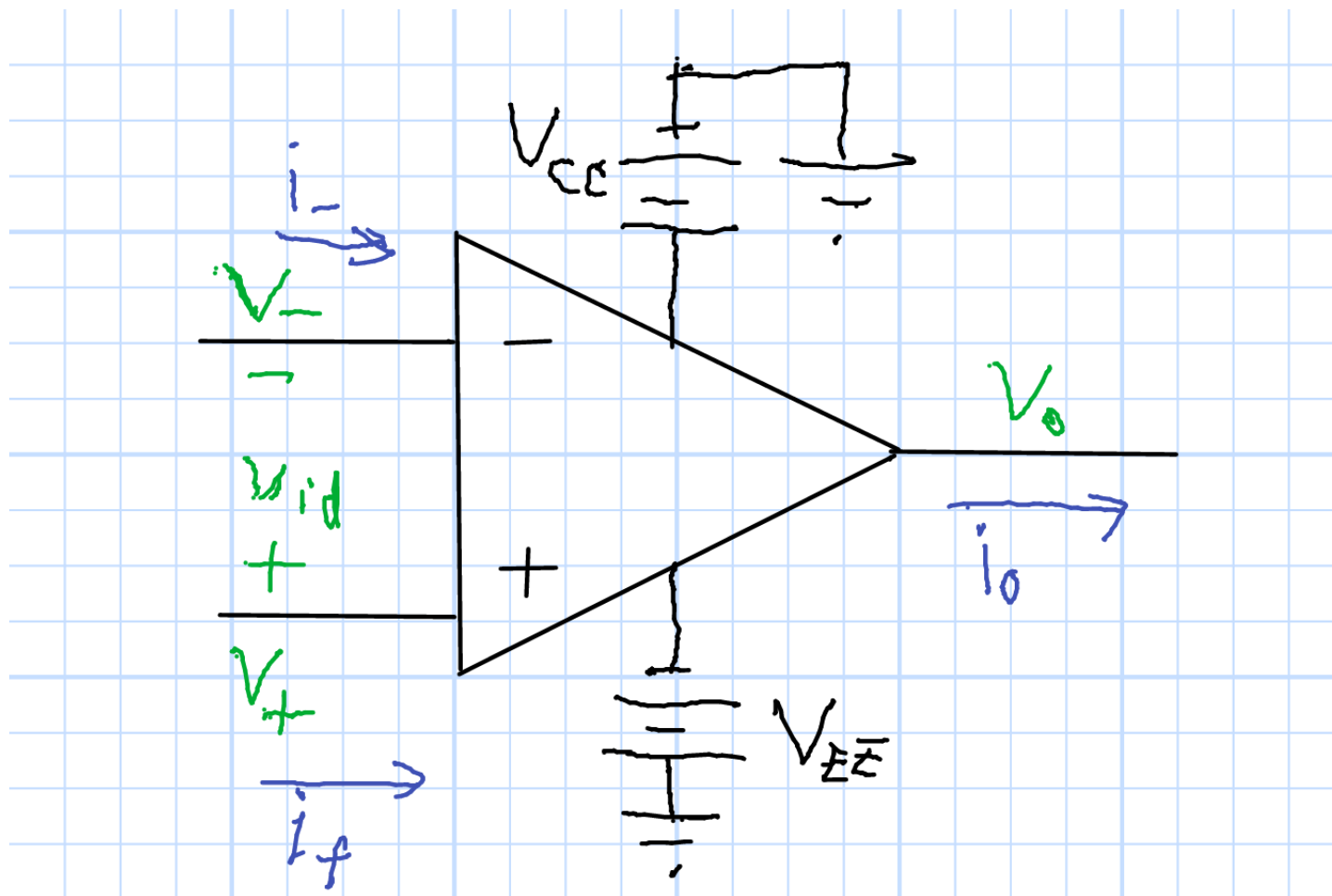


$$i_+ = 0 \quad i_- = 0 \quad v_o = Av_{id} \quad A \rightarrow \infty$$

“Common Mode” $((v_+ + v_-)/2)$ Gain is Zero.

Implied Power Supplies

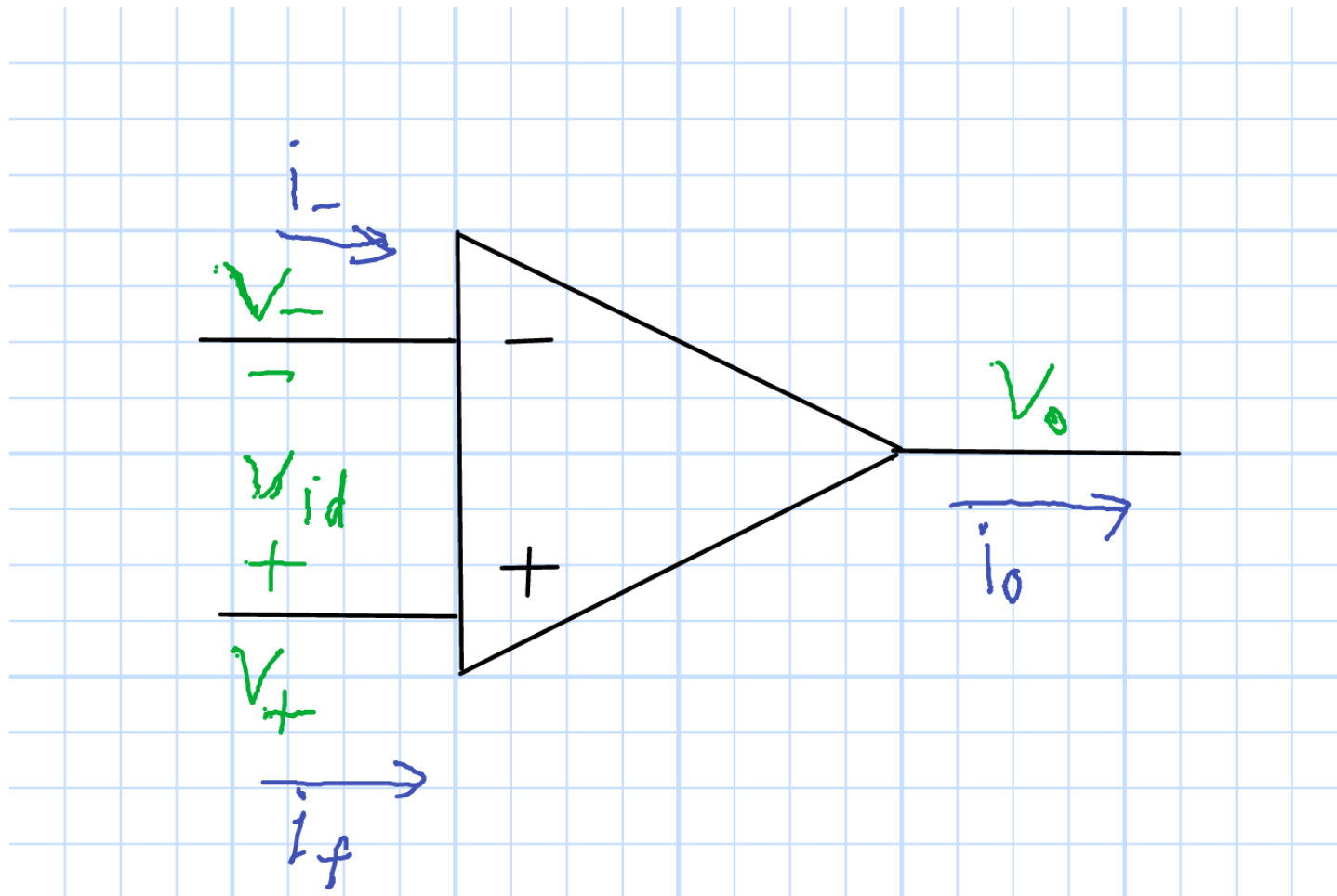


Ideal Op-Amp Model

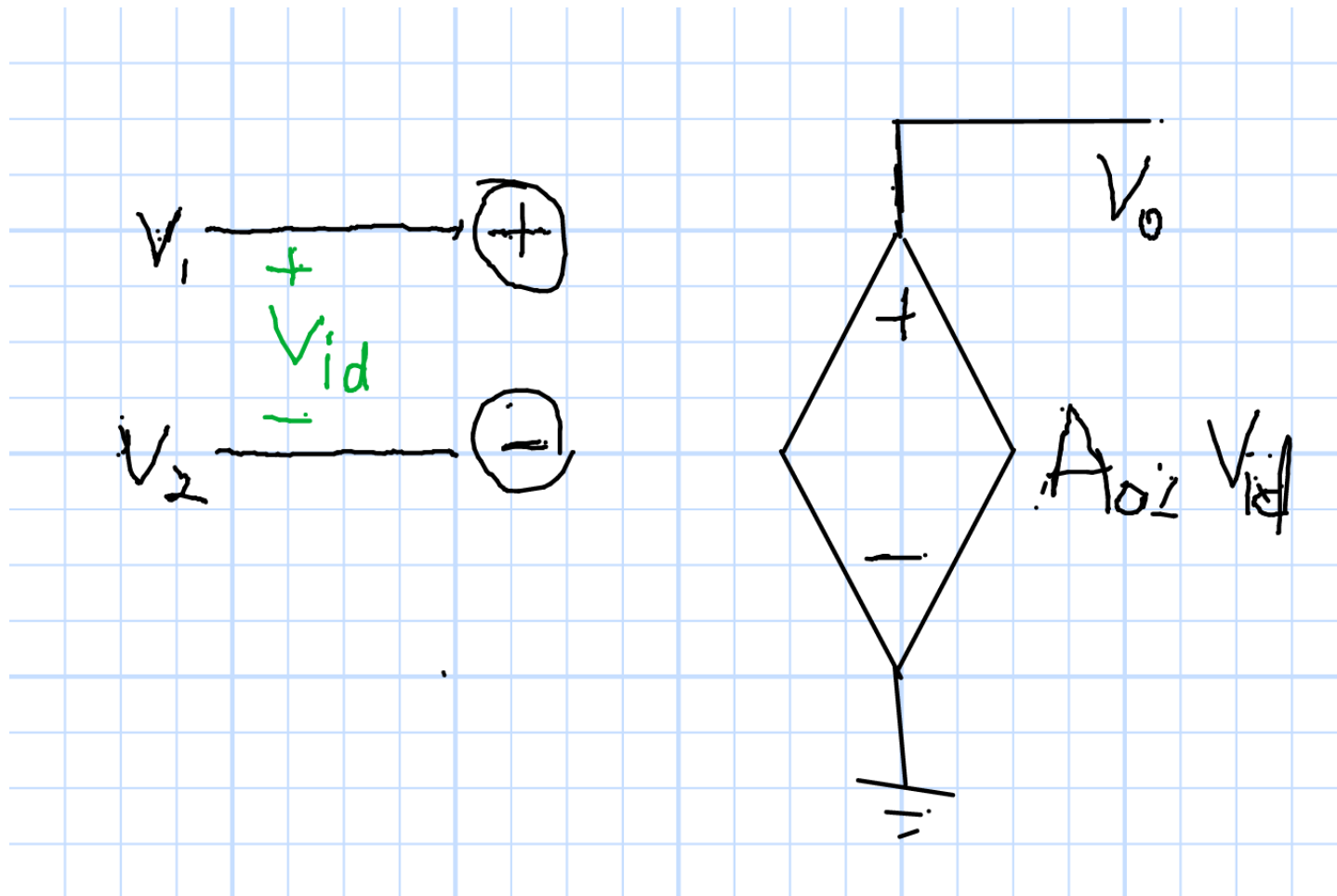

$v_o = A_{OL}v_{id}$ and $A_{OL} \rightarrow \infty$ so $v_{id} = 0$. Note open-circuit inputs.


Inverting Amplifier Circuit

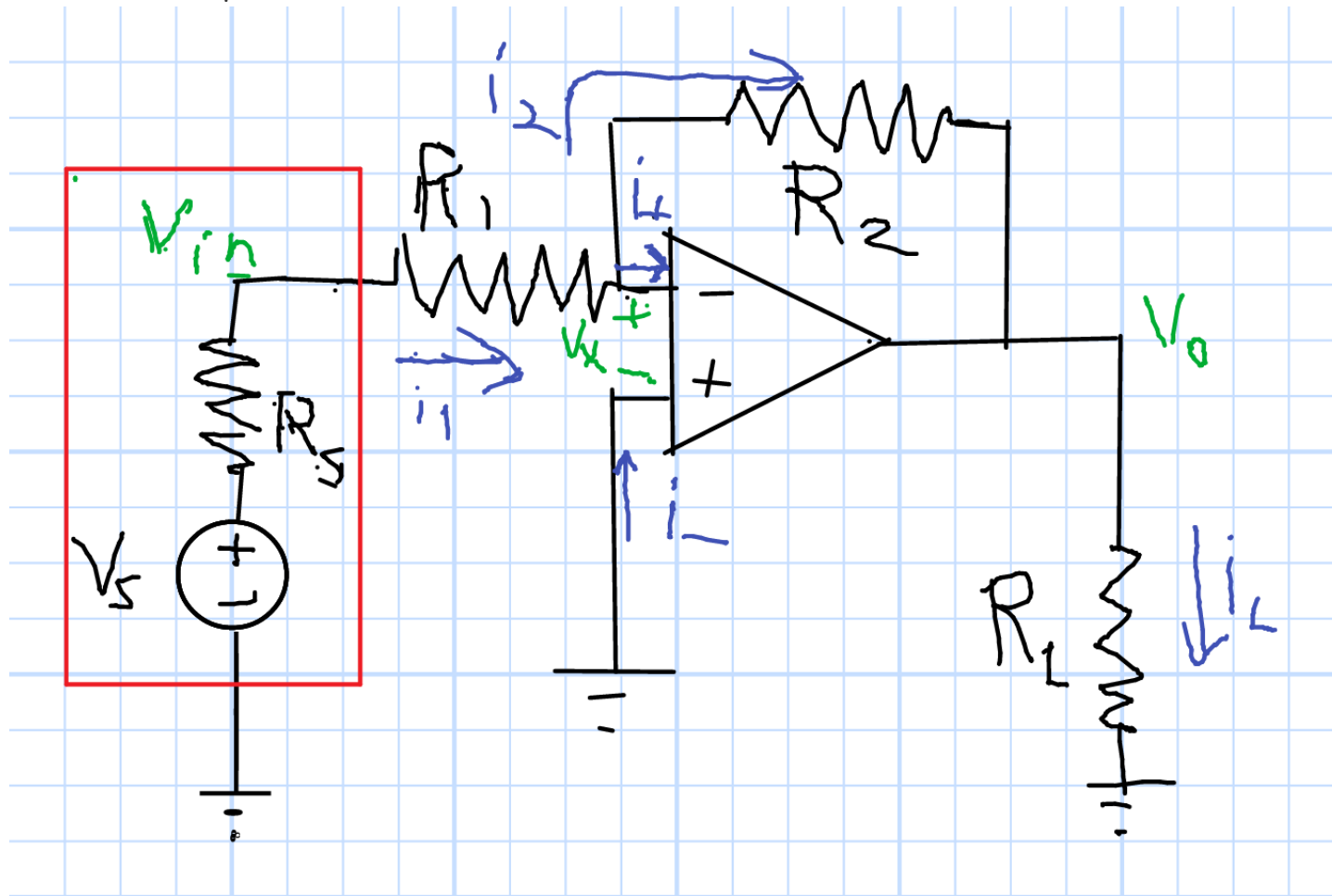$I_+ = 0, I_- = 0, v_x = 0$: Virtual Ground



$$i_1 = i_2 \text{ so } v_o = -v_{in} \frac{R_2}{R_1} \text{ or } A_v = -\frac{R_2}{R_1}, R_{in} = R_1, R_{out} = 0$$


Negative Feedback

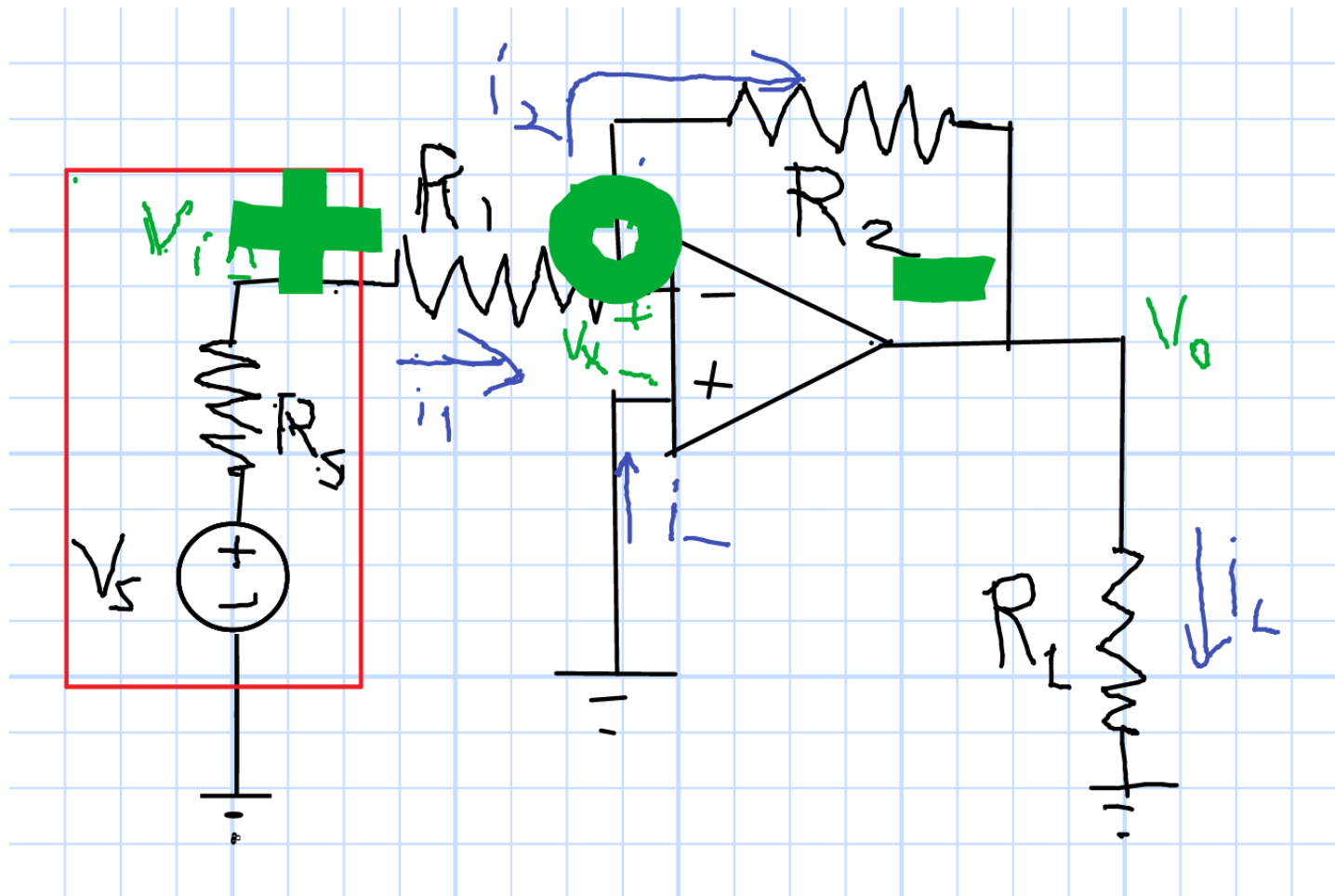

if $v_{in} > 0$, then $v_o < 0$, so v_- can be zero.

if $v_{in} < 0$, then $v_o > 0$, so v_- can be zero.

Inverting Amplifier in Lab

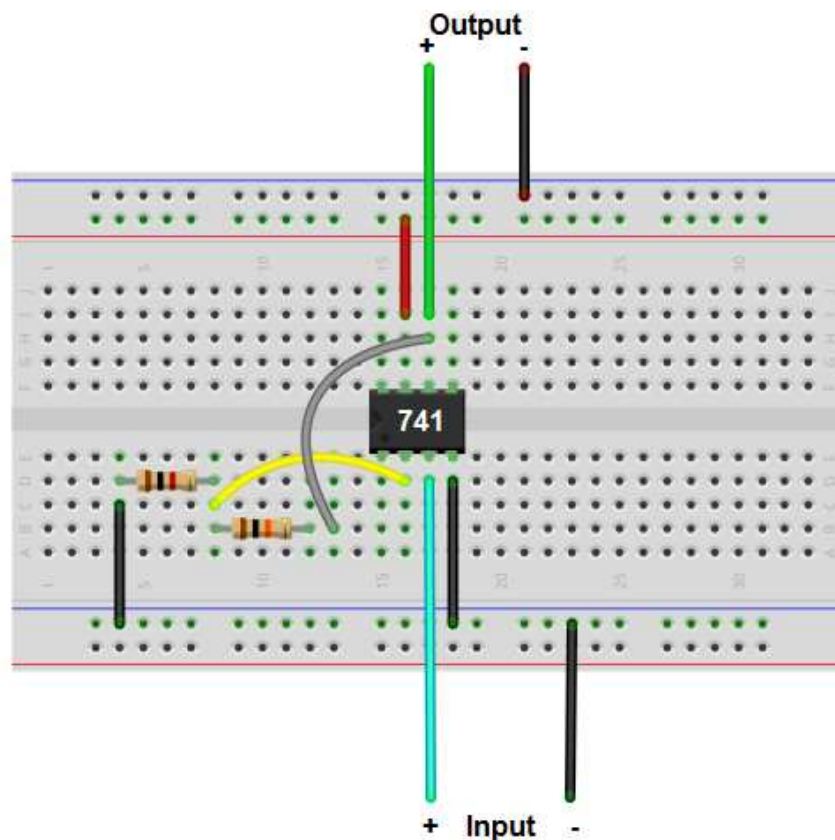


Proto-Board Connections
Power Rails
Signals



Measure Voltage (P-P)
Frequency or Period
Phase (Now 0 or 180 Deg.)

Inverting Amp Circuit?

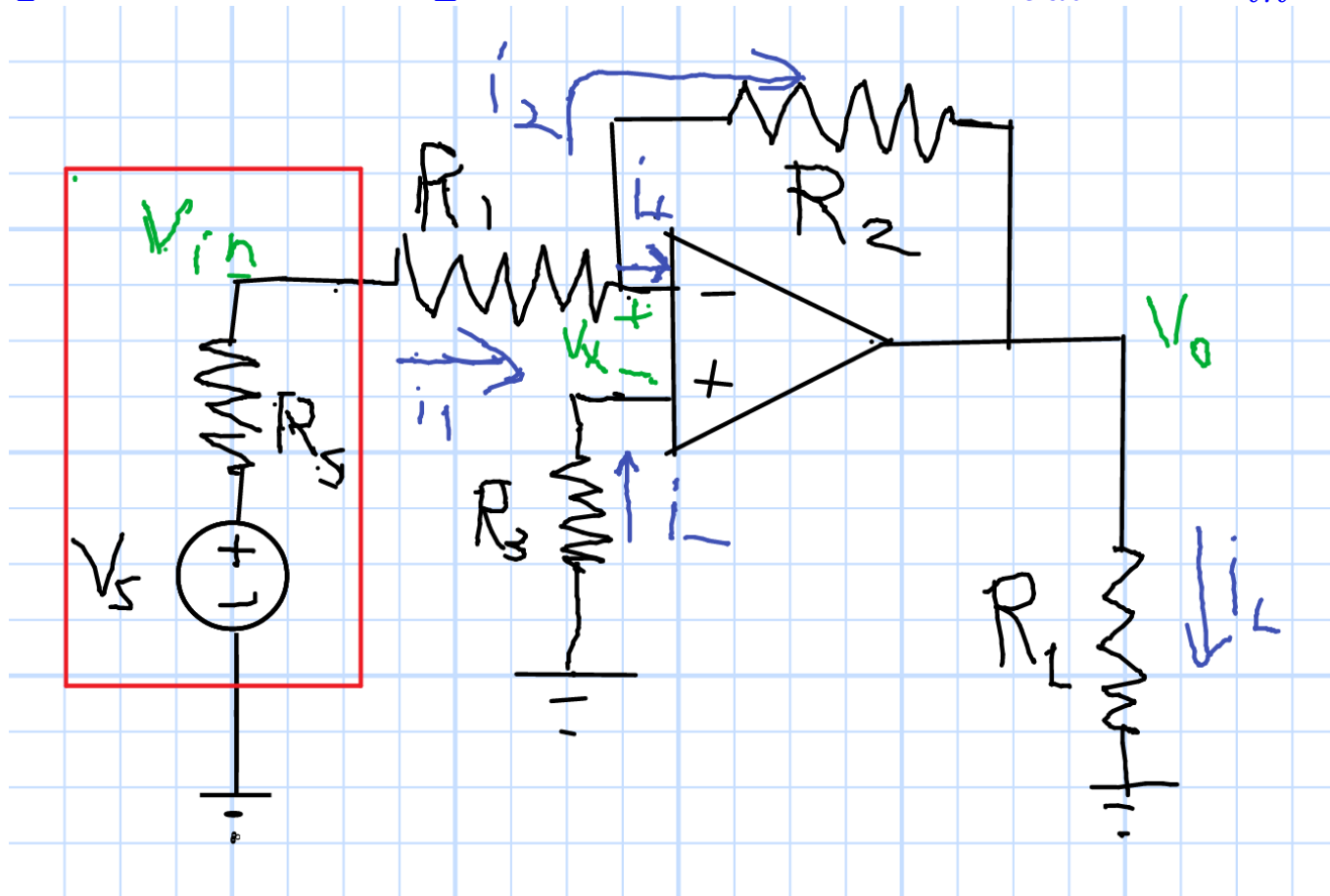
$R_1 = 500\text{Ohm}$, $R_2 = 1\text{kOhm}$, $A_v = ?$, $R_{out} = ?$ $R_{in} = ?$



Hint: What is i_+ in R_3 ? What is v_+ ?


A virtual short circuit is different from a real one.

Limits on v_o

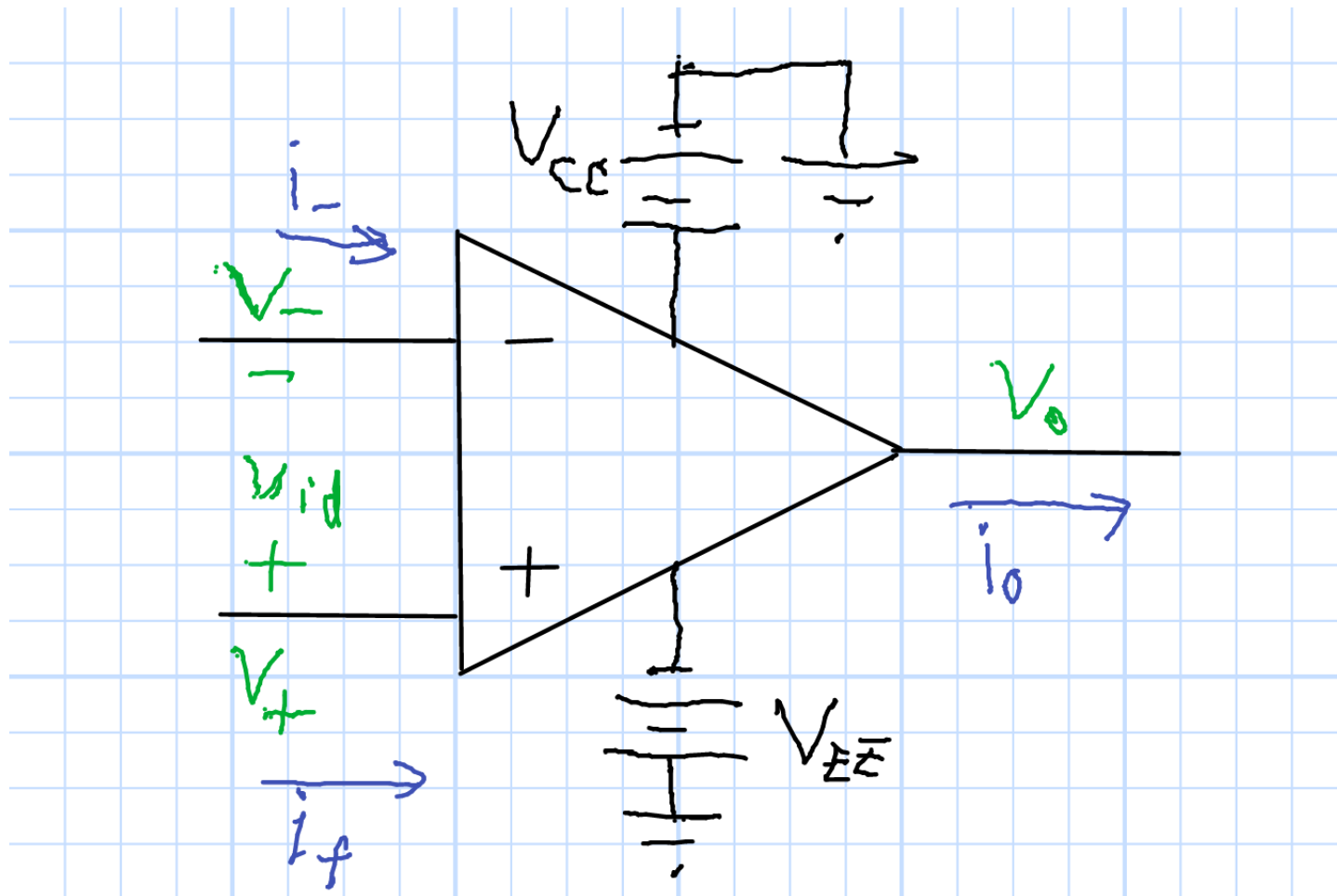


$$-V_{EE} \leq v_o \leq V_{CC}$$

High Gain (1)

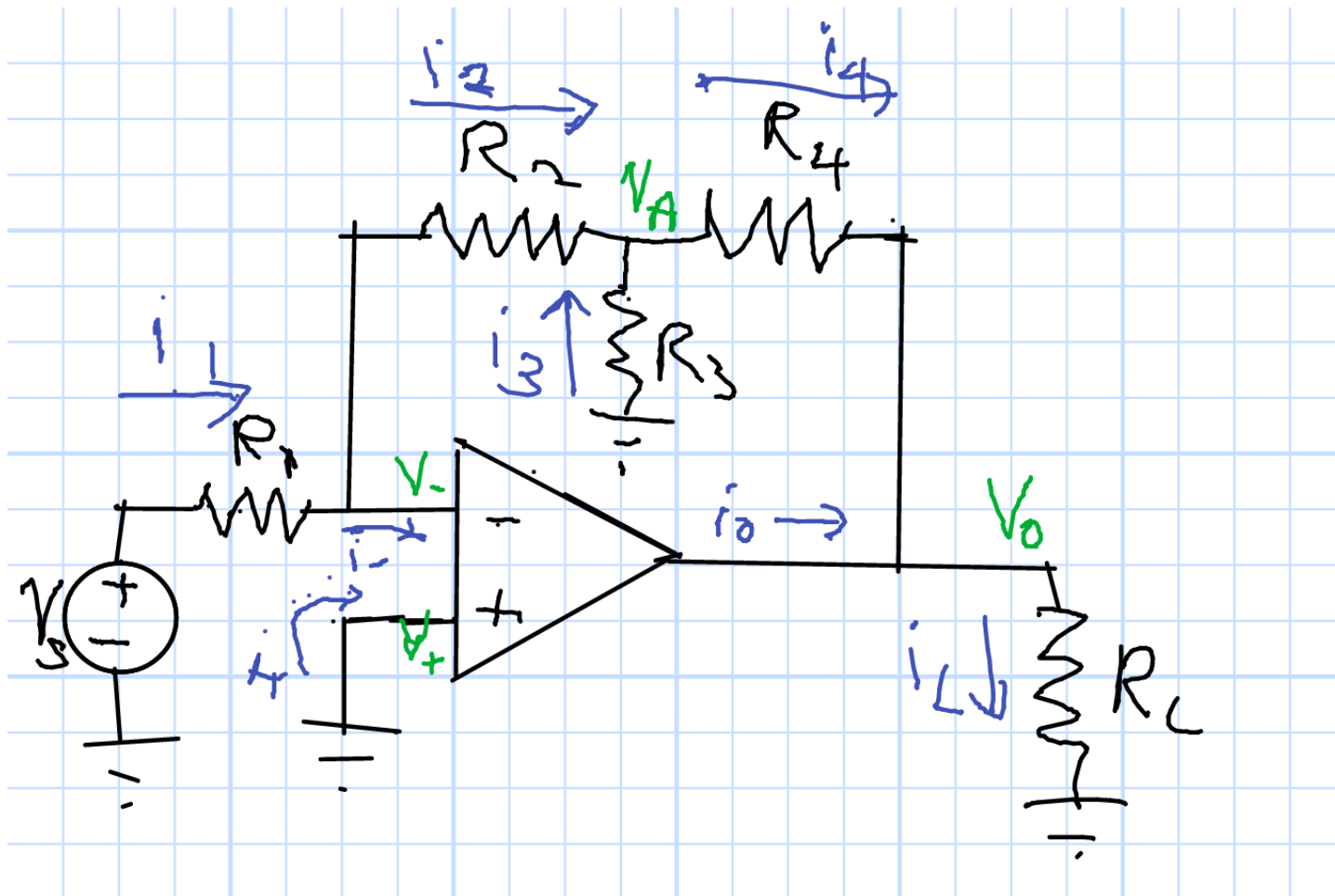

High Gain (2)

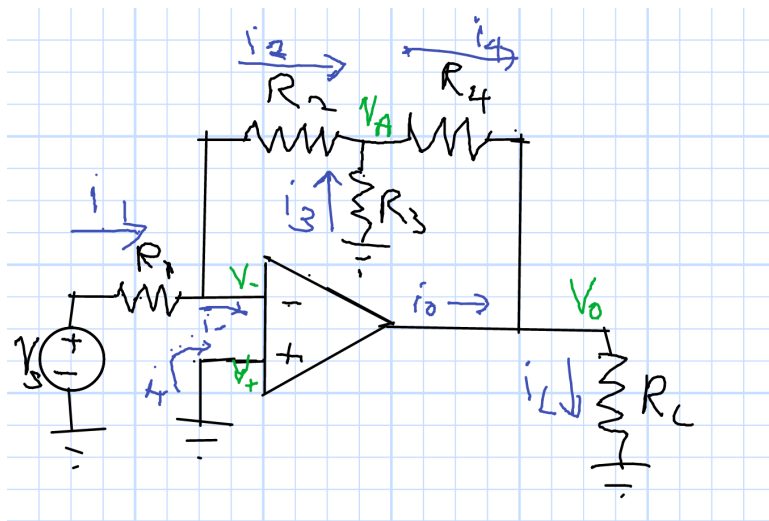

$$i_1 = \frac{v_s}{R_1} \quad i_2 = i_1$$

Current Divider,
Virtual and Real Grounds

$$i_2 = i_4 \frac{R_3}{R_3 + R_2}$$


Series and Parallel Combinations

$$v_o = -i_4 [R_4 + (R_2 \parallel R_3)]$$

$$v_o = i_2 \frac{R_3 + R_2}{R_3} \left[R_4 + \frac{R_2 R_3}{R_2 + R_3} \right] = \frac{v_{in}}{R_1} \frac{R_3 + R_2}{R_3} \left[R_4 + \frac{R_2 R_3}{R_2 + R_3} \right]$$

$$= v_{in} \frac{R_4 R_3 + R_4 R_2 + R_2 R_3}{R_1 R_3} = v_{in} \left[\frac{R_4}{R_1} + \frac{R_2}{R_1} + \frac{R_2 R_4}{R_1 R_3} \right]$$

High Gain (3)

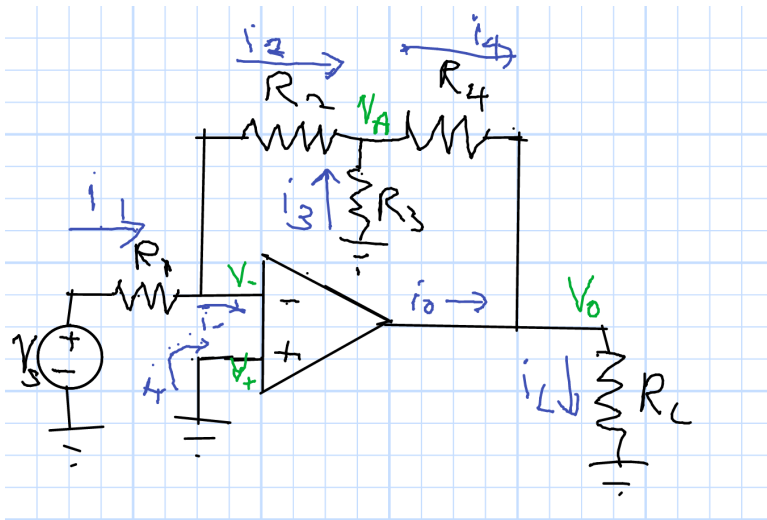

Example Values

$$R_1 = R_3 = 1\text{k}\Omega$$

$$R_2 = R_4 = 20\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$

$$v_o = v_{in} \left[\frac{R_4}{R_1} + \frac{R_2}{R_1} + \frac{R_2 R_4}{R_1 R_3} \right]$$

$$v_o = v_{in} (20 + 20 + 400) = 440v_s$$

$$i_{in} = i_1 = \frac{v_s}{R_1}$$


$$i_L = \frac{v_o}{R_L} = 440 \frac{v_s}{R_L}$$

$$R_L = R_1 \quad i_L = 440i_{in}$$

Power Gain


$$v_o i_L = 440^2 v_s i_{in} = 193,600 v_s i_{in}$$

Summing Junction

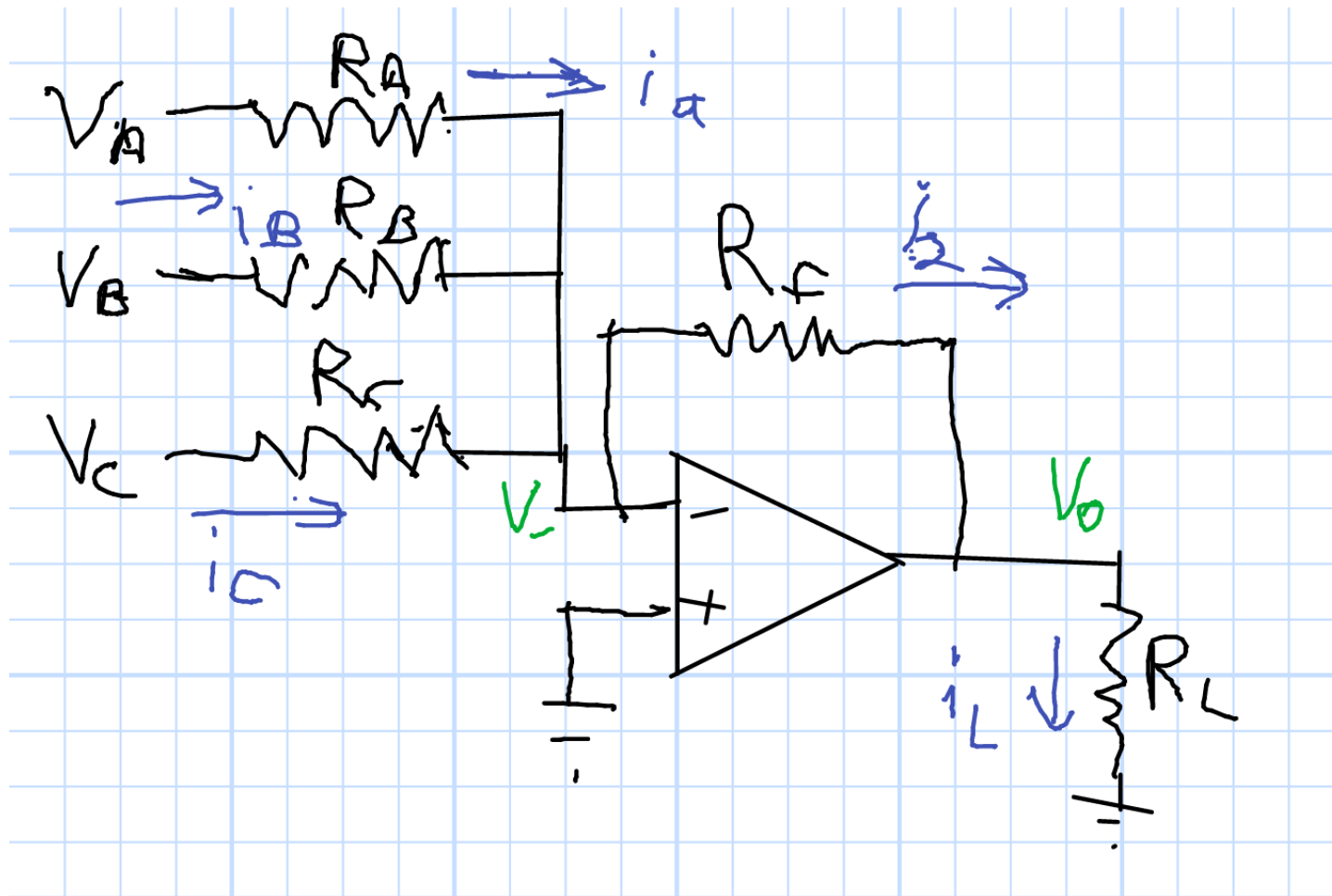

$$v_0 = - \left[\frac{R_f}{R_A} v_A + \frac{R_f}{R_B} v_B + \frac{R_f}{R_C} v_C \right]$$

Summing Junction Example

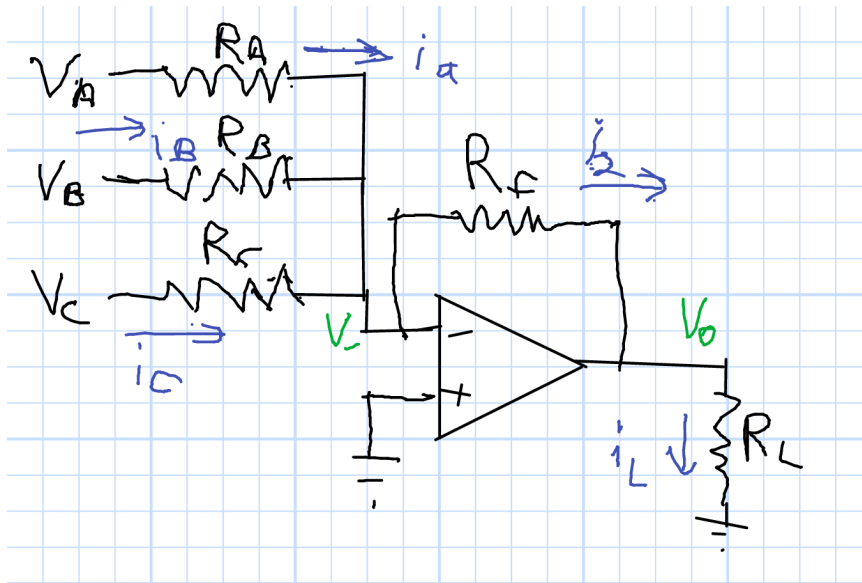

$$v_0 = - \left[\frac{R_f}{R_A} v_A + \frac{R_f}{R_B} v_B + \frac{R_f}{R_C} v_C \right]$$

V_A	V_B	V_C	V_o
0	0	0	0
1	0	0	1
0	1	0	2
1	1	0	3
0	0	1	4
1	0	1	5
0	1	1	6
1	1	1	7

$$v_{A,B,C} = 0 \text{ or } 1$$


$$R_f = 10\text{k}\Omega$$

$$R_A = 10\text{k}\Omega \quad R_B = 5\text{k}\Omega$$

$$R_C = 2.5\text{k}\Omega$$


3–Bit D/A Converter

Summing Junction

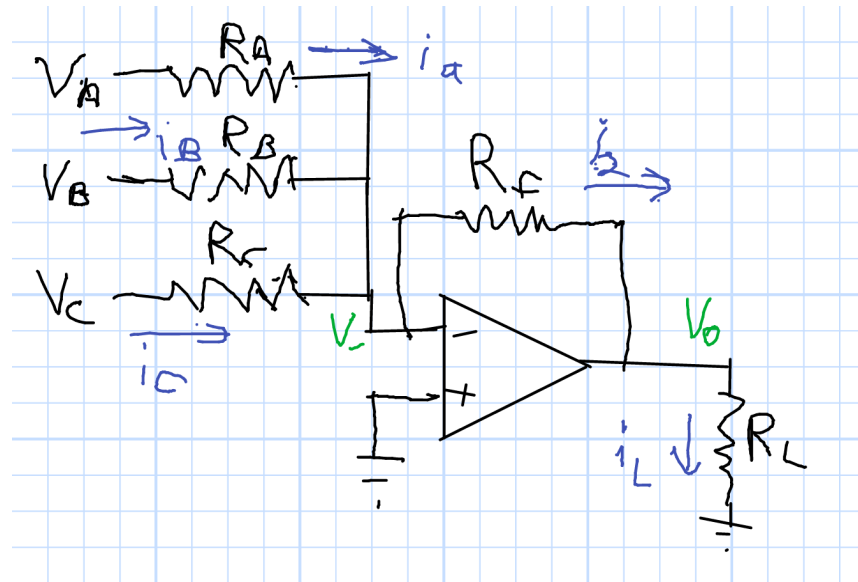

Would this Work Without the Op Amp?

Summing Junction

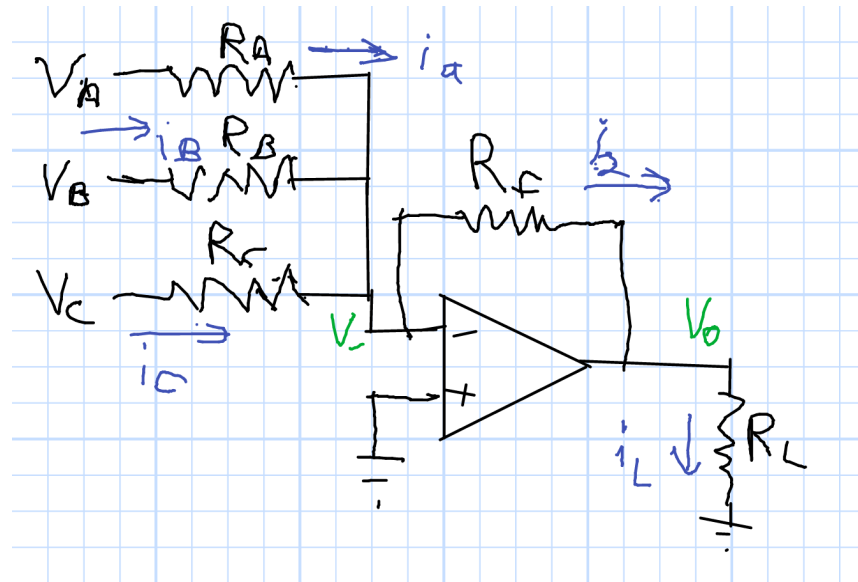


Would this Work Without the Op Amp?

No. Connect the node v_- to R_L and remove the amplifier. Calculate the voltage at that node.


Each input circuit's voltage is affected by the other two input circuits.

The virtual ground is what makes this work.

Positive Feedback (1)

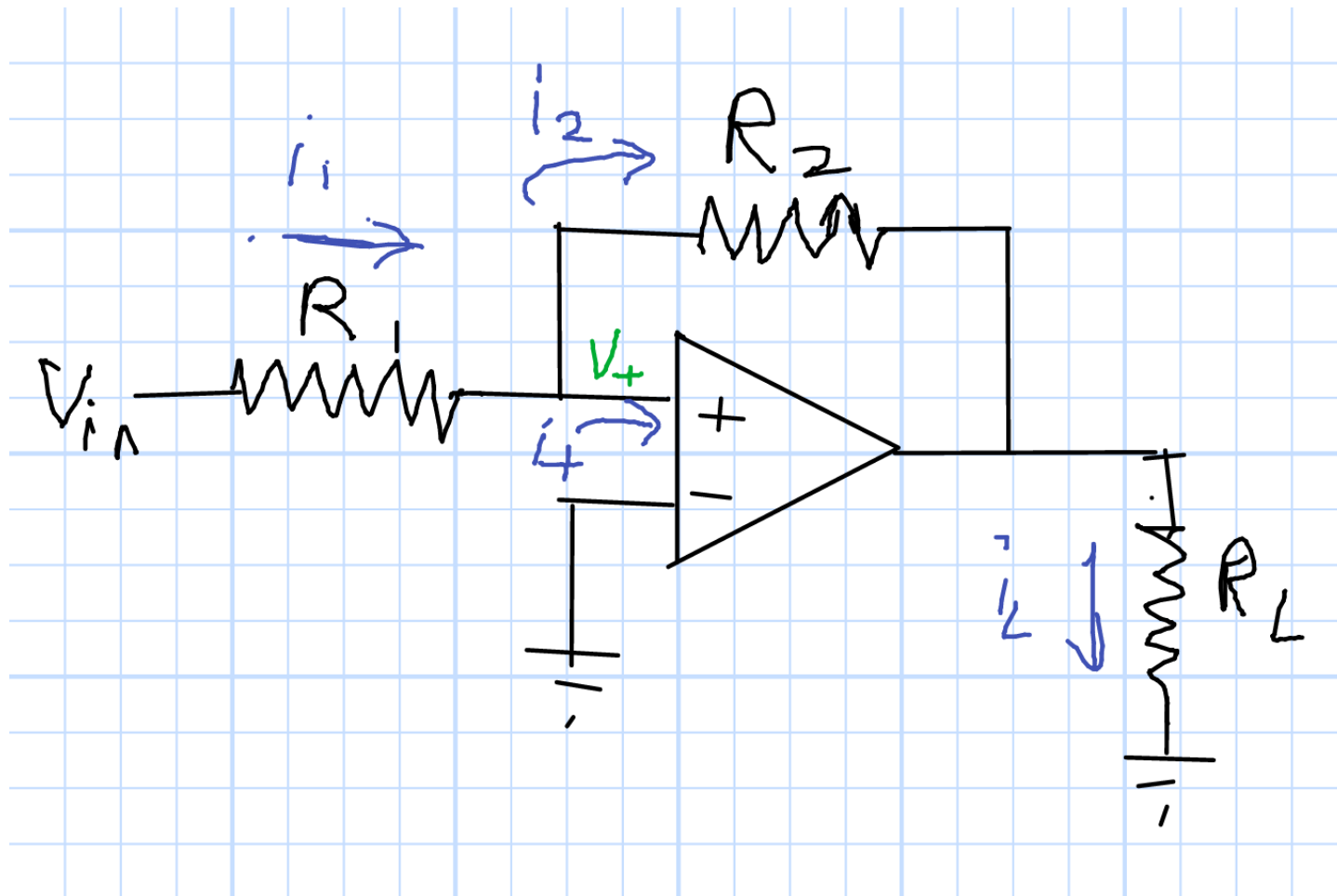


Positive Feedback (2)

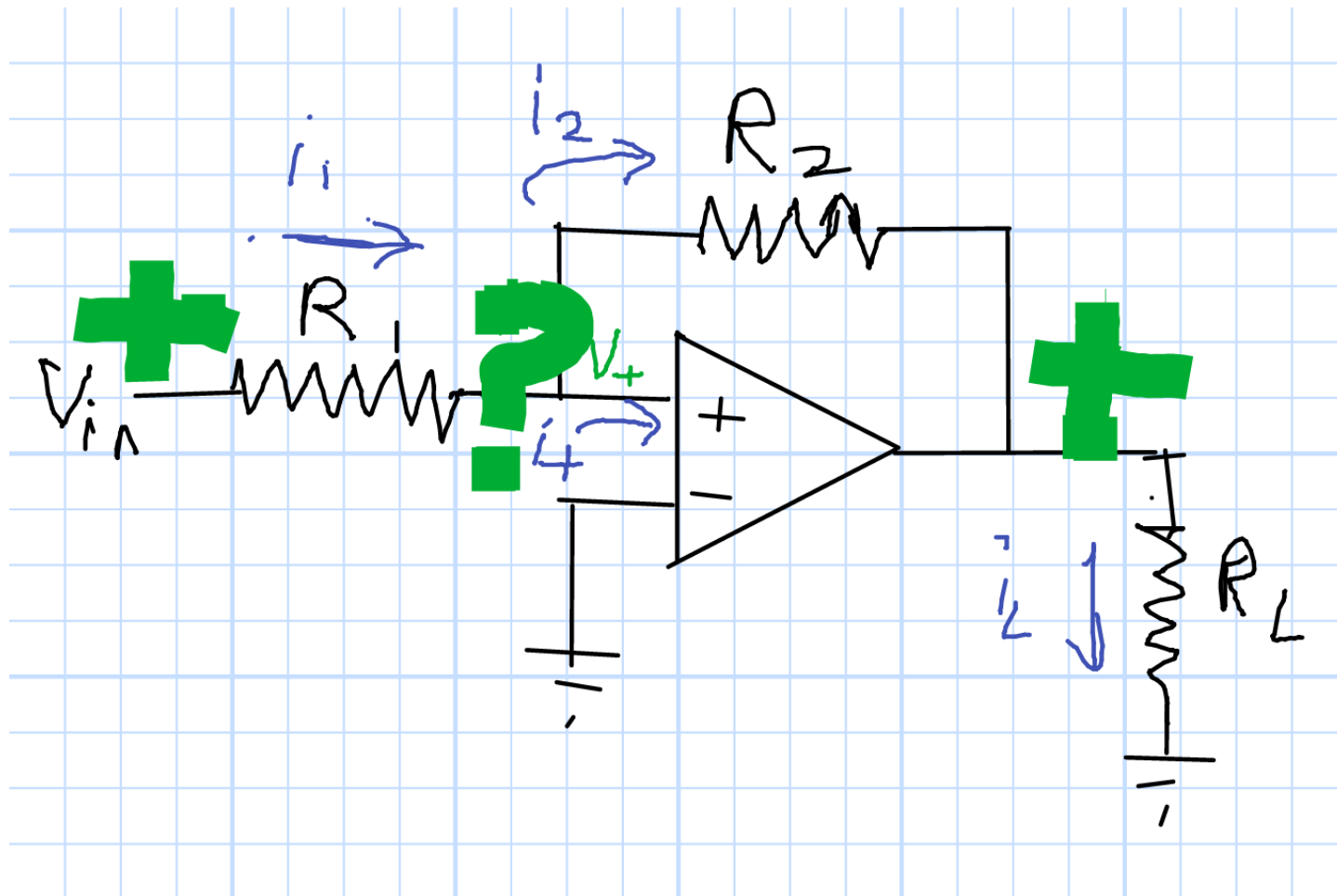

v_0 and v_{in} have the same sign, so v_+ cannot be zero
 v_0 "goes to the rail." $v_0 = V_{CC}$ or $v_0 = -V_{EE}$ (actually a bit less).

Positive Feedback (3)

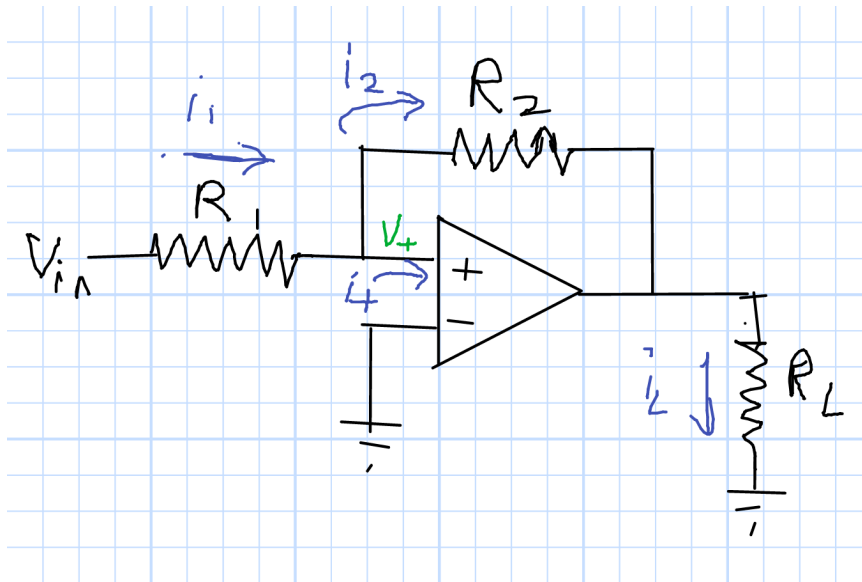

$$v_+ = v_{in} + (v_o - v_{in}) \frac{R_1}{R_1 + R_2} =$$

$$v_{in} \frac{R_2}{R_1 + R_2} + v_o \frac{R_1}{R_1 + R_2}$$

v_o is limited by the power rails

At what v_{in} does it switch?

v_{id} is not zero;

Virtual ground fails.



v_+ has same sign as v_o

v_o "goes to the rail."

$$v_+ = 0$$

$$v_{in} = -v_{rail} \frac{R_1}{R_2}$$

Positive Feedback (4)

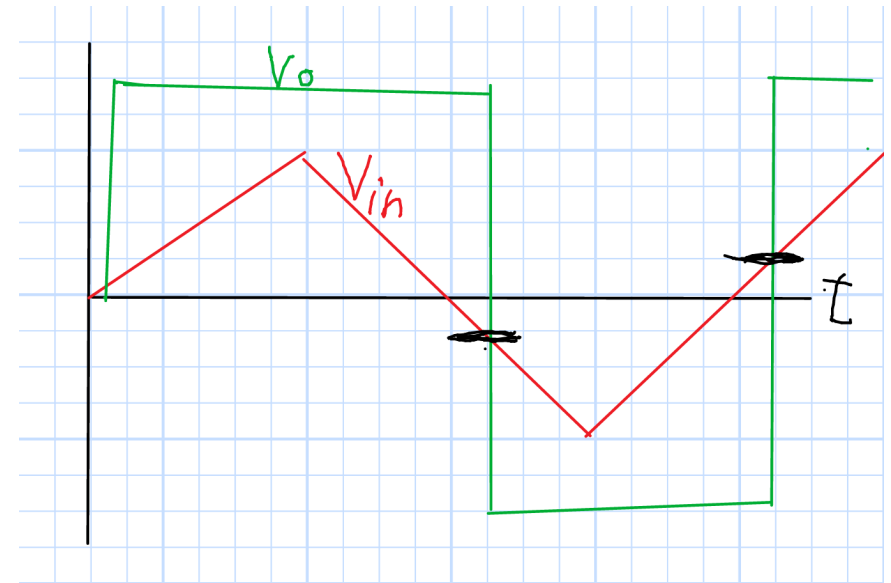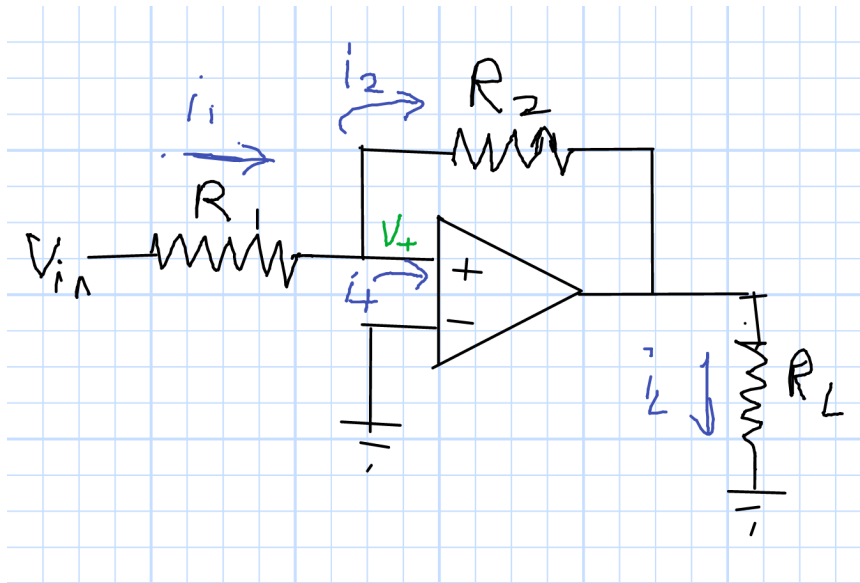

If $v_o = V_{CC}$, then it will not switch until $v_{in} < -V_{CC} \frac{R_1}{R_2}$


If $v_o = -V_{EE}$, then it will not switch until $v_{in} > +V_{EE} \frac{R_1}{R_2}$

The circuit is bistable.

It “remembers” how it was set until it is switched.


Normally, V_{in} could just be positive and negative pulses.

Non-Inverting Amplifier

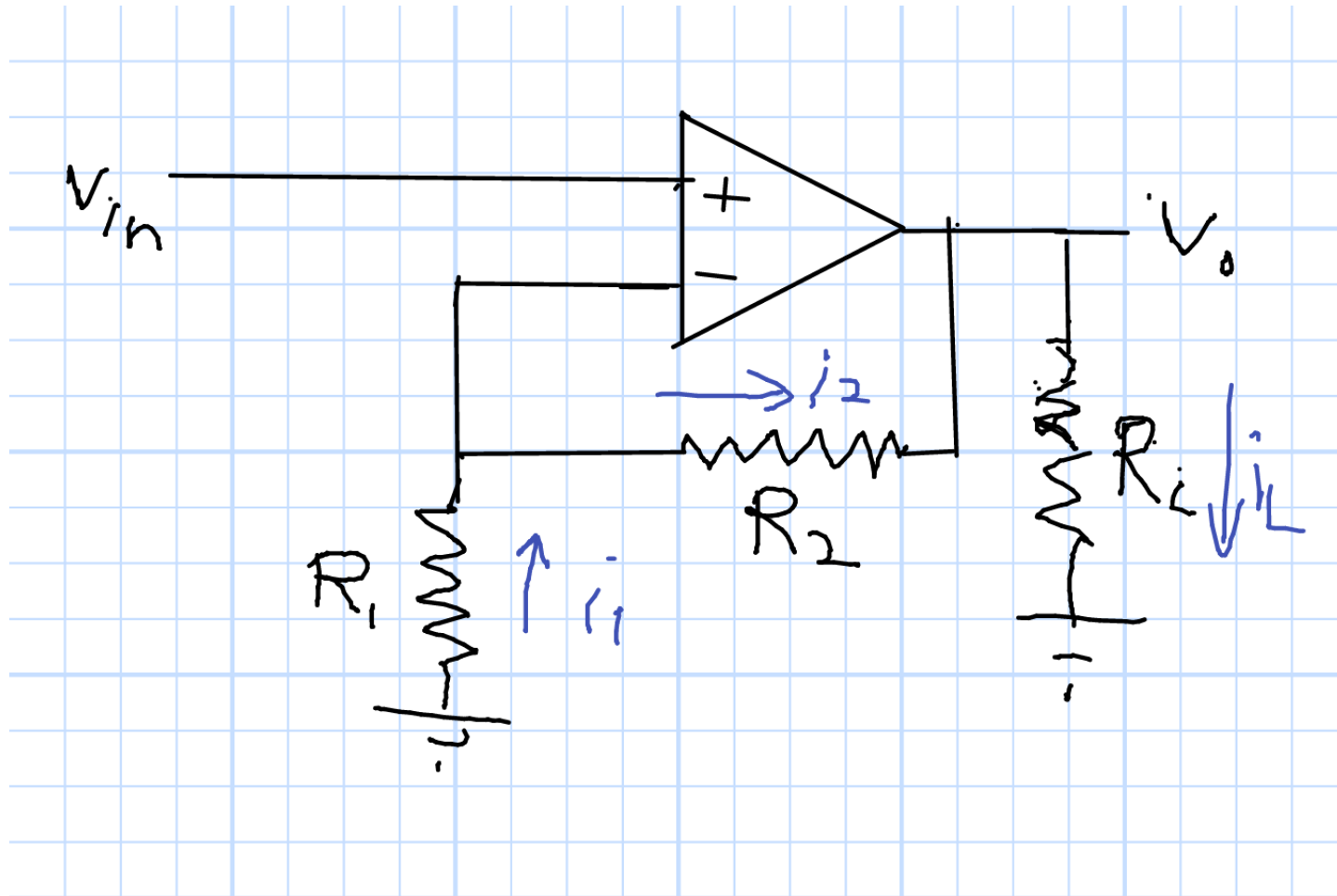


$$v_+ = v_- \quad v_o = v_{in} \left(\frac{R_2}{R_1} + 1 \right)$$

Voltage Follower

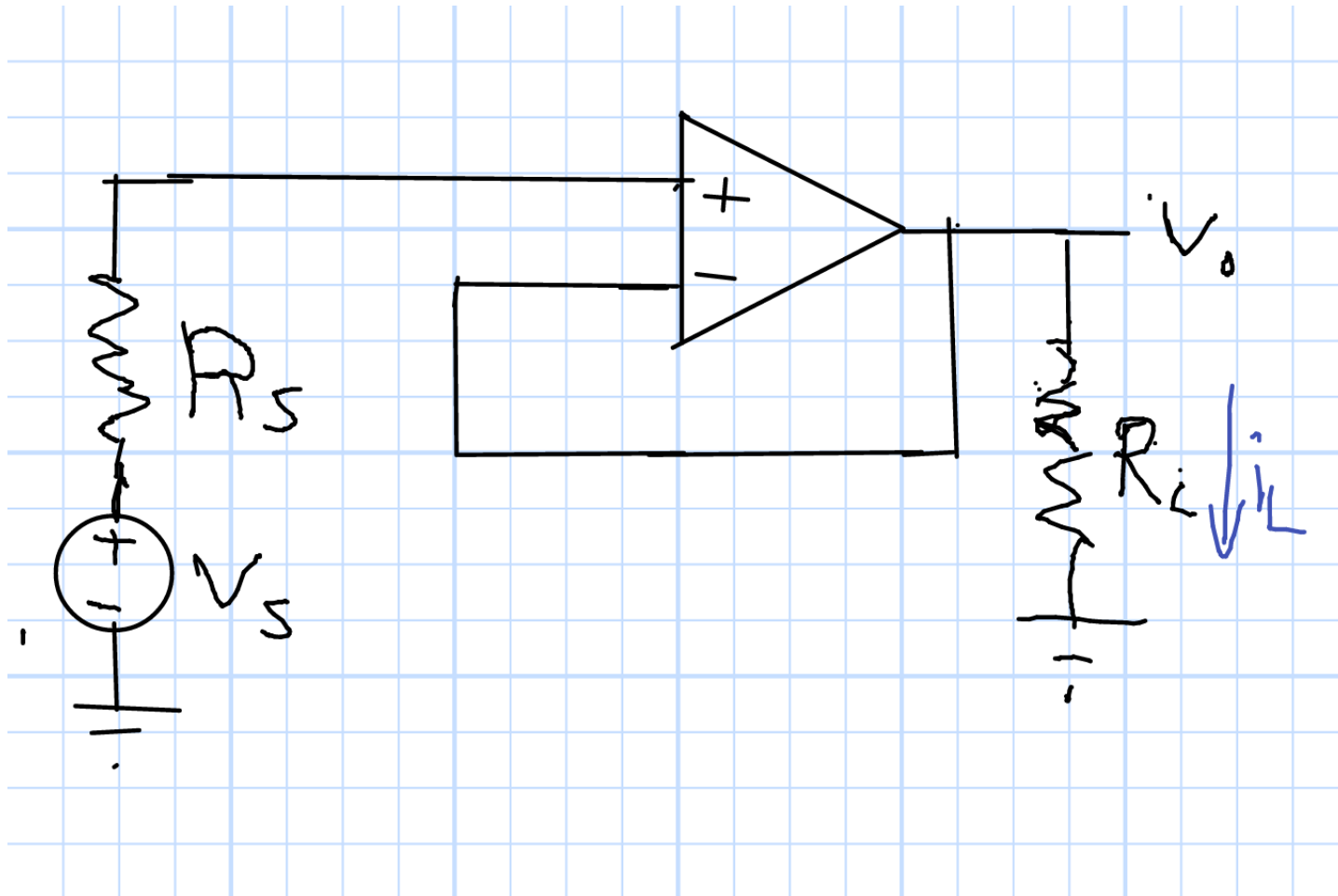


$$v_o = v_{in} = v_s \quad i_s = 0$$

Why Voltage Follower?

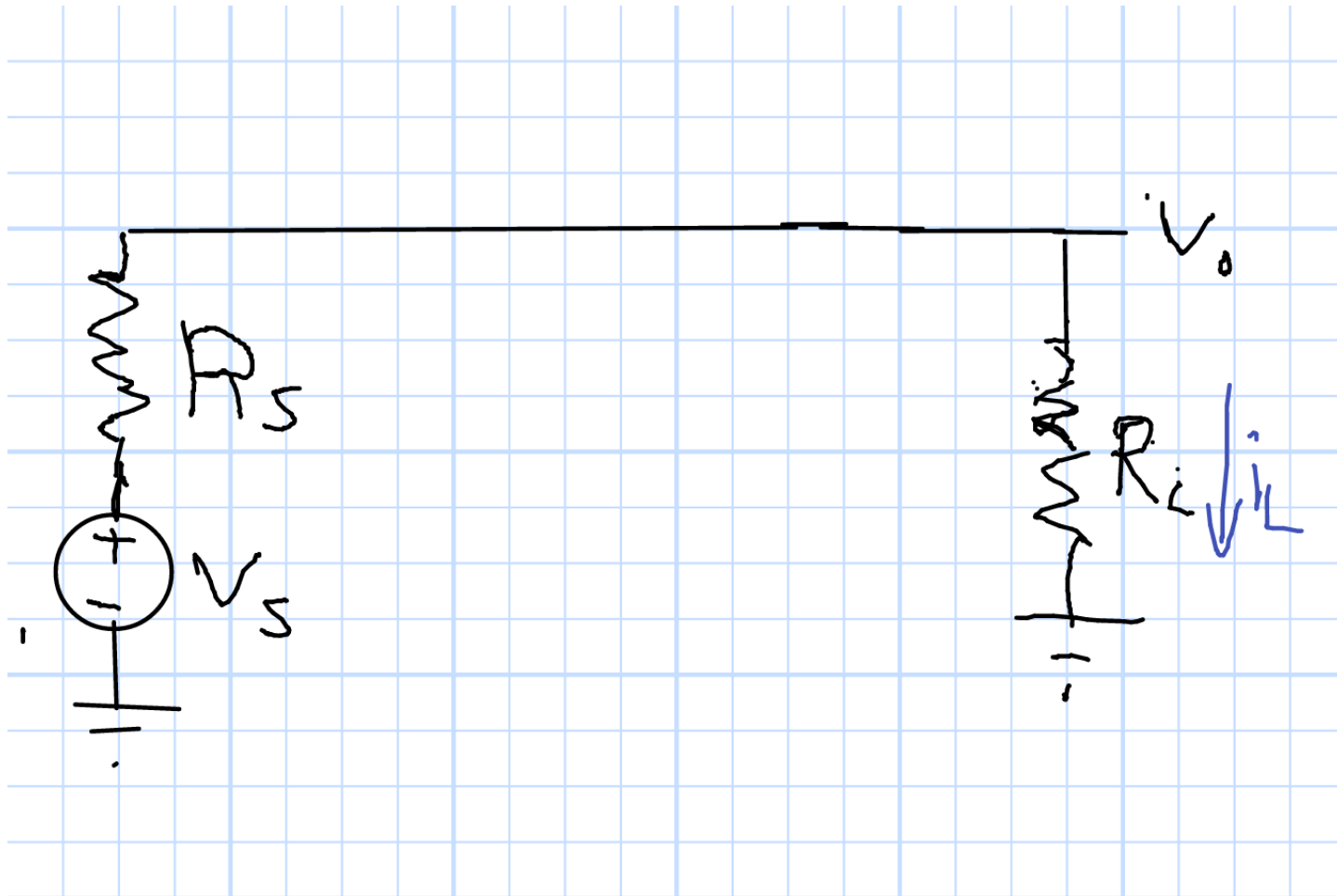


Here, $v_o = v_s \frac{R_L}{R_L + R_s}$. This is important for small R_L , large R_s .
The amplifier provides the needed current.

Transimpedance Amplifier

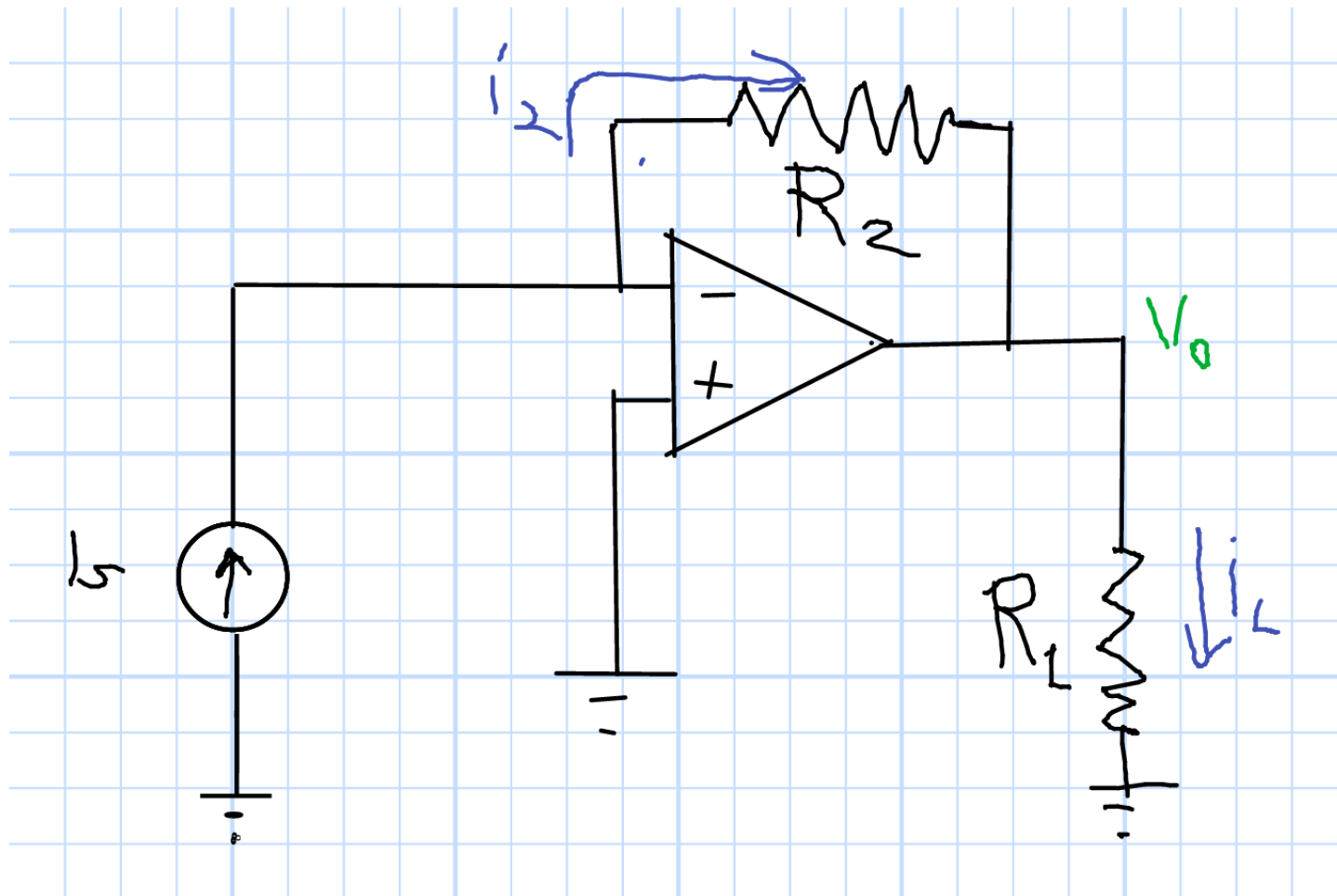

$v_o = -R_2 i_s$. Useful for photodiodes among other applications


Speaking of Photodiodes...

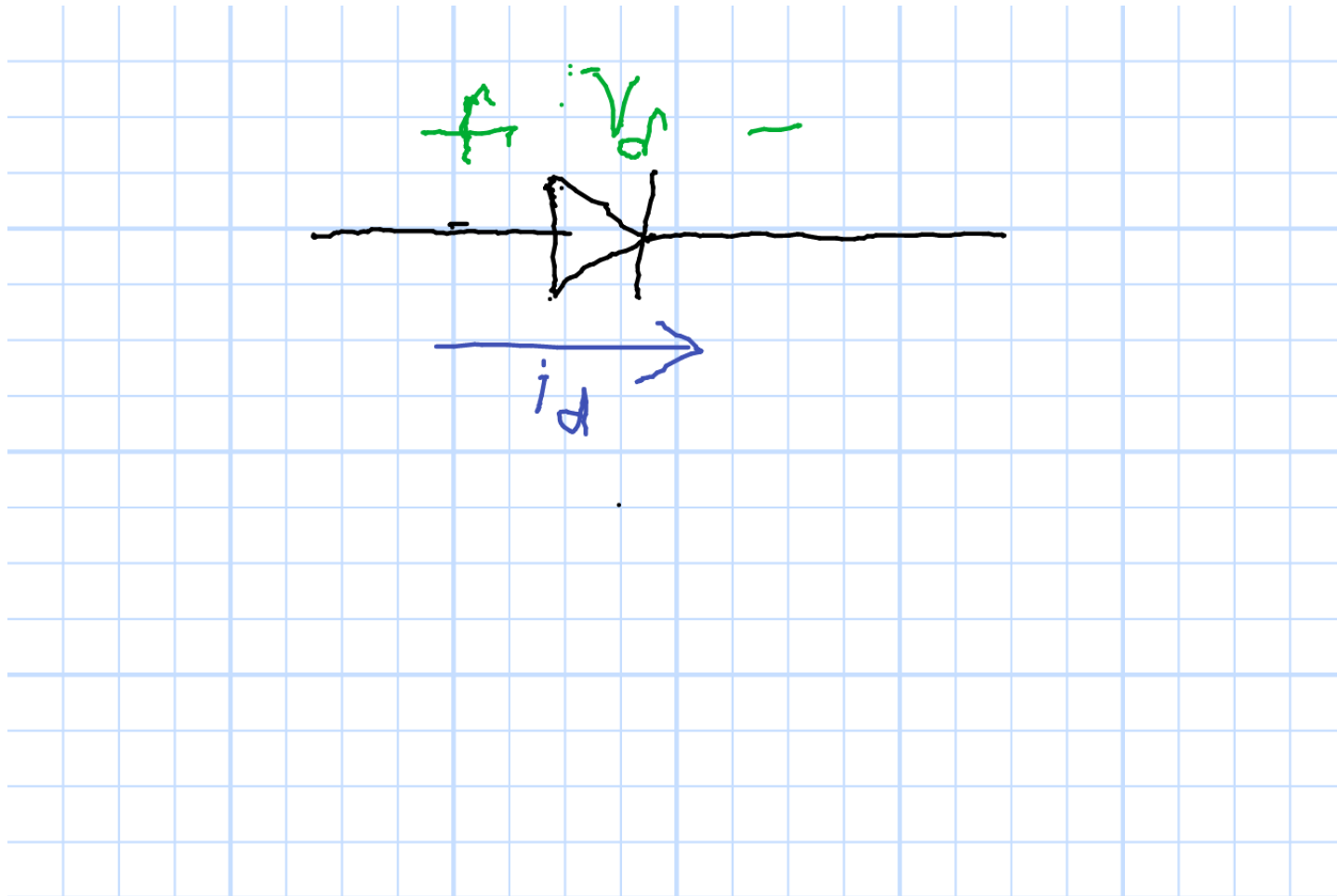

Diode: Small reverse current & Large forward current

Photodiode: Reverse current increases with optical power.



Photodiode Curves

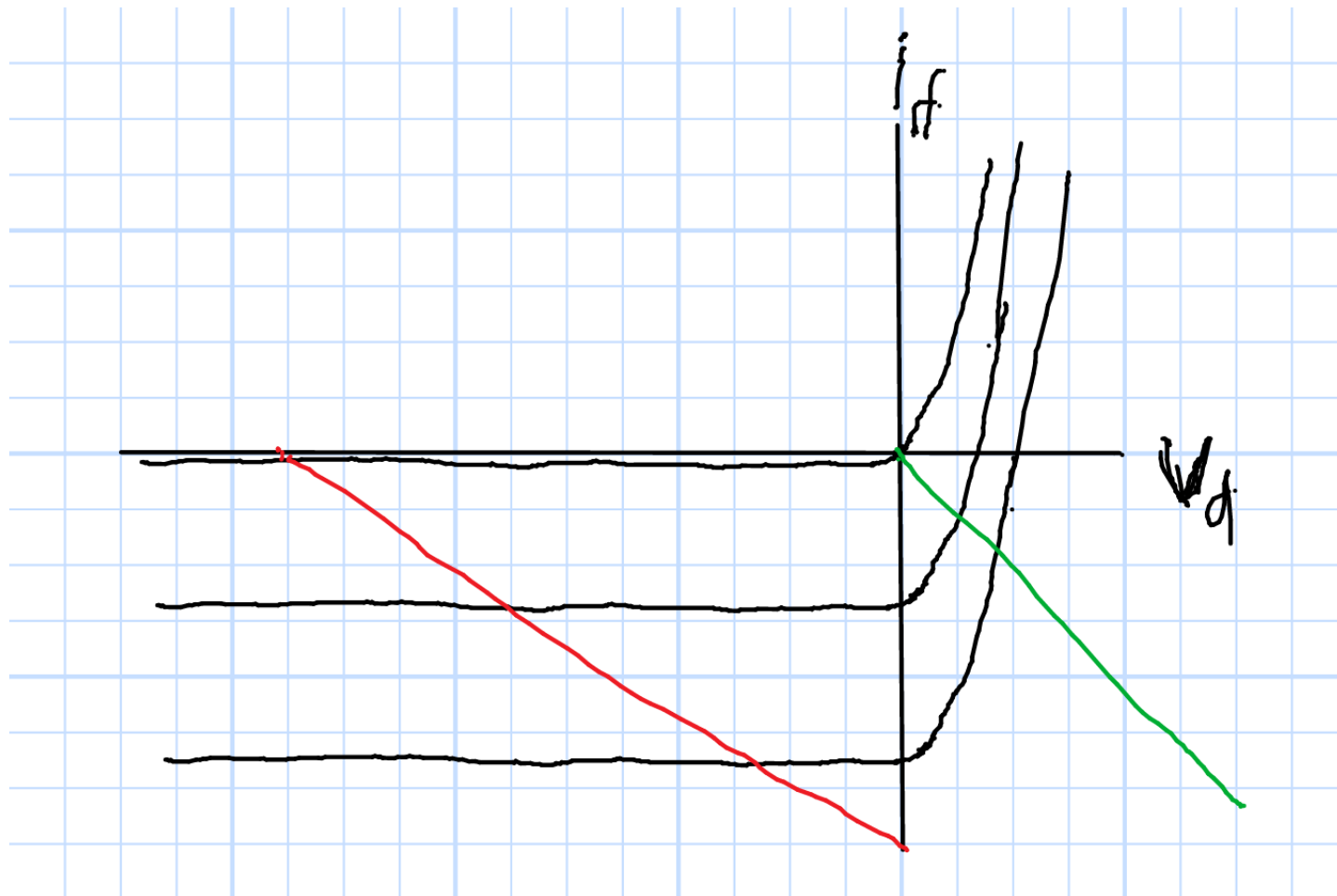

Diode (Top Curve); $i_d = I_s \left(-1 + e^{v_d/V_T} \right)$

Photocurrent adds: $i_{photo} = -\rho_i P_{optical}$ (Lower Lines).

Photodiode Circuit

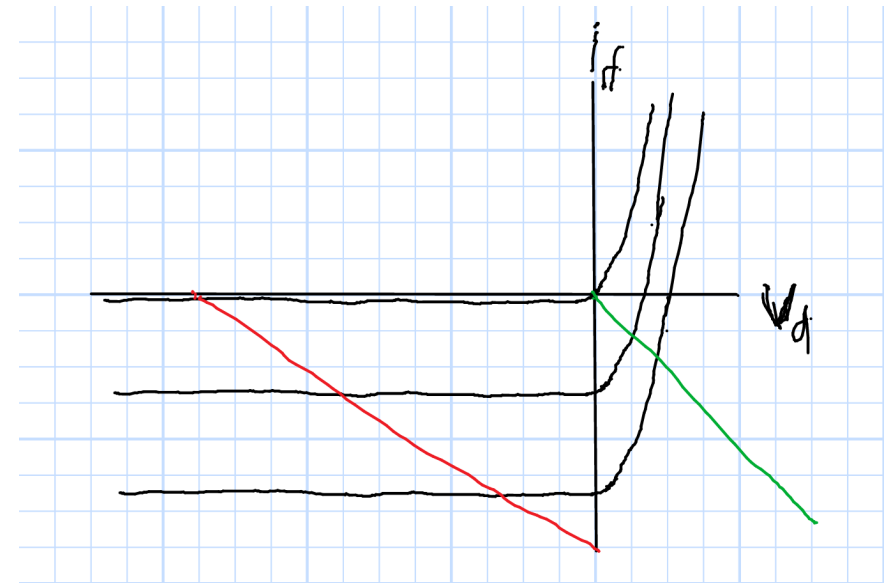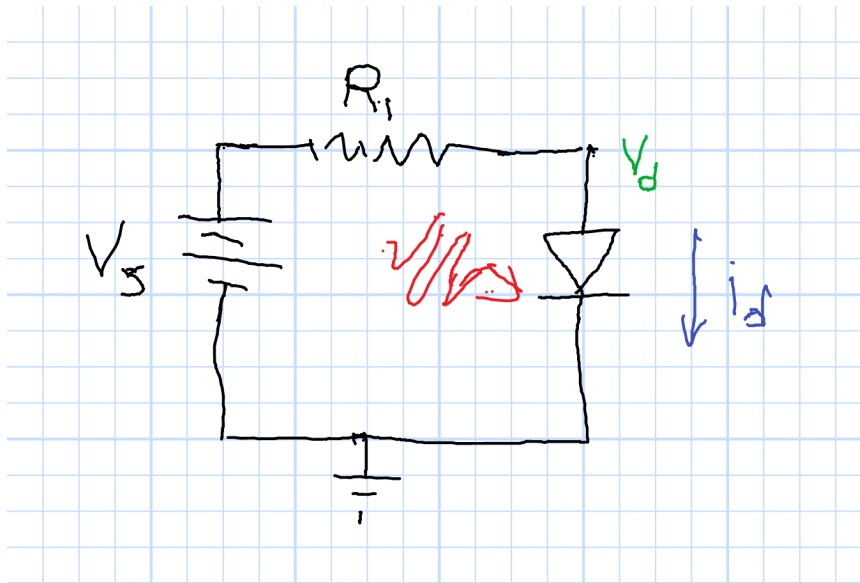

$$v_d = v_s + \rho_i P_{optical} R_1$$



Photocurrent is Negative

$$v_s < 0 \quad \text{Red Line}$$

Useful as a detector of light.

Negative Bias also helps with speed.

Solar Cell

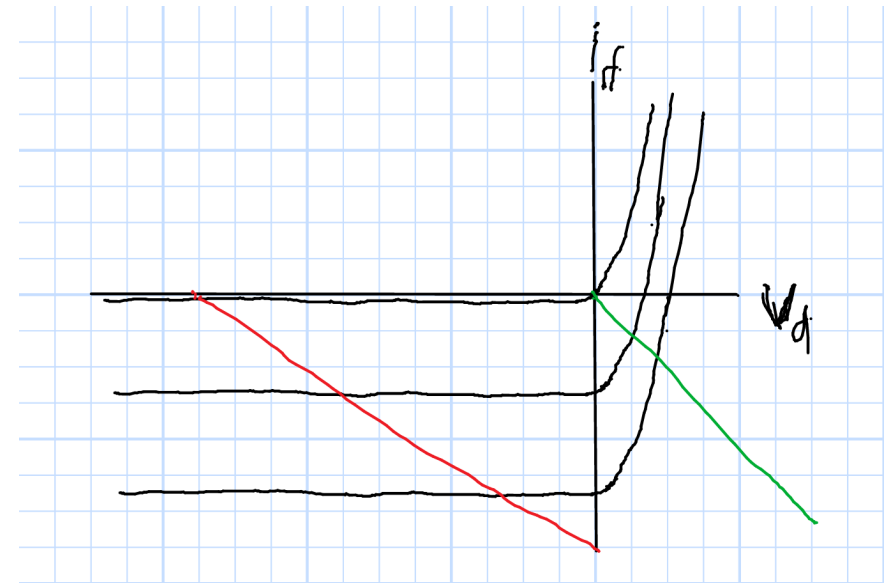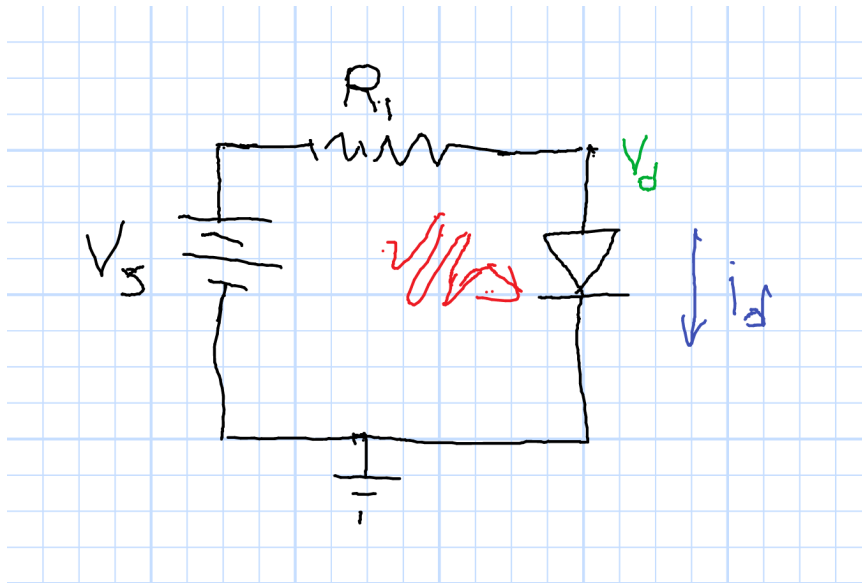

$$v_s = 0 \quad P_{diode} < 0$$

Green Line

Diode is a source of power.

R_l is the load.

$$P_L = -P_{diode}$$