

Electrical Engineering

Week 6

Charles A. DiMarzio
EECE-2210
Northeastern University

Oct 2021


Week 6 Agenda: Operational Amplifiers

- Linear Effects
 - Input and Output Impedances
 - Finite Gain, A_{OL}
 - Gain–Bandwidth Product
- Nonlinear Effects
 - Voltage Limit
 - Current Limit
 - Slew Rate
- DC Imperfections
 - Bias and Offset Currents
 - Offset Voltage
- Differential Amplifiers

The Story so Far

- Assume Ideal Linear Operation
 - $v_{id} = 0, v_+ = v_-$ (Virtual short/virtual ground)
 - $i_+ = 0$ and $i_- = 0$
 - Calculate v_o to make this happen
 - Solve for any other variable
- Check Validity of Assumptions
 - v_o Is Between the Rails
 - Currents and Voltages Are “Large Enough”
 - More on that this Week



Op-Amp Impedances

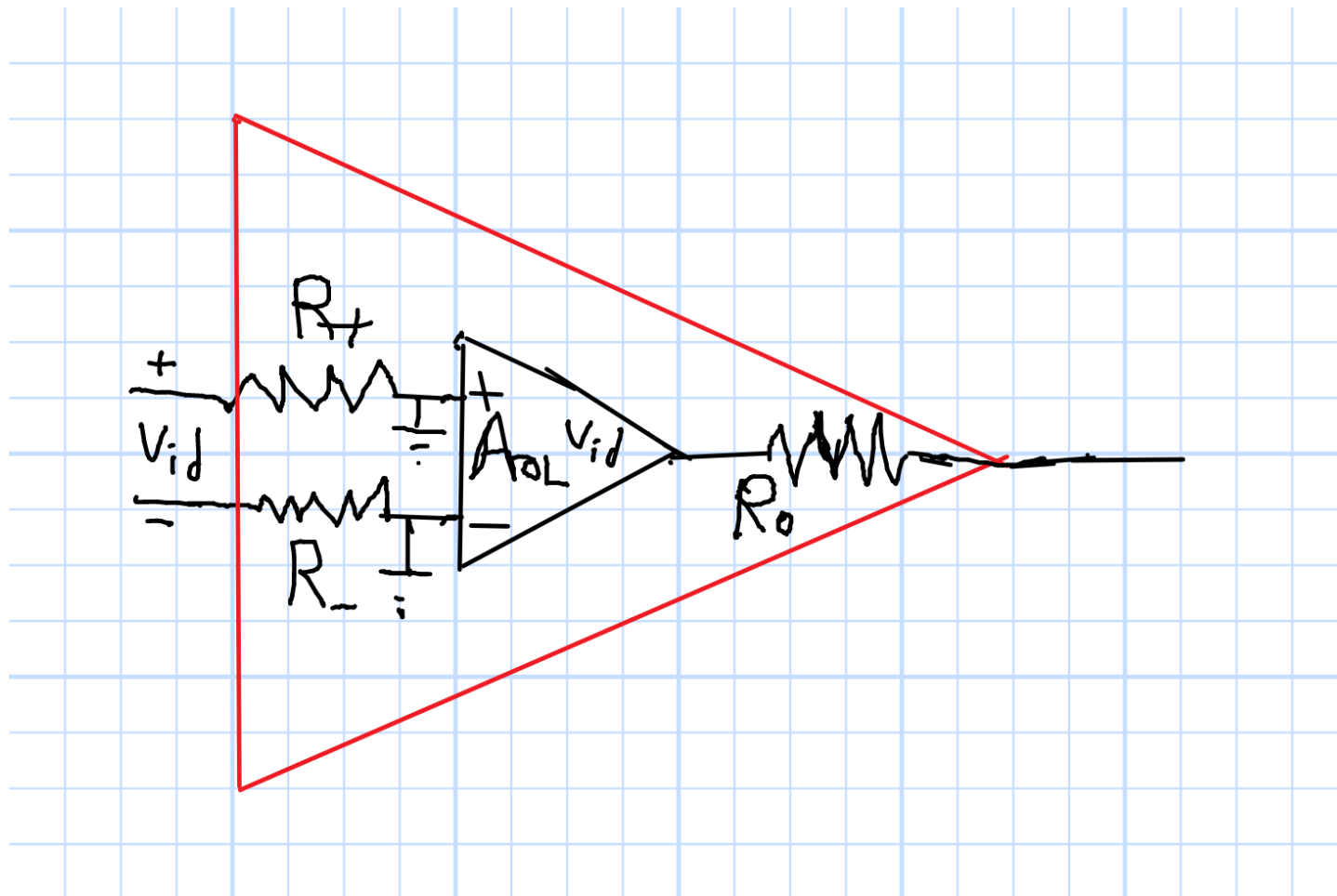

$$R_+ \rightarrow \infty \quad R_- \rightarrow \infty \quad R_o \approx 0$$

Usually OK

Impedances in a Circuit

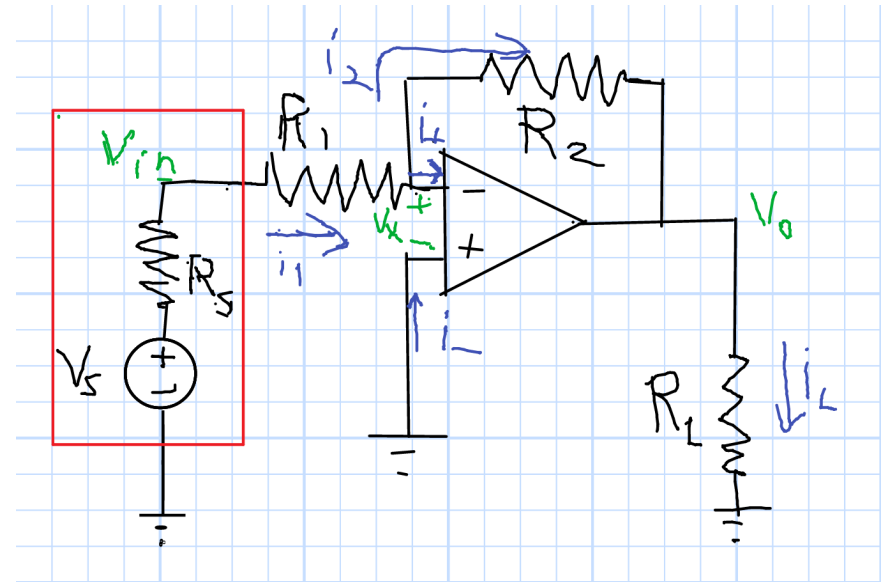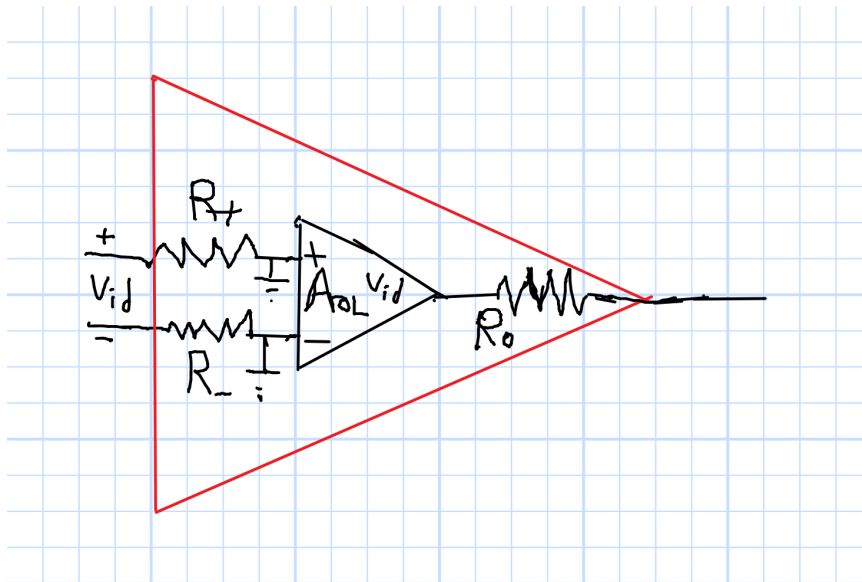

$$R_+ \rightarrow \infty$$

$$R_- \rightarrow \infty$$


$$R_o \approx 0$$

$$i_1 \approx i_2$$

$$A = -\frac{R_2}{R_1}$$

v_o independent of R_L

Finite Gain Effects (1)

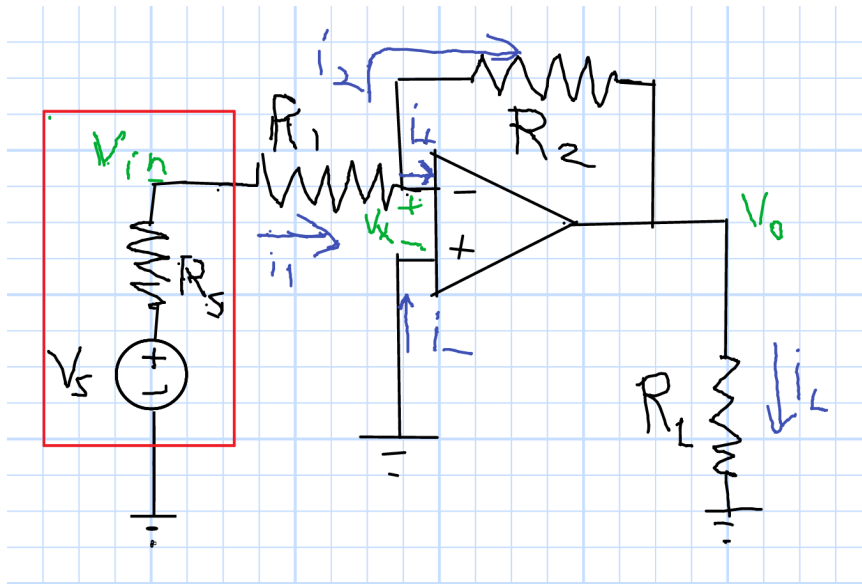

$$v_o = A_{OL} (v_+ - v_-)$$

$$v_+ = 0$$

$$v_- = -\frac{v_o}{A_{OL}}$$

Virtual Ground Fails.

$$v_- = v_{in} + (v_o - v_{in}) \frac{R_1}{R_1 + R_2}$$

$$-\frac{v_o}{A_{OL}} = v_{in} + (v_o - v_{in}) \frac{R_1}{R_1 + R_2}$$

$$-\frac{v_o}{A_{OL}} - v_o \frac{R_1}{R_1 + R_2} = v_{in} \frac{R_2}{R_1 + R_2}$$


multiply by $A_{OL} (R_1 + R_2)$

$$-v_o (R_1 + R_2 + A_{OL} R_1) = v_{in} R_2 A_{OL}$$

$$\frac{v_o}{v_{in}} = -\frac{R_2 A_{OL}}{R_1 + R_2 + A_{OL} R_1}$$

$$\frac{v_o}{v_{in}} = -\frac{R_2}{R_1} \frac{A_{OL}}{\frac{R_2}{R_1} + A_{OL} + 1}$$


Finite Gain Effects (2)

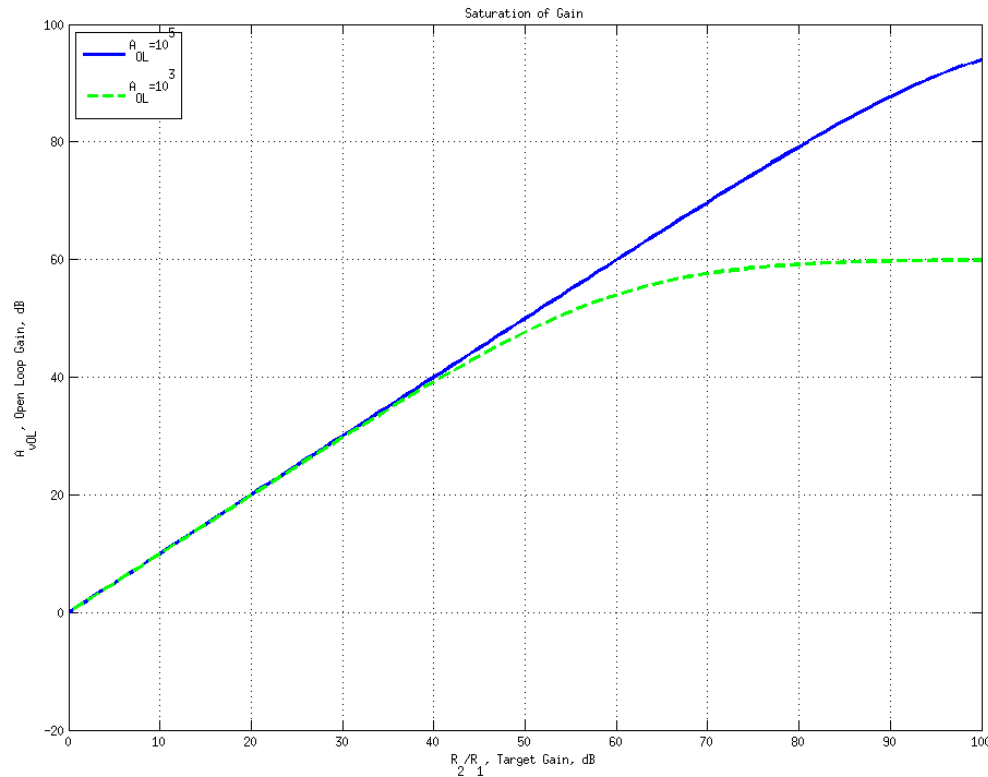

$$\frac{v_o}{v_{in}} = -\frac{R_2}{R_1} \frac{A_{OL}}{\frac{R_2}{R_1} + A_{OL} + 1}$$


A_{OL} is unpredictable; Don't trust it. Keep $R_2/R_1 \ll A_{OL}$

Op-Amp Gain Spectrum

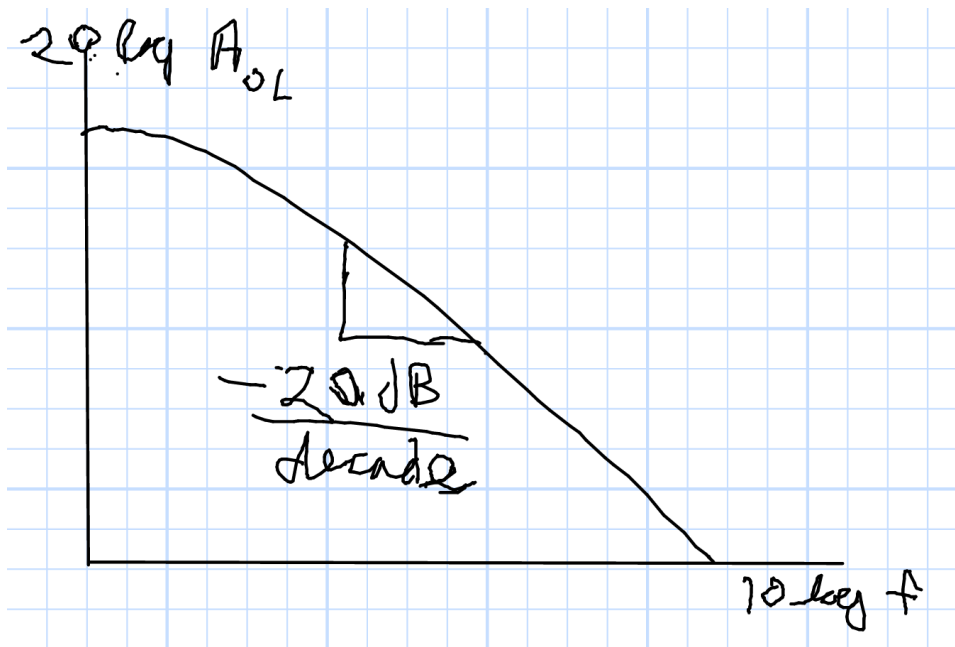


- A_{OL} Varies with Frequency
- $A_{OL}(0)$ is Maximum
- f_{oOL} is Cutoff Frequency
- $A_{OL}(f_{oOL}) = \frac{A_{OL}(0)}{\sqrt{2}}$
- Why Square Root of 2?

Open-Loop Gain Spectrum

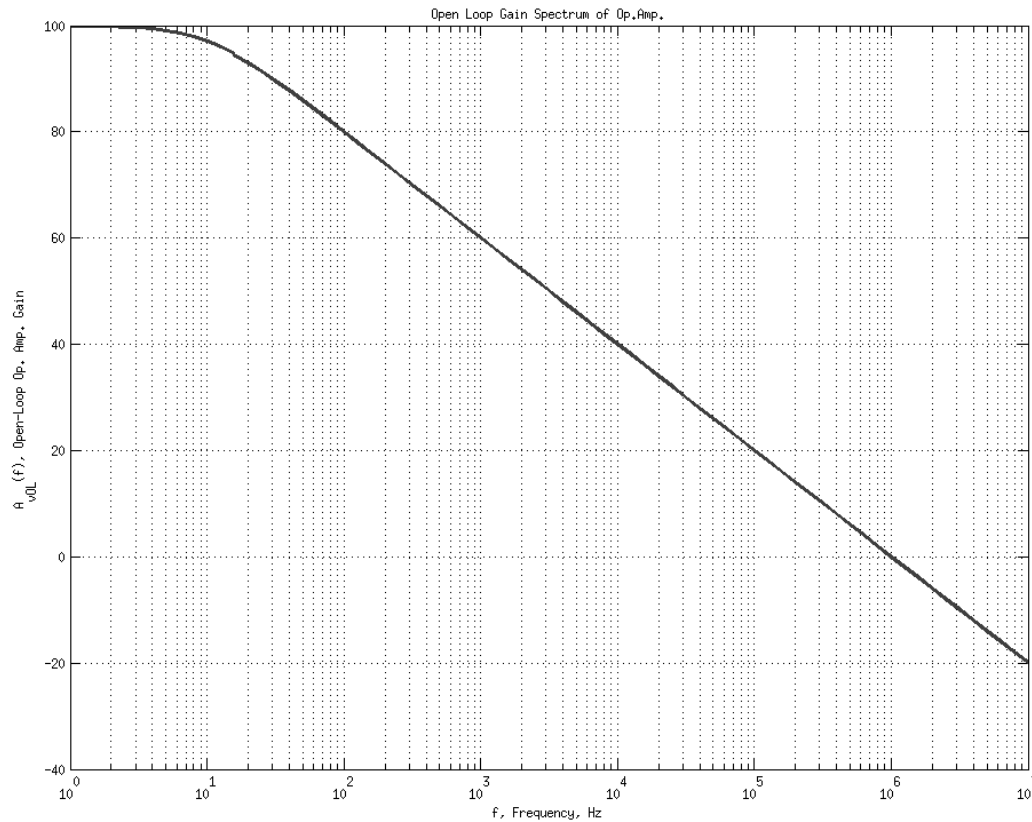

$$A_{OL}^2(f) = \frac{A_{OL}^2(0)}{1 + \left(\frac{f}{f_{0OL}}\right)^2} \quad A_{OL}(f_{0OL}) = \frac{A_{OL}(0)}{\sqrt{2}}$$

Closed-Loop Gain Spectrum

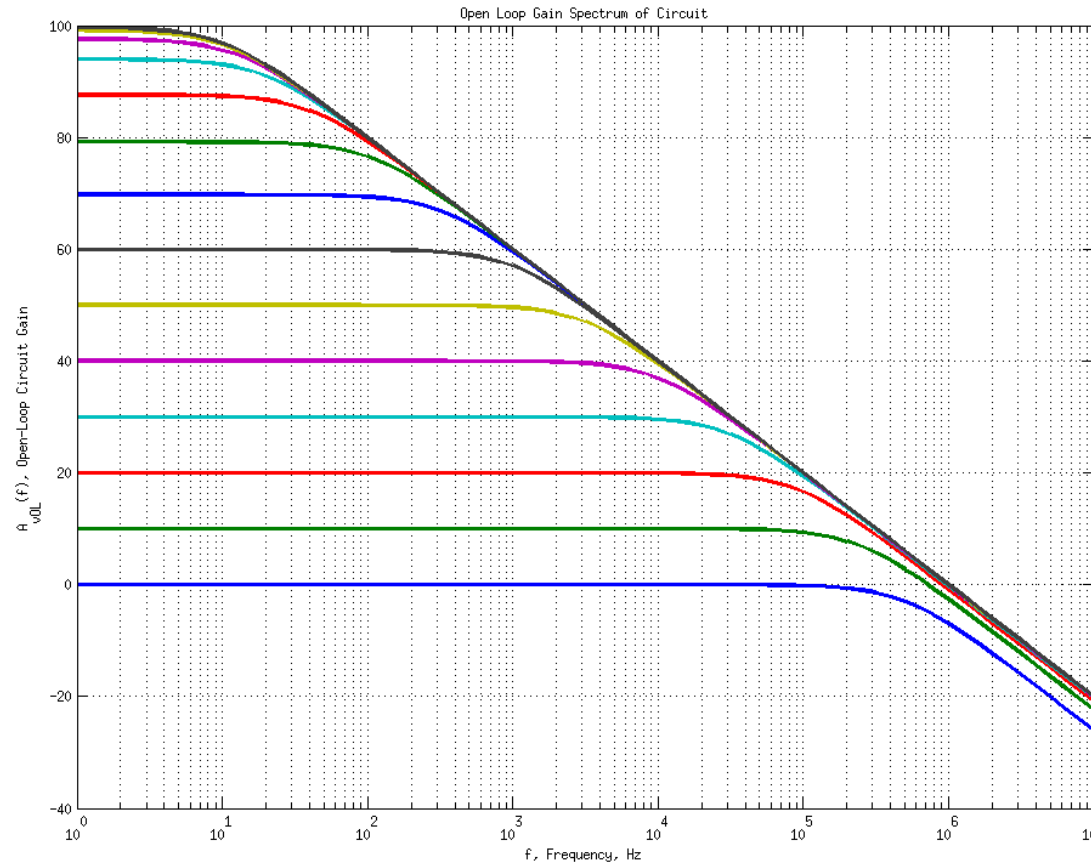


$$A_{CL}f_{0CL} = A_{OL}f_{0OL} \quad \text{Gain-Bandwidth Product}$$

Week 6 Agenda: Operational Amplifiers


- Linear Effects
 - Input and Output Impedances
 - Finite Gain, A_{OL}
 - Gain–Bandwidth Product
- Nonlinear Effects
 - Voltage Limit
 - Current Limit
 - Slew Rate
- DC Imperfections
 - Bias and Offset Currents
 - Offset Voltage
- Differential Amplifiers

Voltage Limits

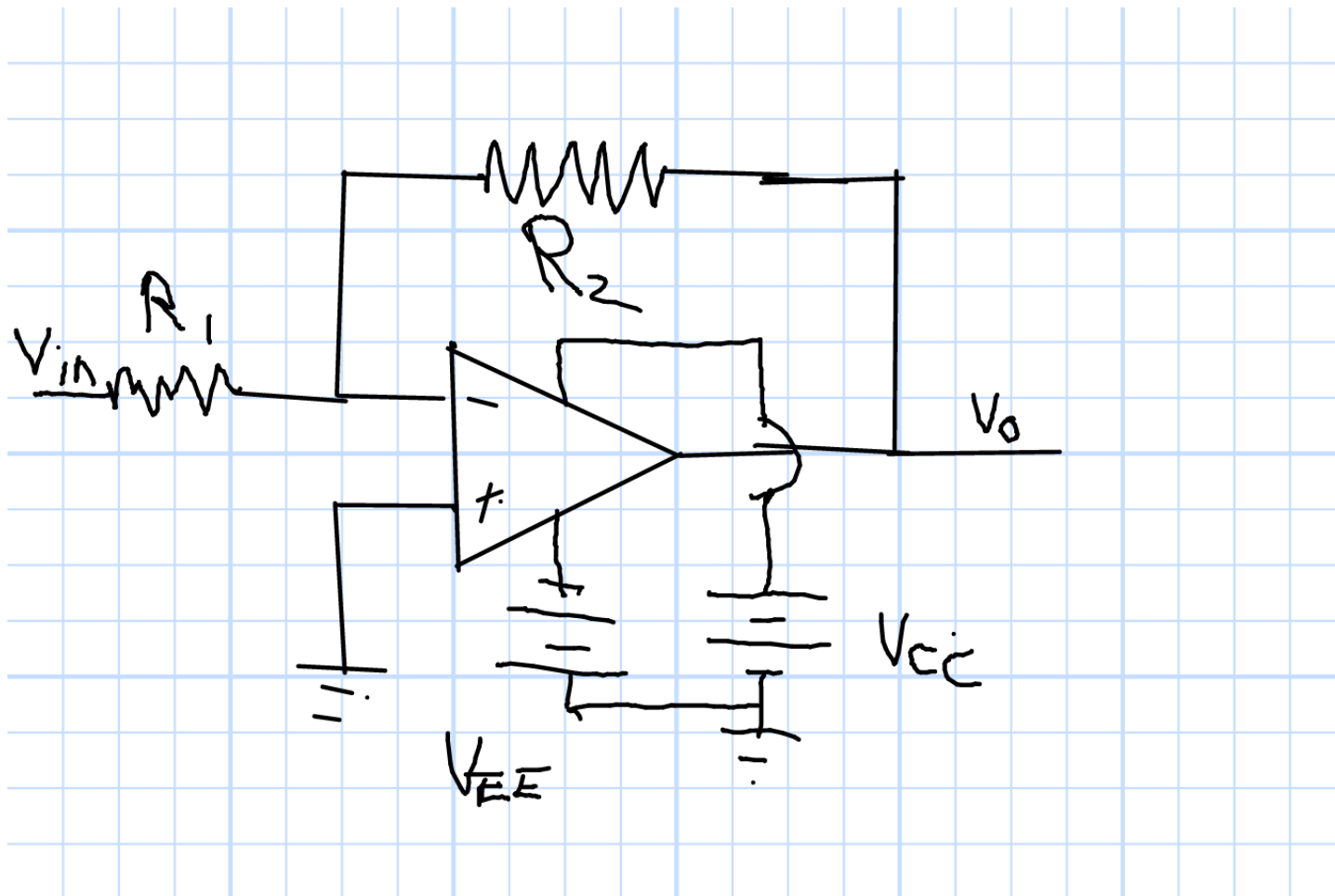


$$\text{Ideal Gain: } -R_2/R_1 = -5$$

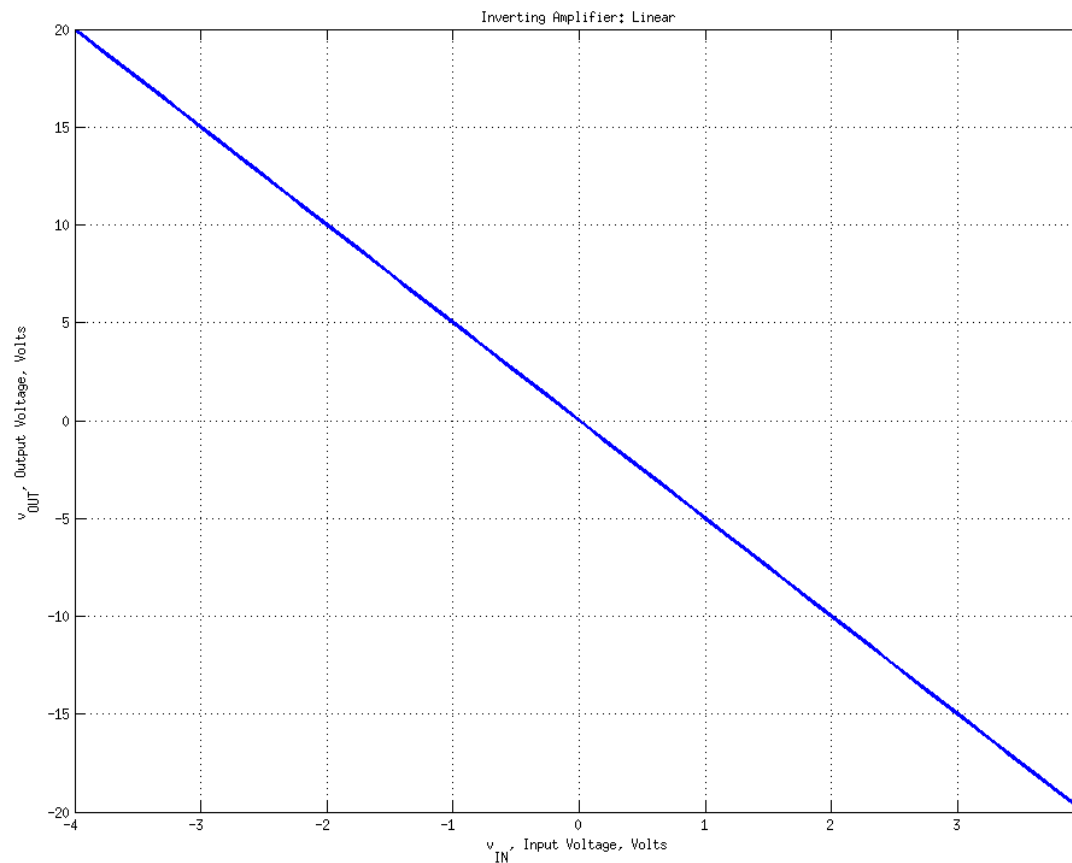New Concept: Transfer Function (Plot of output vs. input)




Voltage Limits Example

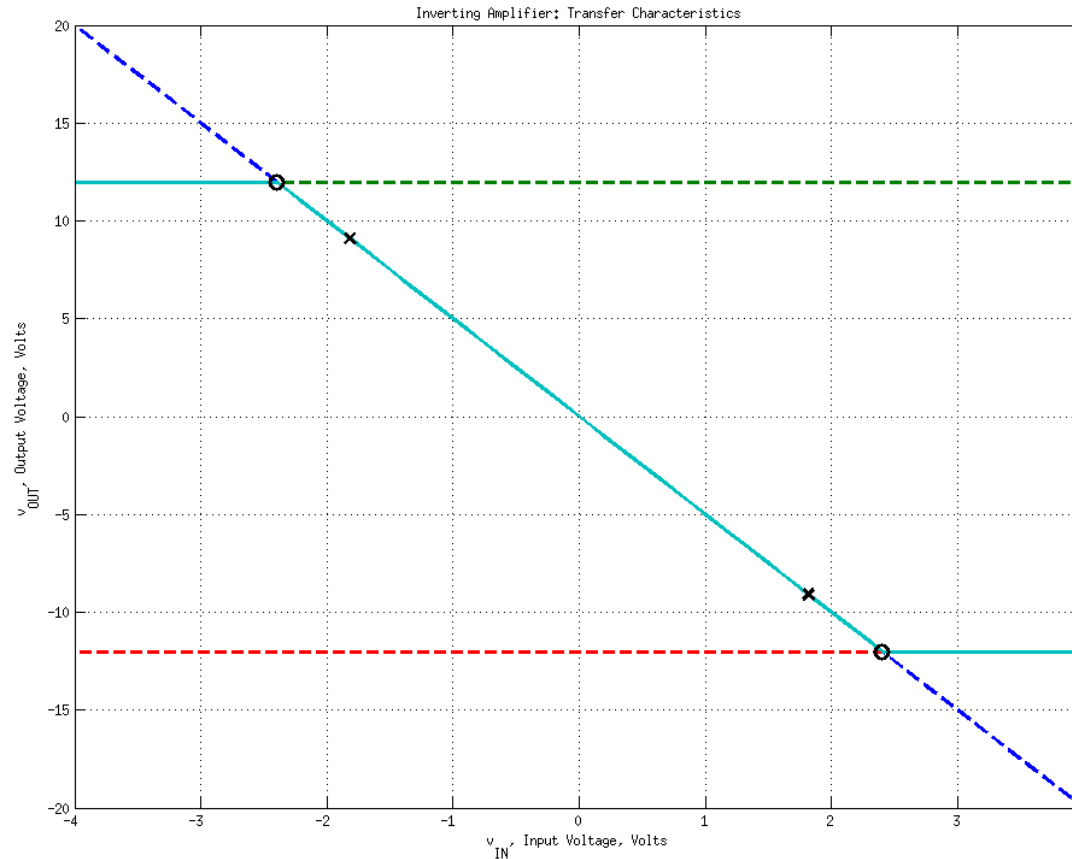


± 12 -Volt Power Rails. Blue dash is ideal. Cyan solid is actual.

Voltage on $-$ Input

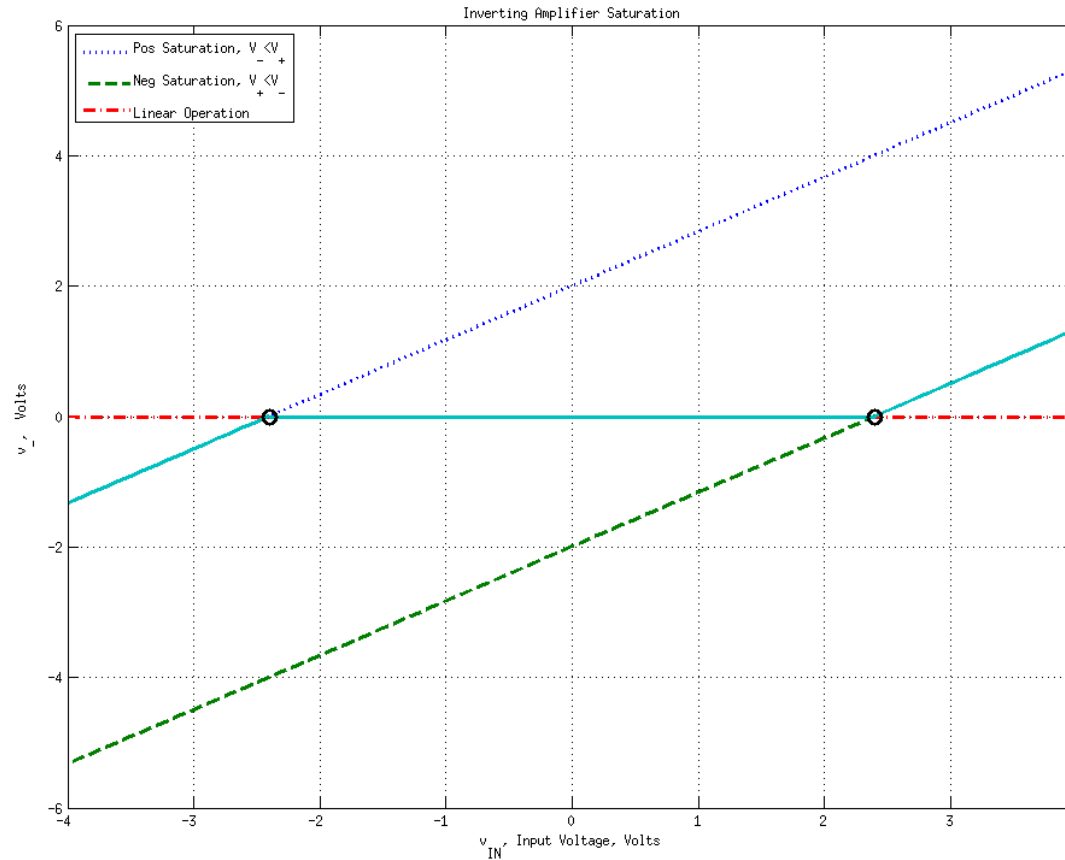


Virtual Ground Fails.

Gain Saturation Example

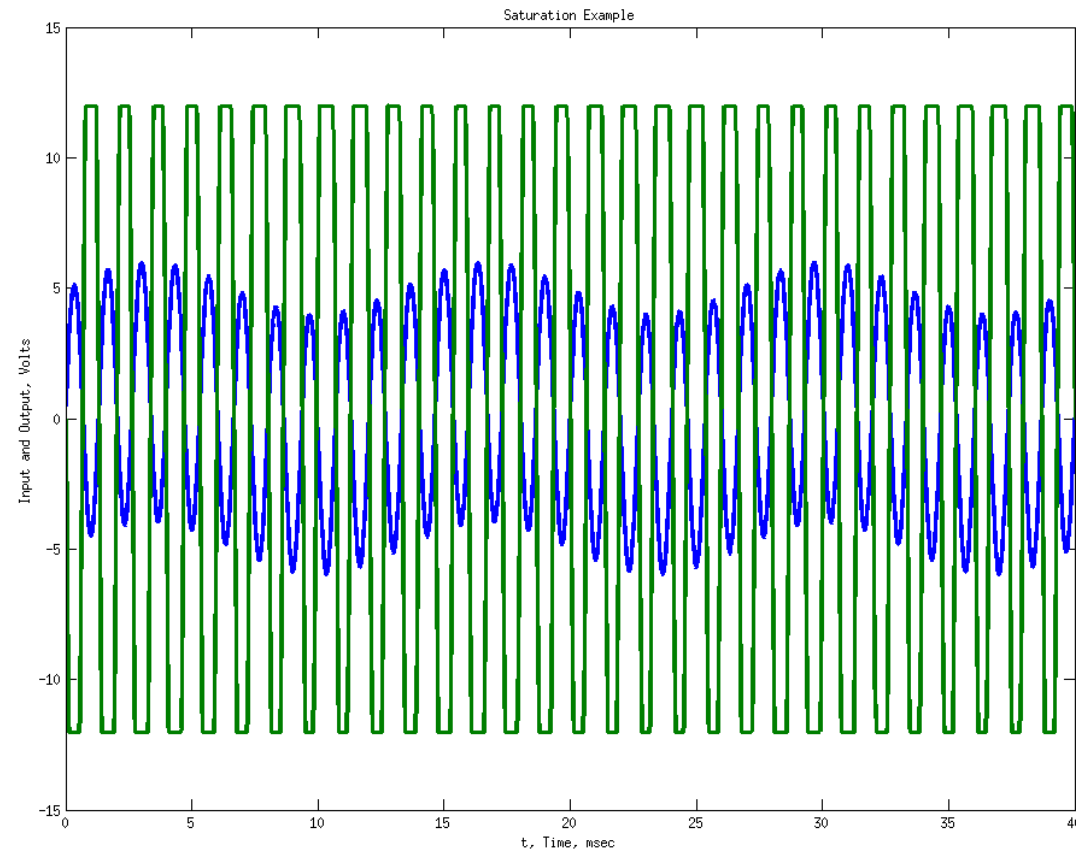

Blue in, green out. 1V at 75Hz 5V at 750Hz
 $R_2/R_1 = 5000/1000, \pm 12 \text{ V rails}$


Current Limits

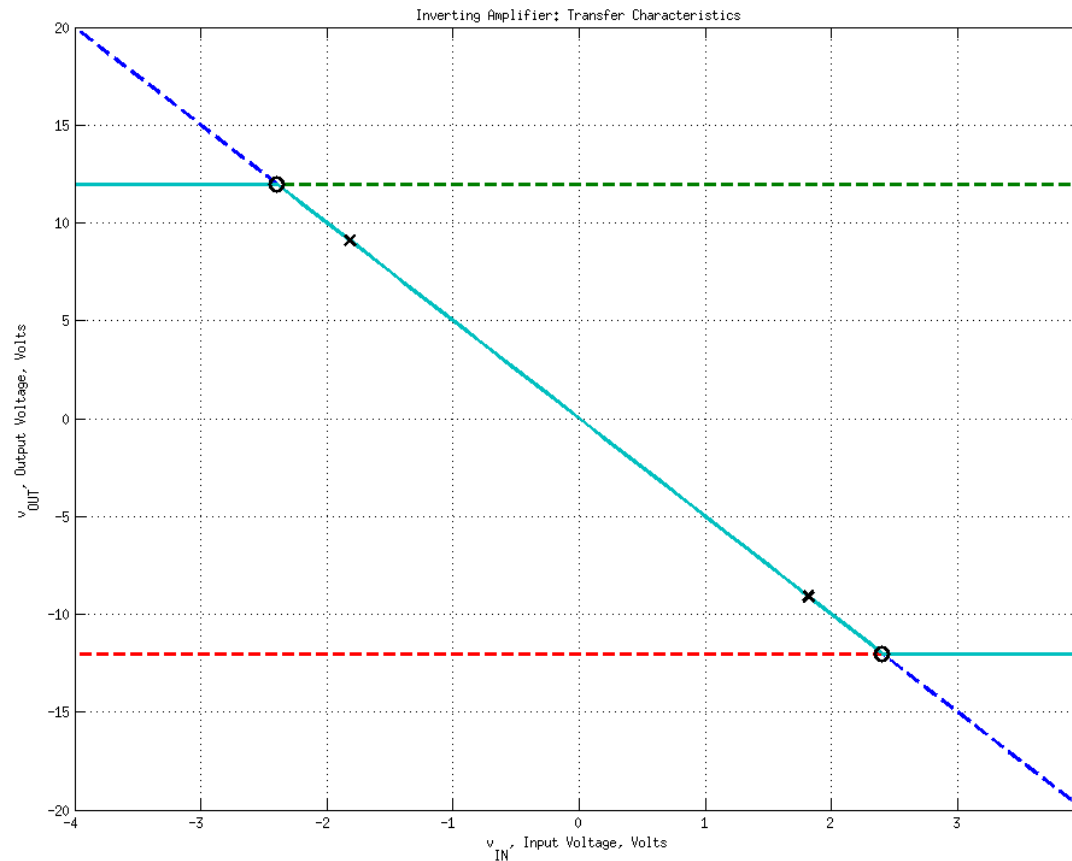

x shows current limit, $I_{max} = 20\text{mA}$ at $v = i_{max}R_L \parallel R_2$.
 $R_L = 500\Omega$, $R_2 = 5\text{k}\Omega$

Slew Rate Limit

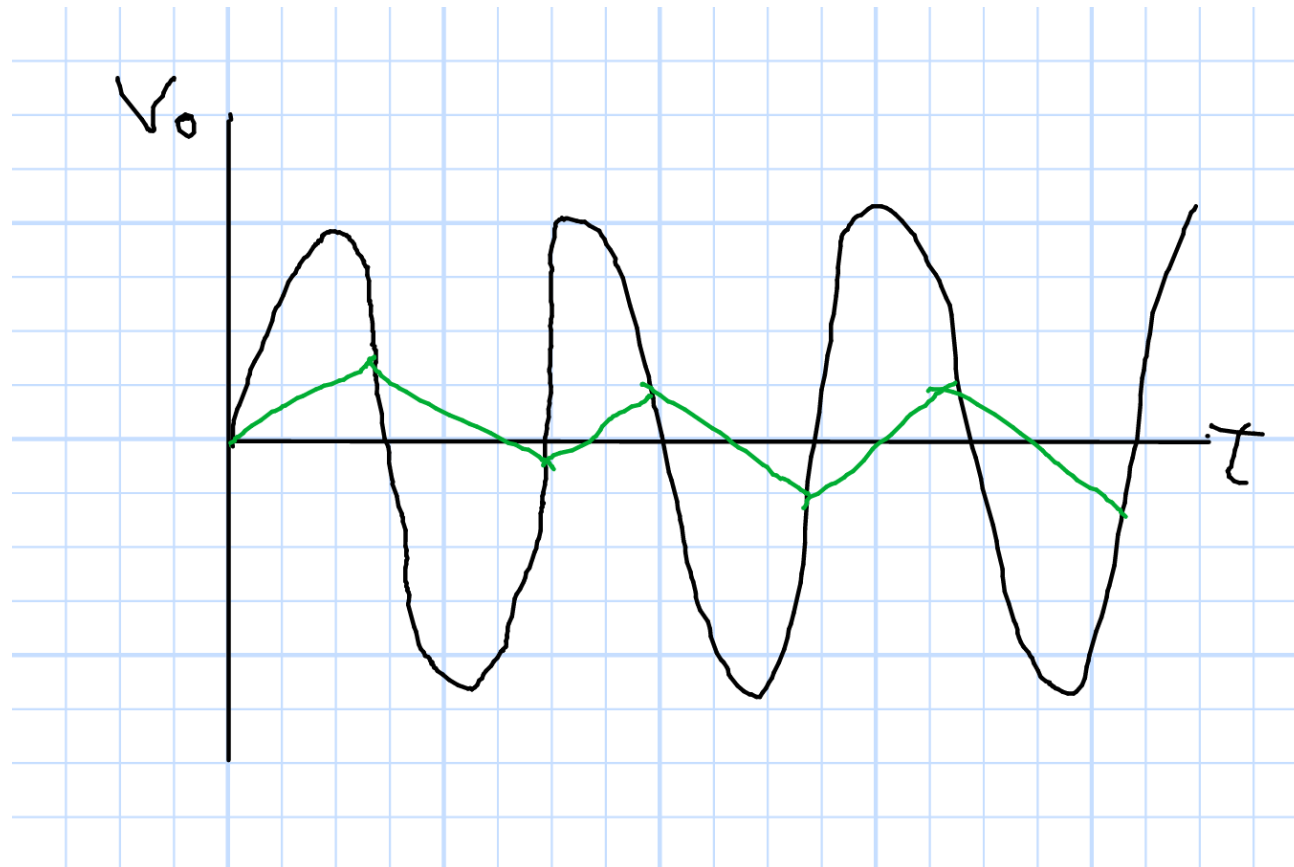
Desired voltage, $A_V v_{in}$ in Black varies too fast.
Result is Green.



Week 6 Agenda: Operational Amplifiers


- Linear Effects
 - Input and Output Impedances
 - Finite Gain, A_{OL}
 - Gain–Bandwidth Product
- Nonlinear Effects
 - Voltage Limit
 - Current Limit
 - Slew Rate
- DC Imperfections
 - Bias and Offset Currents
 - Offset Voltage
- Differential Amplifiers

DC Imperfections

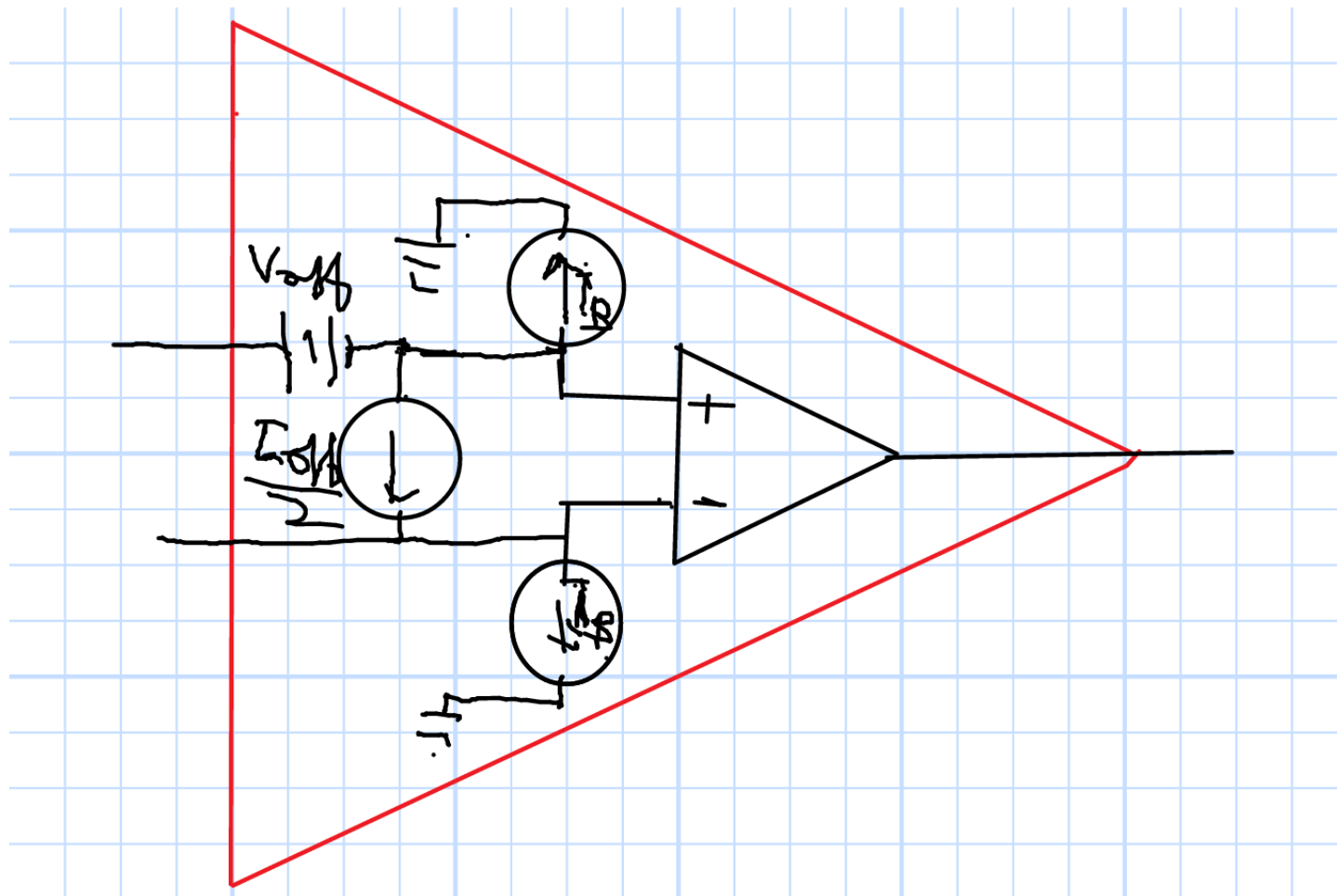


Adjustment for v_{off} , Circuit design for currents.
Not needed for typical applications.

Differential Amplifier

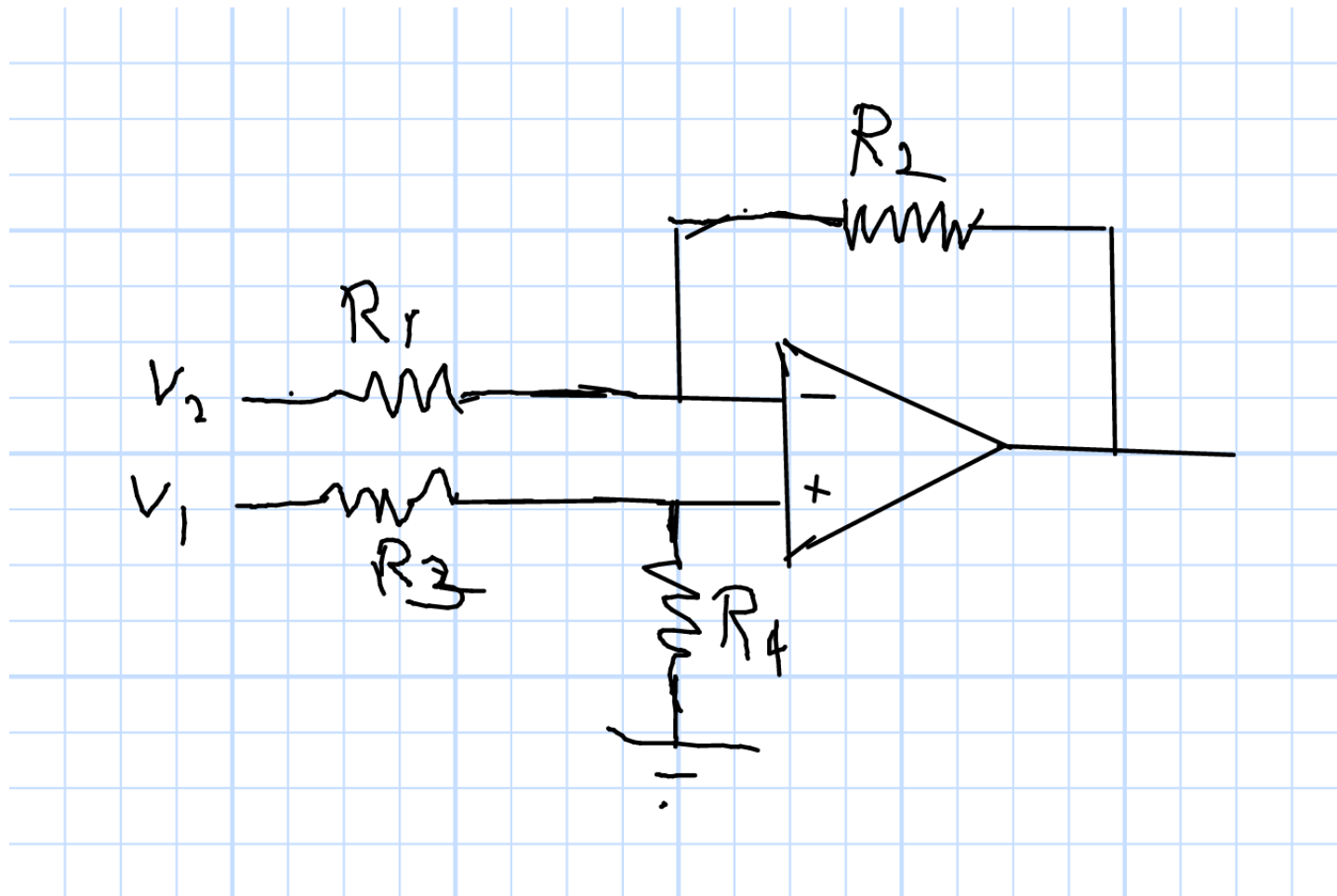

v_2 affects current in v_1 source (try superposition)

Good Differential Amplifier

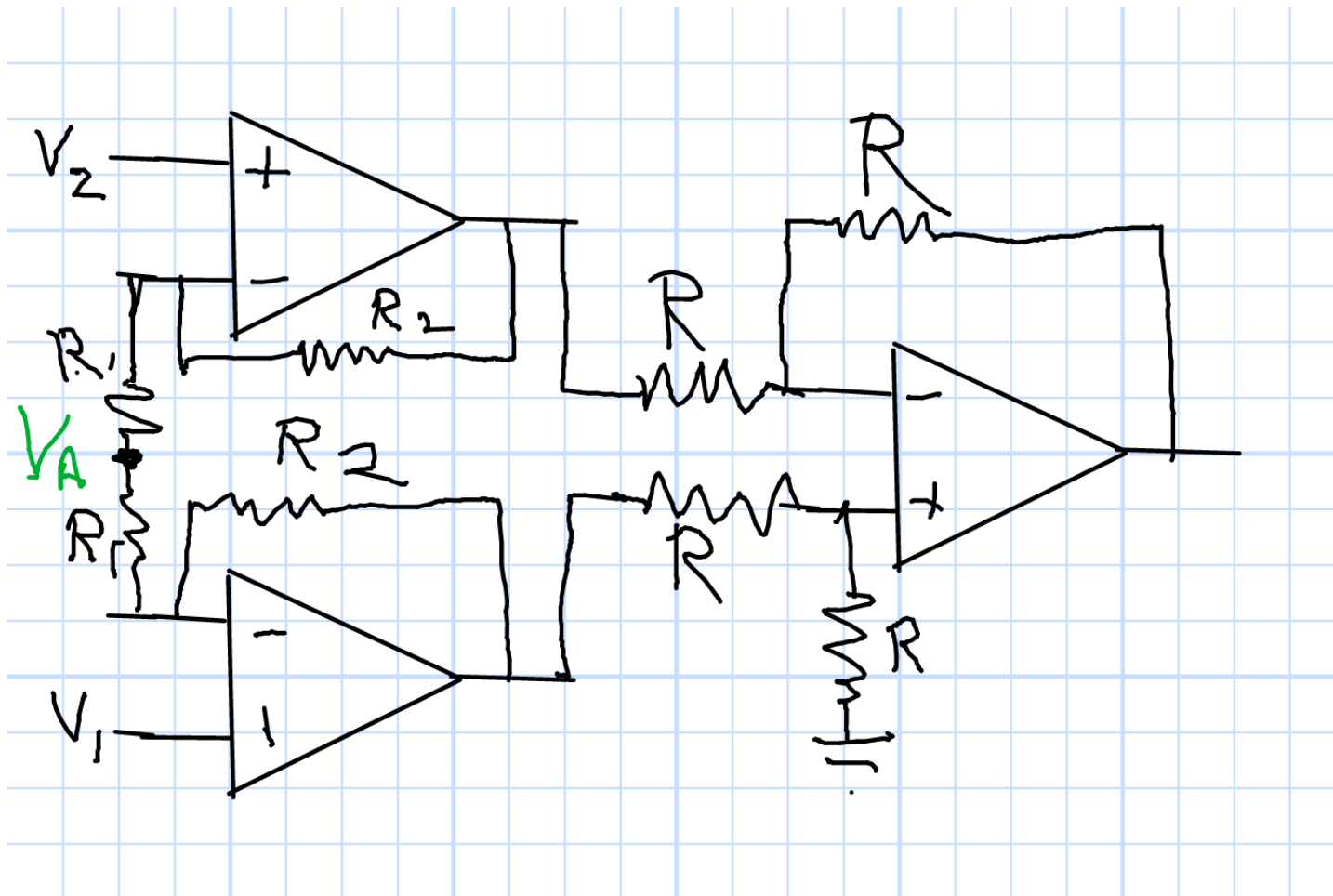

Infinite input impedance. Low common-mode gain.

A Little Review

- Circuit Concepts
- KCL, KVL
- Ohm's Law, Resistivity, Resistance and Geometry
- Series and Parallel Combinations
- Node and Mesh Analysis
- Superposition
- Wheatstone Bridge Circuit
- Op-Amps; Inverting, Non-inverting, Impedances, Limits