

Electrical Engineering

Week 9

Charles A. DiMarzio
EECE-2210
Northeastern University

Oct 2021


Week 9 Agenda: First-Order Circuits

- RC Circuits
- Boundary Conditions
- Steady State Solutions
- Charge and Discharge a Capacitor
- RL Circuits
- Some Examples

Time-Varying Sources


- Transient Analysis (Now)
 - Differential Equations
 - First Order for RL, RC
 - Second Order for RLC
 - Circuits Usually Involve Switches
 - Transient and Steady-State Solutions
- Sinusoidal Solution (Later)
 - Phasor Analysis ($\frac{d}{dt} = j2\pi f$)
 - Complex Impedance
 - “Easy” Solutions
 - Fourier Series and Transforms

RC Circuit

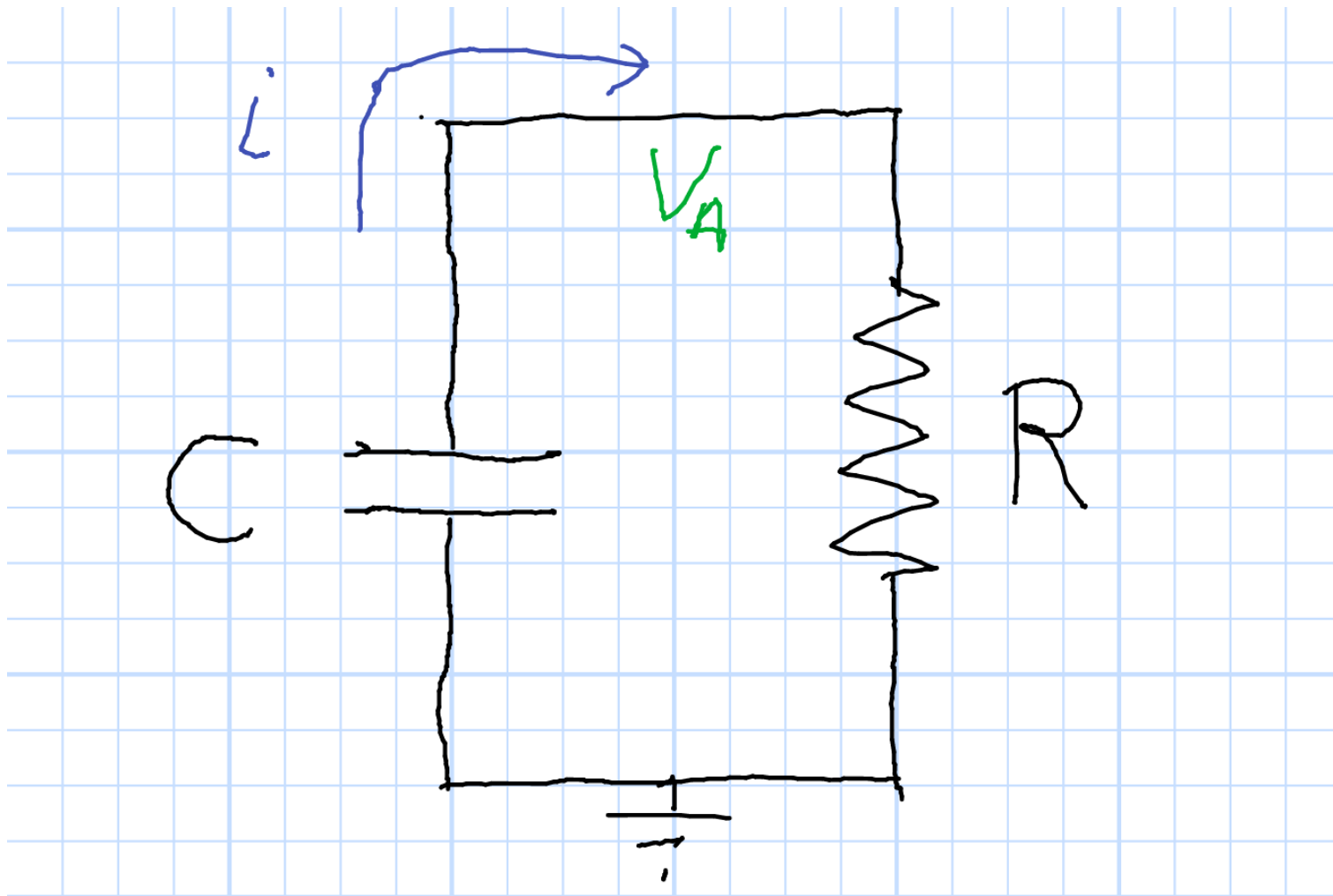

$$i = C \frac{dv}{dt} \quad i = -C \frac{dv_A}{dt} \quad v_A = iR$$

RC Equations

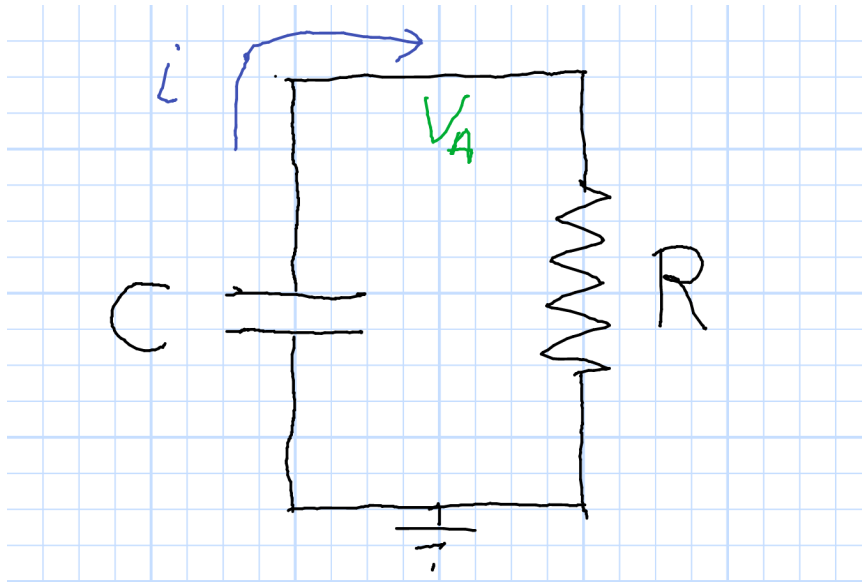

$$i = -C \frac{dv_A}{dt}$$

$$i = \frac{v}{R}$$

- Differential Equation

$$v_A = -RC \frac{dv_A}{dt}$$

- Test Solution

$$v_A = k_1 e^{st} + k_2$$

- Substitute

$$k_1 e^{st} + k_2 = -RC \frac{d}{dt} (k_1 e^{st} + k_2)$$


- Take the Derivative

$$k_1 e^{st} + k_2 = -RC s k_1 e^{st}$$

- Group

$$k_1 (1 + RCs) e^{st} - k_2 = 0$$

RC Solution

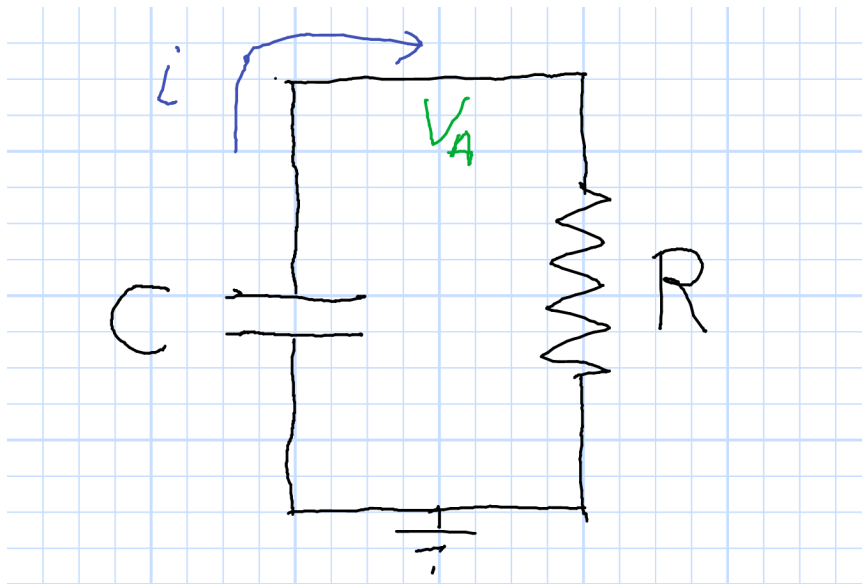

$$i = -C \frac{dv_A}{dt}$$

$$i = \frac{v}{R}$$

$$v_A = k_1 e^{st} + k_2$$

- From Previous Page

$$k_1 (1 + RCs) e^{st} - k_2 = 0$$

- True for All Time

$$k_2 = 0 \quad s = -\frac{1}{RC}$$

- Solution

$$v_A = k_1 e^{-t/(RC)} + 0$$


- Time Constant

$$v_A = k_1 e^{-t/\tau}$$


$$\tau = RC$$

- Still One Unknown (k_1)


General Boundary Conditions

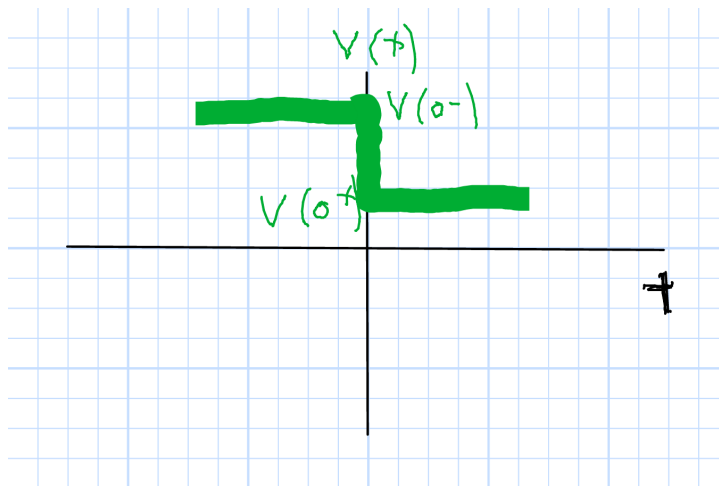


Not Valid for Capacitors

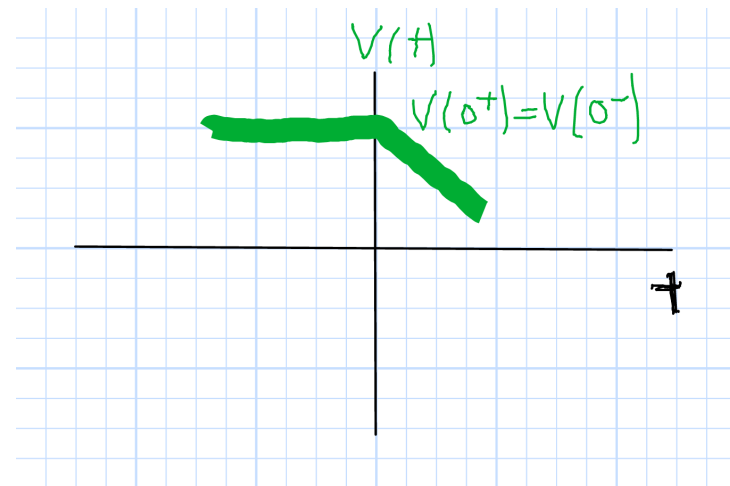

OK

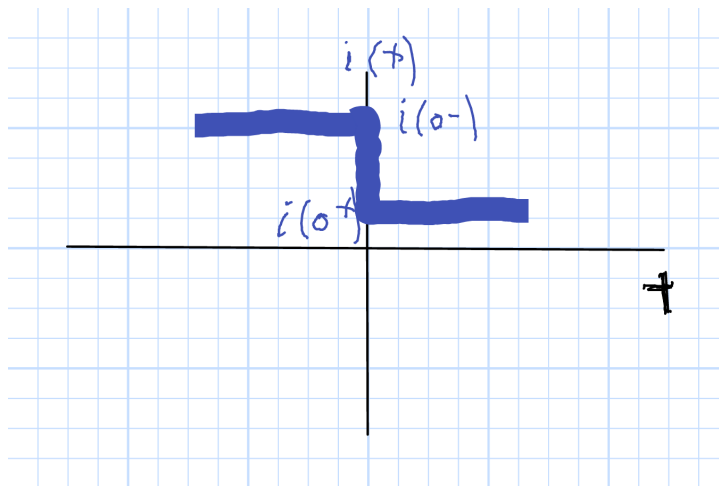


Not Valid for Inductors

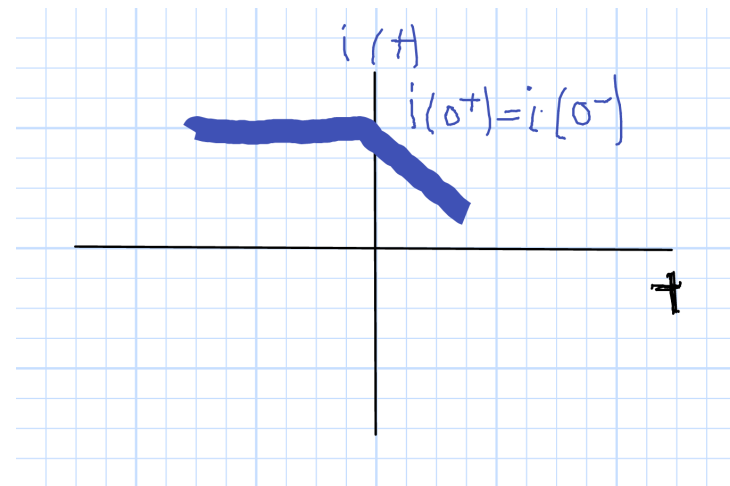

OK

Initial Conditions

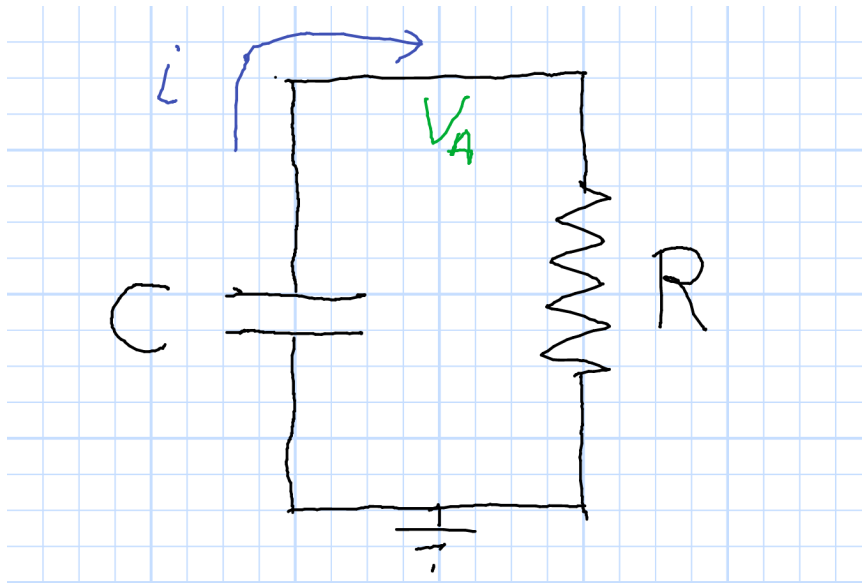

$$i = -C \frac{dv_A}{dt}$$

$$i = \frac{v}{R}$$

$$v_A = k_1 e^{st} + k_2$$

- From Earlier Page

$$v_A = k_1 e^{-t/\tau}$$

$$\tau = RC$$

- Original Voltage $V(0^-)$
- Boundary Condition

$$V(0^+) = V(0^-)$$


- At $t = 0$

$$k_1 e^{-0/\tau} = k_1 = V(0^+)$$

- Solution

$$v_A = V(0^-) e^{-t/\tau}$$


Exponential Solutions

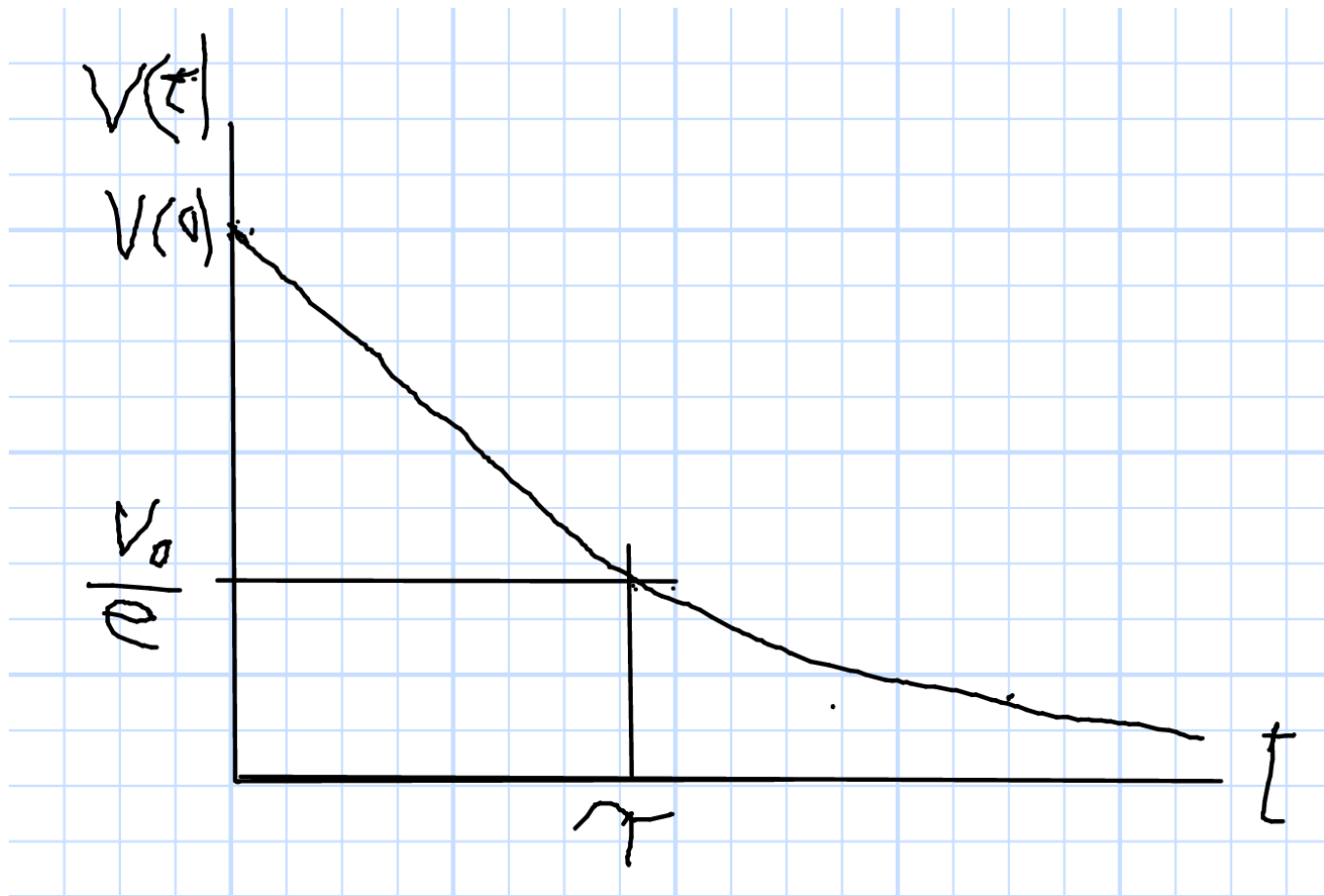

$$v_a = v_a(0) e^{-t/\tau} \quad v_a(\tau) = v_a(0) \times \frac{1}{e} \approx v_a(0) \times 0.3679$$

$$v_a(2\tau) \approx v_a(0) \times 0.1353 \quad v_a(10\tau) \approx v_a(0) \times 4.540 \times 10^{-5}$$

Steady-State Solution

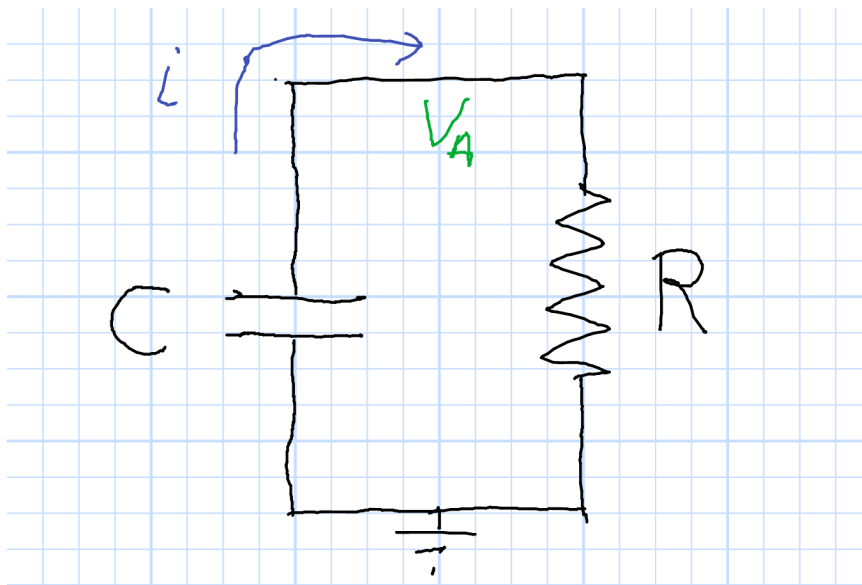

$$i = -C \frac{dv_A}{dt}$$

$$i = \frac{v}{R}$$

$$v_A = k_1 e^{st} + k_2$$

- Steady State

$$t \rightarrow \infty$$

- Anything that is going to happen has happened

$$\frac{d\text{Anything}}{dt} = 0$$

- Transient Solution is Zero


$$\frac{dv_A}{dt} = 0 \quad i = 0$$

- Solution

$$k_2 = 0 = v_{A\infty}$$


Q: Why would the steady-state solution not be zero?

Charge and Discharge

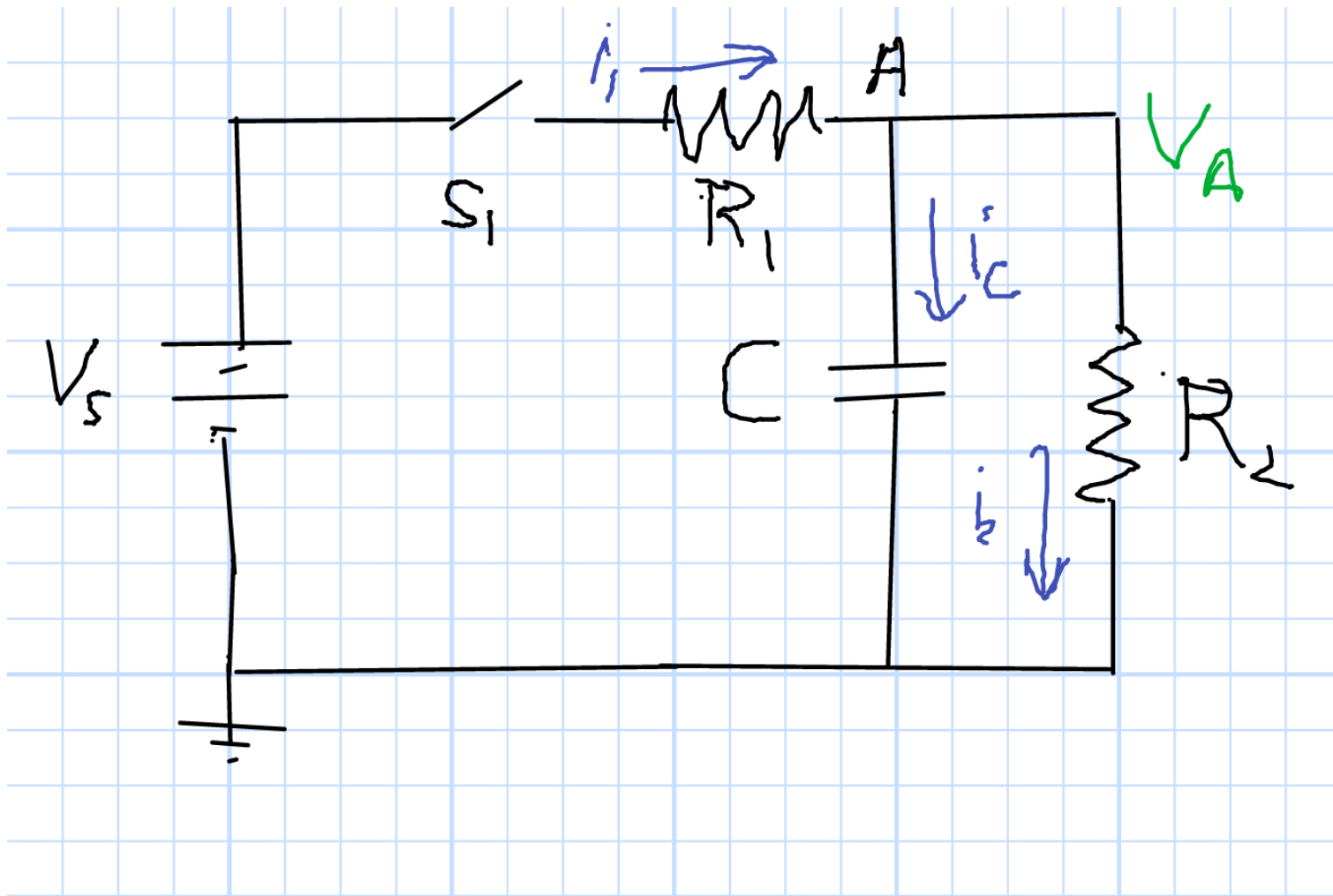

Close S_1 at $t = 0$. Open S_1 at $t = t_1$. What will happen?

Charge!

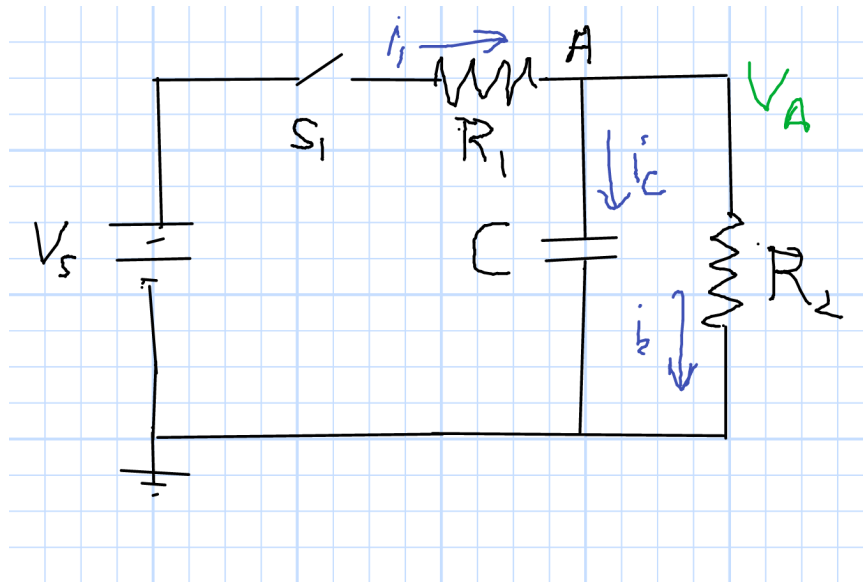


Thévenin Equivalent Charging

$$v_T = v_S \frac{R_2}{R_1 + R_2}$$


$$R_T = R_1 \parallel R_2$$

Assume

$$v_A(0) = 0$$

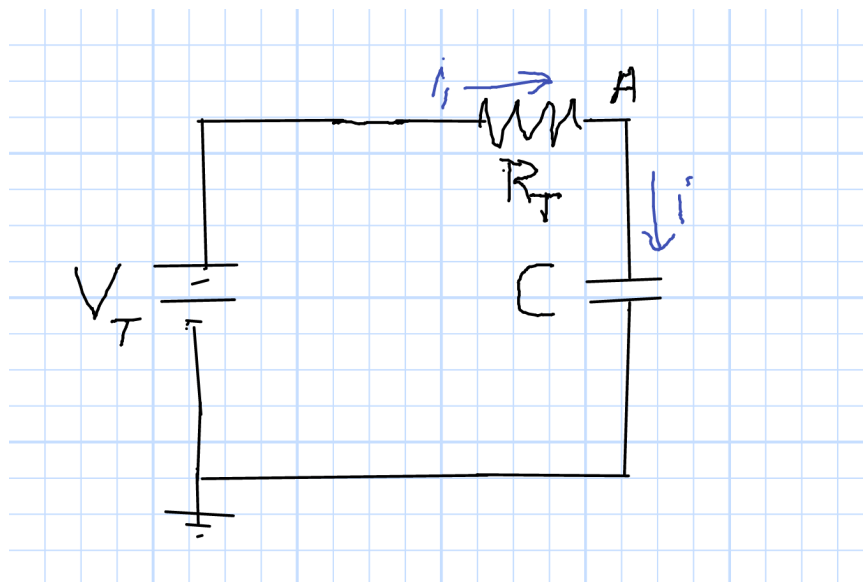

Charging Equations

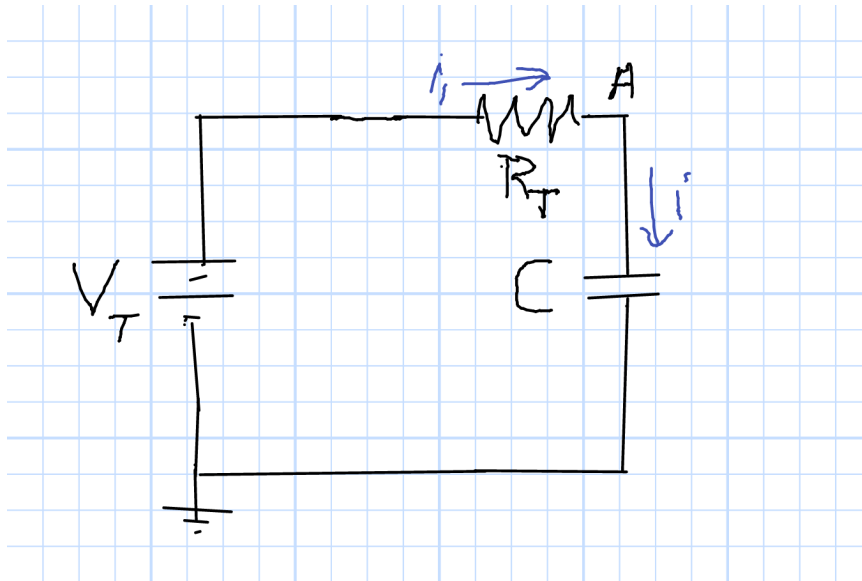

$$i = \frac{v_T - v_A}{R_T} = C \frac{dv_A}{dt}$$

$$v_T - v_A = R_T C \frac{dv_A}{dt}$$

$$v_A + R_T C \frac{dv_A}{dt} = v_T$$

Proposed Solution

$$v_A = k_1 e^{st} + k_2$$

$$k_1 e^{st} + k_2 + R_T C \frac{d}{dt} (k_1 e^{st} + k_2) = v_T$$

$$k_1 e^{st} (1 + R_T C s) + k_2 = v_T$$


$$s = \frac{-1}{R_T C} \quad k_2 = v_T$$

$$v_T = v_S \frac{R_2}{R_1 + R_2}$$

$$R_T = R_1 \parallel R_2$$

$$v_A(0) = 0$$

Charging Solution

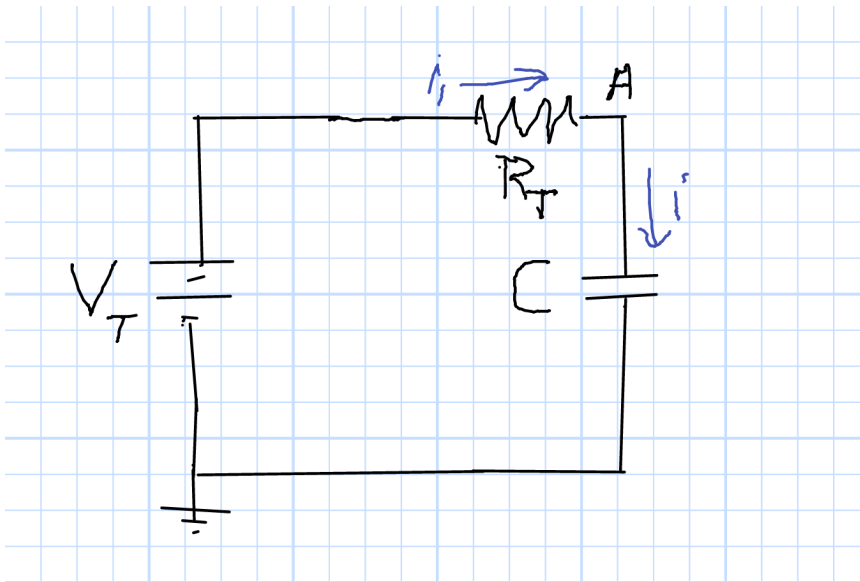

$$v_T = v_S \frac{R_2}{R_1 + R_2}$$

$$R_T = R_1 \parallel R_2$$

$$v_A(0) = 0$$

- From Previous Page

$$v_A = k_1 e^{st} + k_2$$

$$s = \frac{1}{R_T C} \quad k_2 = v_T$$

$$v_A = k_1 e^{-t/(R_T C)} + v_T$$

- Initial Condition


$$v_A(0) = k_1 + v_T$$

$$v_A(0) = 0 \quad k_1 = -v_T$$

- Solution

$$v_A = v_T \left(1 - e^{-t/(R_T C)} \right)$$

Charging Result

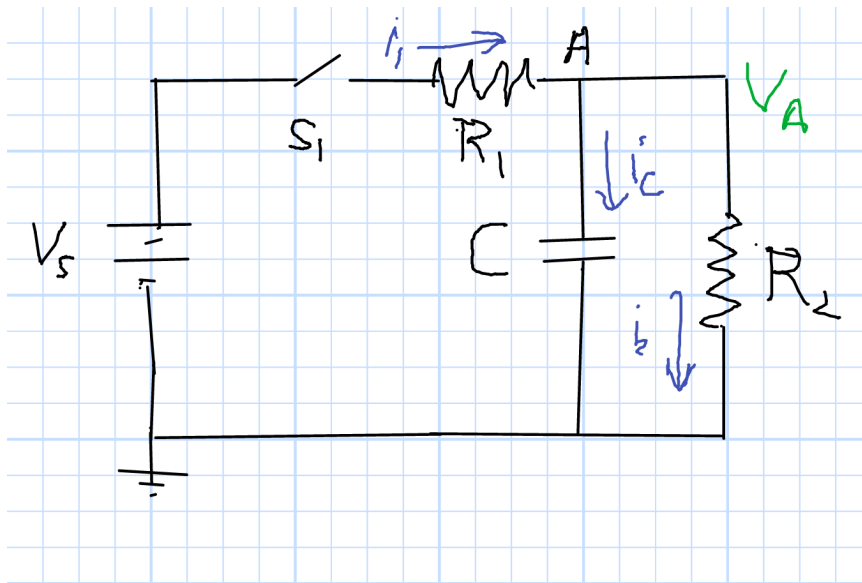

$$v_T = v_S \frac{R_2}{R_1 + R_2}$$

$$R_T = R_1 \parallel R_2$$

$$v_A(0) = 0$$

- From Previous Page

$$v_A = v_T \left(1 - e^{-t/(R_T C)} \right)$$

- Use v_T and R_T

$$v_A = v_S \frac{R_2}{R_1 + R_2} \times$$

$$\left\{ 1 - e^{-t/((R_1 \parallel R_2)C)} \right\}$$

- Assume $R_1 \ll R_2$


$$v_A \approx v_S \times \left\{ 1 - e^{-t/(R_1 C)} \right\}$$

- Example

$$R_1 = 100\Omega \quad C = 100\mu\text{F}$$

$$\tau \approx R_1 C = 10\text{ms}$$

Charging Voltage


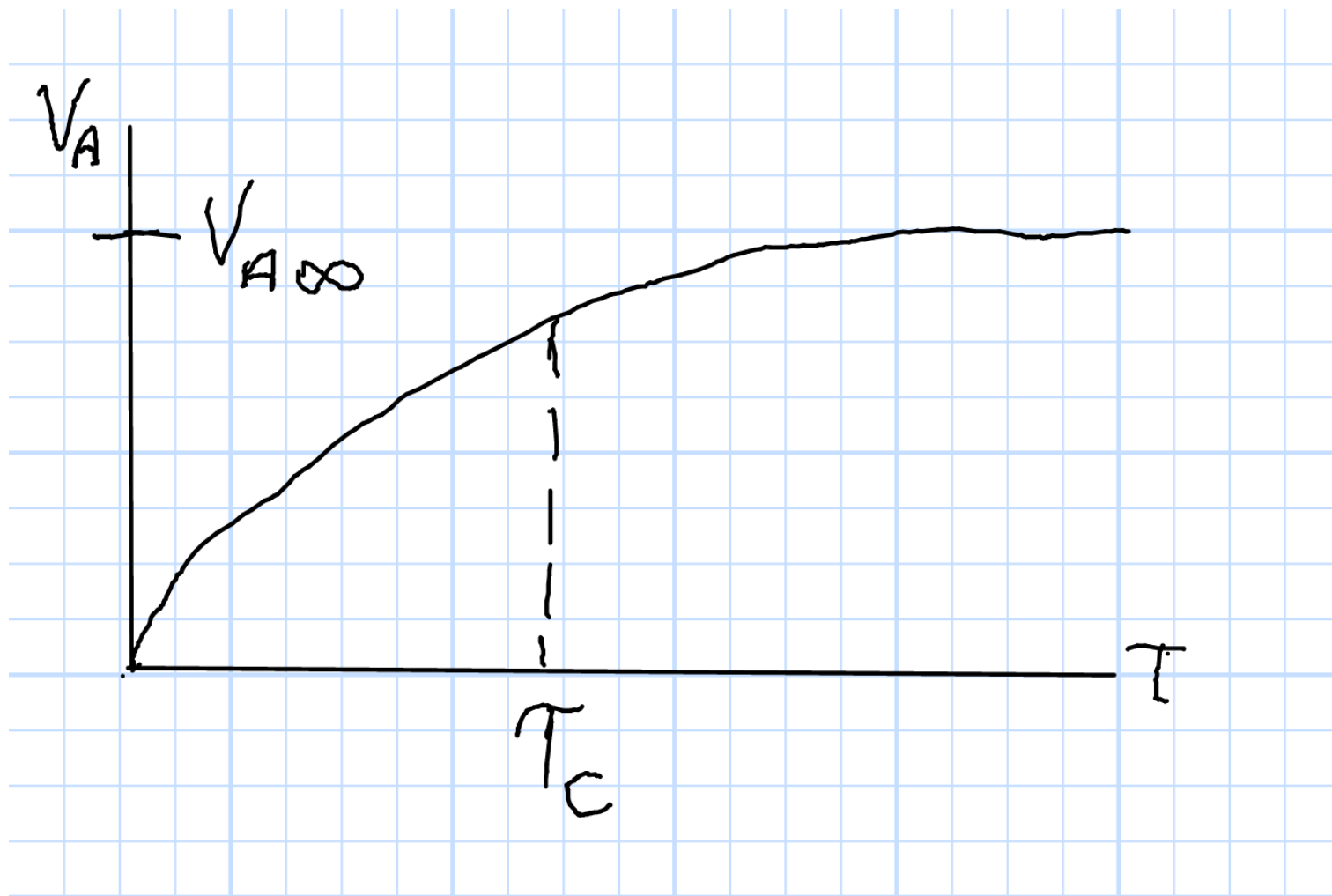


$$v_{A\infty} = v_T \approx v_s$$

$$\tau_C \approx R_1 C$$

$$v_A(\tau_C) \approx (1 - 0.3679) v_s = 0.6321 v_s$$

Discharge!

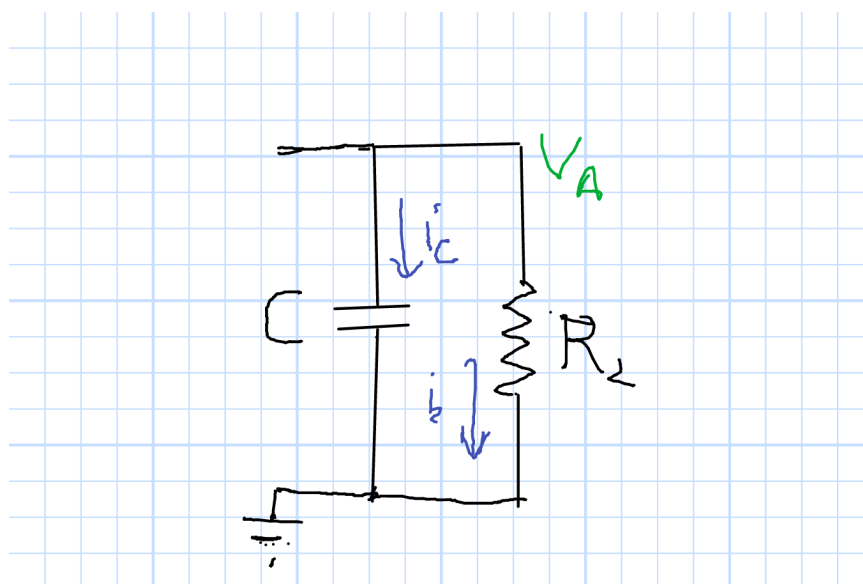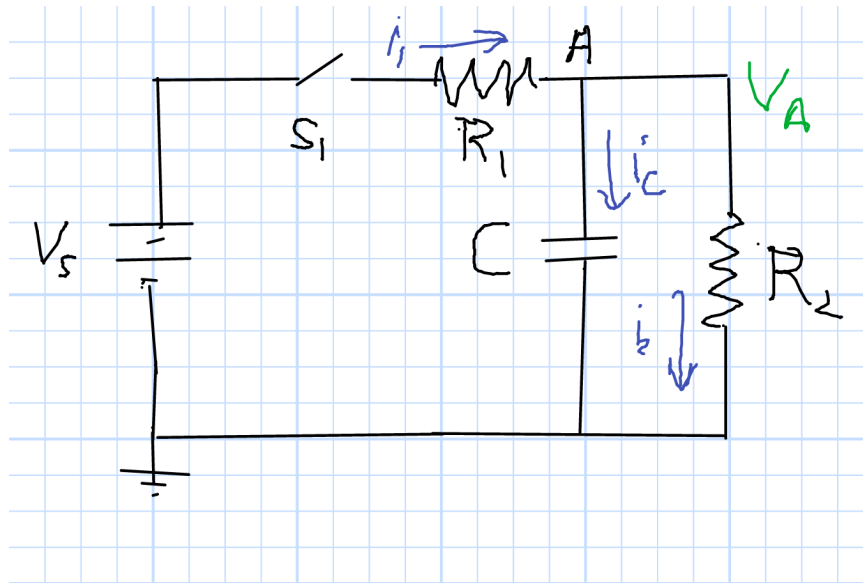

- Thévenin Equivalent

$$v_T = 0 \quad R_T = R_2$$

- Initial Voltage
- Open S_1 at $t = t_1$

$$v_A(t_1) = v_s \frac{R_2}{R_1 + R_2} \times \left\{ 1 - e^{-t_1 / ((R_1 \parallel R_2)C)} \right\}$$


- We've seen this before

$$v_A = v_A(t_1) e^{-(t-t_1)/(R_2 C)}$$

- Example: $R_2 = 10\text{k}\Omega$

$$v_A = v_A(t_1) e^{-(t-t_1)/\tau_D}$$

Summary

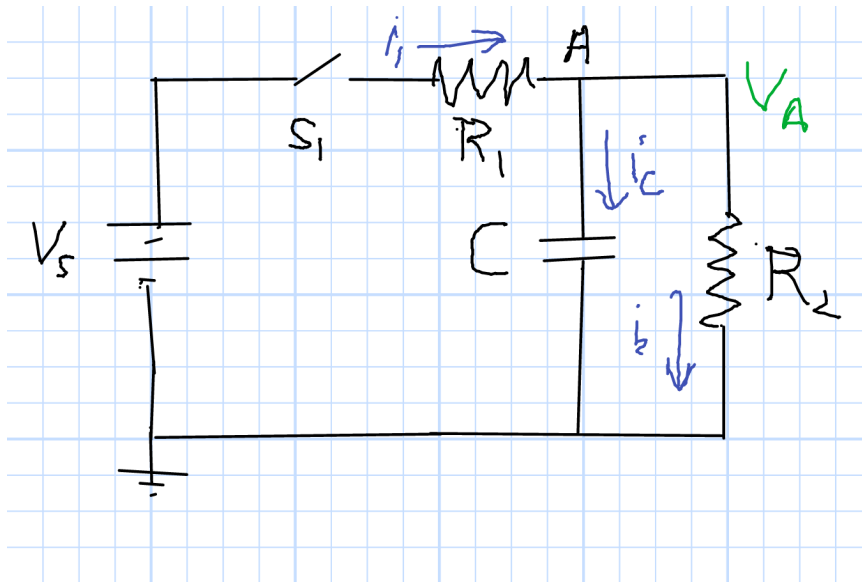

- Charge

$$v_A = v_s \frac{R_2}{R_1 + R_2} \left\{ 1 - e^{-t/\tau_C} \right\}$$

- Charging Time Constant

$$\tau_C = (R_1 \parallel R_2) C$$

- End of Actual Charge

$$v_C = v_s \frac{R_2}{R_1 + R_2} \left\{ 1 - e^{-t_1/\tau_C} \right\}$$


- Discharge

$$v_A = v_C(t_1) e^{-(t-t_1)/\tau_D}$$


- Discharge Time Constant

$$\tau_D = R_2 C$$


Charging and Discharging Voltage

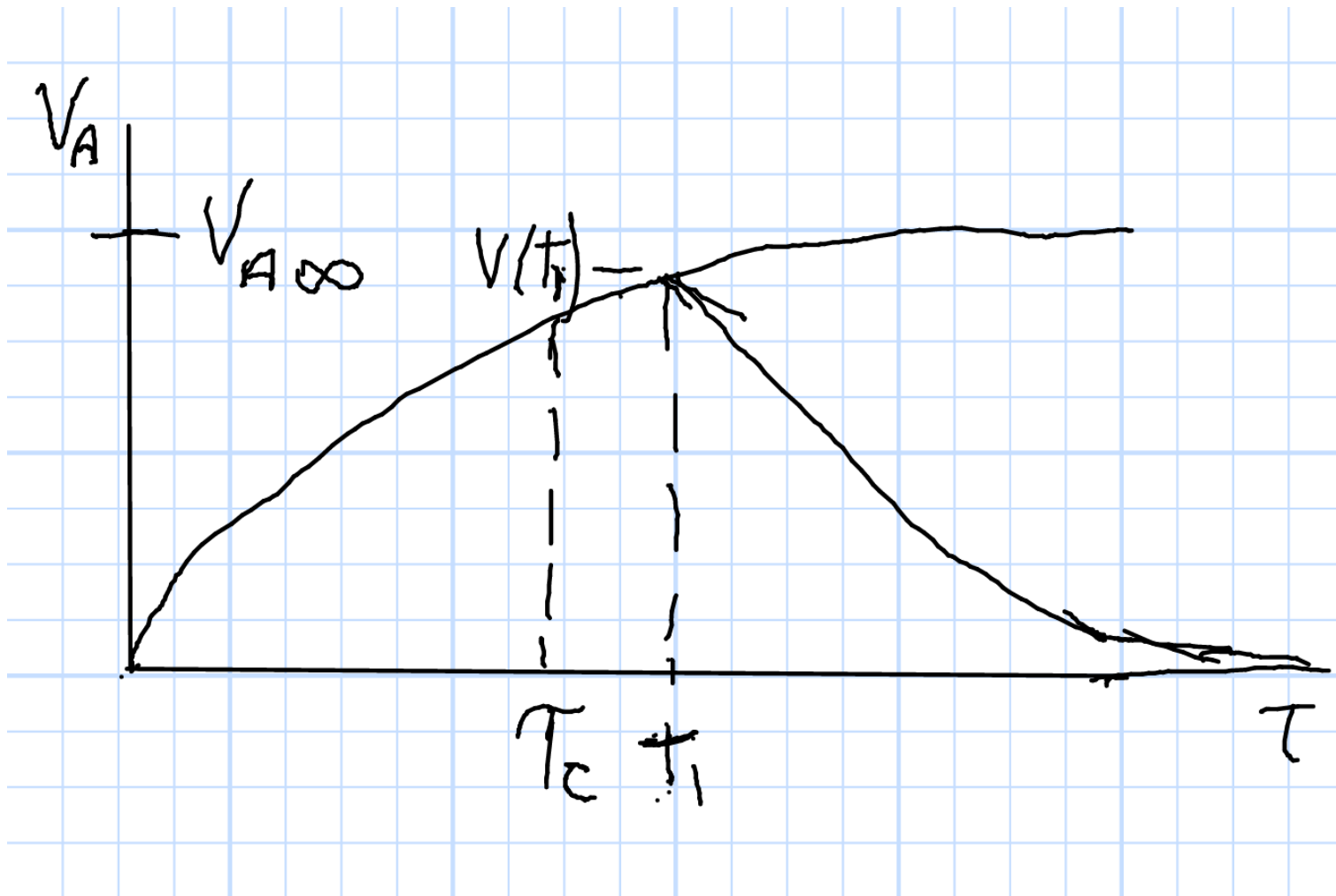

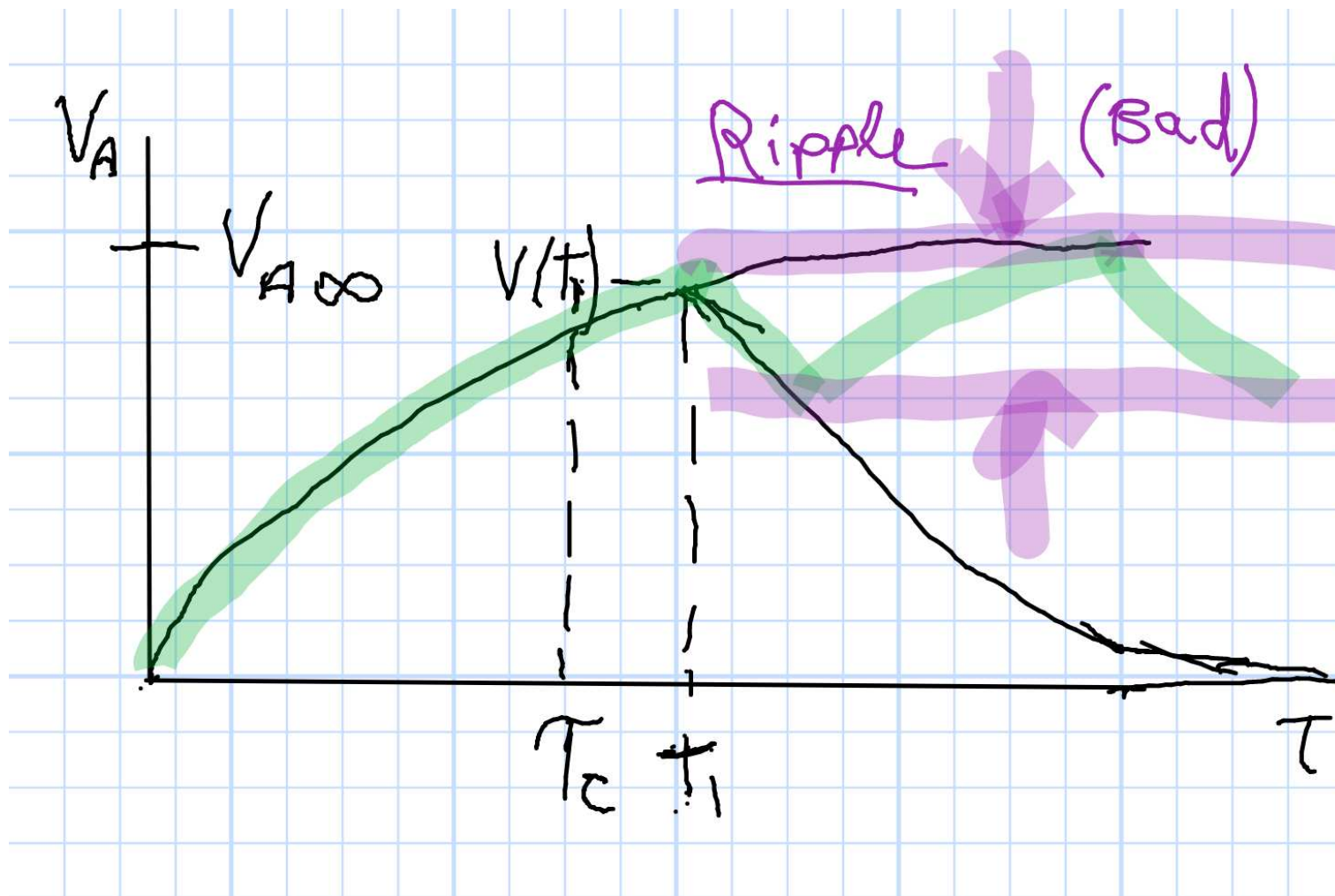Repeated Charging and Discharging Voltage




Neon Light Blinker


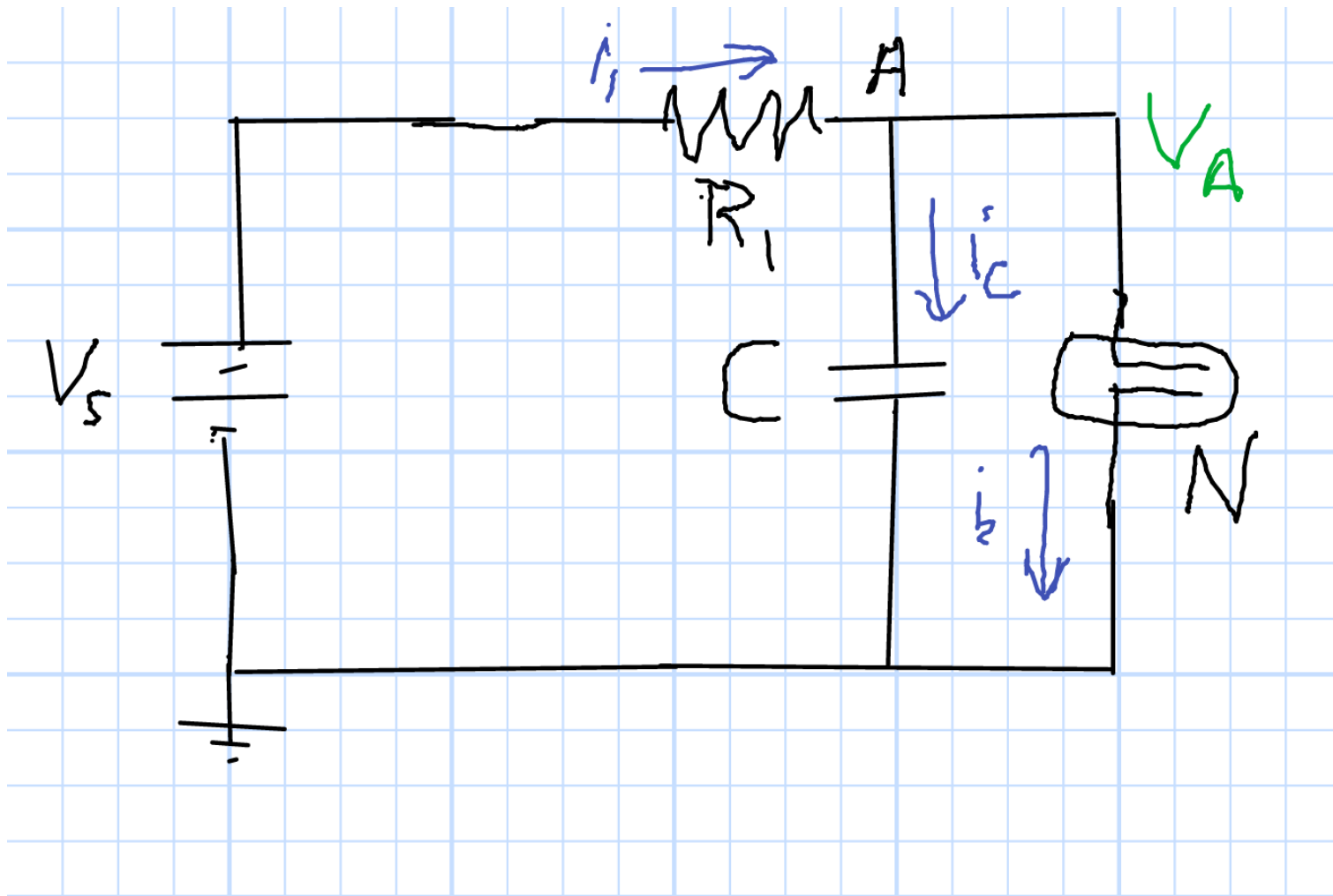


Neon Light is open for low voltage, low resistance for high voltage.
 $R = 1\text{M}\Omega$, $C = 1\mu\text{F}$, $\tau = 1\text{s}$, $v_S \approx 100\text{V}$ or more.

RL Circuit

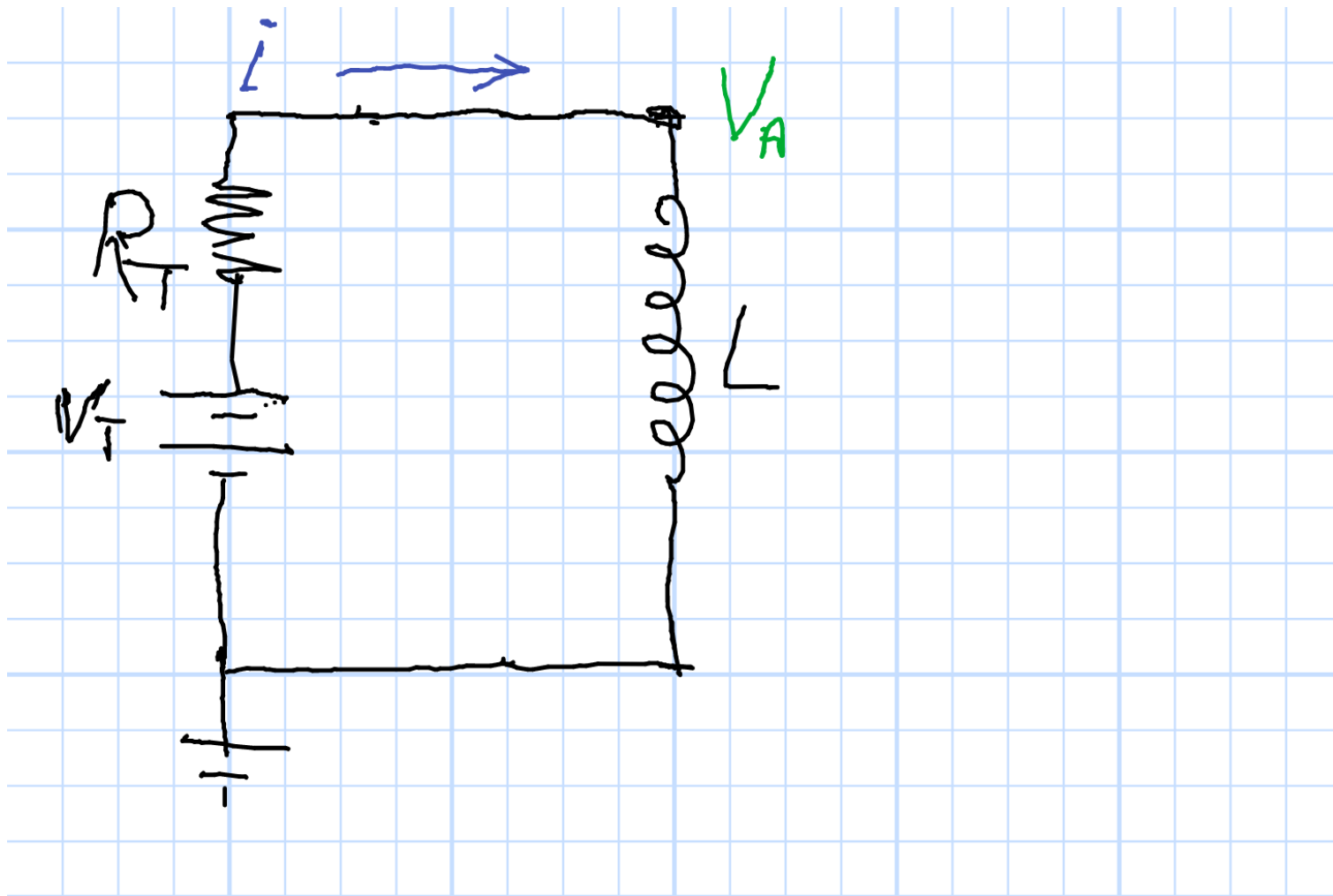


Simplified RL Circuit

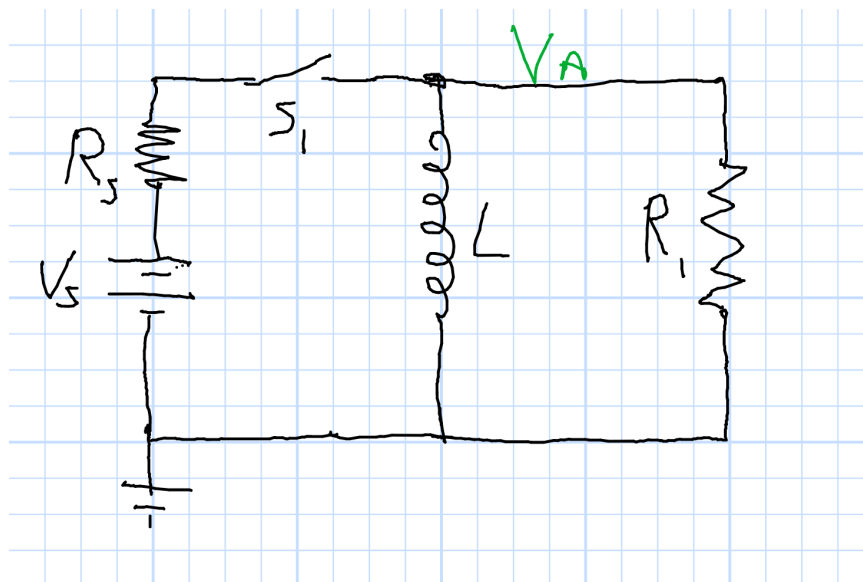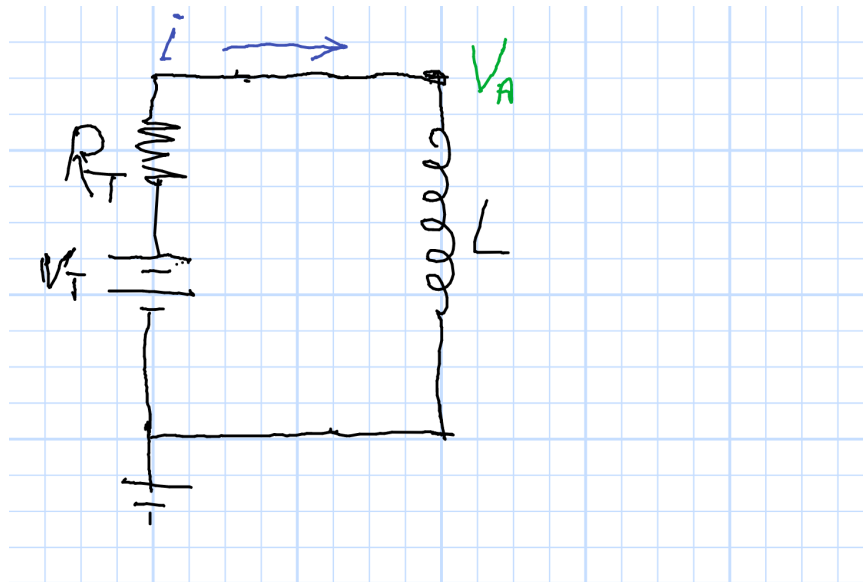

$$v_T = v_S \frac{R_1}{R_1 + R_s}$$

$$R_T = R_1 \parallel R_s$$

RL Equations

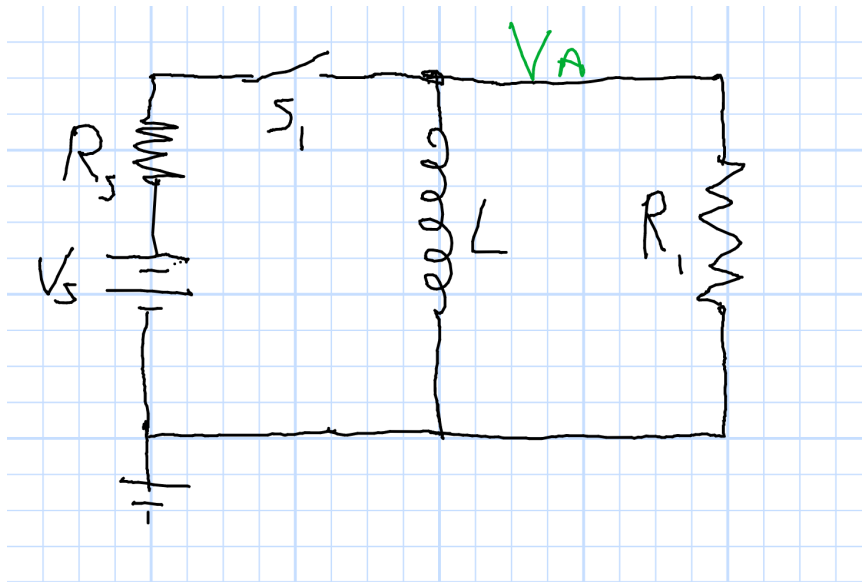

$$V_A = L \frac{di}{dt}$$

$$v_A = L \frac{d}{dt} \frac{v_T - v_A}{R_T}$$

Try

$$v_A = k_1 e^{st} + k_2$$


Solve

$$k_1 e^{st} + k_2 = -\frac{L}{R_T} \frac{dv_A}{dt} = -\frac{L}{R_T} k_1 s e^{st}$$

$$\left(1 + \frac{L}{R_T} s\right) k_1 e^{st} + k_2 = 0$$

$$s = -\frac{L}{R_T} \quad k_2 = 0$$

RL Solution

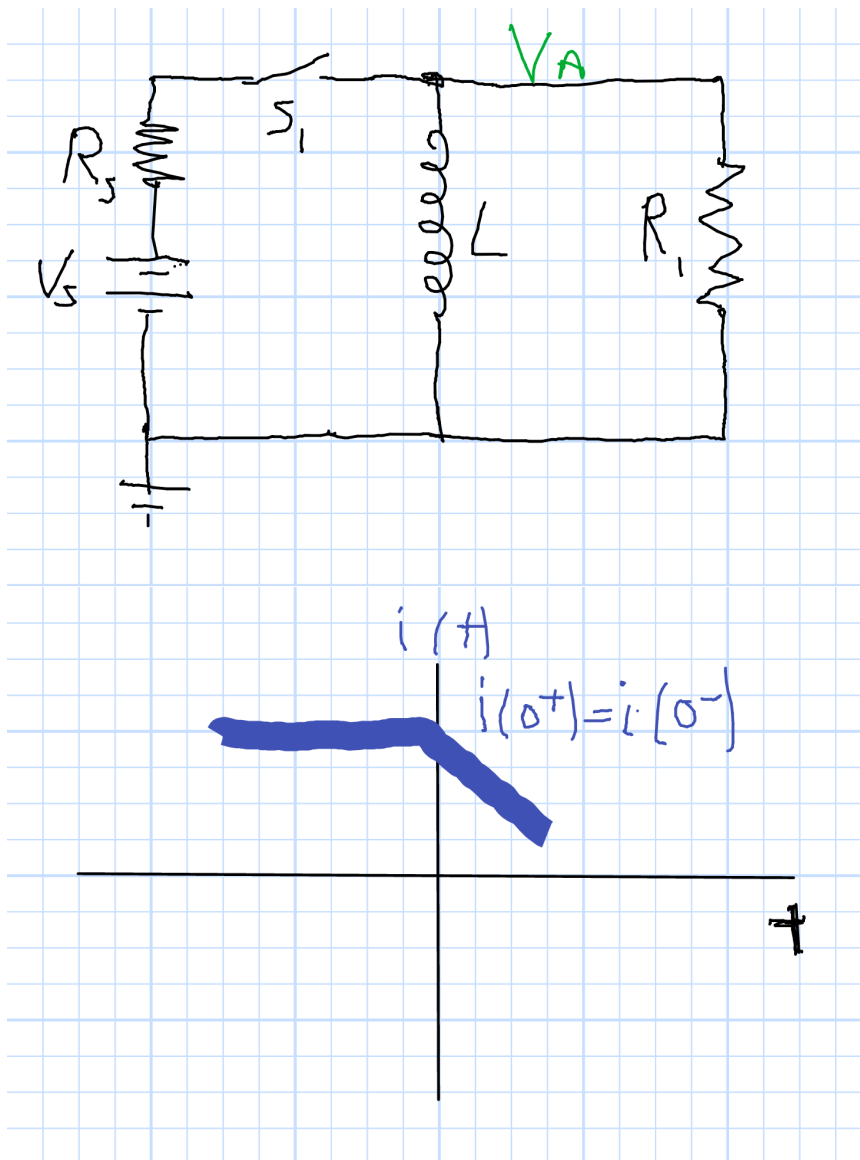

- From Previous Page

$$v_A = k_1 e^{st} + k_2$$

$$s = -\frac{L}{R_T} \quad k_2 = 0$$

- Result

$$v_A = k_1 e^{-\frac{L}{R_T}t}$$

- Boundary Condition:

$$i(0) = 0, \quad v_A(0) = v_T$$

$$v_A = v_T e^{\frac{L}{R_T}t}$$

- Time Constant

$$v_A = v_T e^{-t/\tau} \quad \tau = \frac{R_T}{L}$$

AC Coupled Amplifier

