


**Problem 3.15**

- (a) The diode is on.  $V = 0$  and  $I = (10 \text{ volts}) / (2.7 \text{ k}\Omega) = 3.70 \text{ mA}$ .
- (b) The diode is off.  $I = 0$  and  $V = 10 \text{ volts}$ .
- (c) The diode is on.  $V = 0$  and  $I = 0$ .
- (d) The diode is on.  $I = 5 \text{ mA}$  and  $V = 5 \text{ volts}$ .

**Problem 3.16**

- (a)  $D_1$  is on and  $D_2$  is off.  $V = 10 \text{ volts}$  and  $I = 0$ .
- (b)  $D_1$  is on and  $D_2$  is off.  $V = 6 \text{ volts}$  and  $I = 6 \text{ mA}$ .
- (c) Both diodes are on.  $V = 30 \text{ volts}$  and  $I = 33.6 \text{ mA}$ .

Problem 3.24

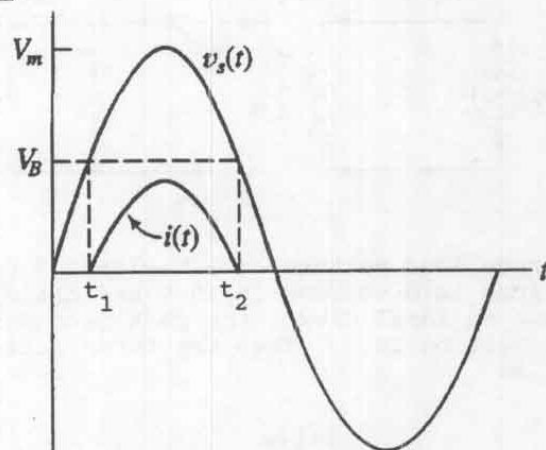

Peak current flows at the instant for which  $v_s(t)$  attains its maximum value. The maximum current is

$$I_{\max} = \frac{V_m - V_B}{R} = \frac{20 - 14}{10} = 0.6 \text{ A}$$

As a function of time, the current is

$$i(t) = \frac{V_m \sin(\omega t) - V_B}{R}$$


provided that this expression yields a positive result. Otherwise  $i(t) = 0$ . To determine the interval for which the diode is in the on state we must solve this equation:

$$i(t) = 0 = \frac{V_m \sin(\omega t) - V_B}{R} = \frac{20 \sin(\omega t) - 14}{10}$$

Solving we find two roots:  $t_1 = 0.775/\omega$  and  $t_2 = 2.37/\omega$  radian.  $t_1$  and  $t_2$  are indicated on the waveforms shown on the preceding page. The period of the sine wave is  $T = 2\pi/\omega$ . Thus the percentage of the time that the diode is on is

$$\text{diode on} = \frac{2.37/\omega - 0.775/\omega}{2\pi/\omega} \times 100\% = 25.3\%$$

Problem 3.32

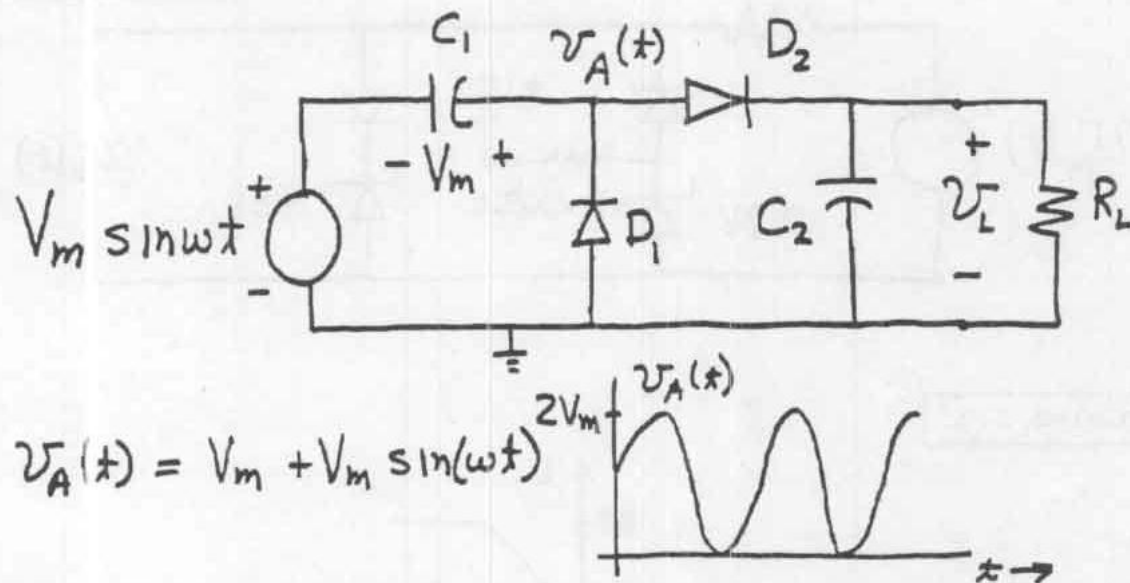

Notice that  $C_1$  and  $D_1$  form a clamp circuit. Furthermore,  $D_2$  and  $C_2$  form a peak rectifier so the load voltage is approximately equal to  $2V_m$  which is why this circuit is called a voltage doubler.