

Homework Solution Set 4  
EECE2412: Electronics – Spring 2013  
Due Thursday, 14 March 2013

Prof. Charles A. DiMarzio  
TA: Joseph Hollmann

March 20, 2013

**Problem 4.25**

Assuming that current is constant at 2 mA we have

$$\begin{aligned} V_{\text{BE}2} &= V_{\text{BE}1} + (2 \text{ mV})(T_2 - T_1) \\ &= -0.7 + 0.002(180 - 30) \\ &= -0.4 \text{ V} \end{aligned}$$

At 180° we have  $V_T = kT/q = \frac{1.38 \times 10^{-23}(273 + 180)}{1.60 \times 10^{-19}} = 39.1 \text{ mV}$ .

Now we compute the value of  $I_S$  for a temperature of 180°.

$$I_S = \frac{I_C}{\exp(V_{\text{BE}}/V_T - 1)} = \frac{2 \times 10^{-3}}{\exp(0.4/0.0391 - 1)} = 71.6 \text{ nA}$$

Finally we compute  $V_{\text{BE}}$  for a current of 0.1 mA at 180°C.

$$\begin{aligned} V_{\text{BE}} &= V_T \ln(I_C/I_S + 1) = 0.0391 \ln[10^{-4}/(71.6 \times 10^{-9} + 1)] \\ &= 0.283 \text{ V} \end{aligned}$$

**Problem 4.34**


| Circuit | $\beta$ | Region           | I (mA) | V (V)  |
|---------|---------|------------------|--------|--------|
| (a)     | 100     | active           | 2.38   | 5.25   |
| (a)     | 300     | saturation       | 4.45   | 9.80   |
| (b)     | 100     | cutoff           | 0      | 10     |
| (b)     | 300     | cutoff           | 0      | 10     |
| (c)     | 100     | active           | 4.26   | -10.74 |
| (c)     | 300     | active           | 4.29   | -10.71 |
| (d)     | 100     | $Q_1$ active     | 10     | 10     |
|         |         | $Q_2$ active     |        |        |
| (d)     | 300     | $Q_1$ active     | 14.8   | 14.8   |
|         |         | $Q_2$ saturation |        |        |

Problem 4.45

Dc circuit:

$$\beta = 100$$

$$V_{BEQ} = 0.7 \text{ V}$$

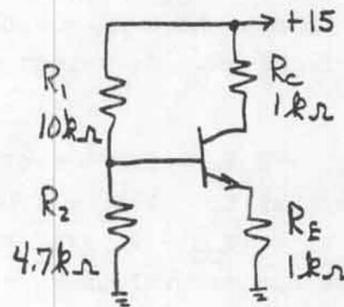

$$V_B = V_{CC} R_2 / (R_1 + R_2) = 4.80 \text{ V} \quad R_B = R_1 || R_2 = 3.20 \text{ k}\Omega$$

$$I_{BQ} = \frac{V_B - V_{BEQ}}{R_B + (\beta + 1)R_E} = 0.0393 \text{ mA} \quad I_{CQ} = \beta I_B = 3.93 \text{ mA}$$


$$r_{\pi} = \beta V_T / I_{CQ} = 662 \text{ }\Omega \quad R'_L = R_L || R_C = 500 \text{ }\Omega$$

$$A_v = -\beta R'_L / r_{\pi} = -75.5 \quad A_{vO} = -\beta R_L / r_{\pi} = -151$$

$$Z_{in} = R_1 || R_2 || r_{\pi} = 548 \text{ }\Omega \quad A_i = A_v Z_{in} / R_L = -41.4$$

$$G = A_v A_i = 3124 \quad Z_o = R_C = 1 \text{ k}\Omega$$

Problem 4.56

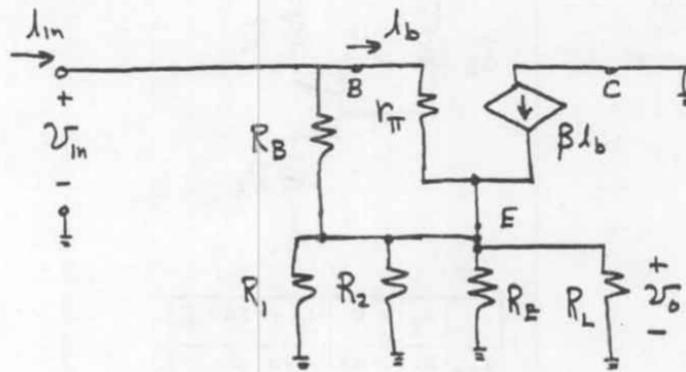

Let  $R'_L = R_1 || R_2 || R_E || R_L$


$$v_o = R'_L \left( i_b + \beta i_b + \frac{r_\pi i_b}{R_B} \right) \quad v_{in} = r_\pi i_b + v_o$$

$$A_v = \frac{v_o}{v_{in}} = \frac{R'_L \left( 1 + \beta + \frac{r_\pi}{R_B} \right)}{r_\pi + R'_L \left( 1 + \beta + \frac{r_\pi}{R_B} \right)}$$

$$i_{in} = \frac{v_{in} - v_o}{R_B || r_\pi} = \frac{v_{in} - A_v v_{in}}{R_B || r_\pi} \quad z_{in} = \frac{v_{in}}{i_{in}} = \frac{R_B || r_\pi}{1 - A_v}$$


Problem 4.59

(a)

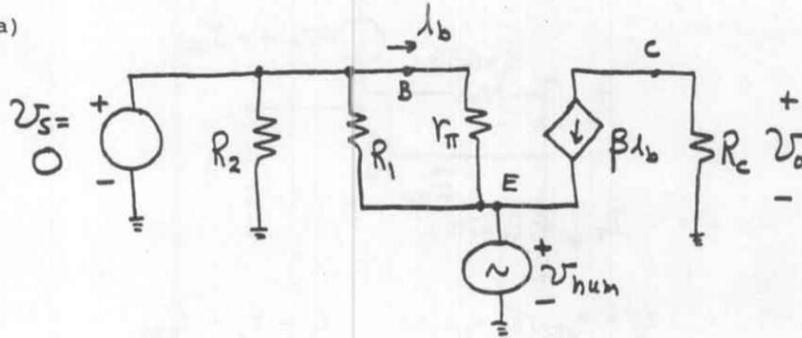

$$A_{\text{hum}} = \frac{v_o}{v_{\text{hum}}} = \frac{-\beta i_b R_C}{-r_{\pi} i_b} = \frac{\beta R_C}{r_{\pi}}$$

(b)

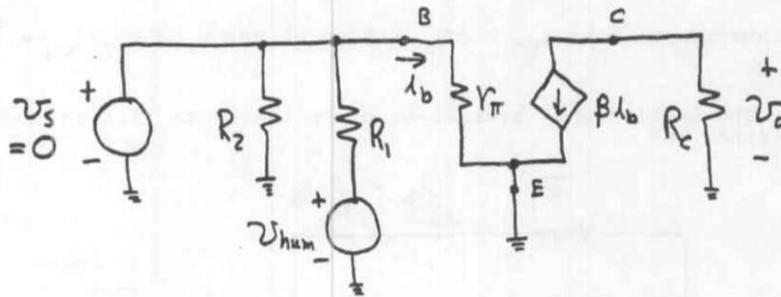

Because  $v_s = 0$  we have  $i_b = 0$  and  $v_o = 0$ . Thus  $A_{\text{hum}} = 0$ .

Because of lower sensitivity to power-supply hum, the circuit of Figure P4.59b is preferable to that of Figure P4.59a. In other words, the emitter bypass capacitor should be connected from emitter to ground.

## 6 Audio Amplifier Design

The purpose of this assignment was to get you to apply the various principals you have learned throughout your undergraduate career to create an audio amplifier.

### 6.1 Initial Analysis

#### 6.1.1 Number of Stages

There are three stages in this amplifier circuit. Please refer to Figure 1 to see each stage.

#### 6.1.2 Types of Stages

Stage 1 and 2 are common emitters and the stage 3 is in a push-pull configuration. The third stage is utilized to deliver a lot of power to the speaker relatively efficiently. The common emitter amplifiers are known as "Class-A" amplifiers and the push-pull is known as a "Class AB" amp.

#### 6.1.3 Voltage at Q1's base

$\approx 0.7$  V

### 6.2 Desired Input and Output Impedance

To obtain the maximum power transfer with minimum distortion, we must match impedances into and out of the circuit. Therefore, the input should be  $\approx 300$  Ohms and the output impedance should be  $\approx 8$  Ohms.

### 6.3 Purpose of $D_1$ and $D_2$

They serve to bias the circuit. This accounts for the drop across base-to-emitter for both  $Q_3$  and  $Q_4$ .

### 6.4 Purpose of $C_1$

Both  $C_1$  and  $C_3$  serve as decoupling capacitors. They remove the DC component of the previous stage so it does not contribute to the DC bias of the

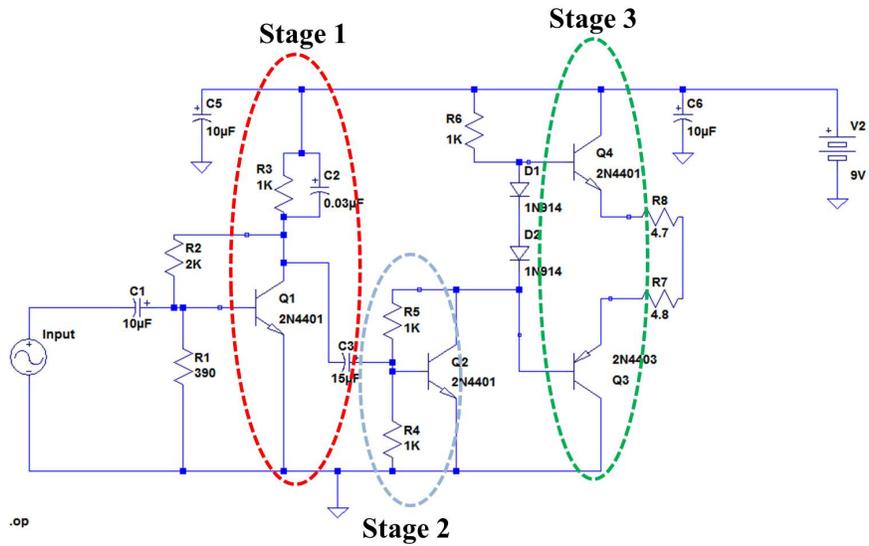


Figure 1: Amplifier Stages

current stage. It is important to note that  $C_2$  does not do this. **note:** → I erroneously referred to  $C_5$  and  $C_6$  as decoupling capacitors in the homework. ←

#### 6.4.1 Purpose of $C_5$ and $C_6$

The capacitors reduce the effect of power supply noise. On a schematic, we assume a 0 Ohm connection between points. However, in a real implementation of a circuit, this is not true. This means a connection between two points might experience a voltage drop across the connection if there is a sudden influx of current. These capacitors help "smooth out" the effects of this resistivity.

## 6.5 DC analysis

Design limitations (in order of importance)

$$1. V_{be} = 0.7V = \frac{R_2}{R_1 + R_2} V_{out}$$

$$2. R_{in} = 300\Omega = \frac{R_2 R_1}{R_1 + R_2}$$


$$3. V_{out} = 4.5V \text{ (allow for maximum voltage)}$$

I chose the following easy-to-obtain resistors


$$R_1 = 390\Omega$$

$$R_2 = 2k\Omega$$

## DC Analysis:

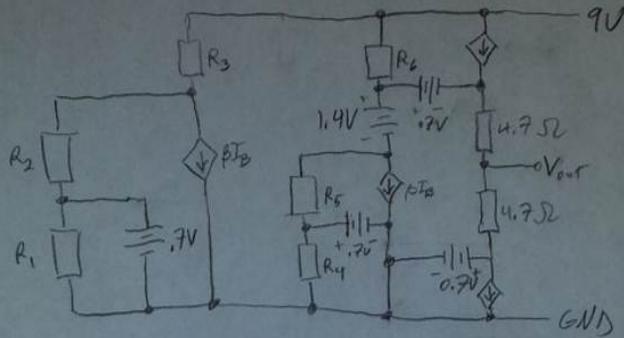

## AC Analysis:

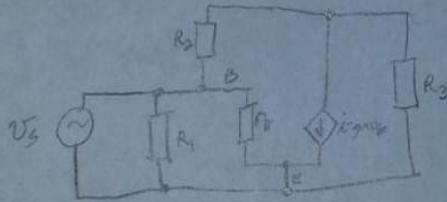

1<sup>st</sup> stage

$$R_T = R_3 \parallel (R_2 + R_1 \parallel R_{\pi})$$

$$i = -g_m v_{be}$$


$$G_v = -R_T \cdot g_m$$

2<sup>nd</sup> stage


$$R_T = R_5 + (R_{\pi} \parallel R_4)$$

$$i = -g_m v_{be}$$

$$G_v = -R_T \cdot g_m$$

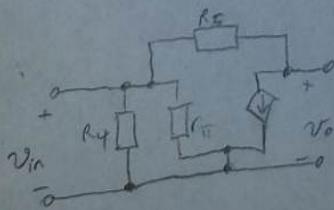

3<sup>rd</sup> stage

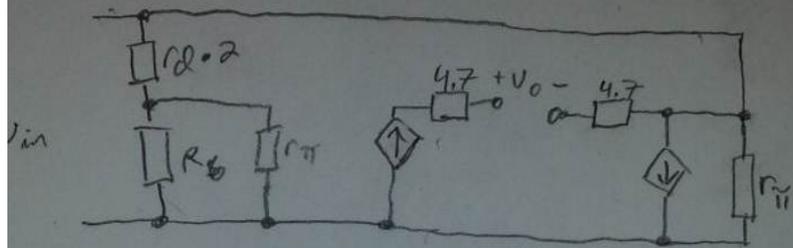

$$R_T = [2.2 + (R_b \parallel r_{\pi})] \parallel r_L$$

with no load,

$$V_{out} = -g_m v_{be} \cdot r_{\pi}$$

Assume an  $8 \Omega$  load

$$V_{out} \approx g_m v_{be} (2 \cdot 4.7 + 8)$$

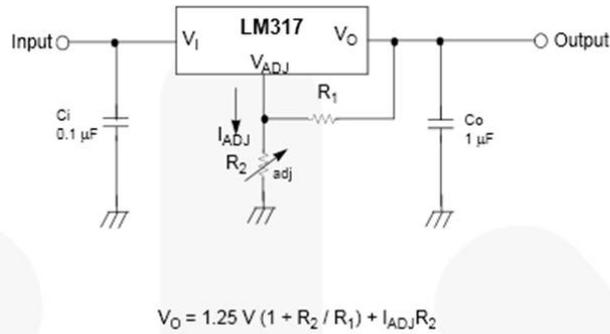


Figure 2: Example implementation from Fairchild spec sheet.

## 7 Extra Credit

One example implementation of the LM317 is shown in Figure 2 (As described in the Fairchild spec sheet). Note, this chip is produced by many different manufacturers and some included a diode between the output and input of the chip to protect against reverse biasing the chip. It is important to note that this is only required in a situation where multiple voltages are used in a circuit. If this is the case, it still may not be advisable to use the diode for battery-powered electronics.