

BJT Amplifiers

Chuck DiMarzio, Northeastern University

15 November 2010 — 11401.tex, Revision 3

1 AC Parameters

Transconductance: $g_m = \frac{I_C^{(DC)}}{V_T}$, tens of mA/V typical.

Pi resistance: $r_\pi = \beta \frac{V_T}{I_C^{(DC)}}$. few $k\Omega$ typical.

Emitter Resistance: $r_e = \frac{r_\pi}{\beta+1}$, tens of Ω typical.

Early-Voltage resistance: $r_0 = \frac{V_A}{I_C^{(DC)}}$. tens to hundreds of $k\Omega$ typical.

2 Amplifier Characteristics

Voltage gain: $A_V = \frac{v_{out}^{(ac)}}{v_{in}^{(ac)}}$.

Input impedance: $R_{in} = \frac{v_{in}^{(ac)}}{i_{in}^{(ac)}}$.

Output impedance: $R_{out} = \frac{v_{out}^{(ac)}}{i_{out}^{(ac)}}$.


Open-circuit Voltage gain: $A_{Vo} = A_V$ with $R_L/R_{out} \rightarrow \infty$.

Voltage gain relative to source measured in open-circuit conditions:

$$A_{Vs} = A_V \frac{R_{in}}{R_s + R_{in}}$$

.

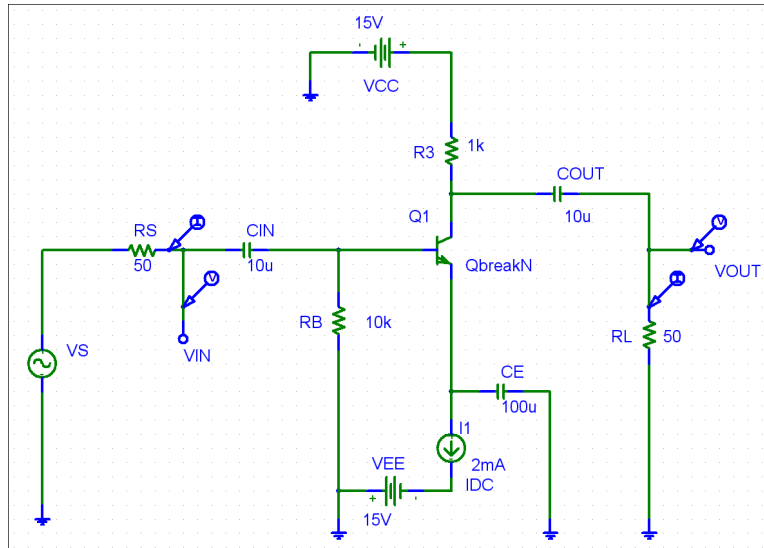Current gain: $A_i = \frac{i_{out}^{(ac)}}{i_{in}^{(ac)}}$.



Common Emitter Amplifier

$$R_{in} = R_B \parallel r_{\pi}$$


$$R_{out} = R_C \quad (R_C = R_3 \text{ in Figure})$$

$$A_V = -g_m (r_o \parallel R_C \parallel R_L)$$

$$A_{Vo} = -g_m (r_o \parallel R_C)$$

$$A_{Vs} = A_V \frac{R_B \parallel r_{\pi}}{R_B \parallel r_{\pi} + R_s}$$

$$A_i = \frac{R_{in}}{R_L} A_V$$

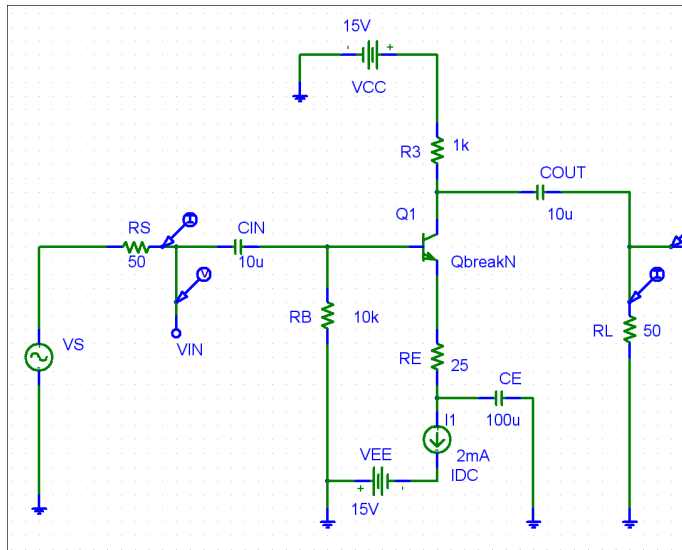

Common Emitter Amplifier with R_E

$$R_{in} = R_B \parallel [r_{\pi} + (\beta + 1) R_E]$$


$$R_{out} = r_o \parallel R_C$$

$$A_V = -\alpha \frac{R_C \parallel R_L}{r_e + R_E} \quad \text{where } r_e = \frac{r_{\pi}}{\beta + 1}$$

$$A_{Vo} = -\alpha \frac{R_C}{r_e + R_E}$$

$$A_{Vs} = -\frac{\beta (R_C \parallel R_L)}{r_{\pi} + (\beta + 1) R_E R_s}$$

$$A_i = \frac{R_{in}}{R_L} A_V$$

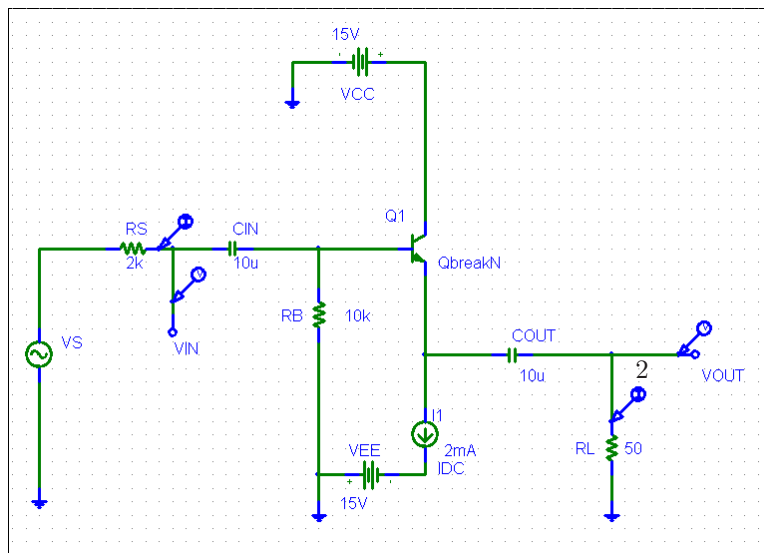

Common Collector Amplifier

$$R_{in} = R_B \parallel [r_{\pi} + (\beta + 1) (r_o \parallel R_L)]$$

$$R_{out} = r_o \parallel \left(r_e + \frac{R_s \parallel R_B}{\beta + 1} \right)$$

$$A_V = \frac{r_o \parallel R_L}{r_o \parallel R_L + r_e}$$


$$A_{Vo} = \frac{r_o}{r_o + r_e} \approx 1$$

$$A_{Vs} = \frac{R_b}{R_B + R_s} \frac{r_o \parallel R_L}{\frac{R_s \parallel R_B}{\beta + 1} + r_e + (r_o \parallel R_L)}$$


$$A_i = \frac{R_{in}}{R_L} A_V$$

3 Applications

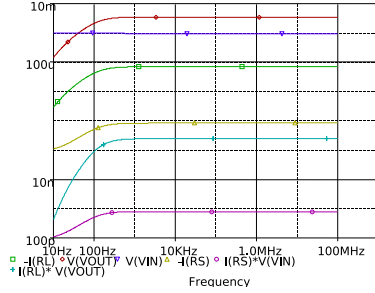
Common Emitter Amplifier For Voltage Gain



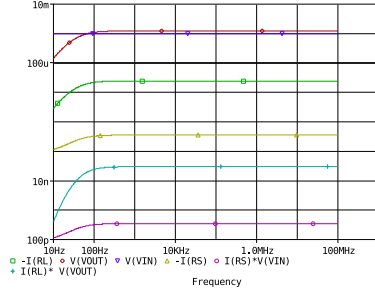Common Emitter Amplifier with R_E Lower Gain, Higher R_{in}



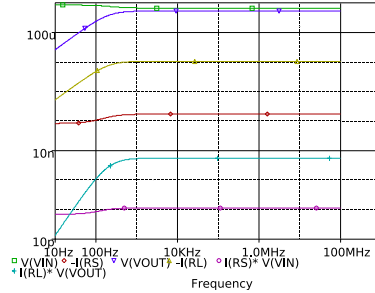Common Collector Amplifier for Voltage Buffer



Common Base Amplifier for Current Buffer (Not shown)

$$R_{in} = R_B \parallel r_\pi$$

Want large 1.5k typical

$$R_{out} = R_C$$

Want small 10k typical

$$A_V = -g_m (r_o \parallel R_C \parallel R_L)$$

Want large 100s typical

$$A_{Vo} = -g_m (r_o \parallel R_C)$$

Want large 10's to 100's typical

$$A_{Vs} = A_V \frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_s}$$

$$A_i = \frac{R_{in}}{R_L} A_V$$

$$R_{in} = R_B \parallel [r_\pi + (\beta + 1) R_E]$$

Want very large 100's k typical

$$R_{out} = r_o \parallel R_C \parallel r_o$$

Want small 10k typical

$$A_V = -\alpha \frac{R_C \parallel R_L}{r_e + R_E} \text{ where } r_e = \frac{r_\pi}{\beta + 1}$$

Few to 10s Typical

$$A_{Vo} = -\alpha \frac{R_C}{r_e + R_E}$$

$$A_{Vs} = -\frac{\beta (R_C \parallel R_L)}{r_\pi + (\beta + 1) R_E R_s}$$

$$A_i = \frac{R_{in}}{R_L} A_V$$

$$R_{in} = R_B \parallel [r_\pi + (\beta + 1) (r_o \parallel R_L)]$$

Want large $(\beta + 1) R_L$ typical

$$R_{out} = r_o \parallel \left(r_e + \frac{R_s \parallel R_B}{\beta + 1} \right)$$

Want small $R_s/(\beta + 1)$ typical

$$A_V = \frac{r_o \parallel R_L}{r_o \parallel R_L + r_e}$$

Want Unit Gain

$$A_{Vo} = \frac{r_o}{r_o + r_e}$$

$$A_{Vs} = \frac{R_b}{R_B + R_s} \frac{r_o \parallel R_L}{\frac{R_s \parallel R_B}{\beta + 1} + r_e + (r_o \parallel R_L)}$$

$$A_i = \frac{R_{in}}{R_L} A_V$$

$$R_{in} = \frac{1}{g_m} \frac{\beta}{\beta + 1}$$

Want small 25Ω typical

$$R_{out} = R_C$$

Want large kΩ typical

$$A_V = \frac{\beta}{\beta + 1} \frac{R_C \parallel R_L}{R_s + \frac{1}{g_m}}$$

$$A_{Vo} = -g_m (r_o \parallel R_C)$$

$$A_{Vs} = \frac{R_b}{R_B + R_s} \frac{r_o \parallel R_L}{\frac{R_s \parallel R_B}{\beta + 1} + r_e + (r_o \parallel R_L)}$$

$$A_i = \frac{\beta}{\beta + 1} \frac{R_C}{R_C + R_L}$$

Want Unit Gain