

Electronics
EECE2412 — Fall 2009
Final Exam **with Solutions**

Prof. Charles A. DiMarzio
Department of Electrical and Computer Engineering
Northeastern University

Doc:11419

16 December 2009

1 BJT Amplifier

A BJT circuit is shown in Figure 1.1. The capacitor is large enough to be considered a short circuit in the AC model.

1.1 Transistor Pi Model

What is the value of the resistor in the Pi model, r_π ? Write the equation and evaluate.

$$r_\pi = \beta \frac{V_T}{I_C^{(DC)}} = (\beta + 1) \frac{V_T}{I_E^{(DC)}}$$
$$r_\pi = (160 + 1) \frac{25 \times 10^{-3} V}{1 \times 10^{-3} A}$$

ANSWER: 4025Ω.

r_π	4025Ω.
---------	---------------

1

1.2 Early Effect

Compute r_0 , the resistor associated with the Early Effect.

$$r_0 = \frac{V_A}{I_C^{(DC)}} \approx \frac{V_A}{I_e^{(DC)}} = \frac{V_A}{I_C^{(DC)}} = 125 \text{ k}\Omega \quad (1.1)$$

r_0	125 kΩ
-------	---------------

 


Figure 1.1: BJT circuit for Amplifier in Problem 1. The DC current is set at $I_E^{(DC)} = 1\text{mA}$, the transistor has a gain of $\beta = 160$, and $R_1 = 4\text{k}\Omega$. The Early Voltage is 125V .

1.3 Transconductance

Compute g_m , the transconductance.

$$g_m = \frac{I_C^{(DC)}}{V_T} = \frac{1\text{mA}}{25\text{mV}} = 0.04\text{A/V} \quad (1.2)$$

g_m	0.04 A/V
-------	-------------------

1.4 AC Circuit

Draw the AC circuit using a Pi model for the transistor.

See Figure 1.2.

 


Figure 1.2: BJT Pi Model for Problem 1.

1.5 Voltage Gain

Write an equation for the voltage gain of the amplifier.

$$A_V = -g_m (r_o \parallel R_1 \parallel R_L). \quad (1.3)$$

1.6 Application

What is the open-circuit gain? What is the gain with a load matched to the output resistance?

$$A_{Voc} = -g_m (r_o \parallel R_1) = -155. \quad (1.4)$$

With a matched load, it is half that, or

$$A_V = -g_m (r_o \parallel R_1 \parallel R_1) \approx -78. \quad (1.5)$$

A_{Voc}	-155
$A_{vMatched}$	-78

2 FET Amplifier

Consider the circuit in Figure 2.1. Here the transistor has the characteristics shown in Figure 2.2.

 


Figure 2.1: N-MOSFET Amplifier.

2.1 Bias

Find the bias point graphically, so that $I_D^{(DC)} = 4 \text{ mA}$. What is the Drain-Source voltage?

$$V_{GS} = 5V \quad (2.1)$$

From the voltage divider.

Therefore,

from the curves,

$$V_{DS}^{(DC)} = 2 \text{ V}. \quad (2.2)$$

$V_{DS}^{(DC)}$	2 V
-----------------	-----

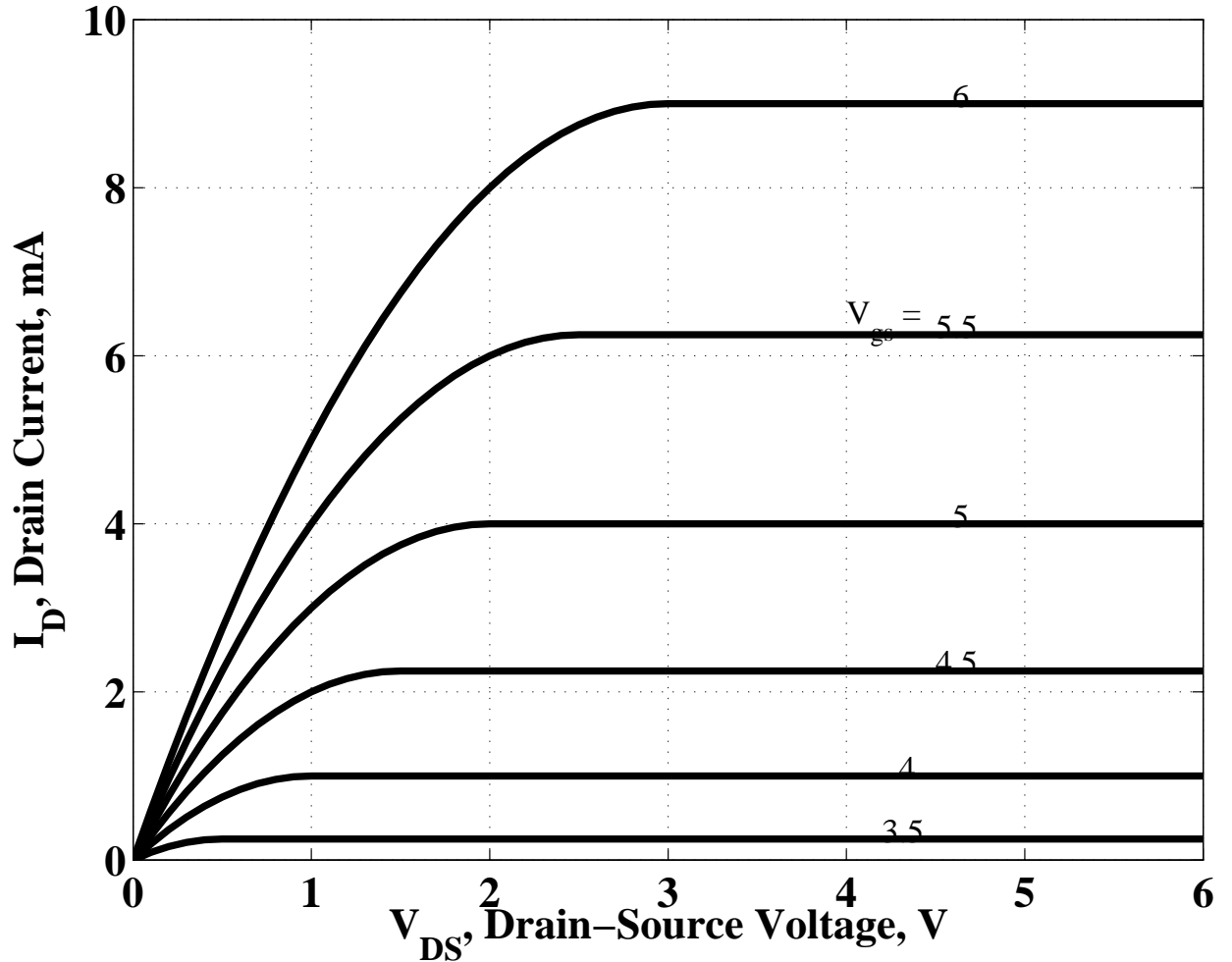


Figure 2.2: Curves for Transistors in the FET Amplifier. The output is at the connection between the drain and R3.

2.2 Transconductance

Compute the transconductance.

$$g_m = \frac{2I_D^{(DC)}}{V_{GS}^{(DC)} - V_{Thr}} \quad (2.3)$$

We need V_{thr} , which, from the curves must be 3 Volts.

$$g_m = \frac{2 \times 4 \text{ mA}}{5V - 3V} = 4 \times 10^{-3} \text{ A/V} \quad (2.4)$$

g_m	$4 \times 10^{-3} \text{ A/V}$
-------	--------------------------------

2.3 AC Circuit

Draw the AC circuit, using a Pi model for the transistor.

Usual with just the resistor R_3 .

2.4 Open-Circuit Voltage Gain

Compute the open-circuit voltage gain.

$$A_{Voc} = -g_m R_3 = 4 \times 10^{-3} \text{ A/V} \times 10^3 \Omega = -4 \quad (2.5)$$

A_{Voc}	-4
-----------	------

3 2-Stage Amplifier

Consider the circuit in Figure 3.1.

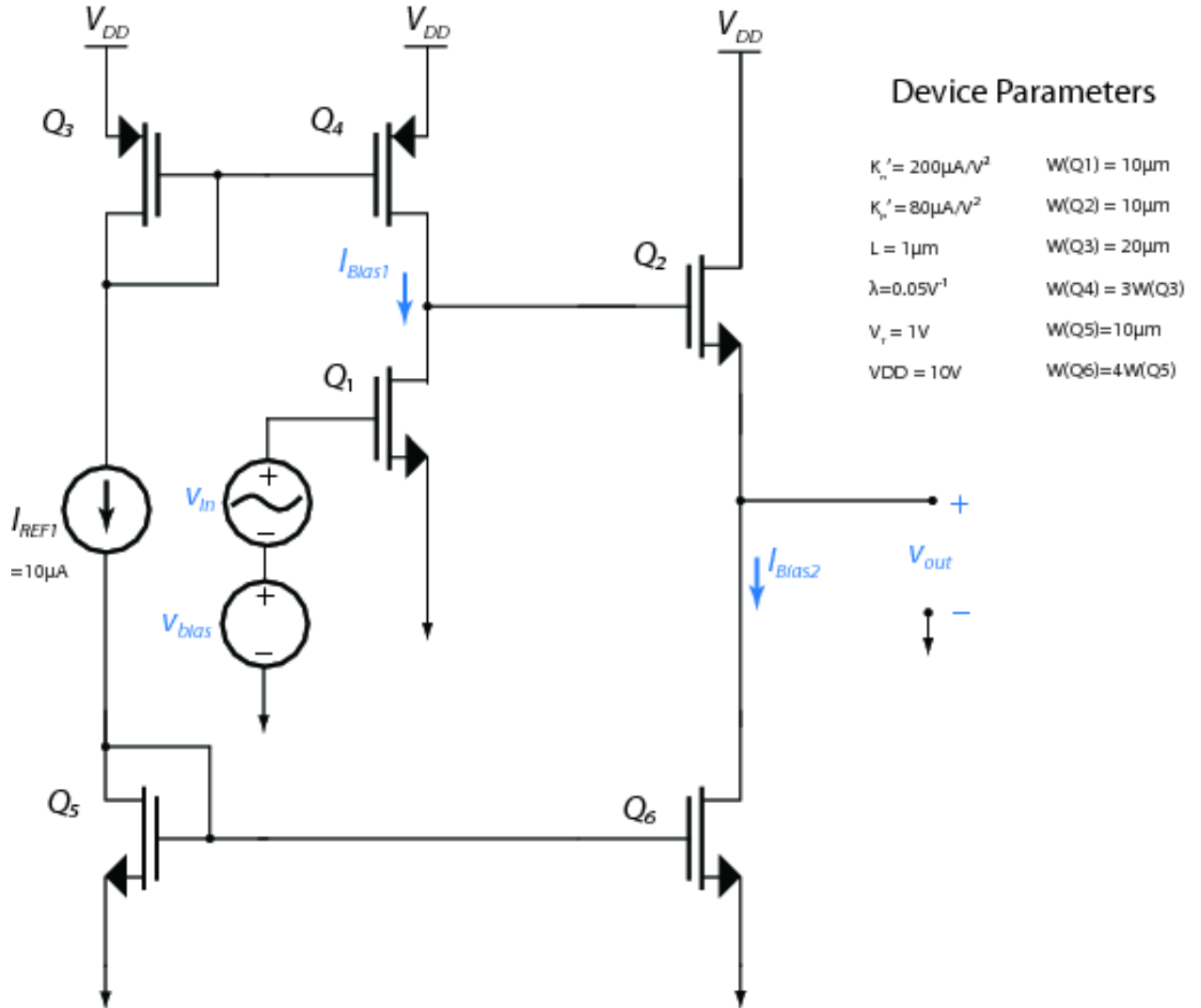


Figure 3.1: Two-Stage FET Amplifier. The device parameters (also shown in the upper right of the figure), are $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ for the n-channel devices, $\mu_p C_{ox} = 80 \mu\text{A}/\text{V}^2$ for the p-channel devices, $L = 1 \mu\text{m}$ for all, $\lambda = 0.05 \text{V}^{-1}$ for all, $V_{thr} = 1 \text{V}$ for all, $W(Q1) = 10 \mu\text{m}$, $W(Q2) = 10 \mu\text{m}$, $W(Q3) = 20 \mu\text{m}$, $W(Q4) = 3W(Q3)$, $W(Q5) = 10 \mu\text{m}$, $W(Q6) = 4W(Q5)$, and $V_{DD} = 10 \text{V}$.

3.1 Bias Currents

For parts 3.1 and 3.2, neglect channel length modulation ($\lambda = 0$ or $V_A \rightarrow \infty$)

Find the bias currents I_{bias1} and I_{bias2} and verify that Q1 and Q2 are in saturation.

$$I_{bias1} = 3I_{ref} = 30 \mu\text{A} \quad (3.1)$$

$$I_{bias2} = 4I_{ref} = 40 \mu\text{A} \quad (3.2)$$

I _{bias1}	30 μ A
I _{bias2}	40 μ A

3.2 Bias Voltage

For parts 3.1 and 3.2, neglect channel length modulation ($\lambda = 0$ or $V_A \rightarrow \infty$)

Determine the bias voltage (VBias) on Q1.

$$I_d = \mu_n C_{ox} \frac{W}{L} \frac{(V_{gs} - V_{thr})^2}{2} \quad (3.3)$$

Solve for V_{gs}

$$V_{gs} = \sqrt{2I_{bias1} \frac{L}{\mu_n C_{ox} W}} + V_t =$$

$$\sqrt{2 \times 30 \times 10^{-6} \text{ A} \frac{1 \mu\text{m}}{10 \mu\text{m} \times 200 \times 10^{-6} \text{ A/V}^2}} + 1 \text{ V} \quad (3.4)$$

V _{bias}	1.17 V
-------------------	--------

3.3 Small-Signal Parameters

Find g_{m1} , g_{m2} , r_{o1} , r_{o2} and draw the small signal model for the two-stage amplifier. Don't forget the "Early" resistances of the current source transistors!

We use two different expressions for the transconductance, because it is hard to find V_{GS} for the second amplifier. For the first one,

$$g_{m1} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{thr}) \quad (3.5)$$

and for the second

$$g_{m2} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}. \quad (3.6)$$

$$r_0 = \frac{1}{\lambda I_D} \quad (3.7)$$

g_{m1}	346 $\mu\text{A}/\text{V}$
g_{m2}	400 $\mu\text{A}/\text{V}$
r_{o1}	667 $\text{k}\Omega$
r_{o2}	500 $\text{k}\Omega$

The small-signal circuit is shown in Figure 3.2. The two additional resistors (associated with the current sources, Q4 and Q6) are calculated from

$$r_0 = \frac{1}{\lambda I_D} \quad (3.8)$$

and are thus the same as those of the corresponding amplifier transistors.

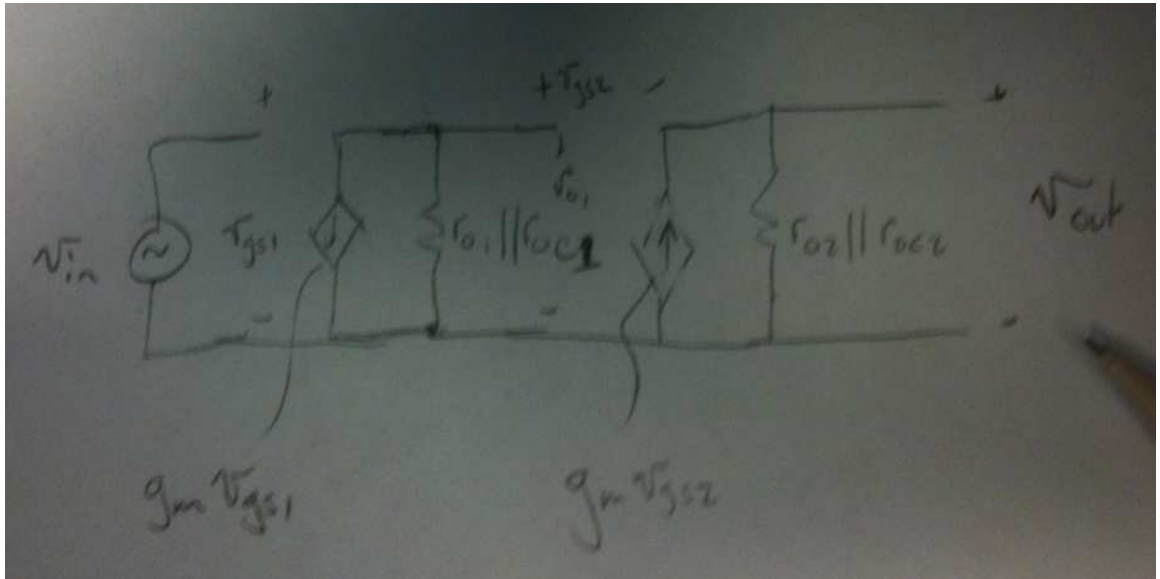


Figure 3.2: Small-Signal Model for Two-Stage Amplifier

3.4 Performance

Find A_{Voc1} , A_{Voc2} , and the total voltage gain of the amplifier.

$$A_{voc1} = -g_{m1} (r_{01} \parallel r_{01}) = -g_{m1} \frac{r_{01}}{2} \quad (3.9)$$

$$V_{in2} = V_{GS2} + V_{out} \quad (3.10)$$

$$V_{out} = g_{m2} V_{GS2} (r_{02} \parallel r_{02}) \quad (3.11)$$

$$A_{Voc2} = \frac{g_m}{g_m + \frac{2}{r_{02}}} \quad (3.12)$$

A_{Voc1}	-1.3×10^6
A_{Voc2}	≈ 1

3.5 Analysis

What do you notice about the gain of the second stage (The common-drain stage)? Why is it beneficial in this circumstance?

The output stage is a common-drain amplifier. As we discussed in class, the gain is near unity, and the purpose of using it is the low output impedance. Specifically

$$R_{out} = \frac{1}{g_{m2} + \frac{2}{r_{02}}} \approx g_{m2} \quad (3.13)$$

4 FET Logic

Consider the logic inverter shown in Figure 4.1, with the parameters shown in the caption.

4.1 Triode Equation

Write equations for i_D for the P-FET in triode operation, as a function of the supply voltage, V_1 , the input voltage, V_2 , and the output voltage, V_{out} at the location of the voltage marker in the figure.

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{SG} - V_{Thr}) V_{SD} - \frac{1}{2} V_{SD}^2 \right] \quad (4.1)$$

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[(V_1 - V_2) (V_1 - V_{out}) - \frac{1}{2} (V_1 - V_{out})^2 \right] \quad (4.2)$$

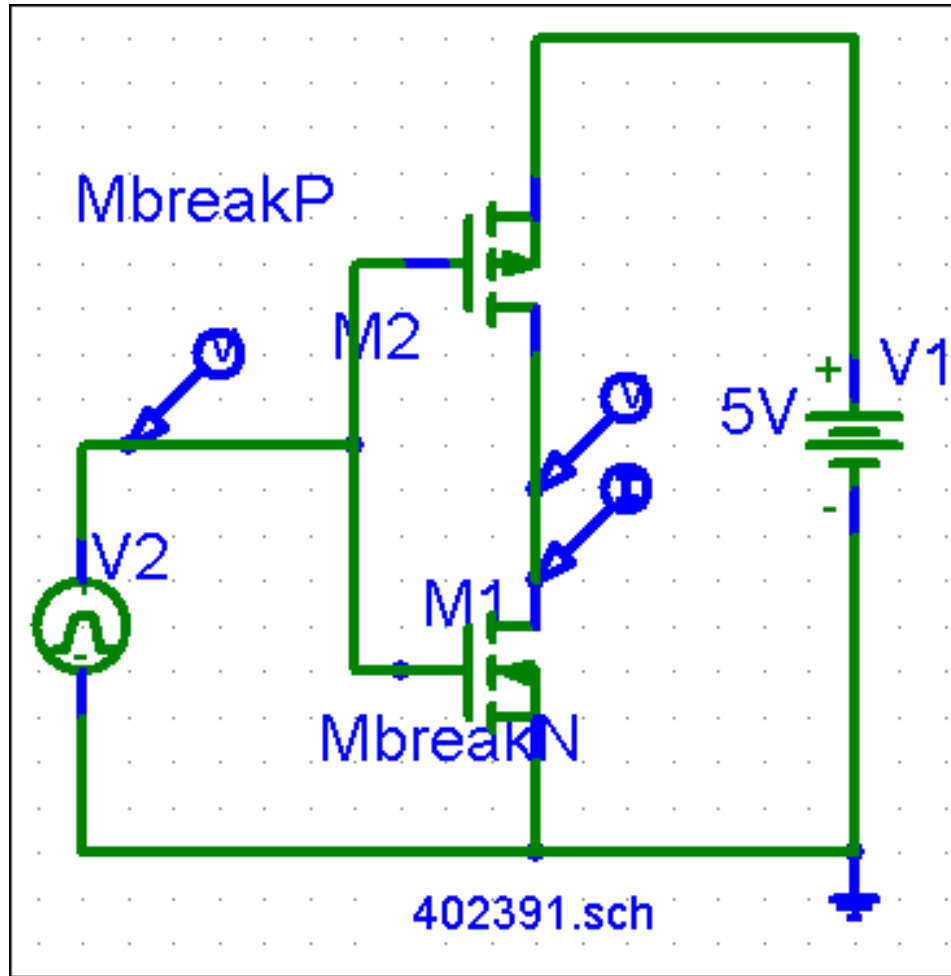


Figure 4.1: Circuit for the FET Inverter. Both transistors have thresholds of 0 Volts, and $\mu C_{ox} W/L = 40 \mu\text{A}/\text{V}^2$.

4.2 Saturation Equation

Write equations for i_D for the N-FET in saturation, as a function of the supply voltage, V_1 the input voltage, V_2 , and the output voltage, V_{out} at the location of the voltage marker in the figure. .

$$i_D = \mu_n C_{ox} \frac{W}{L} \frac{(V_{GS} - V_{Thr})^2}{2} \quad (4.3)$$

$$i_D = \mu_n C_{ox} \frac{W}{L} \frac{V_2^2}{2} \quad (4.4)$$

4.3 Solution

Let the input voltage be either $V_2 = 4.8 \text{ V}$ or $V_2 = 0.2 \text{ V}$. Solve the equations for the output voltage, V_{out} , and determine which of the two input voltages is appropriate for this situation.

Combine Equations 4.2 and 4.4.

$$(V_1 - V_2)(V_1 - V_{out}) - \frac{1}{2}(V_1 - V_{out})^2 = \frac{V_2^2}{2} \quad (4.5)$$

$$V_1^2 + V_2V_{out} - V_1V_{out} - V_1V_2 - \frac{V_1^2}{2} + V_1V_{out} - \frac{V_{out}^2}{2} - \frac{V_2^2}{2} = 0 \quad (4.6)$$

$$\frac{V_1^2}{2} + V_2V_{out} - V_1V_2 - \frac{V_{out}^2}{2} - \frac{V_2^2}{2} = 0 \quad (4.7)$$

$$V_{out}^2 - 2V_2V_{out} - V_1^2 + 2V_1V_2 + V_2^2 = 0 \quad (4.8)$$

In the quadratic equation, for $V_2 = 4.8 \text{ V}$ or $V_2 = 0.2 \text{ V}$

$$a = 1 \quad (4.9)$$

$$b = -2V_2 (= -9.6, -0.4 \text{ V}) \quad (4.10)$$

$$c = -V_1^2 + 2V_1V_2 + V_2^2 (= 46, -23 \text{ V}^2) \quad (4.11)$$

Then,

$$b^2 - 4ac = (-92, 92 \text{ V}^2) \quad (4.12)$$

The result must be positive. Therefore, the LOWER INPUT VOLTAGE is the correct one.

$$v_{out} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = 4.99 \text{ V} \quad (4.13)$$

4.4 Power Consumption

Compute the current and the power consumed by the inverter in this condition.

Use Equation 4.4 to find the current

$$i_D = \mu_n C_{ox} \frac{W}{L} \frac{V_2^2}{2} = 40 \times 10^{-6} \text{ A/V}^2 \frac{0.262}{2} = 8 \times 10^{-7} \text{ A} \quad (4.14)$$

The current passes through both transistors, so the total voltage drop is V_1 , so

$$P = i_D \times V_1 = 4 \times 10^{-6} \text{ W} \quad (4.15)$$

Current	$8 \times 10^{-7} \text{ A}$
Power	$4 \times 10^{-6} \text{ W}$