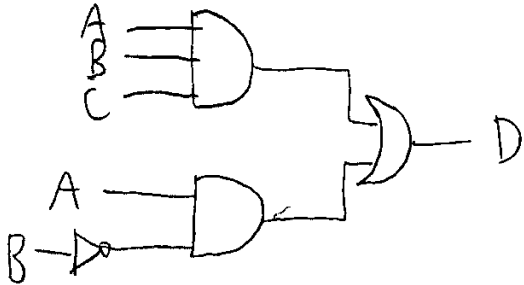


P.1

EECE 24/2 - HW 10 solutions


Problem 1

a) $D = ABC + AB\bar{B}$




| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

b) $E = AB + A\bar{B}C + \bar{C}D$

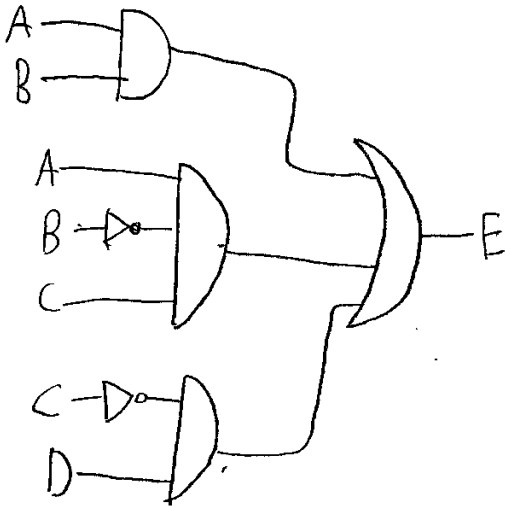

| A | B | C | D | E |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

c) $Z = WX + \overline{(W+Y)}$

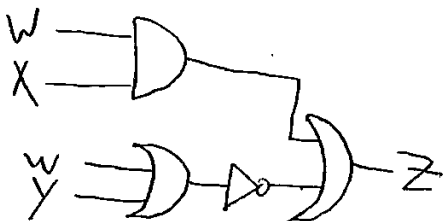

| W | X | Y | Z |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

Hint:
Find which inputs result in "1", then fill the rest with "0"

2

Problem 2

$$NM_H = V_{OH} - V_{IH} = 4.5V - 3V = 1.5V = NM_H$$

$$NM_L = V_{IL} - V_{OL} = 1.5V - 1V = 0.5V = NM_L$$

Problem 3

$$a) t_{PHL} = \frac{C_L \cdot V_{OD}}{\left(\frac{W}{L}\right)_n \cdot K_{PN} \cdot (V_{DD} - V_{thn})^2} = \frac{2 \times 10^{-12} \cdot 5}{\left(\frac{3}{1}\right) \cdot 50 \times 10^{-6} (5-1)^2}$$

$$t_{PHL} = 4.167 \times 10^{-9} s = 4.167 ns = t_{PHL}$$

$$t_{PLH} = \frac{C_L V_{OD}}{\left(\frac{W}{L}\right)_p \cdot K_{PP} \cdot (V_{DD} - |V_{thp}|)^2} = \frac{2 \times 10^{-12} \cdot 5}{\left(\frac{6}{1}\right) \cdot 25 \times 10^{-6} (5-1)^2}$$

$$t_{PLH} = 4.167 ns$$

b) same equations, but with $\left(\frac{W}{L}\right)_n = 3$ (no change)
 $\left(\frac{W}{L}\right)_p = 60$ (new)

$$t_{PHL} = 4.167 ns$$

$$t_{PLH} = 0.4167 ns$$

c) same equations with $\left(\frac{W}{L}\right)_n = 30$
 $\left(\frac{W}{L}\right)_p = 6$

$$t_{PHL} = 0.4167 ns$$

$$t_{PLH} = 4.167 ns$$


3

Problem 4

a) Conditions at the trip point:

$$V_I = \frac{V_{DD}}{2} = 2.5V$$

$$V_{GSN} = V_I - 0 = 2.5V$$

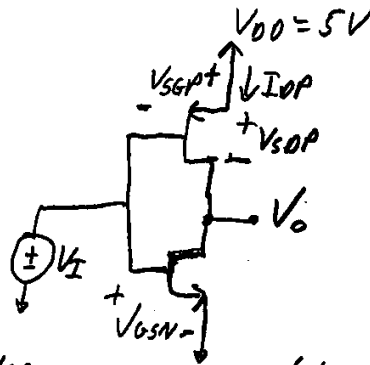

It is required that $V_O = \frac{V_{DD}}{2} = 2.5V$, which implies that $I_{DP} = I_{ON}$

$$V_{DSN} = V_O - 0V = 2.5V > V_{GSN} - V_{t0N} = 2.5V - 0.7V = 1.8V$$

$V_{GSN} > V_{GSN} - V_{t0N}$ & $V_{GSN} > V_{t0N} \rightarrow$ The NMOS is in saturation at the trip point

$$V_{SGP} = 5V - V_I = 2.5V > |V_{t0P}| = 1V$$

$$V_{SGP} - |V_{t0P}| = 2.5V - (1V) = 1.5V$$

$V_{SGP} = 5V - V_O = 2.5V > V_{SGP} = |V_{t0P}| \rightarrow$ The PMOS is in saturation

Equating the currents at the trip point, using the equations for the saturation region:

$$I_{DP} = I_{ON}$$

$$\left(\frac{W_p}{L_{min}}\right) \cdot \left(\frac{K_{Pp}}{2}\right) \cdot (V_{SGP} - |V_{t0P}|)^2 \cdot (1 + \lambda \cdot V_{SDP})$$

$$= \left(\frac{W_n}{L_{min}}\right) \cdot \left(\frac{K_{Pn}}{2}\right) \cdot (V_{GSN} - V_{t0N})^2 \cdot (1 + \lambda \cdot V_{DSN})$$

$$W_p \cdot (50 \times 10^{-6}) \cdot (2.5 - 1)^2 \cdot (1 + 0.02 \cdot 2.5)$$

$$= W_n \cdot (150 \times 10^{-6}) \cdot (2.5 - 0.7)^2 \cdot (1 + 0.02 \cdot 2.5)$$

$$\hookrightarrow \boxed{\frac{W_p}{W_n} = 4.32}$$

4 ... Prob. 14 cont.:


b) The peak current occurs at the trip point
(Fig. 6.33 in the textbook)

$$I_{DN} = 3 \times 10^{-3} = \left(\frac{W_N}{L_{min}} \right) \cdot \left(\frac{K_P N}{2} \right) \cdot (V_{GSN} - V_{TON})^2 \cdot (1 + \lambda \cdot V_{GSN})$$

$$3 \times 10^{-3} = \left(\frac{W_N}{0.6 \times 10^{-6}} \right) \cdot \left(\frac{150 \times 10^{-6}}{2} \right) \cdot (2.5 - 0.7)^2 \cdot (1 + 0.02 \cdot 2.5)$$

$$\hookrightarrow \boxed{W_N = 6.8 \mu\text{m}}$$

$$W_P = \left(\frac{W_P}{W_N} \right) \cdot W_N = 4.32 \cdot 6.8 \times 10^{-6} = \boxed{29.4 \mu\text{m} = W_P}$$

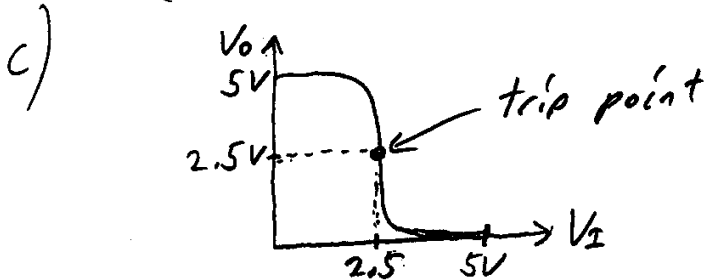

Problem 5

Using equation 6.7 in the textbook:


$$P_{dynamic} = f \cdot C_L \cdot (V_{DD})^2 = (100 \times 10^6 \text{ Hz}) \cdot (100 \times 10^{-15} \text{ F}) \cdot (3 \text{ V})^2$$

$$\boxed{P_{dynamic} = 90 \mu\text{W}}$$

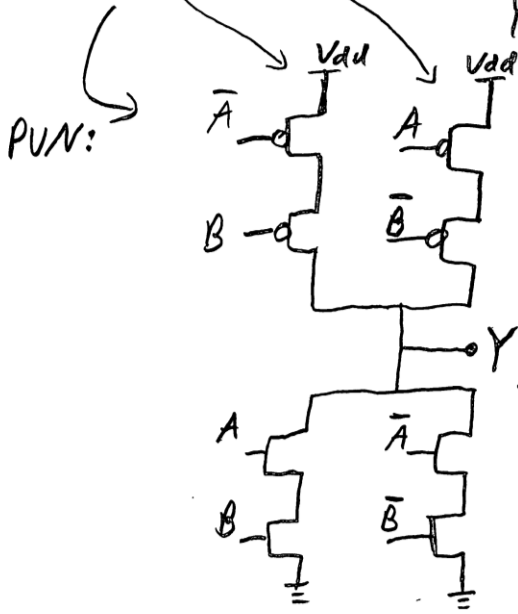Problem 6

$$Y = A\bar{B} + \bar{A}B \rightarrow \bar{Y} = \overline{A\bar{B} + \bar{A}B} = \overline{A\bar{B}} \cdot \overline{\bar{A}B}$$

$$\bar{Y} = (\bar{A} + B) \cdot (A + \bar{B}) = \bar{A}B + A\bar{B}$$




PDN

(other solutions are possible)

6

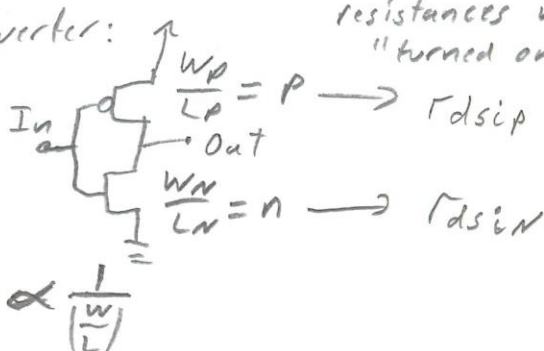Problem 7

basic inverter: resistances when "turned on":



$$t_{PHL}, t_{PLH} \propto r_{ds}$$

$$r_{ds} \propto \frac{1}{\left(\frac{W}{L}\right)}$$

$$t_{PHL}, t_{PLH} \propto \frac{1}{\left(\frac{W}{L}\right)}$$

The series resistances of the transistors in the gate should sum up to an equivalent resistance $\leq r_{dsip}$ (or $\leq r_{dsin}$) for all input combinations, where the series resistances of the transistors between the output V and V_{dd} (or ground) are added when the transistors are "turned on".

\Downarrow $\frac{W}{L}$ ratios of the transistors in the gate

$$M_1: \frac{W}{L} = P$$

$$M_2, M_3: \frac{W}{L} = 2 \cdot P$$

\hookrightarrow When "on": two transistors in series, each having a resistance of $r_{ds2,3} = \frac{r_{dsip}}{2}$

$$M_4, M_5, M_6: \frac{W}{L} = 2 \cdot n$$

\hookrightarrow worst case M_4 and (M_5 or M_6) are "on": each transistor has a resistance of $\frac{r_{dsin}}{2}$, such that the sum is equal to r_{dsin}

\hookrightarrow equivalent resistance if all transistors are "on":

$$R_{eq} = \frac{r_{dsin}}{2} + \left(\frac{r_{dsin}}{2} \parallel \frac{r_{dsin}}{2} \right) = \frac{3 \cdot r_{dsin}}{4} < r_{dsin}$$

(M_4)
($M_5 \parallel M_6$)