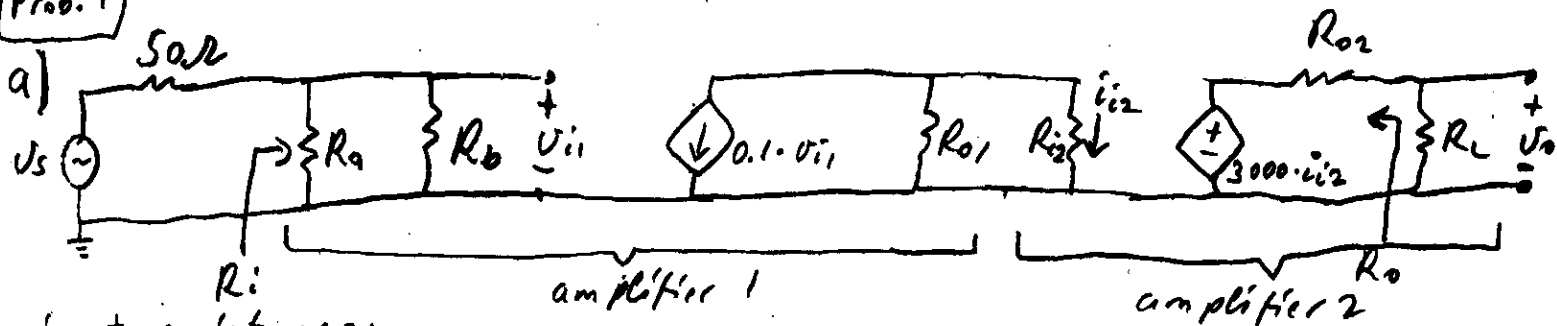


Prob. 1




input resistance:

$$R_i = R_a \parallel R_b = \frac{1}{\frac{1}{1000} + \frac{1}{2000}} = \boxed{666.67 \Omega = R_i}$$

Output resistance (with R_L disconnected):

$$\hookrightarrow \text{set } v_s = 0 \rightarrow v_{i1} = 0 \rightarrow 0.1 \cdot v_{i1} = 0 \rightarrow 3000 \cdot i_{i2} = 0$$

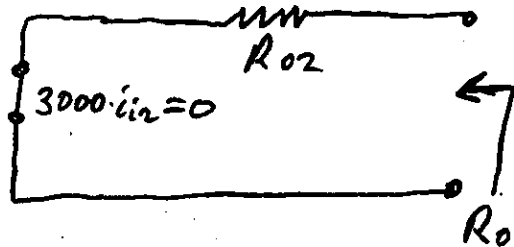\hookrightarrow output stage with $v_s = 0$:



$$\boxed{R_o = R_{02} = 200 \Omega}$$

voltage gain:

$$\frac{v_{i1}}{v_s} = \frac{R_i}{50 \Omega + R_i} = \frac{R_a \parallel R_b}{50 \Omega + (R_a \parallel R_b)} = \frac{666.67 \Omega}{50 \Omega + 666.67 \Omega} = 0.9302$$

$$i_{i2} = -0.1 \cdot v_{i1} \cdot \left(\frac{R_{01}}{R_{01} + R_{i2}} \right) \leftarrow \text{note: negative sign because } i_{i2} \text{ flows into the opposite direction compared to } (0.1 \cdot v_{i1}) \text{ in the divider}$$

$$\hookrightarrow \frac{i_{i2}}{v_{i1}} = -0.1 \cdot \left(\frac{R_{01}}{R_{01} + R_{i2}} \right) = -0.1 \cdot \left(\frac{3000}{3000 + 100} \right) = -96.77 \times 10^{-3} \frac{A}{V}$$

$$v_o = 3000 \cdot i_{i2} \cdot \left(\frac{R_L}{R_L + R_{02}} \right)$$


$$\hookrightarrow \frac{v_o}{i_{i2}} = 3000 \left(\frac{4000}{4000 + 200} \right) = 2857 \frac{V}{A}$$

$$A_{vs} = \frac{v_o}{v_s} = \frac{v_{i1}}{v_s} \times \frac{i_{i2}}{v_{i1}} \times \frac{v_o}{i_{i2}} = (0.9302) \times (-96.77 \times 10^{-3} \frac{A}{V}) \times (2857 \frac{V}{A})$$

$$\boxed{A_{vs} = -257.2}$$

$$A_{vs|dB} = 20 \log(|A_{vs}|) = \boxed{48.2 \text{ dB} = A_{vs|dB}}$$

(2) ... Prob. 1 cont.:

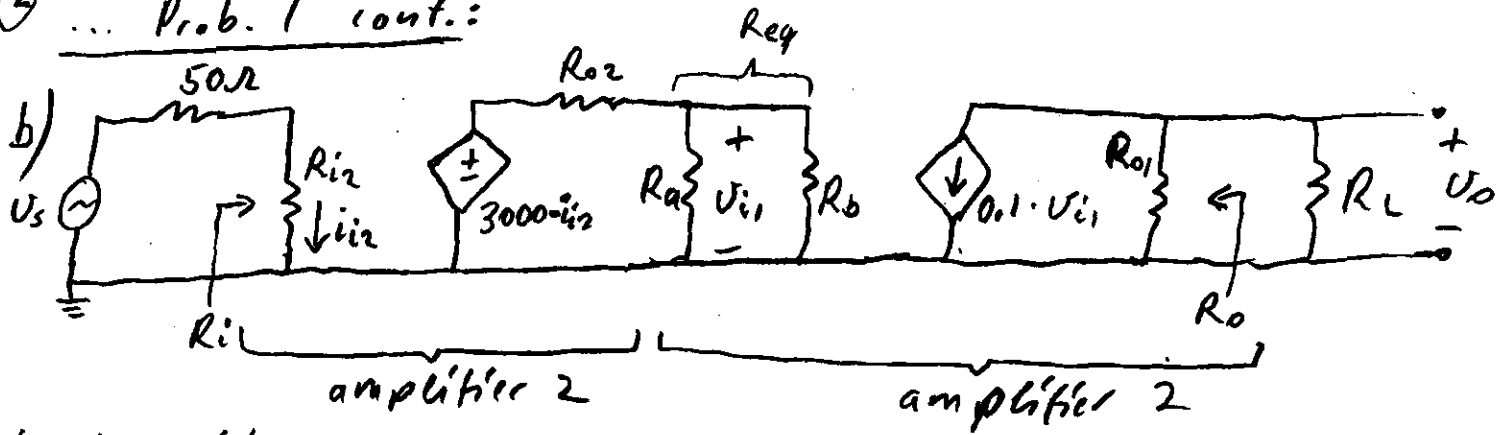

input resistance:

$$R_i = R_{i2} = 100\Omega$$

output resistance:

$$R_o = R_{o1} = 3\text{ k}\Omega$$

voltage gain:

$$i_{i2} = \frac{V_s}{50\Omega + R_{i2}} \rightarrow \frac{i_{i2}}{V_s} = \frac{1}{50\Omega + 100\Omega} = 6.6667 \times 10^{-3} \frac{\text{A}}{\text{V}}$$

$$R_{eq} = R_{a1} \parallel R_b = 1\text{ k}\Omega \parallel 2\text{ k}\Omega = 666.67\Omega$$

$$V_{i1} = 3000 \cdot i_{i2} \cdot \left(\frac{R_{eq}}{R_{eq} + R_{o2}} \right)$$

$$\hookrightarrow \frac{V_{i1}}{i_{i2}} = 3000 \cdot \left(\frac{666.67}{666.67 + 200} \right) = 2308 \frac{\text{V}}{\text{A}}$$

$$V_o = -0.1 \cdot V_{i1} \times (R_{o1} \parallel R_L)$$

$$\hookrightarrow \frac{V_o}{V_{i1}} = -0.1 \times \left(\frac{1}{\frac{1}{3000} + \frac{1}{4000}} \right) = -171.4$$


$$A_{vs} = \frac{V_o}{V_s} = \frac{i_{i2}}{V_s} \times \frac{V_{i1}}{i_{i2}} \times \frac{V_o}{V_{i1}} = (6.6667 \times 10^{-3} \frac{\text{A}}{\text{V}}) \times (2308 \frac{\text{V}}{\text{A}}) \times (-171.4)$$

$$A_{vs} = -2637$$

$$A_{vs\text{dB}} = 20 \log(|A_{vs}|) = 68.4 \text{ dB} = A_{vs\text{dB}}$$

→ The second configuration results in higher voltage gain from the source to the load.


3) Prob. 2

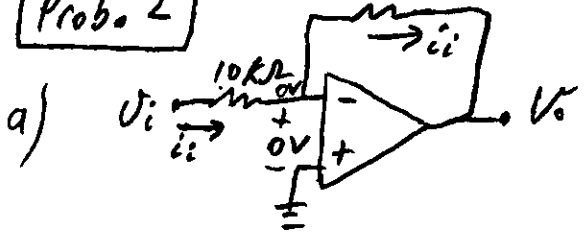

$$i_i = \frac{V_i - 0V}{10k\Omega} = \frac{0V - V_o}{150k\Omega}$$

$$\hookrightarrow \frac{V_o}{V_i} = -\frac{150k\Omega}{10k\Omega} = -15$$

$$R_i = \frac{V_i}{i_i} = 10k\Omega$$

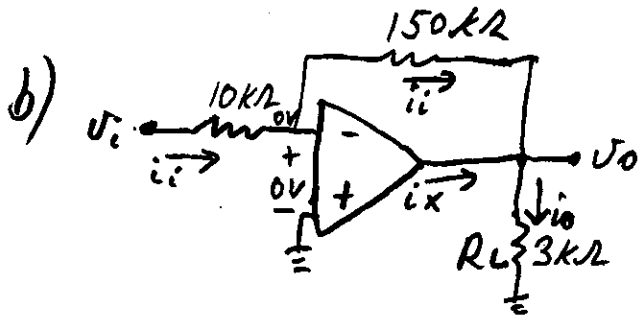

The extra 3kΩ resistor at the output does not affect the KCL at the inverting terminal.


$$\hookrightarrow i_i = \frac{V_i - 0V}{10k\Omega} = \frac{0V - V_o}{150k\Omega}$$

$$\hookrightarrow \frac{V_o}{V_i} = -15$$

$$R_i = \frac{V_i}{i_i} = 10k\Omega$$

Comments:

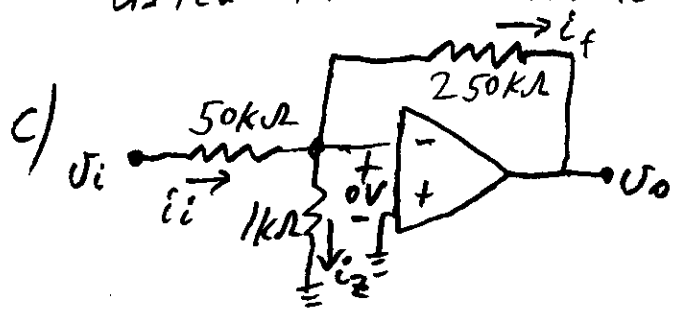- * An ideal op-amp supplies/sinks any value of i_x such that $i_o = i_x + i_i$ and $\frac{V_o}{V_i} = -15$ are satisfied
- * Practical op-amps have output current limitations listed in the datasheets \rightarrow in reality: A small value of R_L reduces the gain.



$i_z = \frac{0V}{1k\Omega} = 0 \rightarrow i_z \cdot 1k\Omega = 0 \rightarrow$ no voltage drop across the 1kΩ resistor


$$i_i = i_x + i_f = i_f$$

$$\frac{V_i - 0V}{50k\Omega} = \frac{0V - V_o}{250k\Omega} \Rightarrow \frac{V_o}{V_i} = -5$$

$$R_i = \frac{V_i}{i_i} = 50k\Omega$$

④ Prob. 3

With the unity-gain amplifier:

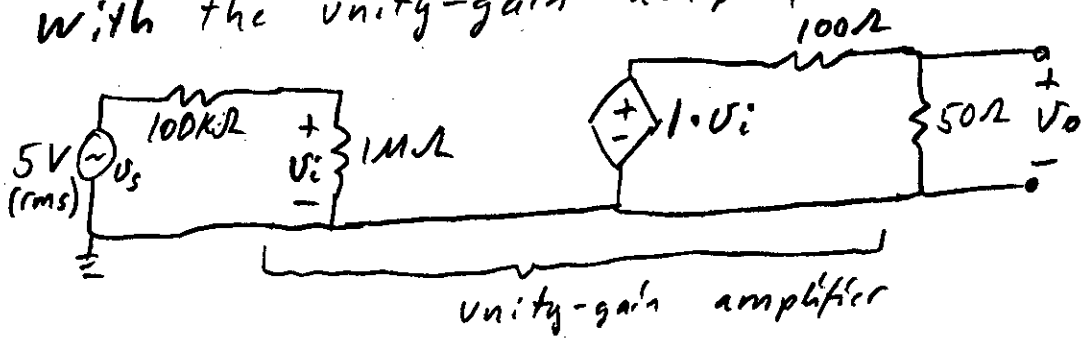

$$\frac{V_i}{V_s} = \frac{1M\Omega}{1M\Omega + 100k\Omega} = 0.90909$$

$$\frac{V_o}{V_i} = \frac{50}{50 + 100} = 0.3333$$


$$\frac{V_o}{V_s} = \frac{V_i}{V_s} \times \frac{V_o}{V_i} = (0.90909) \times (0.3333) = 0.30303$$

$$V_o = 0.30303 \times 5V = \boxed{1.5151 \text{ V}_{rms} = V_o}$$

$$P_o = \frac{V_o(rms)^2}{R_L} = \frac{(1.5151)^2}{50} = \boxed{45.91 \text{ mW} = P_o}$$

with
amp.

Without amplifier:

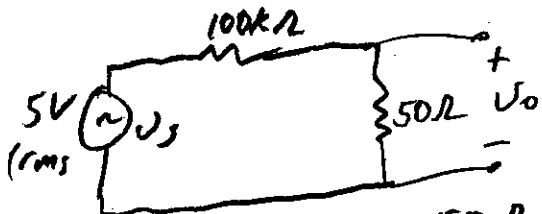

$$V_o = 5V_{rms} \cdot \frac{50\Omega}{50 + 100k\Omega} = \boxed{2.499 \times 10^{-3} \text{ V}_{rms} = V_o}$$

$$P_o = \frac{V_o(rms)^2}{R_L} = \frac{(2.499 \times 10^{-3})^2}{50} = \boxed{124.88 \text{ nW} = P_o}$$

The unity-gain amplifier helps to deliver a significantly higher output power to the load.

5

Problem 4

$$P_{in} = \frac{(V_{in-RMS})^2}{R_{in}} = \frac{(0.1V)^2}{100 \times 10^3 \Omega} = 100 \times 10^{-9} W = 0.1 \mu W$$

$$P_{supply} = V_{supply} \cdot I_{supply} = 15V \cdot 2A = 30W$$

$$P_{out} = \frac{(V_{o-RMS})^2}{R_L} = \frac{(10V)^2}{8} = 12.5W$$

dissipated power: $P_d = P_{in} + P_{supply} - P_{out} = 17.5000001W$

efficiency: $\eta = \frac{P_{out}}{P_{supply}} \times 100\%$

$$\rightarrow P_d \approx 17.5W$$

$$\eta = \frac{12.5W}{30W} \times 100\% = 41.67\% = \eta$$

Problem 5

a) Frequency-dependent impedance of the capacitor: $Z_c = \frac{1}{j\omega c}$

$$V_i(j\omega) = i_s(j\omega) \cdot (Z_c \parallel R_i) = i_s(j\omega) \cdot \frac{1}{\frac{1}{Z_c} + \frac{1}{R_i}} = i_s(j\omega) \cdot \frac{1}{j\omega c + \frac{1}{R_i}}$$

$$\textcircled{1}: V_i(j\omega) = i_s(j\omega) \cdot \frac{R_i}{1 + j\omega c R_i}$$

$$\textcircled{2}: V_o(j\omega) = 100 \cdot V_i(j\omega) \cdot \left(\frac{R_L}{R_o + R_L} \right)$$

substituting $\textcircled{1}$ into $\textcircled{2}$:

$$V_o(j\omega) = 100 \cdot i_s(j\omega) \cdot \left(\frac{R_i}{1 + j\omega c R_i} \right) \cdot \left(\frac{R_L}{R_o + R_L} \right)$$

$$T(j\omega) = \frac{V_o(j\omega)}{i_s(j\omega)} = \frac{100 \cdot (1000) \cdot (500)}{[1 + j\omega \cdot (10 \times 10^{-6}) \cdot (1000)] \cdot (20 + 500)}$$

$$T(j\omega) = \frac{9.615 \times 10^4}{1 + j\omega \cdot (0.01)} = \frac{9.615 \times 10^4}{1 + j \frac{\omega}{100}}$$

Note: The 3dB frequency of this single-pole amplifier is at $\omega_{3dB} = 100 \text{ rad/s}$.

⑥ ... Prob. 5 continued:

b) $\omega_{in} = 10 \text{ rad/s}$ ($f_{in} = \frac{10}{2\pi} = 1.59 \text{ Hz}$) $\omega = \omega_{in} = 10$
 $\hookrightarrow i_s(t) = 2 \text{ mA} \cdot \sin(10 \cdot t) \leftrightarrow \hat{i}_s(j \cdot 10) = (2 \angle 0^\circ) \text{ mA}$

Transfer function at $\omega = \omega_{in} = 10$:

$$T(j \cdot 10) = \frac{9.615 \times 10^4}{1 + j \cdot \left(\frac{10}{100}\right)} = (9.568 \times 10^4 \angle -5.71^\circ)$$

$$\hookrightarrow V_o(j \cdot 10) = T(j \cdot 10) \cdot \hat{i}_s(j \cdot 10) = (9.568 \times 10^4 \angle -5.71^\circ) \cdot (2 \times 10^{-3} \angle 0^\circ)$$

$$V_o(j \cdot 10) = 191.4 \angle -5.71^\circ \text{ [V]}$$

$$\hookrightarrow \boxed{V_o(t) = 191.4 \text{ V} \times \sin(10t - 5.71^\circ)}$$

c) $\omega_{in} = 1000 \text{ rad/s} \rightarrow \hat{i}_s(t) = 2 \text{ mA} \cdot \sin(1000t)$

$$T(j \cdot 1000) = \frac{9.615 \times 10^4}{1 + j \cdot \left(\frac{1000}{100}\right)} = (9.568 \times 10^3 \angle -84.29^\circ)$$

$$V_o(j \cdot 1000) = T(j \cdot 1000) \cdot \hat{i}_s(j \cdot 1000), \text{ where: } \hat{i}_s(j \cdot 1000) = 2 \angle 0^\circ \text{ mA}$$


\downarrow
 $2 \text{ mA} \cdot \sin(1000t)$

$$V_o(j \cdot 1000) = (9.568 \times 10^3 \angle -84.29^\circ) \cdot (2 \angle 0^\circ \times 10^{-3})$$

$$V_o(j \cdot 1000) = 19.14 \angle -84.29^\circ \text{ [V]}$$

$$\hookrightarrow \boxed{V_o(t) = 19.14 \text{ V} \times \sin(1000t - 84.29^\circ)}$$

② Prob. 6

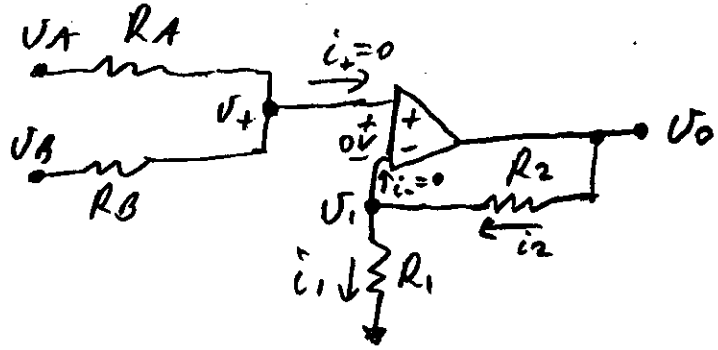

$$V_+ - 0V = V_1 \rightarrow V_+ = V_1$$

$$i_1 = \frac{V_1}{R_1}$$

$$i_2 = i_1 + i_+ = i_1 = \frac{V_1}{R_1}$$

KCL at the non-inverting terminal:

$$0 = \frac{V_A - V_+}{R_A} + \frac{V_B - V_+}{R_B} \rightarrow 0 = \frac{V_A - V_1}{R_A} + \frac{V_B - V_1}{R_B}$$

$$\rightarrow \frac{V_A}{R_A} + \frac{V_B}{R_B} = \frac{V_1}{R_A} + \frac{V_1}{R_B} \rightarrow V_1 \cdot \left(\frac{R_A + R_B}{R_A \cdot R_B} \right) = \frac{V_A}{R_A} + \frac{V_B}{R_B}$$

$$\textcircled{1}: V_1 = \frac{R_B \cdot V_A + R_A \cdot V_B}{R_A + R_B}$$

KVL at the output:

$$0 = -V_0 + i_2 R_2 + V_1 \xrightarrow[\text{sub. } i_1 = i_2]{\text{sub.}} V_0 = i_1 R_2 + V_1$$

$$\textcircled{2}: V_0 \stackrel{i_1 = \frac{V_1}{R_1}}{=} \frac{R_2}{R_1} \cdot V_1 + V_1 = V_1 \left(1 + \frac{R_2}{R_1} \right)$$

Sub. ① into ②:

$$V_0 = \left(1 + \frac{R_2}{R_1} \right) \times \left(\frac{R_B \cdot V_A + R_A \cdot V_B}{R_A + R_B} \right) = \left(\frac{R_1 + R_2}{R_1} \right) \times \left(\frac{R_B \cdot V_A + R_A \cdot V_B}{R_A + R_B} \right)$$