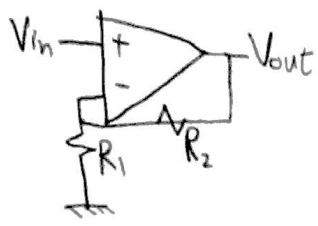


① **Pr. 6.1**

Non-inverting amplifier
 gain = $A_v = 1 + \frac{R_2}{R_1}$



Case 1:-

$A_v = 100 = 1 + \frac{R_2}{R_1} \rightarrow \frac{R_2}{R_1} = 99$


Gain-BW product = $10^6 = A_{OL} \cdot F_o$

$A_{OL}(f) = \frac{A_{OL}}{1 + \frac{jf}{F_o}} = \frac{1}{\frac{1}{A_{OL}} + \frac{jf}{A_{OL} F_o}} \rightarrow$ Assume $A_{OL} = \infty \rightarrow A_{OL}(f) = \frac{GBW}{jf}$

$\therefore V_{out} = (V_{in} - V_{out} \left(\frac{R_1}{R_1 + R_2}\right)) A_{OL}(f) \rightarrow \frac{V_{out}}{V_{in}}(f) = \frac{100}{1 + \frac{100jf}{GBW \times 10^6}} = \frac{100}{1 + \frac{jf}{10^4}} \rightarrow F_{3-dB} = 10^4 \text{ Hz}$

Case 2:-

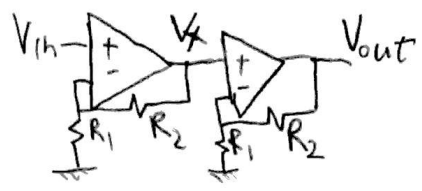$A_v = 10 = 1 + \frac{R_2}{R_1} \rightarrow \frac{R_2}{R_1} = 9$



$\therefore \frac{V_{out}}{V_{in}}(f) = \frac{V_x(f)}{V_{in}(f)} \times \frac{V_{out}(f)}{V_x}$

$V_x = (V_{in} - V_x \left(\frac{R_1}{R_1 + R_2}\right)) A_{OL}(f) \quad V_{out} = (V_x - V_{out} \left(\frac{R_1}{R_1 + R_2}\right)) A_{OL}(f)$

$\therefore f_{3-dB}$ of each stage = 10^5 Hz

$\therefore \frac{V_x}{V_{in}}(f) = \frac{10}{1 + \frac{10jf}{GBW}} = \frac{10}{1 + \frac{jf}{10^5}}$

$\frac{V_{out}}{V_x}(f) = \frac{10}{1 + \frac{10jf}{GBW}} = \frac{10}{1 + \frac{jf}{10^5}}$

$\therefore \frac{V_{out}}{V_{in}}(f) = \frac{100}{\left(1 + \frac{jf}{10^5}\right)^2}$

to get the OVERALL 3-dB BW, we set $\left| \frac{V_{out}}{V_{in}}(f) \right| = \frac{100}{\sqrt{2}}$

$\therefore \left| \frac{V_{out}}{V_{in}}(f) \right| = \frac{100}{1 + \left(\frac{f}{10^5}\right)^2} = \frac{100}{\sqrt{2}} \rightarrow F_{3-dB} = \sqrt{\sqrt{2} - 1} \times 10^5$

$\therefore F_{3-dB} \approx 64.4 \text{ KHz}$

②

Prob. 2

a) $v_d = v_1 - v_2 = 150 \mu V - 100 \mu V$

$v_d = 50 \mu V$

b) $v_{cm} = \frac{v_1 + v_2}{2} = \frac{150 \mu V + 100 \mu V}{2}$

$v_{cm} = 125 \mu V$

c) $A_d = 10^{\frac{Ad(dB)}{20}} = 10^{\frac{60}{20}} = 10^3$

$CMRR = 20 \log \frac{|A_d|}{|A_{cm}|} = 120 \text{ dB}$

$10^{\frac{120}{20}} = \frac{|A_d|}{|A_{cm}|}$

$\rightarrow |A_{cm}| = \frac{10^3}{10^6} = 0.001 = |A_{cm}|$

$\rightarrow A_{cm} = \pm 0.001$

d) $v_o = A_d \cdot v_d + A_{cm} \cdot v_{cm}$
 $= (10^3) \cdot (50 \mu V) \pm (0.001) \cdot (125 \mu V)$
 $= 0.05 \pm 125 \times 10^{-9} \text{ V}$

$v_o = 0.050000125 \text{ V}$

or $v_o = 0.049999875 \text{ V}$

3

Prob. 3

a) KCL at the inverting input of the circuit in Fig. P2.43:

$$0 = \frac{V_s - (-v_i)}{R_1} + \frac{v_i}{R_{in}} + \frac{V_o - (-v_i)}{R_2}$$

$$0 = V_s + v_i + \frac{R_1}{R_{in}} \cdot v_i + \frac{R_1}{R_2} \cdot V_o + \frac{R_1}{R_2} \cdot v_i$$

$$v_i \cdot \left(1 + \frac{R_1}{R_{in}} + \frac{R_1}{R_2}\right) = - \left(V_s + \frac{R_1}{R_2} \cdot V_o\right)$$

$$\hookrightarrow \textcircled{1}: v_i = - \frac{V_s}{1 + \frac{R_1}{R_{in}} + \frac{R_1}{R_2}} - \frac{R_1 \cdot V_o}{R_2 + \frac{R_1 R_2}{R_{in}} + R_1}$$

KCL at the output:

$$0 = \frac{V_o - A_{OL} \cdot v_i}{R_o} + \frac{V_o - (-v_i)}{R_2}$$

$$0 = V_o - A_{OL} \cdot v_i + \frac{R_o}{R_2} \cdot V_o + \frac{R_o}{R_2} \cdot v_i$$

$$\textcircled{2}: V_o \cdot \left(1 + \frac{R_o}{R_2}\right) = v_i \cdot \left(A_{OL} - \frac{R_o}{R_2}\right)$$

Substituting eqn. $\textcircled{1}$ in to $\textcircled{2}$:

$$V_o \cdot \left(1 + \frac{R_o}{R_2}\right) = - \frac{V_s \cdot \left(A_{OL} - \frac{R_o}{R_2}\right)}{1 + \frac{R_1}{R_{in}} + \frac{R_1}{R_2}} - \frac{V_o \cdot R_1 \cdot \left(A_{OL} - \frac{R_o}{R_2}\right)}{R_1 + R_2 + \frac{R_1 R_2}{R_{in}}}$$

$$V_o \cdot \left(1 + \frac{R_o}{R_2} + \frac{R_1 \cdot \left(A_{OL} - \frac{R_o}{R_2}\right)}{R_1 + R_2 + \frac{R_1 R_2}{R_{in}}}\right) = - \frac{V_s \cdot \left(A_{OL} - \frac{R_o}{R_2}\right)}{1 + \frac{R_1}{R_{in}} + \frac{R_1}{R_2}}$$

$$A_{vs} = \frac{V_o}{V_s} = \frac{- \left(A_{OL} - \frac{R_o}{R_2}\right)}{\left(1 + \frac{R_1}{R_{in}} + \frac{R_1}{R_2}\right) \cdot \left(1 + \frac{R_o}{R_2} + \frac{R_1 \cdot \left(A_{OL} - \frac{R_o}{R_2}\right)}{R_1 + R_2 + \frac{R_1 R_2}{R_{in}}}\right)}$$

ⓧ ... Prob. 1 a) continued:

$$A_{vs} = \frac{-(10^5 - \frac{25}{10000})}{(1 + \frac{1000}{10^6} + \frac{10000}{1000}) \cdot (1 + \frac{25}{10000} + \frac{1000 \cdot (10^5 - \frac{25}{10000})}{1000 + 10000 + \frac{(1000) \cdot (10000)}{10^6}})}$$

$$A_{vs} = -9.998896$$

with $A_{OL} = \infty$: $A_{vs}/ideal = 10$

b) KVL at the input:

$$0 = -v_s + R_1 i_s - v_i \rightarrow \textcircled{1}: v_i = R_1 \cdot i_s - v_s$$

KVL in the outer loop:

$$0 = v_i + (i_s + \frac{v_i}{R_{in}}) \cdot R_2 + (i_s + \frac{v_i}{R_{in}}) \cdot R_o + A_{OL} \cdot v_i$$

$$\textcircled{2}: 0 = v_i + (i_s + \frac{v_i}{R_{in}}) \cdot (R_2 + R_o) + A_{OL} \cdot v_i$$

sub. $\textcircled{1}$ into $\textcircled{2}$:

$$0 = R_1 \cdot i_s - v_s + (i_s + \frac{R_1 i_s - v_s}{R_{in}}) \cdot (R_2 + R_o) + A_{OL} \cdot R_1 \cdot i_s - A_{OL} \cdot v_s$$

$$v_s \cdot [1 + \frac{R_2 + R_o}{R_{in}} + A_{OL}] = i_s \cdot [1 + R_2 + R_o + \frac{R_1 \cdot (R_2 + R_o)}{R_{in}} + A_{OL} \cdot R_1]$$


$$Z_{in} = \frac{v_s}{i_s} = \frac{1 + R_2 + R_o + \frac{R_1 \cdot (R_2 + R_o)}{R_{in}} + A_{OL} \cdot R_1}{1 + \frac{R_2 + R_o}{R_{in}} + A_{OL}}$$

$$Z_{in} = \frac{1 + 10000 + 25 + 1000 \cdot (10000 + 25) / 10^6 + 10^5 \cdot 1000}{1 + (10000 + 25) / 10^6 + 10^5}$$

$$Z_{in} = 1.00009 \text{ k}\Omega$$

with $A_{OL} = \infty$: $Z_{in}/ideal = 1 \text{ k}\Omega$

⑤ ... Prob. 3 cont.:

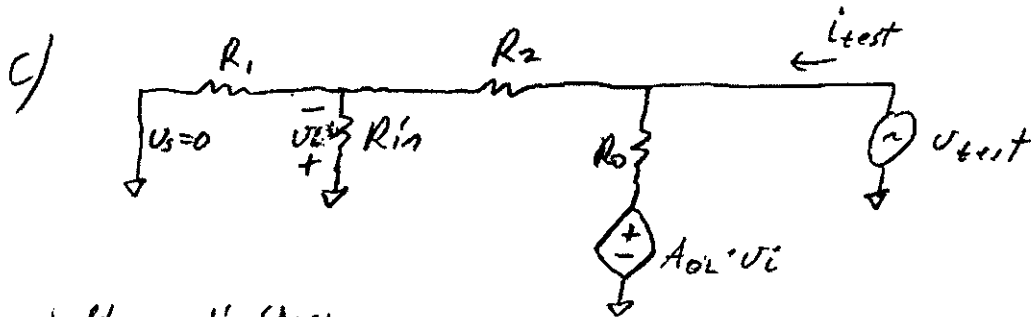

Voltage divider:

$$\textcircled{1}: V_i = -V_{test} \cdot \left(\frac{R_{in} \parallel R_1}{R_2 + R_{in} \parallel R_1} \right)$$

KCL at the output:

$$\textcircled{2}: i_{test} = \frac{V_{test} - A_{OL} \cdot V_i}{R_o} + \frac{V_{test}}{R_2 + R_{in} \parallel R_1}$$

Substituting $\textcircled{1}$ into $\textcircled{2}$:

$$i_{test} = \frac{V_{test}}{R_o} + V_{test} \cdot \frac{A_{OL}}{R_o} \cdot \left(\frac{R_{in} \parallel R_1}{R_2 + R_{in} \parallel R_1} \right) + \frac{V_{test}}{R_2 + R_{in} \parallel R_1}$$

$$Z_o = \frac{V_{test}}{i_{test}} = \frac{1}{\frac{1}{R_o} + \frac{A_{OL}}{R_o} \cdot \left(\frac{R_{in} \parallel R_1}{R_2 + R_{in} \parallel R_1} \right) + \frac{1}{R_2 + R_{in} \parallel R_1}}$$

$$R_{in} \parallel R_1 = \frac{1}{\frac{1}{10^5} + \frac{1}{1000}} = 999.000999 \Omega$$


$$Z_o = \frac{1}{\frac{1}{25} + \frac{10^5}{25} \cdot \left(\frac{999}{10000 + 999} \right) + \frac{1}{10000 + 999}}$$

$$Z_o = 2.752 \times 10^{-3} \Omega$$

with $A_{OL} = \infty$: $Z_{o(ideal)} = 0$

⑥

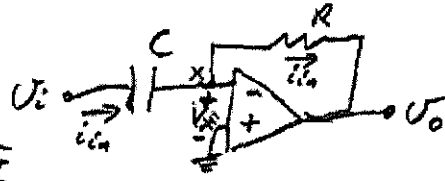a) Capacitor impedance: $Z_c = \frac{1}{sC} = \frac{1}{j\omega C}$



$$\textcircled{1}: i_{in} = \frac{v_i - v_x}{Z_c} = j\omega C (v_i - v_x) = j\omega C \left(v_i + \frac{v_o}{A_{OL}} \right)$$

Sub. $v_x = -\frac{v_o}{A_{OL}}$

$$(v_x \neq 0 \text{ with finite gain} \rightarrow v_o = (v_+ - v_-) \cdot A_{OL} = -v_x \cdot A_{OL})$$

$$\textcircled{2}: i_{in} = \frac{v_x - v_o}{R} = \frac{-\frac{v_o}{A_{OL}} - v_o}{R}$$

Setting $\textcircled{1}$ equal to $\textcircled{2}$:

$$j\omega C \cdot \left(v_i + \frac{v_o}{A_{OL}} \right) = \frac{-\frac{v_o}{A_{OL}} - v_o}{R} \rightarrow j\omega RC \cdot v_i = -\frac{j\omega RC}{A_{OL}} \cdot v_o - \frac{v_o}{A_{OL}} - v_o$$


$$\rightarrow A_{CL}(j\omega) = \frac{v_o}{v_i} = \frac{-j\omega RC}{1 + \frac{1}{A_{OL}} + j\frac{\omega RC}{A_{OL}}}$$

b) with $A_{OL} = \infty$:


$$A_{CL}(j\omega) \Big|_{A_{OL}=\infty} = -j\omega RC$$

FYI: This is a differentiator circuit (same equation as in eq. 2.56 in the book)

Bode Plot:

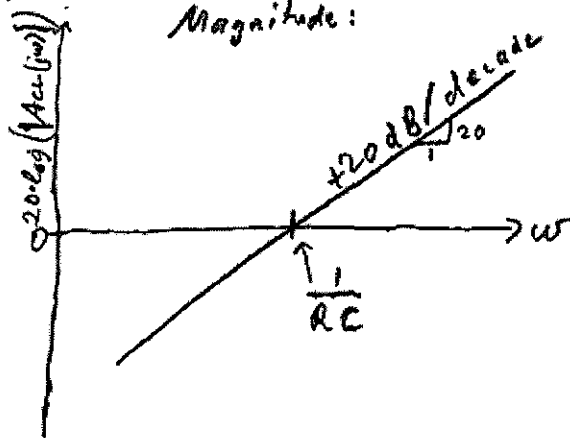

Phase of $A_{CL}(j\omega)$:

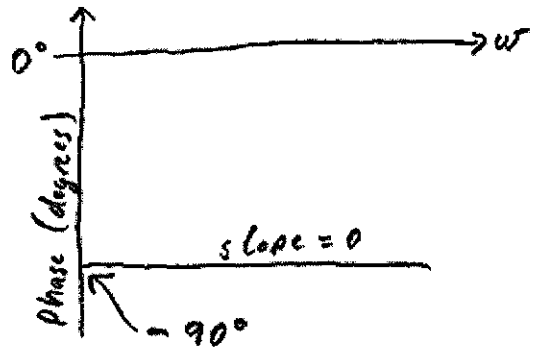

7

c) Substituting $\omega = 2\pi f$ and the given values into the equation from part a):

$$A_{CL}(j2\pi \cdot 500) = \frac{V_o(j2\pi \cdot 500)}{V_i(j2\pi \cdot 500)} = \frac{-j \cdot 2\pi \cdot 1000 \cdot 50 \times 10^3 \cdot 10 \times 10^{-6}}{1 + \frac{1}{2 \times 10^4} + j \cdot \frac{2\pi \cdot 1000 \cdot 50 \times 10^3 \cdot 10 \times 10^{-6}}{2 \times 10^4}}$$

$$A_{CL}(j2\pi \cdot 500) = 3103.4 \angle -98.9266$$

[Just for comparison A_{CL} at 500 Hz with ideal op-amp:
 $A_{CL}(j2\pi \cdot 500) / A_{OL=\infty} = -j2\pi \cdot f \cdot R \cdot C = 3141.6 \angle -90$]

Output at 1000 Hz:

$$V_o(j2\pi \cdot 1000) = A_{CL}(j2\pi \cdot 1000) \cdot \sin(j2\pi \cdot 1000) \\ = (3103.4 \angle -98.9) \cdot (1 \text{ mV} \angle 0^\circ)$$

$$= 3.1034 \angle -98.9 \text{ [V]}$$

$$V_o(t) = 3.1034 \sin(2\pi \cdot 1000 \cdot t - 98.9^\circ)$$

Output Amplitude = 3.1034 V

d) Closed-loop voltage gain in decibels = $20 \log_{10}(|A_{CL}|) = 20 \log_{10}(3103.4) = 69.945 \text{ dB}$

8

Problem 5

a) From the analysis in example 2.10 (page 96) in the book:


$$V_o = -\left(1 + \frac{R_2}{R_1}\right) \cdot V_{off} \rightarrow V_{off, \max} = \frac{\pm 100 \text{ mV}}{-\left(1 + \frac{R_2}{R_1}\right)} = \frac{\pm 100 \text{ mV}}{-\left(1 + \frac{100 \times 10^3}{10 \times 10^3}\right)}$$

$$V_{off, \max} = \pm 9.091 \text{ mV}$$

b) As in example 2.10, $V_o = R_2 \cdot I_B \rightarrow I_B = \frac{V_o}{R_2}$

$$\rightarrow I_{B, \max} = \frac{\pm 100 \text{ mV}}{100 \times 10^3 \Omega} = \pm 1.0 \mu\text{A} = I_{B, \max}$$

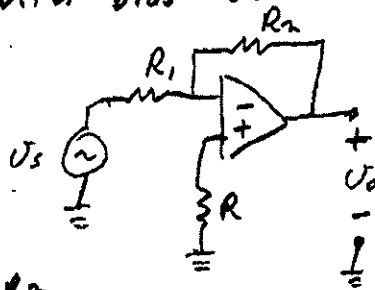
c) Circuit with bias current cancellation:



requires:

$$R = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

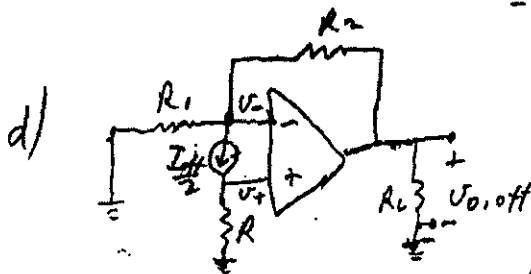↳ shown on the slide entitled "Example DC offset Analysis" in Lecture 7.



Summing point constraint: ① $V_- = V_+ = \frac{I_{off}}{2} \cdot R$

$$\text{KCL at } V_- : \textcircled{2} \frac{V_-}{R_1} + \frac{I_{off}}{2} + \frac{V_x - V_{o, off}}{R_2} = 0$$

Sub. ① into ② and multiplying all terms by R_2 :

$$\frac{R_2}{R_1} \cdot R \cdot \frac{I_{off}}{2} + R_2 \cdot \frac{I_{off}}{2} + R \cdot \frac{I_{off}}{2} - V_{o, off} = 0$$


$$\rightarrow V_{o, off} = \frac{I_{off}}{2} \cdot \left[R_2 + \frac{R R_2 + R R_1}{R_1} \right] = \frac{I_{off}}{2} \cdot \left[R_2 + \frac{R}{R_1} \cdot (R_1 + R_2) \right]$$

$$= \frac{I_{off}}{2} \cdot \left[R_2 + \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{R_1} \cdot (R_1 + R_2) \right] = \frac{I_{off}}{2} \cdot [R_2 + R_2] = R_2 \cdot I_{off}$$


$$\rightarrow I_{off, \max} = \frac{V_{o, off, \max}}{R_2} = \frac{\pm 100 \text{ mV}}{100 \times 10^3 \Omega} = \pm 1.0 \mu\text{A} = I_{off, \max}$$

same solution as with the alternative analysis in the lecture slides.

9

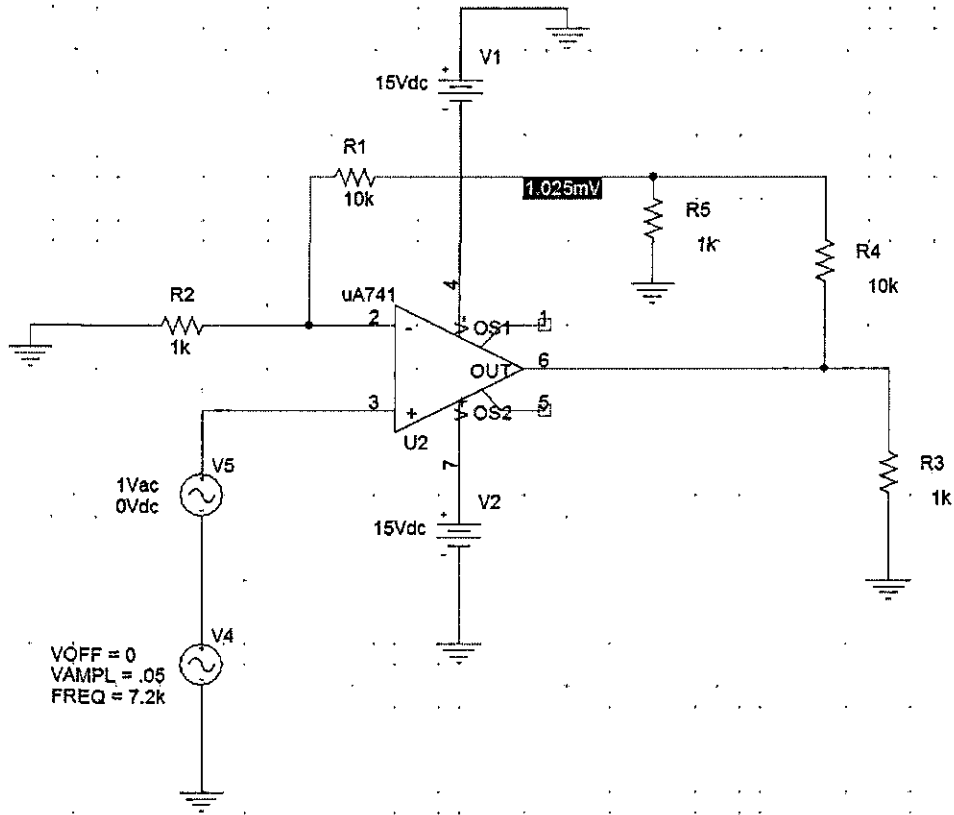

a)

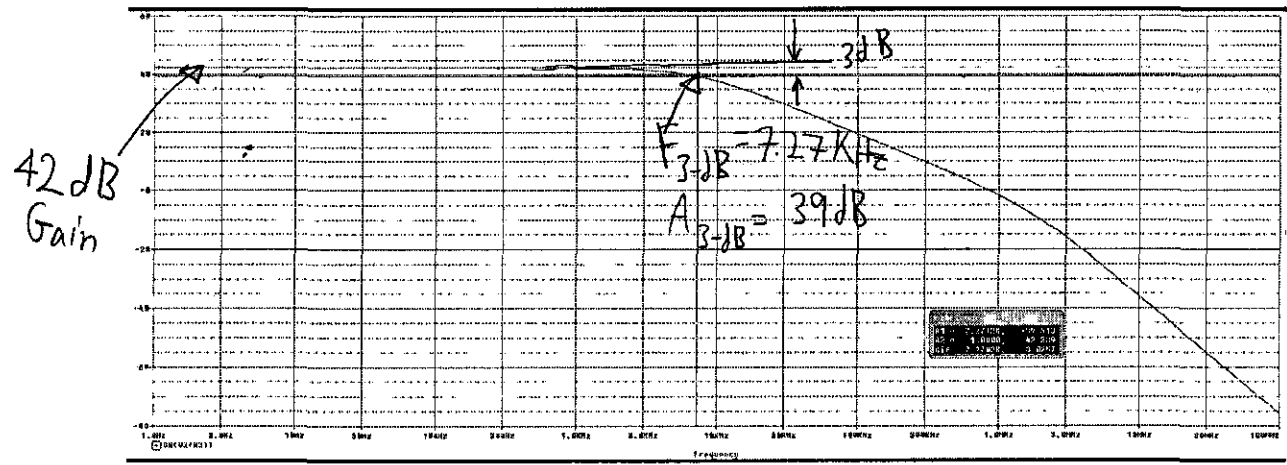


Voltage gain in dB vs. Freq.

10

a) cont.

DC gain ≈ 131

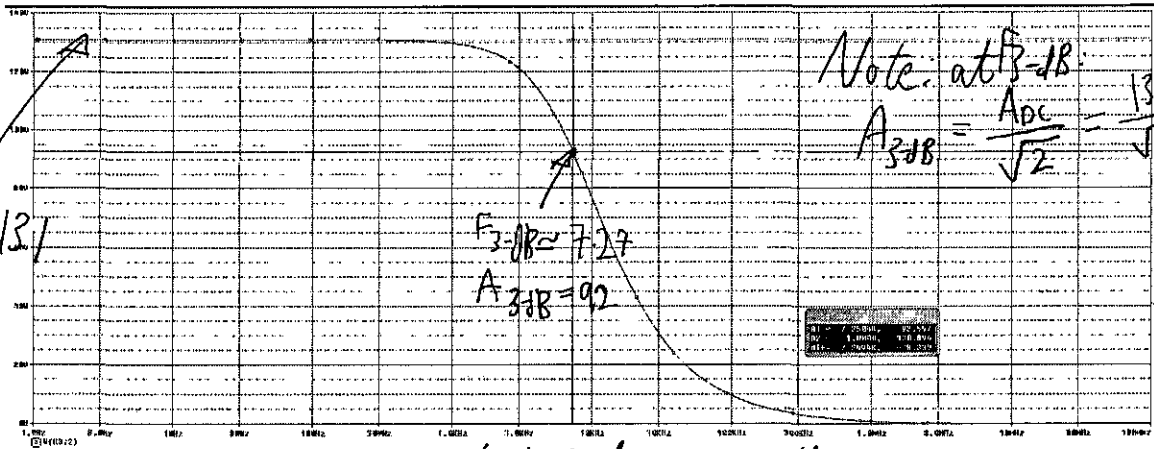


Note: at $\beta = 18$
 $A_{3dB} = \frac{A_{DC}}{\sqrt{2}} = \frac{131}{\sqrt{2}} = 92$


$F_3 = 180 \approx 72.7$
 $A_{3dB} = 92$

absolute voltage gain vs. Freq.

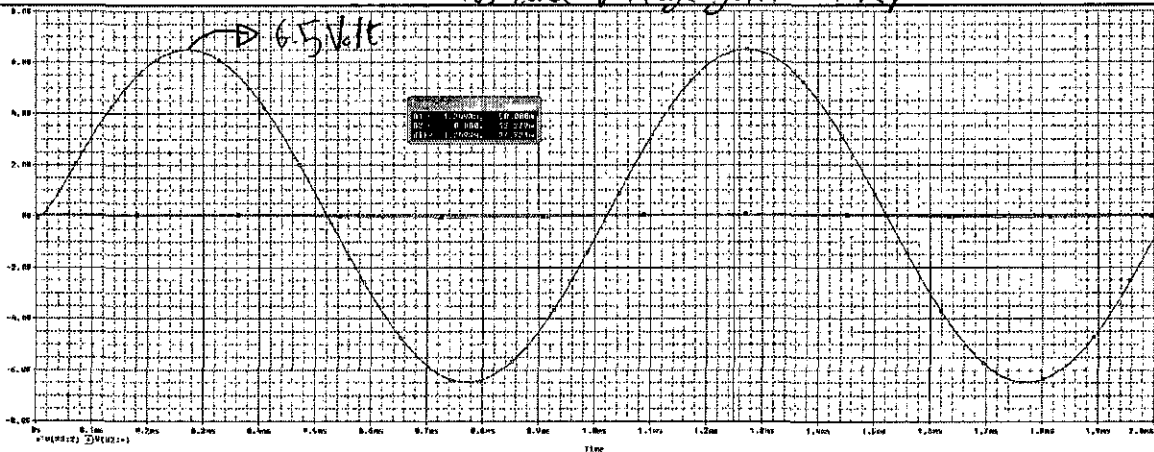b) $A_V = \frac{6.5V}{0.05V} = 130$
 "as expected"




c) clipping

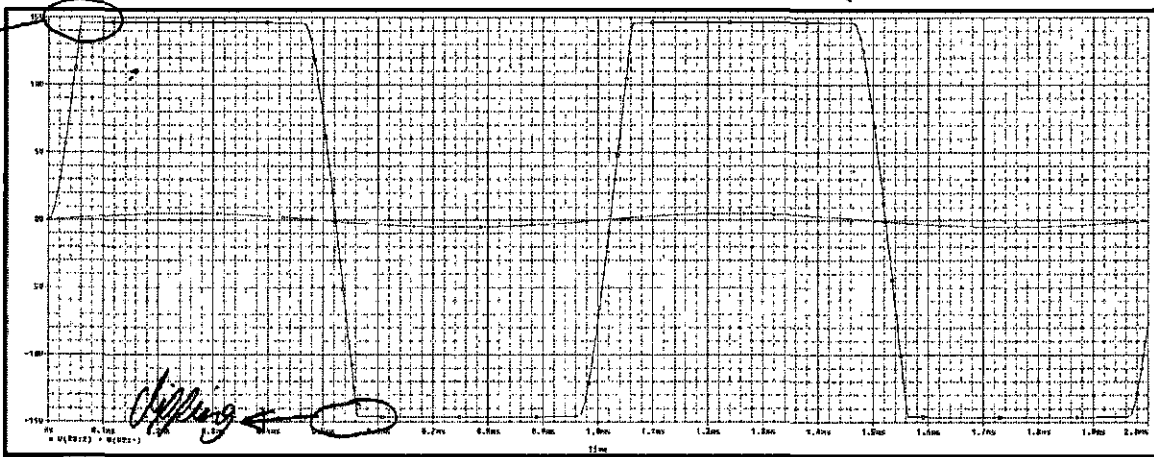

clipping at $\pm 14.5V$
 "due to supply limitation"

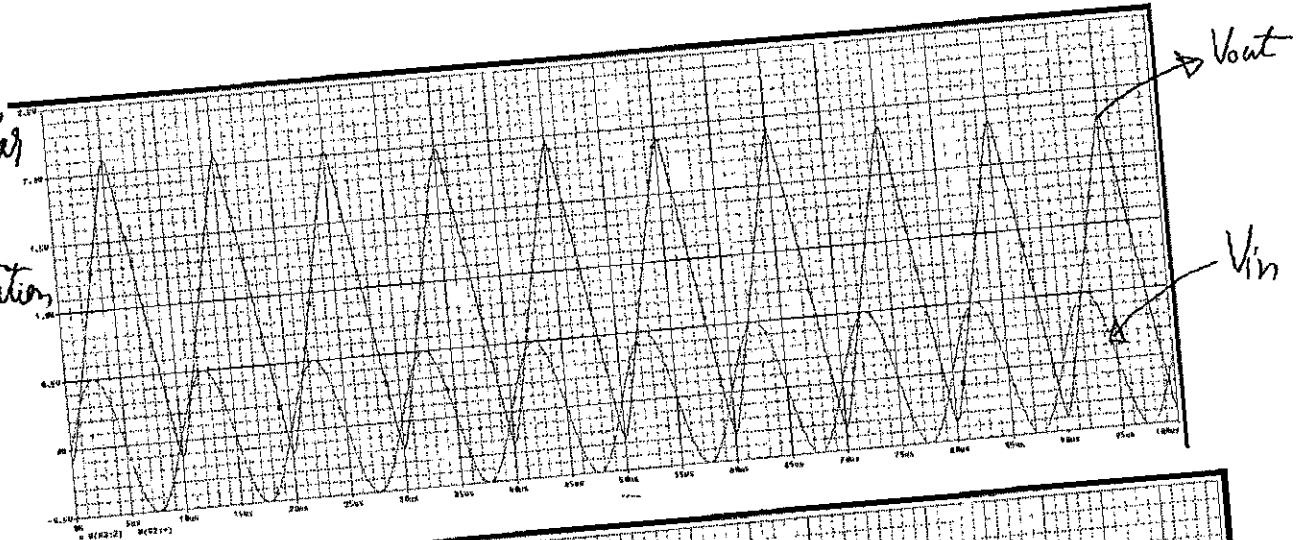11) d)

output is triangular wave due to slew rate limitation



e)

$$V_{out} = 5.16V$$

$$F_{in} = 7.2KHz$$

$$\approx F_{3dB}$$

$$gain = \frac{5V}{0.05V}$$

$$= 100$$

"very close to theoretical prediction of 92"

