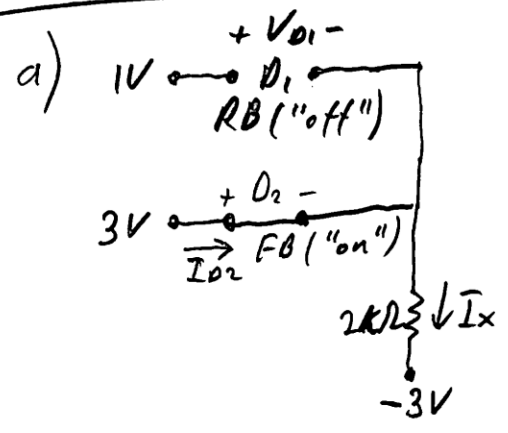


EECE 2412: HW3 Solutions


Problem 1:

$$I_x = \frac{3V - (-3V)}{2k\Omega} = \boxed{3mA = I_x}$$



$$\boxed{V_x = 3V}$$

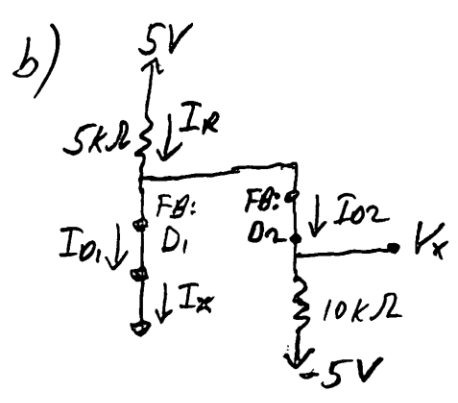checks:
 $V_{01} = 1V - 3V = -2V < 0 \rightarrow D_1$ is reverse-biased (RB)
 $I_{D2} = I_x = 3mA > 0 \rightarrow D_2$ is forward-biased (FB)



$$I_R = \frac{5V - 0V}{5k\Omega} = 1mA$$

$$I_{D2} = \frac{0V - (-5V)}{10k\Omega} = 0.5mA > 0 \rightarrow D_2 \text{ is forward-biased}$$


$$0 = I_{D1} + I_{D2} - I_R$$

$$\rightarrow I_{D1} = I_R - I_{D2} = 1mA - 0.5mA = 0.5mA$$

$I_{D1} > 0 \rightarrow D_1$ is forward-biased

$$I_{D1} = \boxed{I_x = 0.5mA}$$

$$\boxed{V_x = 0V}$$

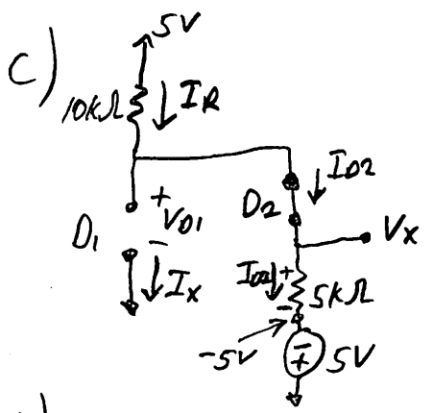


$$I_{D2} = I_R = \frac{5V - (-5V)}{10k\Omega + 5k\Omega} = 0.667mA > 0 \rightarrow D_2 \text{ is FB}$$

$$KVL: 0 = 5V - I_{D2} \cdot 5k\Omega + V_x$$

$$\rightarrow V_x = (5k\Omega)(0.667mA) - 5V = \boxed{-1.667V = V_x}$$

$$\boxed{I_x = 0}$$

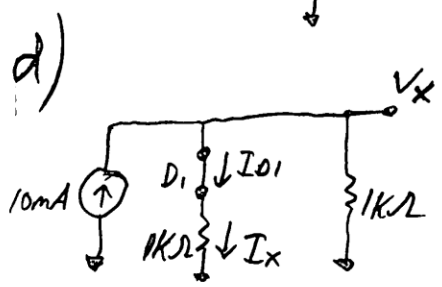check: $V_{01} = V_x - 0V = -1.667V < 0$
 $\rightarrow D_1$ is RB.




$$V_x = 10mA \cdot (1k\Omega \parallel 1k\Omega) = \boxed{5V = V_x}$$

$$I_x = I_{D1} = \frac{V_x}{1k\Omega} = \frac{5V}{1k\Omega} = \boxed{5mA = I_x}$$

check: $I_{D1} > 0 \rightarrow D_1$ is FB.

Problem 2:

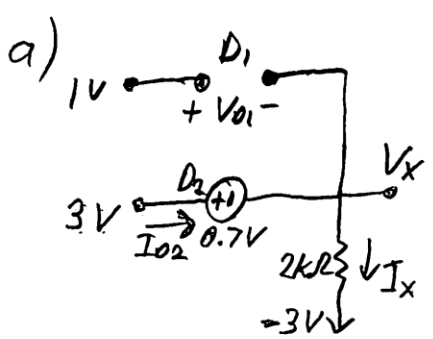


KVL: $0 = -3V + 0.7V + V_x \rightarrow V_x = 2.3V$

$I_x = \frac{V_x - (-3V)}{2k\Omega} = \frac{5.3V}{2k\Omega} = 2.65mA = I_x$

checks:

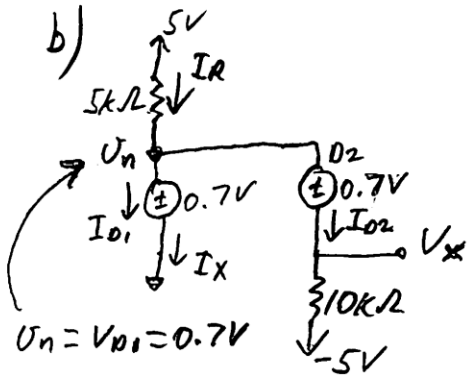$I_{02} = I_x = 2.65mA > 0 \rightarrow D_2$ is FB.
 $V_{01} = 1V - V_x = -1.3V < 0 \rightarrow D_1$ is RB.




$I_R = \frac{5V - 0.7V}{5k\Omega} = 0.86mA$

KVL: $5V = I_R \cdot 5k\Omega + 0.7V + V_x$
 $\hookrightarrow V_x = 5V - (0.86mA) \cdot (5k\Omega) - 0.7V = 0 = V_x$

$I_{02} = \frac{V_x - (-5V)}{10k\Omega} = 0.5mA > 0 \rightarrow D_2$ is FB.

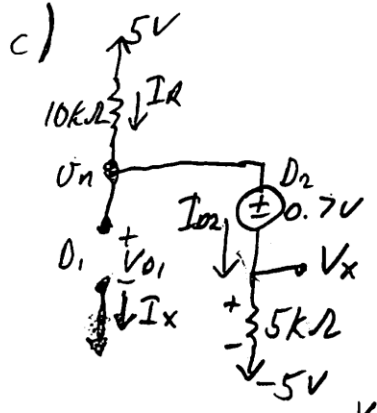$I_x = I_{01} = I_R - I_{02} = 0.86mA - 0.5mA = 0.36mA = I_x$
 $\hookrightarrow I_{01} > 0 \rightarrow D_1$ is FB.




$I_x = 0$ $I_R = I_{02}$

KVL: $5V = I_R \cdot (10k\Omega) + 0.7V + I_R \cdot (5k\Omega) - 5V$
 $\hookrightarrow I_R = 0.62mA = I_{02} > 0 \rightarrow D_2$ is FB.

KVL: $-5V = -I_R \cdot 5k\Omega + V_x$
 $\hookrightarrow V_x = -5V + (0.62mA) \cdot (5k\Omega) = -1.9V = V_x$

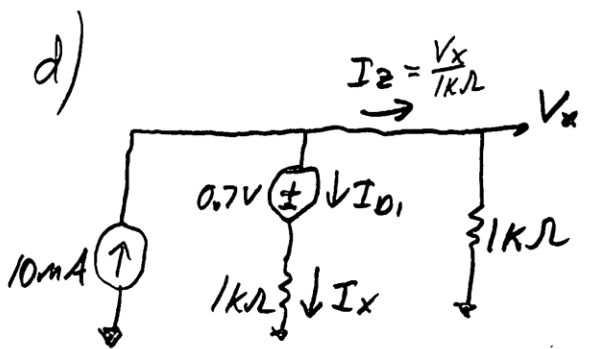$V_{01} = V_n = 5V - I_R \cdot 10k\Omega = 5V - (0.62mA) \cdot (10k\Omega) = -1.2V$
 $V_{01} < 0 \rightarrow D_1$ is RB.



from KCL, ①: $I_x + \frac{V_x}{1k\Omega} = 10mA$

from KVL, ②: $-I_x \cdot 1k\Omega - 0.7V + V_x = 0$

Solving ① and ② simultaneously results in:

$I_x = 4.65mA$ $V_x = 5.35V$

check: $I_{01} = I_x > 0 \rightarrow D_1$ is FB.

Problem 3



$$\text{KVL: } 0 = -V_{SS} + R \cdot i_d + U_d$$


$$\hookrightarrow i_d = \frac{V_{SS} - U_d}{R} = \frac{V_{SS}}{R} - \frac{U_d}{R}$$

$$\text{With } V_{SS} = 1\text{V and } R = 500\Omega: i_d = \frac{1\text{V}}{500\Omega} - \frac{U_d}{500\Omega} = 2\text{mA} - U_d \cdot 2\frac{\text{mA}}{\text{V}}$$

$$\text{With } V_{SS} = 0.5\text{V and } R = 500\Omega: i_d = 1\text{mA} - 2\frac{\text{mA}}{\text{V}} U_d$$

\hookrightarrow slope of the load line in both cases: $-\frac{2\text{mA}}{\text{V}} = -\frac{1}{R}$

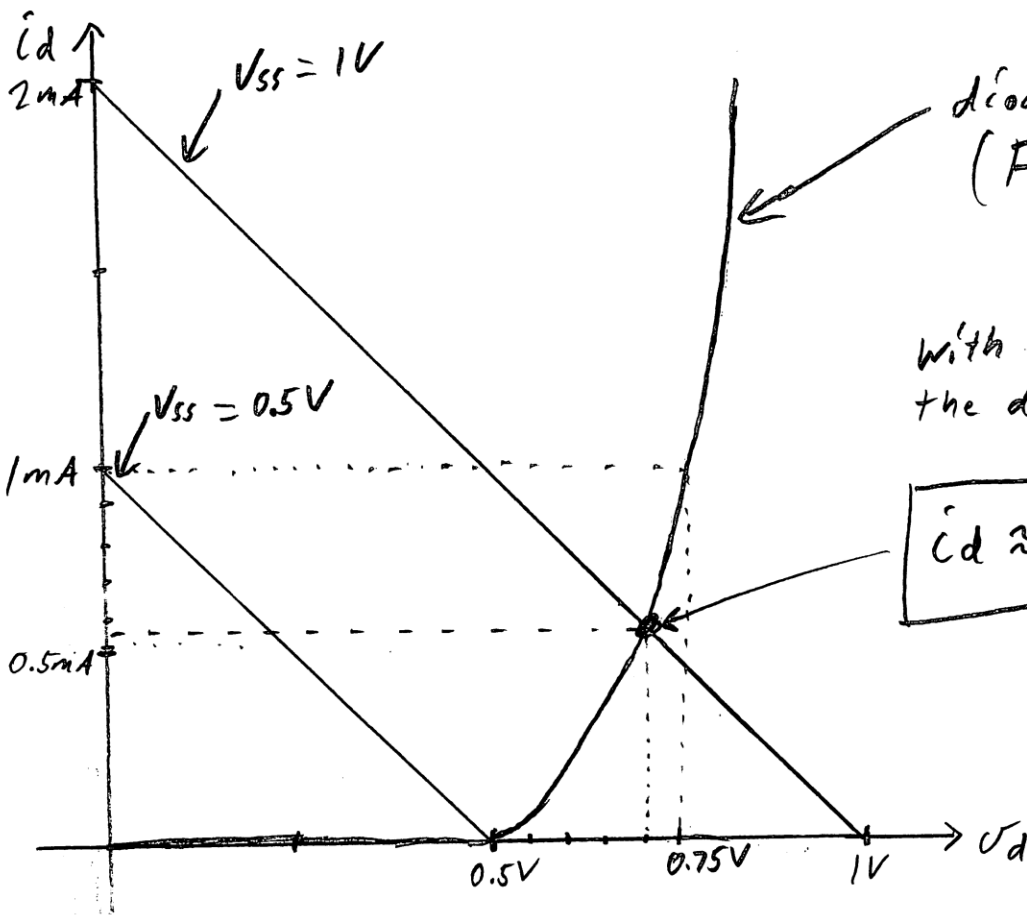\hookrightarrow No, the slope does not change when V_{SS} changes.



diode characteristics
(Fig. 3.9d)

With $V_{SS} = 1\text{V}$ and
the diode characteristics

$$i_d \approx 0.55\text{mA}$$

④ Prob. 4

a) $27^\circ\text{C} = 300\text{K}$

equation 3.16 in the book:

$$V_T = \frac{k \cdot T}{q} = \frac{(1.38 \times 10^{-23}) \cdot (300)}{1.60 \times 10^{-19}} = 25.875 \text{ mV}$$

equation 3.15 in the book:

$$I_0 = I_S \cdot \left[e^{\left(\frac{V_D}{n \cdot V_T} \right)} - 1 \right] \rightarrow V_D = n \cdot V_T \cdot \ln\left(\frac{I_0}{I_S} + 1 \right)$$

Since $\frac{I_0}{I_S} \gg 1$ is assumed here:

$$\textcircled{1}: V_D \approx n \cdot V_T \cdot \ln\left(\frac{I_0}{I_S} \right)$$

Using the two given measurement results to determine the emission coefficient:

$$V_{D2} - V_{D1} = n \cdot V_T \cdot \ln\left(\frac{I_{02}}{I_S} \right) - n \cdot V_T \cdot \ln\left(\frac{I_{01}}{I_S} \right)$$

$$V_{D2} - V_{D1} = n \cdot V_T \cdot \ln\left(\frac{I_{02}}{I_{01}} \right)$$

$$0.6 - 0.5 = n \cdot (25.875 \times 10^{-3}) \cdot \ln\left(\frac{100 \times 10^{-6}}{5 \times 10^{-6}} \right)$$

$$\rightarrow \boxed{n = 1.29}$$


b) Rearranging equation $\textcircled{1}$ above:

$$I_S = \frac{I_0}{e^{\frac{V_D}{n \cdot V_T}}} = \frac{5 \times 10^{-6}}{e^{\frac{0.5}{(1.29) \cdot (25.875 \times 10^{-3})}}}$$

$$\boxed{I_S = 1.561 \times 10^{-12} \text{ A} = 1.561 \text{ pA}}$$

Problem 5

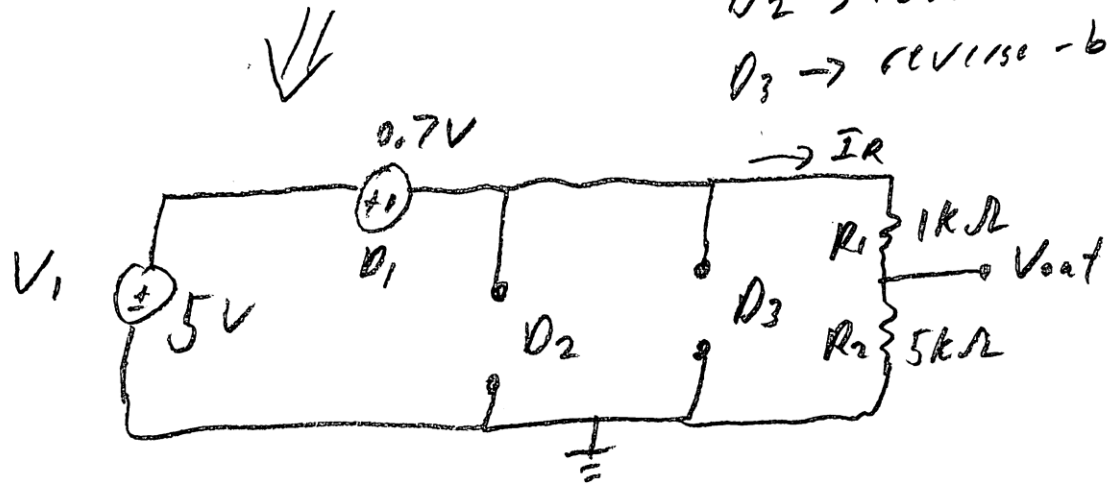a) Equivalent circuit with: $D_1 \rightarrow$ forward-biased
 $D_2 \rightarrow$ reverse-biased
 $D_3 \rightarrow$ reverse-biased



KVL: $0 = -5V + 0.7V + I_R \cdot (R_1 + R_2)$


$\hookrightarrow I_R = \frac{5V - 0.7V}{1k\Omega + 5k\Omega} = 0.717mA$

$V_{out} = I_R \cdot R_2 = (0.717mA) \cdot (5k\Omega) = 3.583V = V_{out}$

\rightarrow The value is close to the simulation result of 3.578V (see next page).

Problem 5 , Part b)

Verification with $V1 = 5V$:

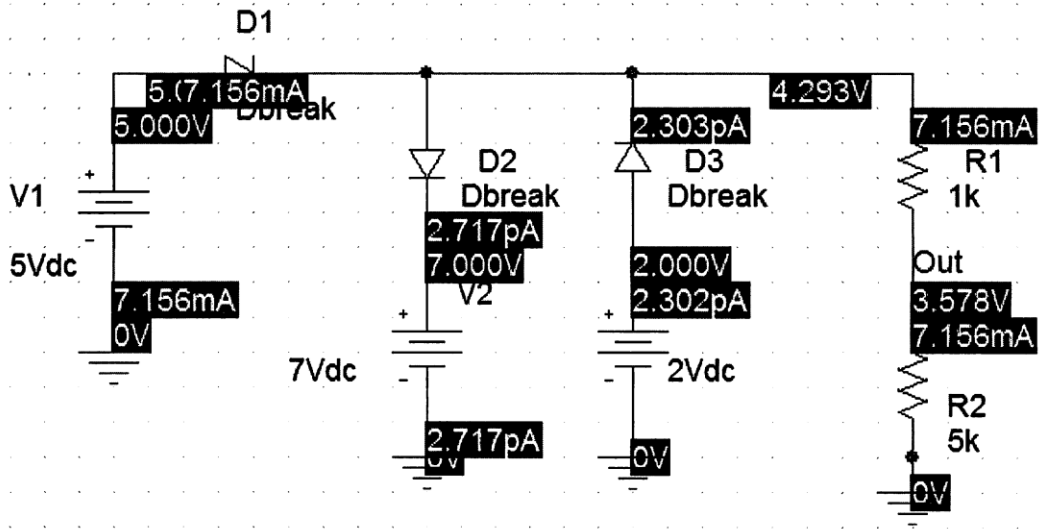

Part c) Transfer characteristic:

** Profile: "SCHEMATIC1-DC_sweep" [C:\MARVIN\NEU\Teaching\EECE 2412\EECE 2412 - Spring 2013\PSpice Fil...
 Date/Time run: 01/15/13 19:28:52 Temperature: 27.0

