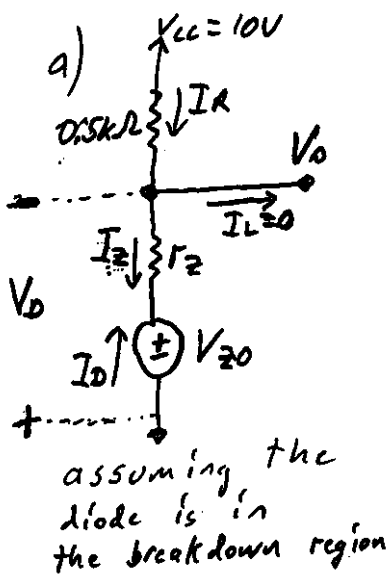


1

Prob. 1



$$I_z = \frac{V_{cc} - V_{z0}}{0.5k\Omega + r_z} = \frac{10V - 6.7V}{0.5k\Omega + 20\Omega} = 6.35mA$$

$$I_z > I_{zk} = 0.2mA \rightarrow \text{The Zener is in breakdown.}$$

$$V_o = I_z \cdot r_z + V_{z0} = (6.35mA) \cdot (20\Omega) + 6.7V$$

$V_o = 6.827V$

b) Repeating the calculation in part a) with $V_{cc} = 11V$ and $V_{cc} = 9V$:


$$V_o(max) = 6.865V$$

$$V_o(min) = 6.788V$$

$$\Delta V_o(max) = V_o(max) - V_o = 38.5mV$$

$$\Delta V_o(min) = V_o(min) - V_o = 38.5mV$$

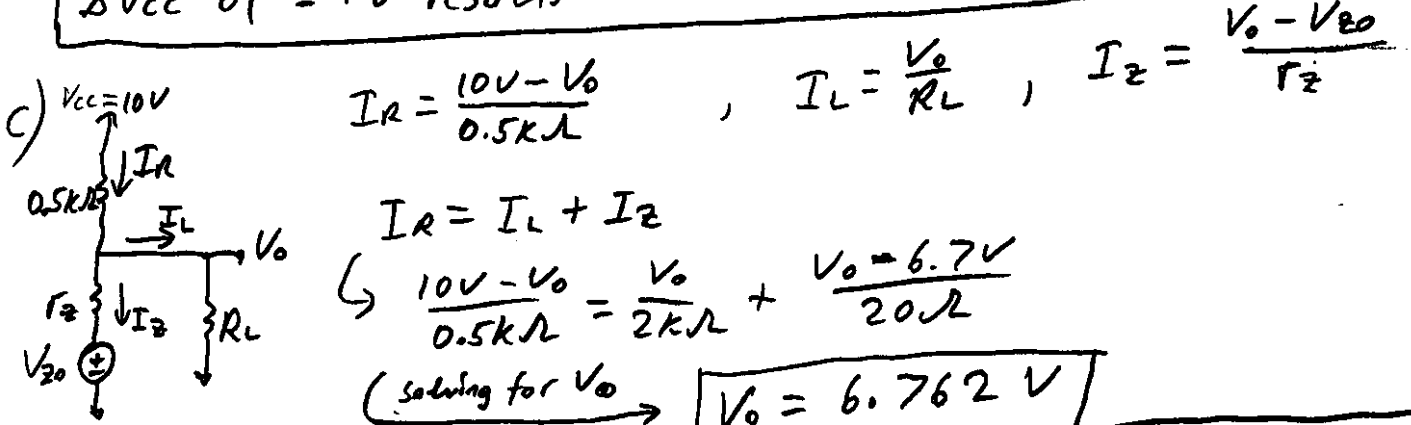ΔV_{cc} of $\pm 1V$ results in ΔV_o of $\pm 38.5mV$



$$I_R = \frac{10V - V_o}{0.5k\Omega}, \quad I_L = \frac{V_o}{R_L}, \quad I_z = \frac{V_o - V_{z0}}{r_z}$$

$$I_R = I_L + I_z$$

$$\hookrightarrow \frac{10V - V_o}{0.5k\Omega} = \frac{V_o}{2k\Omega} + \frac{V_o - 6.7V}{20\Omega}$$

(solving for V_o) $V_o = 6.762V$

$\Delta V_o = 6.762V - 6.827V = -65mV = \Delta V_o$

check: $I_z = \frac{6.762V - 6.7V}{20\Omega} = 3.1mA > I_{zk} \rightarrow$ The Zener is in breakdown.

d) Repeating the analysis in c) with $R_L = 0.5k\Omega$ results in:


$V_o = 6.574V$
 Diode assumption check: $I_z = \frac{6.574V - 6.7V}{20\Omega} = -6.3mA < I_{zk}$

\rightarrow does not satisfy the breakdown region condition

Assuming that the diode is reverse-biased ("off"):

$$V_o = 10V \cdot \left(\frac{R_L}{R_L + 0.5k\Omega} \right) = 10V \cdot \left(\frac{0.5k\Omega}{0.5k\Omega + 0.5k\Omega} \right) = 5V = V_o$$

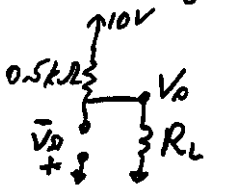check: reverse bias requires that $-V_{z0} = -6.7V < V_o < V_{do} \approx 0.7V$
 \hookrightarrow satisfied because $V_o = -V_o = -5V$



$\Delta V_o = 5V - 6.827V$
 $\Delta V_o = -1.827V$

... Prob. 1 cont.:

e) Using the same diagram as in part c):

$I_{ZK} = 0.2 \text{ mA}$ at the edge of the breakdown region

$$I_{ZK} = 0.2 \text{ mA} = \frac{V_0 - V_{Z0}}{r_z} = \frac{V_0 - 6.7 \text{ V}}{20}$$

$$\rightarrow V_0 = 6.704 \text{ V}$$

$$I_{ZK} = 0.2 \text{ mA} = I_R - I_L$$

$$0.2 \text{ mA} = \frac{V_{CC} - V_0}{0.5 \text{ k}\Omega} - \frac{V_0}{R_L(\text{min.})} = \frac{V_{CC} - 6.704}{500} - \frac{6.704}{R_L(\text{min.})}$$

$$\text{with } V_{CC} = 11 \text{ V} \rightarrow R_L(\text{min.}) = 798.9 \Omega$$

$$\text{with } V_{CC} = 9 \text{ V} \rightarrow R_L(\text{min.}) = 1.526 \text{ k}\Omega$$


$$R_L(\text{min.}) = 1.526 \text{ k}\Omega$$

ensures $I_Z > 0.2 \text{ mA} = I_{ZK}$
(over the complete range of V_{CC})

Prob. 2

for $0 < V_s < 1.4167 \text{ V}$:

D_1 off, D_2 on

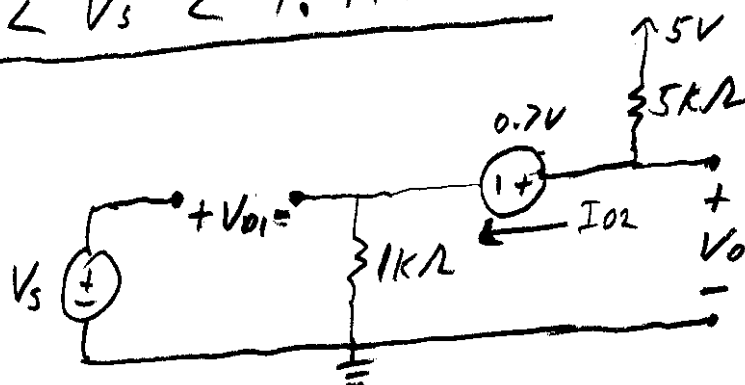

KVL:

$$0 = -I_{02} \cdot 1\text{k}\Omega - 0.7\text{V} - I_{02} \cdot 5\text{k}\Omega + 5\text{V}$$

$$I_{02} = \frac{5\text{V} - 0.7\text{V}}{6\text{k}\Omega} = 0.7167 \text{ mA} > 0 \rightarrow D_2 \text{ is on}$$

$$V_o = 0.7\text{V} + I_{02} \cdot 1\text{k}\Omega = \underline{1.4167 \text{ V} = V_o}$$

D_1 turns on when $V_{o1} \geq 0.7 \text{ V}$:

$$0 = -V_{s(\text{max})} + V_{o1(\text{max})} - 0.7\text{V} + V_o$$

$$\rightarrow V_{s(\text{max})} = 0.7\text{V} - 0.7\text{V} + V_o = 1.4167 \text{ V}$$


for $1.4167 \text{ V} < V_s < 5 \text{ V}$:

D_1 on, D_2 on

$$0 = -V_s + 0.7\text{V} + V_x$$

$$\rightarrow V_x = V_s - 0.7\text{V}$$
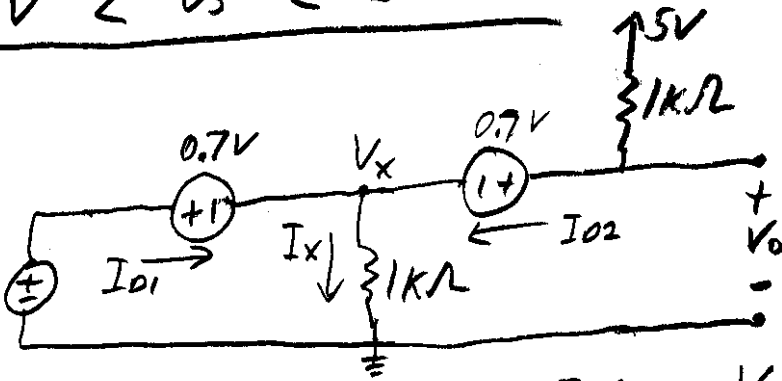
$$I_x = \frac{V_x}{1\text{k}\Omega} = \frac{V_s - 0.7\text{V}}{1\text{k}\Omega}$$



$$0 = -V_o + 0.7\text{V} + V_x \rightarrow V_o = 0.7\text{V} + V_s - 0.7\text{V} = \underline{V_s = V_o}$$

D_2 is on when $I_{02} > 0$:

$$I_{02} = \frac{5\text{V} - V_o}{5\text{k}\Omega} > 0 \rightarrow I_{02} > 0 \text{ requires } V_o = V_s < 5\text{V}$$

$\rightarrow D_2$ is on in this range of V_s

D_1 is on when $I_{01} > 0$:


$$I_{01} = I_x - I_{02} = \frac{V_s - 0.7\text{V}}{1\text{k}\Omega} - \frac{5\text{V} - V_o}{5\text{k}\Omega} = \frac{V_s - 0.7\text{V}}{1\text{k}\Omega} - \frac{5\text{V} - V_s}{5\text{k}\Omega}$$

$\rightarrow I_{01} > 0$ is ensured when $V_s > 1.4167\text{V} \rightarrow D_1$ is on in this range of V_s

... Prob. 2 continued:

for $5V < V_s < 10V$:

D_1 on, D_2 off

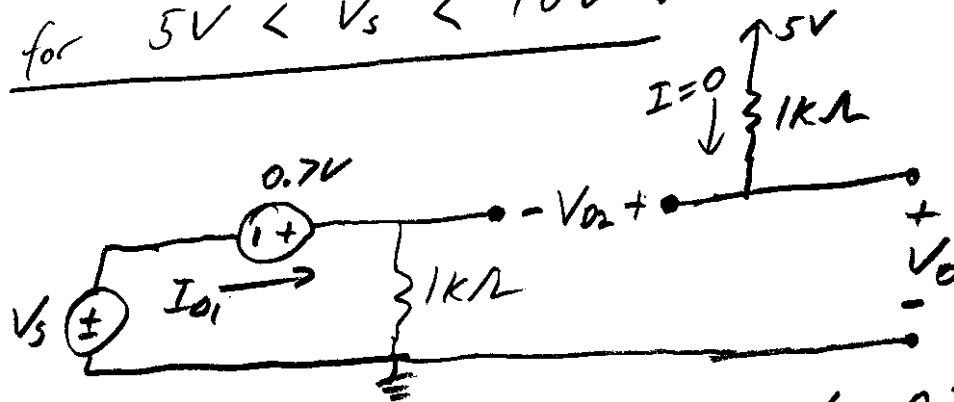

$$0 = -V_s + 0.7V + I_{o1} \cdot 1k\Omega \rightarrow I_{o1} = \frac{V_s - 0.7V}{1k\Omega}$$

check: $I_{o1} > 0$ for $V_s > 0.7V \rightarrow D_1$ is on for this range of V_s


$$0 = -V_o - 5k\Omega \cdot 0 + 5V \rightarrow \underline{V_o = 5V}$$

check: $0 = -I_{o1} \cdot 1k\Omega - V_{o2} + V_o$


$$\rightarrow V_{o2} = V_o - I_{o1} \cdot 1k\Omega = 5V - \frac{V_s - 0.7V}{1k\Omega} \cdot 1k\Omega$$

$$V_{o2}(\min) = 5V - \frac{5V - 0.7V}{1k\Omega} \cdot 1k\Omega = 0.7V$$

$\rightarrow D_2$ is off for $V_s > V_{s(\min)} = 5V$

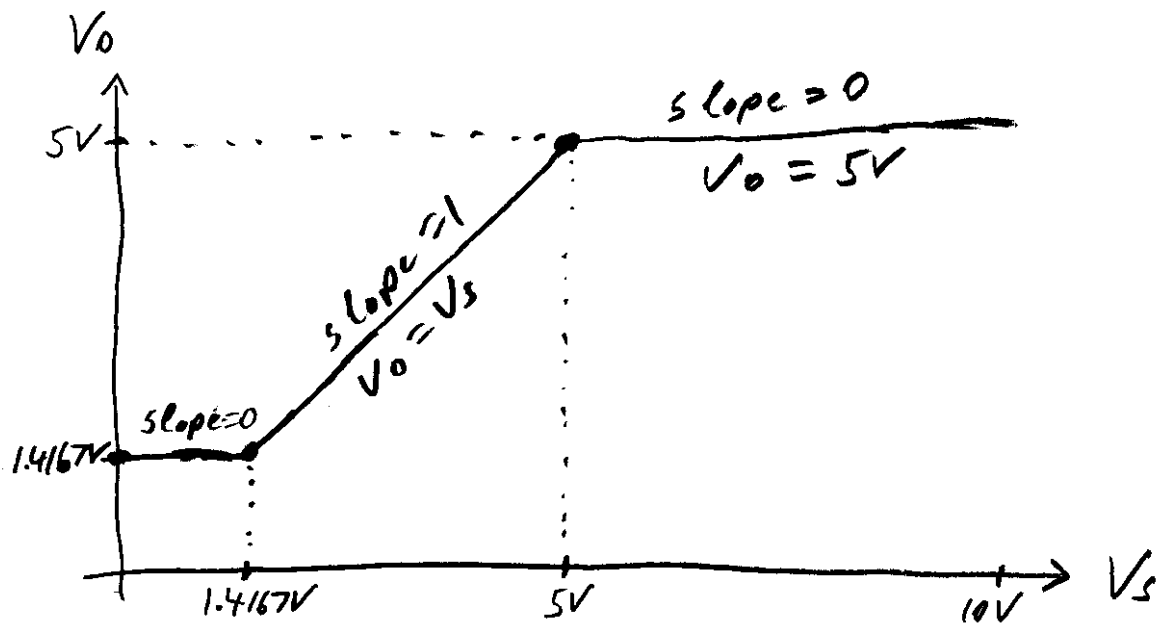

Prob. 3

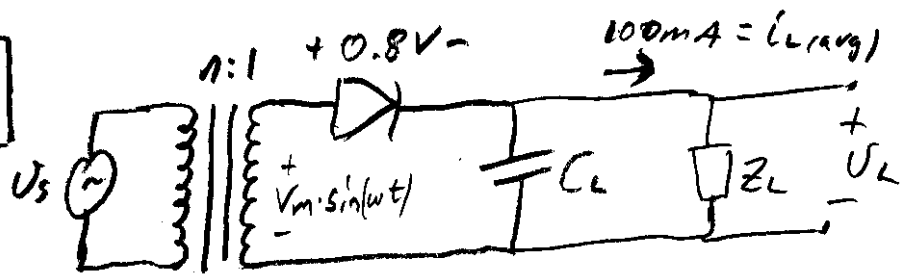

1.) $V_L(\text{avg}) = 9V \pm 1V \text{ ripple}$
 (2V peak-peak) \rightarrow

$$V_L(\text{min}) = 8V$$

$$V_L(\text{max}) = 10V$$

2.) KVL:

$$V_L(\text{peak}) = -0.8V + V_m = 10V \rightarrow$$

$$V_m = 10.8V$$

3.) $V_s(\text{peak}) = V_s(\text{RMS}) \cdot \sqrt{2} = 110V \cdot \sqrt{2} = 155.563V$

$$n = \frac{V_s(\text{peak})}{V_m} = \frac{155.563V}{10.8V} = 14.4 = n$$

4.) Using equation 3.4 in the book:

$$C = \frac{i_L(\text{avg}) \cdot T}{V_r} = \frac{(100mA) \cdot (1/60\text{Hz})}{2V}$$

$$C = 833.3 \mu F$$

Problem 4:

a) DC equivalent circuit:

$$I_{DQ} = \frac{15V - 0.6V}{1k\Omega} = 14.4mA$$



AC equivalent circuit:

$$r_d = \frac{n \cdot V_T}{I_{DQ}} = \frac{1.26mV}{14.4mA}$$

$$r_d = 1.806\Omega$$

total output voltage:
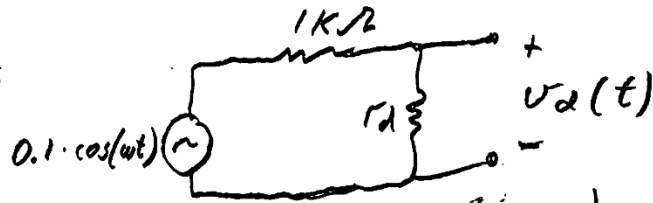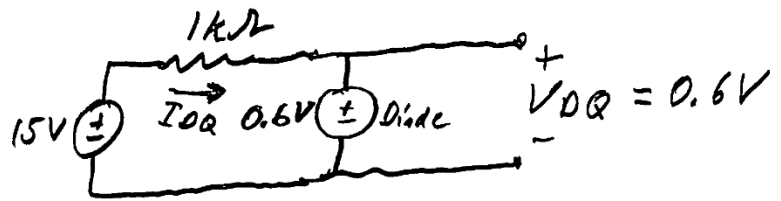
$$V_D(t) = V_{DQ} + v_d(t) = 0.6V + 0.18 \times 10^{-3}V \cdot \cos(\omega t)$$



$$v_d(t) = 0.1 \cdot \cos(\omega t) \times \left(\frac{r_d}{r_d + 1k\Omega} \right) = 0.18 \times 10^{-3}V \cdot \cos(\omega t)$$


b) Source regulation = $\frac{\Delta V_o}{\Delta V_{SS}} \times 100\%$

In part a), the change of the source voltage is $\Delta V_{SS} = 0.1V \cos(\omega t)$, while $\Delta V_o = v_d(t) = 0.18 \times 10^{-3}V \cdot \cos(\omega t)$.


Thus, source regulation = $\frac{0.18 \times 10^{-3}V \cdot \cos(\omega t)}{0.1V \cdot \cos(\omega t)} \times 100\% = 0.18\%$

Problem 5


Schematic:

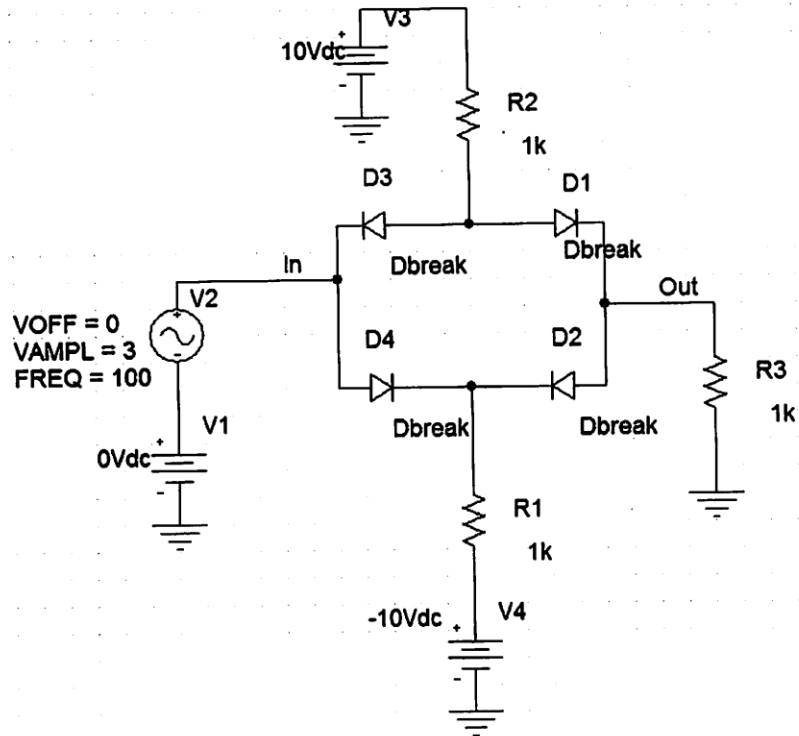

Transfer characteristic:

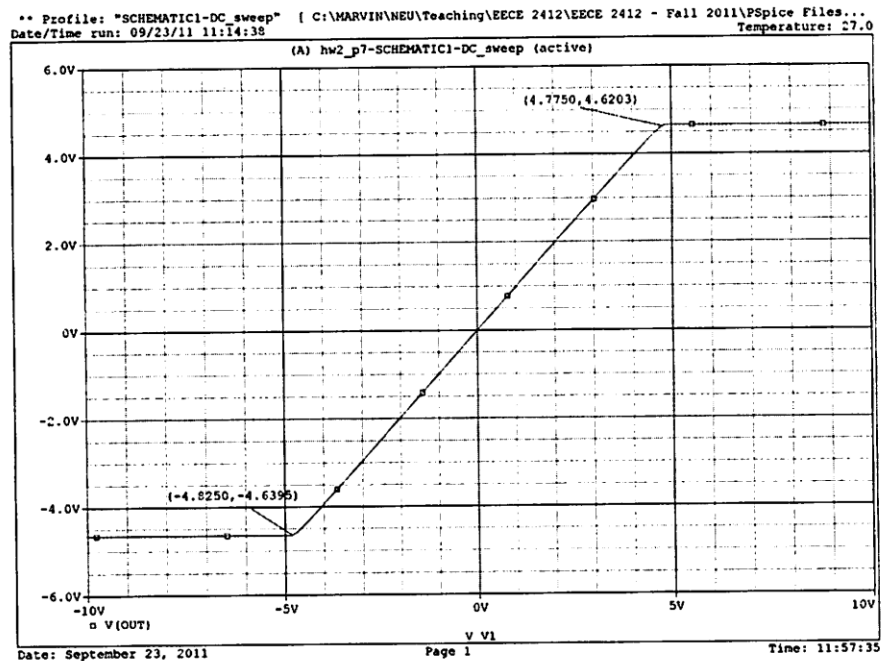
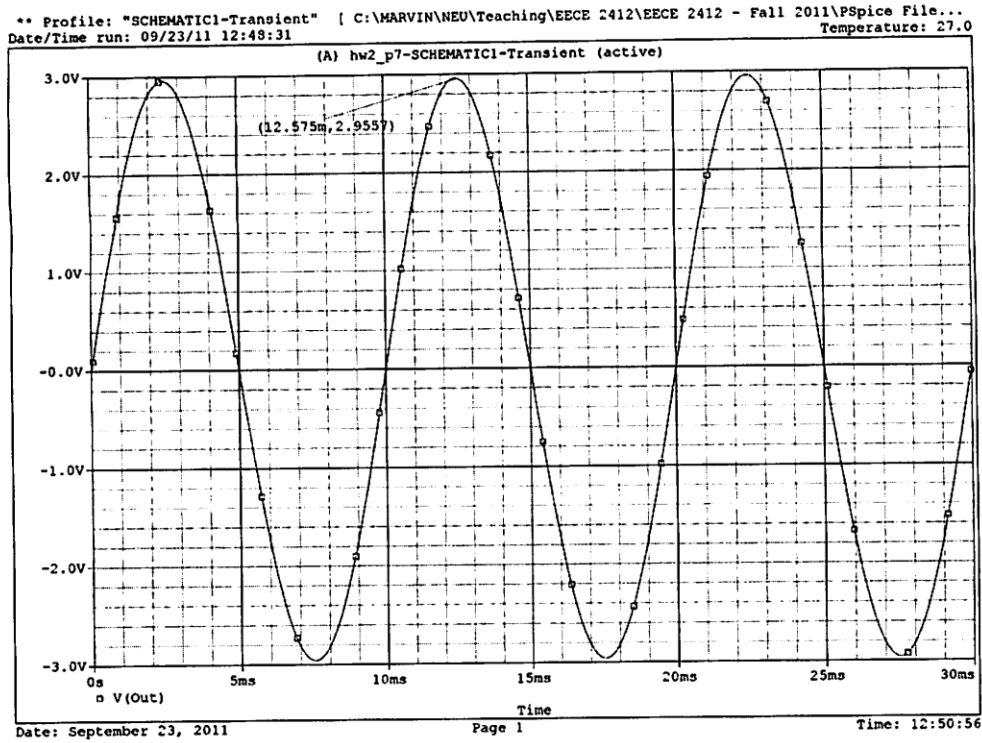
$$V_o(t) \text{ with } V_{in}(t) = 3V \cdot \sin(200\pi t):$$



$$V_o(t) \text{ with } V_{in}(t) = 10V \cdot \sin(200\pi t):$$

