

(P.1)

EECE - HW 5 SolutionsProblem 1:

a) $n \gg p$, therefore: $n + N_A = p + N_D \approx N_D$
 $\rightarrow n \approx N_D - N_A = 10^{17} \text{ cm}^{-3} - 10^{15} \text{ cm}^{-3} = 9.9 \times 10^{16} \text{ cm}^{-3} = n$

$$p = \frac{n_i^2}{n} = \frac{(1.45 \times 10^{10} \text{ cm}^{-3})^2}{9.9 \times 10^{16} \text{ cm}^{-3}} = 2.124 \times 10^{-3} \text{ cm}^{-3} = p$$

b) $N_A = N_D \rightarrow n = p = n_i = 1.45 \times 10^{10} \text{ cm}^{-3}$

Problem 2

equation 4.1: $i_E = I_{ES} \cdot (e^{\frac{V_{BE}}{V_T}} - 1)$

$$V_{BE} = V_T \cdot \ln\left(\frac{i_E}{I_{ES}} + 1\right) = 26 \times 10^{-3} \cdot \ln\left(\frac{10 \times 10^{-3}}{10^{-13}} + 1\right)$$

$$V_{BE} = 658.54 \text{ mV}$$

From page 212 in the book:

$$V_{BC} = V_{BE} - V_{CE} = 0.65854 \text{ V} - 10 \text{ V} = -9.341 \text{ V} = V_{BC}$$

The transistor operates in the active region because $V_{CE} > 0.2 \text{ V}$


and $i_B = (1 - \alpha) \cdot i_E > 0$, where $\alpha = \frac{\beta}{1 + \beta} = \frac{100}{101} = 0.990099 = \alpha$

$$i_B = (1 - 0.990099) \cdot 10 \times 10^{-3} \text{ A} = 99.0099 \mu\text{A} = i_B$$

$$i_C = \alpha \cdot i_E = 0.990099 \times 10 \text{ mA} = 9.90099 \text{ mA} = i_C$$

(p.2) Problem 3

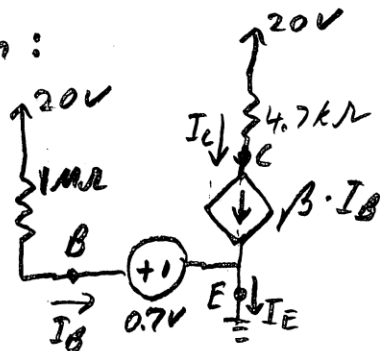a) $\beta = 100$, equivalent circuit assuming operation in the active region:



$$I_B = \frac{20V - 0.7V}{1 \times 10^6 \Omega} = 19.3 \mu A$$

check: $I_B > 0$
(condition 1)

$$I_C = \beta I_B = 100 \cdot I_B = 1.93 mA$$


$$I_C = 1.93 mA$$

$$V_C = 20V - I_C \cdot 4.7k\Omega = 10.929V$$

$$V_{CE} = V_C - 0V = 10.93V = V_{CE}$$

check 2: $V_{CE} > 0.2V \rightarrow$ confirms active mode

$\beta = 300$, assuming saturation:

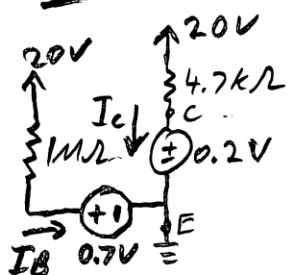

$$I_B = \frac{20V - 0.7V}{1 \times 10^6 \Omega} = 19.3 \mu A > 0 \quad (\text{condition 1 is met})$$


$$I_C = \frac{20V - 0.2V}{4.7 \times 10^3 \Omega} = 4.213 mA = I_C$$

check condition 2: $\beta \cdot I_B > I_C > 0$

$$V_{CE} = 0.2V \quad \hookrightarrow 5.79 mA > 4.213 mA > 0$$

Confirms saturation mode

b) $\beta = 100$, assuming active:

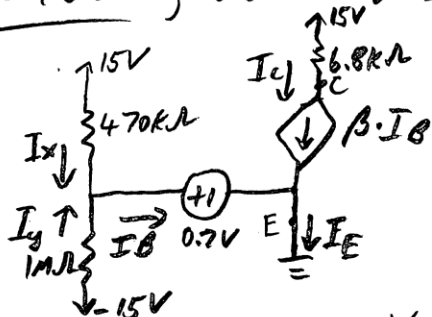

$$I_x = \frac{15V - 0.7V}{470 \times 10^3 \Omega} = 30.426 \mu A$$

$$I_y = \frac{-15V - 0.7V}{1 \times 10^6 \Omega} = -15.7 \mu A$$

$$I_B = I_x + I_y = 14.73 \mu A > 0 \quad (\text{condition 1 is met})$$

$$I_C = \beta \cdot I_B = 1.473 mA = I_C$$


$$V_C = 15V - I_C \times 6.8k\Omega = 4.987V$$

$$V_{CE} = V_C - 0V = 4.987V = V_{CE}$$

$V_{CE} > 0.2V \rightarrow$ confirms active mode

P.3 ... Problem 3 cont.:

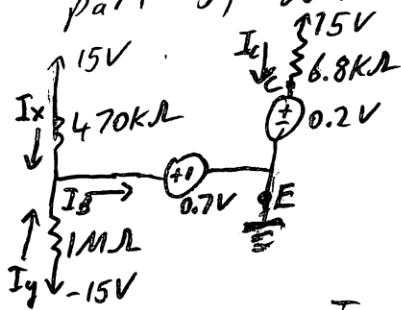part b) with $\beta = 300$, assuming saturation:



$$I_x = \frac{15V - 0.7V}{470k\Omega} = 30.426 \mu A$$

$$I_y = \frac{-15V - 0.7V}{1M\Omega} = -15.7 \mu A$$

$$I_B = I_x + I_y = 14.73 \mu A > 0 \quad (\text{condition 1 is met})$$


$$I_C = \frac{15V - 0.2V}{6.8k\Omega} = \boxed{2.176 \text{ mA} = I_C}$$

$$\boxed{V_{CE} = 0.2V}$$

The BJT is in saturation because condition 2 is satisfied:

$$\beta \cdot I_B > I_C > 0 \rightarrow 4.419 \text{ mA} > 2.176 \text{ mA} > 0$$

c) $\beta = 100$, assuming cutoff:

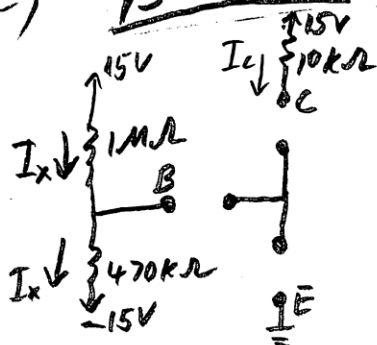

$$I_x = \frac{15V - (-15V)}{1M\Omega + 470k\Omega} = 20.408 \mu A$$

$$V_B = 15V - I_x \cdot 1M\Omega = -5.408V$$

$$V_{BE} = V_B - V_E = -5.408V < 0.5V$$

↳ condition 1 is satisfied


$$V_{BC} = V_B - V_C = -5.408V - 15V = -20.408V$$

↳ condition 2 is met → confirms cutoff

$$\boxed{I_C = 0}$$

$$V_{CE} = V_C - 0V = \boxed{15V = V_{CE}}$$

$\beta = 300$, assuming cutoff:

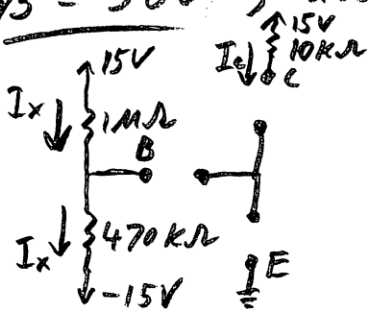

→ same analysis as with $\beta = 300$


$$\boxed{I_C = 0}$$

$$\boxed{V_{CE} = 15V}$$

p.4

... Problem 3 cont.:

d) $\beta = 100$, assuming active:

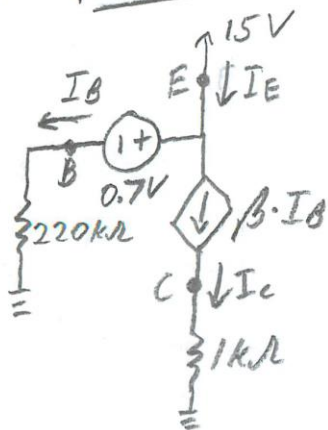

KVL: $0 = -I_B \cdot 220k\Omega - 0.7V + 15V$
 $\rightarrow I_B = \frac{15V - 0.7V}{220 \times 10^3 \Omega} = 65 \times 10^{-6} A$

$I_B > 0 \rightarrow$ condition 1 is met


$I_C = \beta \cdot I_B = 100 \cdot 65 \mu A = \boxed{6.5 mA = I_C}$

$V_C = I_C \cdot 1k\Omega = 6.5V$

$V_{CE} = V_C - V_E = 6.5V - 15V = \boxed{-8.5V = V_{CE}}$

check of condition 2: $V_{CE} < -0.2V \rightarrow$ confirms active mode

$\beta = 300$, assuming saturation:

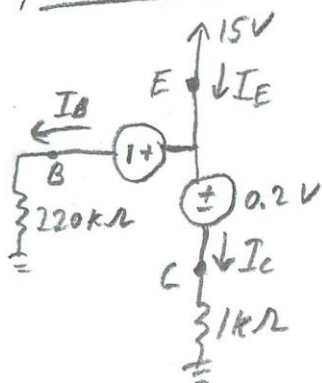

$I_B = \frac{15V - 0.7V}{220k\Omega} = 65 \mu A > 0$ (condition 1 is met)

KVL: $0 = -15V + 0.2V + I_C \cdot 1k\Omega$
 $\rightarrow I_C = \frac{15V - 0.2V}{1000 \Omega} = \boxed{14.8 mA = I_C}$

check for condition 2:

$\beta \cdot I_B > I_C > 0$

$19.5 mA > 14.8 mA > 0 \rightarrow$ confirms saturation

$V_C = 14.8 mA \cdot 1k\Omega = 14.8V$

$V_{CE} = V_C - V_E = 14.8V - 15V = -0.2V$


$\boxed{V_{CE} = -0.2V}$

5

Problem 4

$$I_B = \frac{4.3V - 2.3V}{20k\Omega} = 100\mu A$$

$$I_x = \frac{2.3V}{230\Omega} = 10mA$$

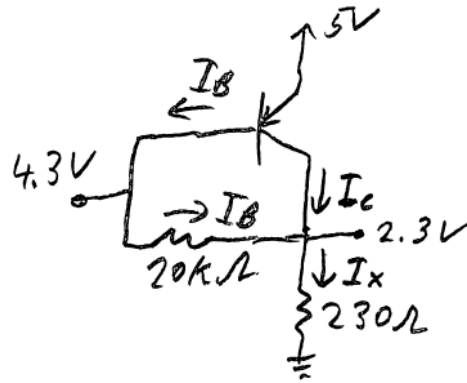

$$\text{KCL: } I_x = I_B + I_C$$

$$\hookrightarrow I_C = I_x - I_B = 10mA - 100\mu A = 9.9mA$$

$$\beta = \frac{I_C}{I_B} = \frac{9.9mA}{100\mu A} = \boxed{99 = \beta}$$

Problem 5, Part b)


Part b)

Qbreakn:

$$\beta_{oc} = \frac{9.169 \text{ mA}}{45.84 \mu\text{A}}$$

$$\beta_{oc} = 200.02$$

**** BJT MODEL PARAMETERS

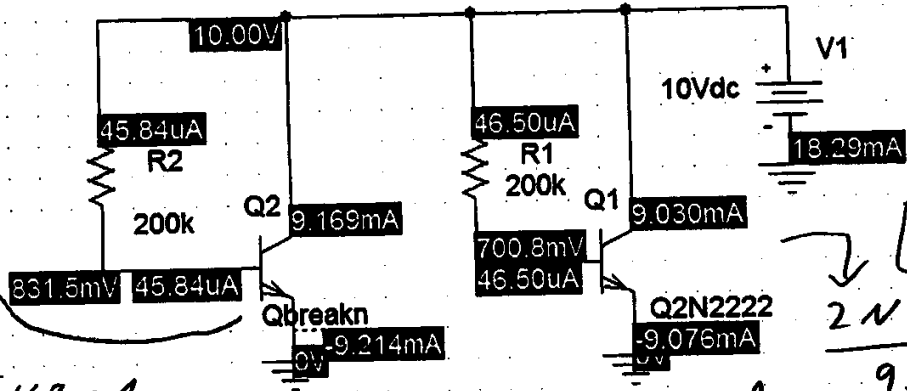

Part a)

2N2222:

$$\beta_{oc} = \frac{9.03 \text{ mA}}{46.50 \mu\text{A}}$$

$$\beta_{oc} = 194.2$$

Problem 5, Part c)

Qbreakn	Q2N2222
NPN	NPN
IS	100.000000E-18 14.340000E-15
BF	200 255.9
NF	1 1
VA	74.03
IKF	.2847
ISE	14.340000E-15
NE	1.307
BR	1 6.092
NR	1 1
RB	10
RC	1
CJE	22.010000E-12
MJE	.377
CJC	7.306000E-12
MJC	.3416
TF	411.100000E-12
XTF	3
VTF	1.7
ITF	.6
TR	46.910000E-09
XTB	1.5
CN	2.42 2.42
D	.87 .87

part c

7

**** OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

**** BIPOLAR JUNCTION TRANSISTORS

NAME	Q_Q1	Q_Q2
MODEL	Q2N2222	Qbreakn
IB	4.65E-05	4.58E-05
IC	9.03E-03	9.17E-03
VBE	7.01E-01	8.32E-01
VBC	-9.30E+00	-9.17E+00
VCE	1.00E+01	1.00E+01

part c)

→ **BETADC** 1.94E+02 2.00E+02

GM	3.40E-01	3.54E-01
RPI	5.99E+02	5.64E+02
RX	1.00E+01	0.00E+00
RO	9.23E+03	1.00E+12
CBE	1.78E-10	0.00E+00
CBC	3.01E-12	0.00E+00
CJS	0.00E+00	0.00E+00

→ **BETAAC** 2.04E+02 2.00E+02

CBX/CBX2	0.00E+00	0.00E+00
FT/FT2	2.99E+08	5.64E+18

NPN switching transistors

2N2222; 2N2222A

CHARACTERISTICS

 $T_J = 25\text{ }^\circ\text{C}$ unless otherwise specified.

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
I_{CBO}	collector cut-off current 2N2222	$I_E = 0; V_{CB} = 50\text{ V}$	-	10	nA
		$I_E = 0; V_{CB} = 50\text{ V}; T_{amb} = 150\text{ }^\circ\text{C}$	-	10	μA
I_{CBO}	collector cut-off current 2N2222A	$I_E = 0; V_{CB} = 60\text{ V}$	-	10	nA
		$I_E = 0; V_{CB} = 60\text{ V}; T_{amb} = 150\text{ }^\circ\text{C}$	-	10	μA
I_{EBO}	emitter cut-off current	$I_C = 0; V_{EB} = 3\text{ V}$	-	10	nA
h_{FE}	DC current gain \uparrow β_{DC}	$I_C = 0.1\text{ mA}; V_{CE} = 10\text{ V}$	35	-	
		$I_C = 1\text{ mA}; V_{CE} = 10\text{ V}$	50	-	
		$I_C = 10\text{ mA}; V_{CE} = 10\text{ V}$	75	-	
		$I_C = 150\text{ mA}; V_{CE} = 1\text{ V}; \text{note 1}$	50	-	
		$I_C = 150\text{ mA}; V_{CE} = 10\text{ V}; \text{note 1}$	100	300	
h_{FE}	DC current gain 2N2222A	$I_C = 10\text{ mA}; V_{CE} = 10\text{ V}; T_{amb} = -55\text{ }^\circ\text{C}$	35	-	
h_{FE}	DC current gain 2N2222 2N2222A	$I_C = 500\text{ mA}; V_{CE} = 10\text{ V}; \text{note 1}$	30	-	
			40	-	
V_{CEsat}	collector-emitter saturation voltage 2N2222	$I_C = 150\text{ mA}; I_B = 15\text{ mA}; \text{note 1}$	-	400	mV
		$I_C = 500\text{ mA}; I_B = 50\text{ mA}; \text{note 1}$	-	1.6	V
V_{CEsat}	collector-emitter saturation voltage 2N2222A	$I_C = 150\text{ mA}; I_B = 15\text{ mA}; \text{note 1}$	-	300	mV
		$I_C = 500\text{ mA}; I_B = 50\text{ mA}; \text{note 1}$	-	1	V
V_{BEsat}	base-emitter saturation voltage 2N2222	$I_C = 150\text{ mA}; I_B = 15\text{ mA}; \text{note 1}$	-	1.3	V
		$I_C = 500\text{ mA}; I_B = 50\text{ mA}; \text{note 1}$	-	2.6	V
V_{BEsat}	base-emitter saturation voltage 2N2222A	$I_C = 150\text{ mA}; I_B = 15\text{ mA}; \text{note 1}$	0.6	1.2	V
		$I_C = 500\text{ mA}; I_B = 50\text{ mA}; \text{note 1}$	-	2	V
C_c	collector capacitance	$I_E = I_C = 0; V_{CB} = 10\text{ V}; f = 1\text{ MHz}$	-	8	pF
C_e	emitter capacitance 2N2222A	$I_C = I_E = 0; V_{EB} = 500\text{ mV}; f = 1\text{ MHz}$	-	25	pF
f_T	transition frequency 2N2222 2N2222A	$I_C = 20\text{ mA}; V_{CE} = 20\text{ V}; f = 100\text{ MHz}$	250	-	MHz
			300	-	MHz
F	noise figure 2N2222A	$I_C = 200\text{ }\mu\text{A}; V_{CE} = 5\text{ V}; R_S = 2\text{ k}\Omega;$ $f = 1\text{ kHz}; B = 200\text{ Hz}$	-	4	dB

temperature \rightarrow

beta:

for this case \rightarrow

notice the variation