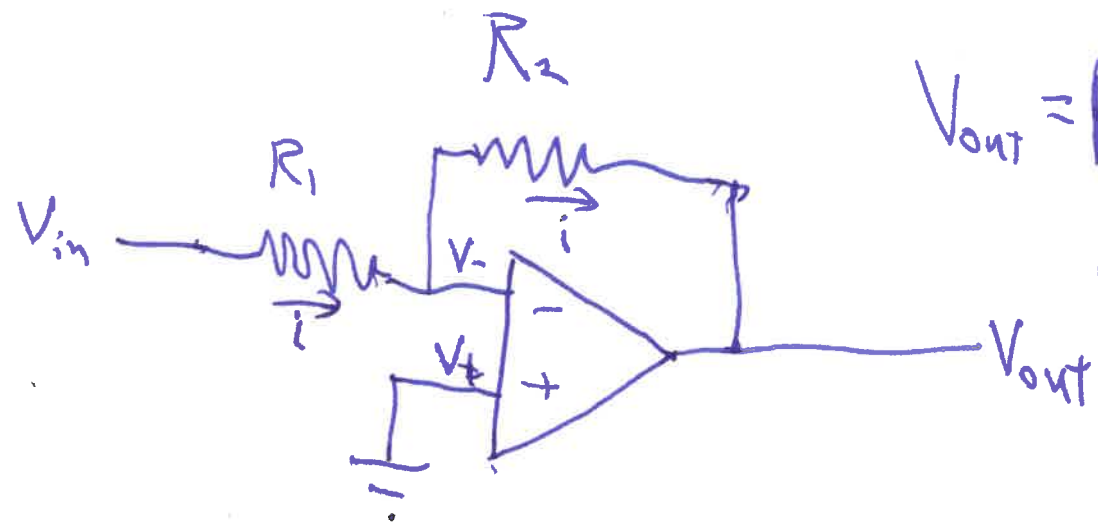


Thu 19 Jun 17

①




$$V_{out} = A_{oc}(V_+ - V_-)$$

$$A_{oc} \rightarrow \infty$$


$$i \Rightarrow \frac{V_{in} - V_-}{R_1} = \frac{V_- - V_{out}}{R_2}$$


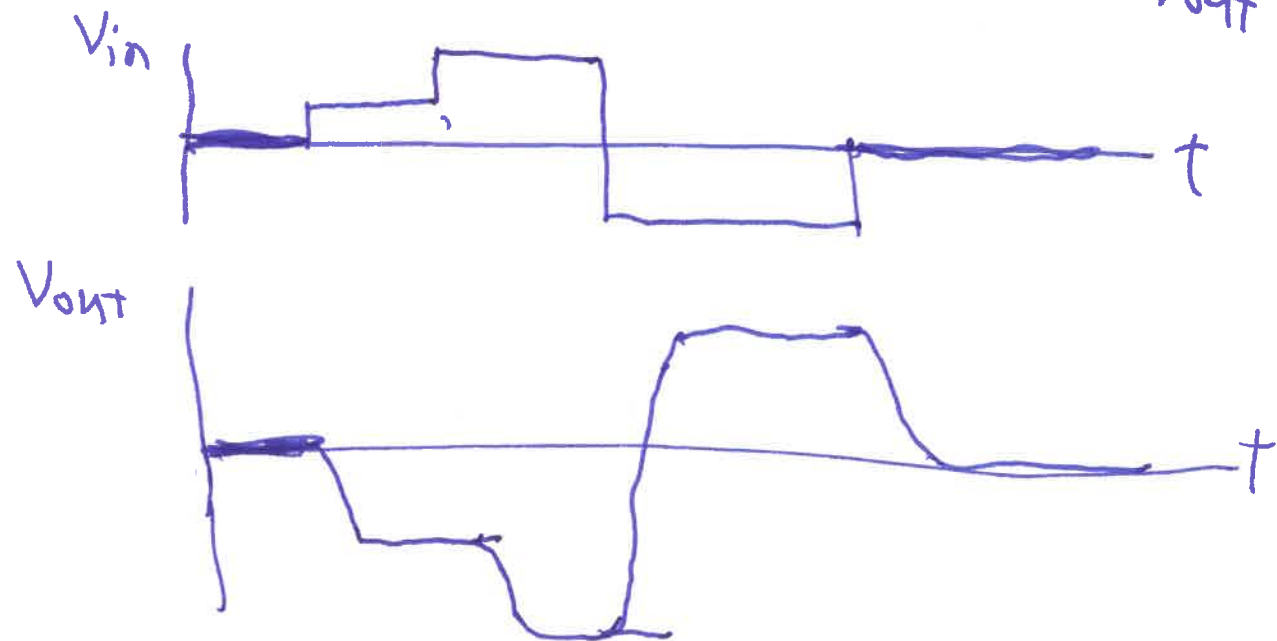
$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$




2

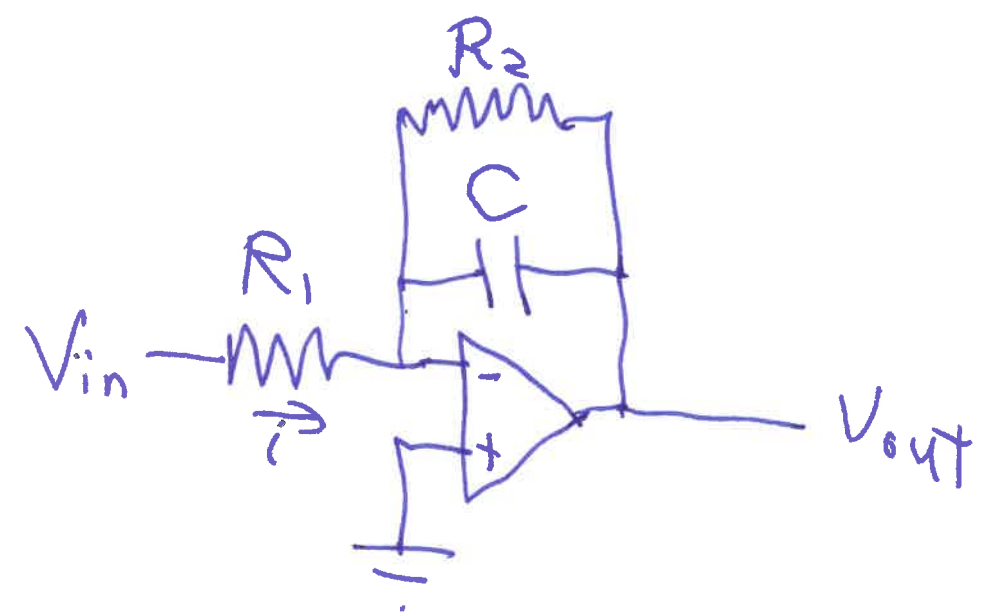

$$i = \frac{V_{in}}{R_1} = \frac{-V_{out}}{R_2 \parallel \frac{1}{j\omega C}}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{-R_2}{R_1 R_2 j\omega C + R_1}$$

$$A_v(0) = -R_2/R_1$$

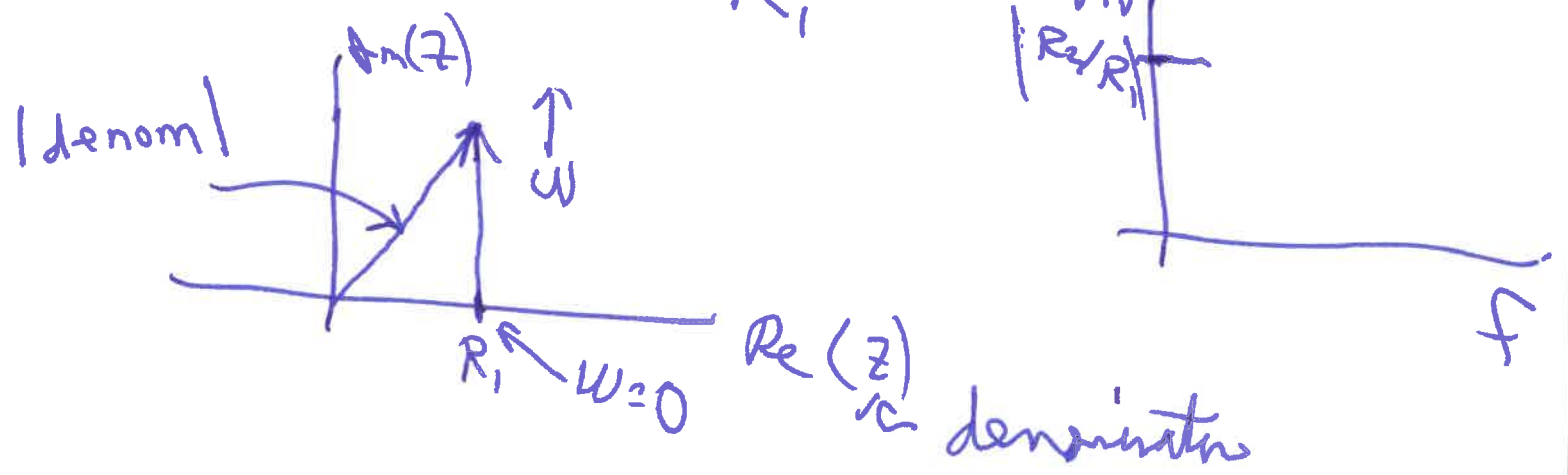

$\omega_c \rightarrow$ Power Gain

(3)

$$\approx \frac{1}{2} \max$$

$$|\text{Denominator}| = \sqrt{2}$$


$$\cancel{R_1} R_2 \omega_c = \cancel{R_1} |$$

$$\omega_c = \frac{1}{R_2 C}$$


$$A_v(\omega_c) = \frac{A_v(0)}{\sqrt{2}}$$

$$A_p(\omega_c) = \frac{A_p(0)}{2}$$


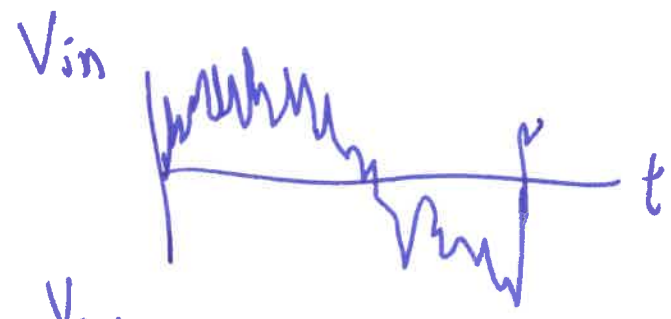
$$10 \log A_p(\omega_c) = 10 \log A_p(0) - 3 \text{ dB}$$



(4)

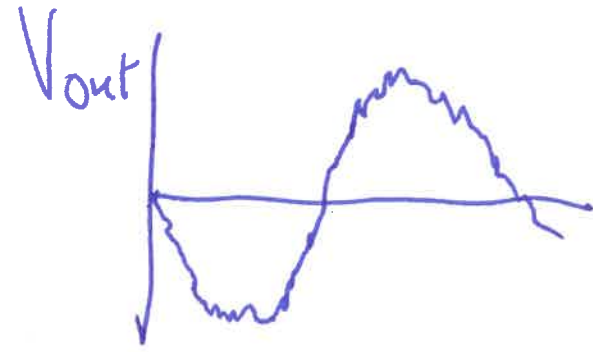



Buffer

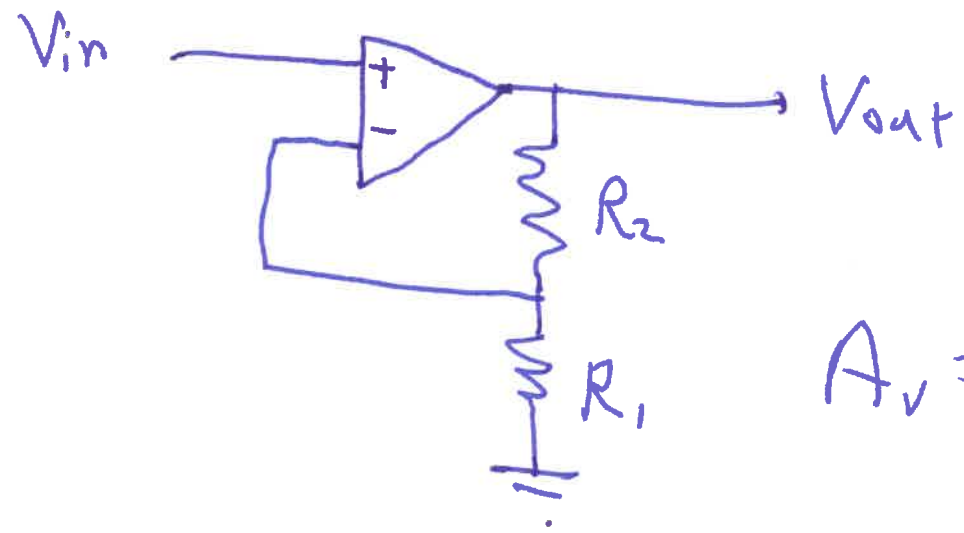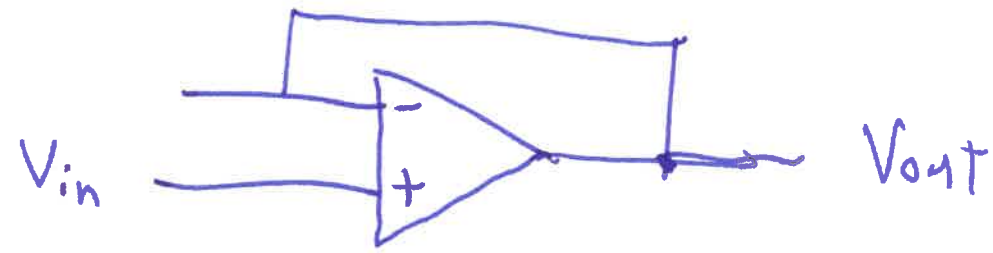

$$A_v = \frac{R_2 + R_1}{R_1}$$

5


Diff. Amp

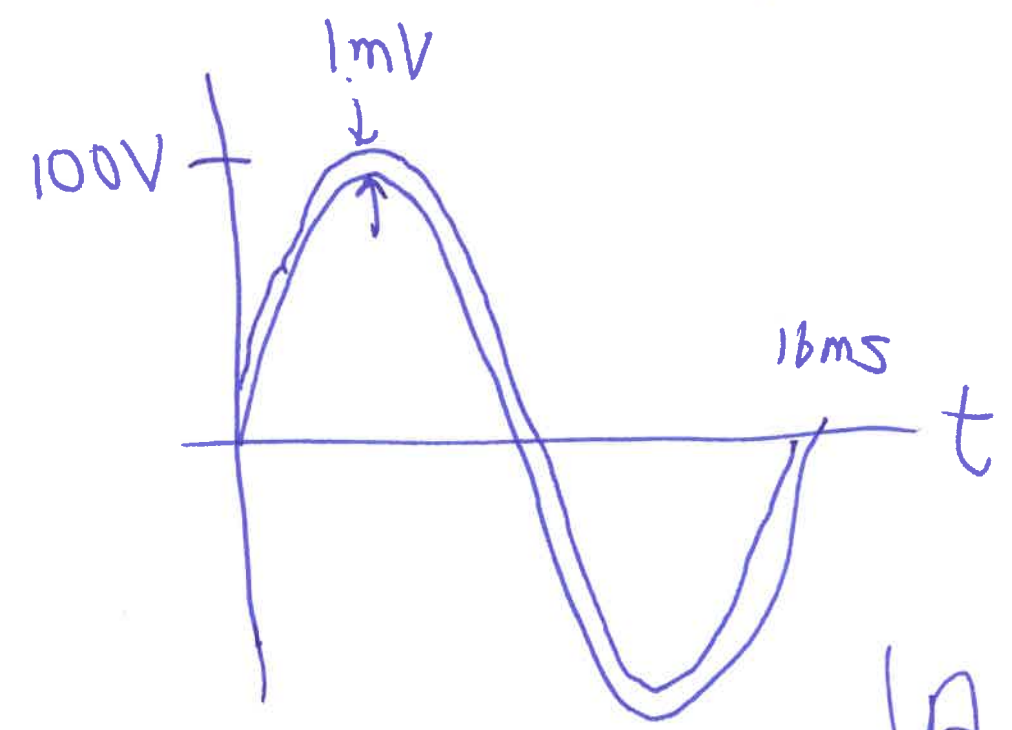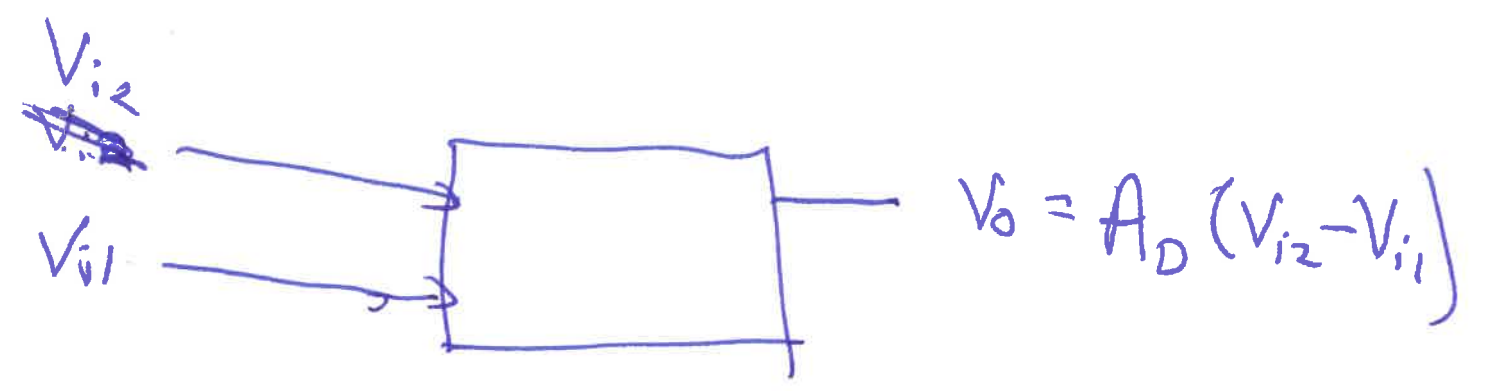

$|A_{cm}| < 10^{-4}$

$|A_D| = 1000$

want $< 10 \text{ mV}$

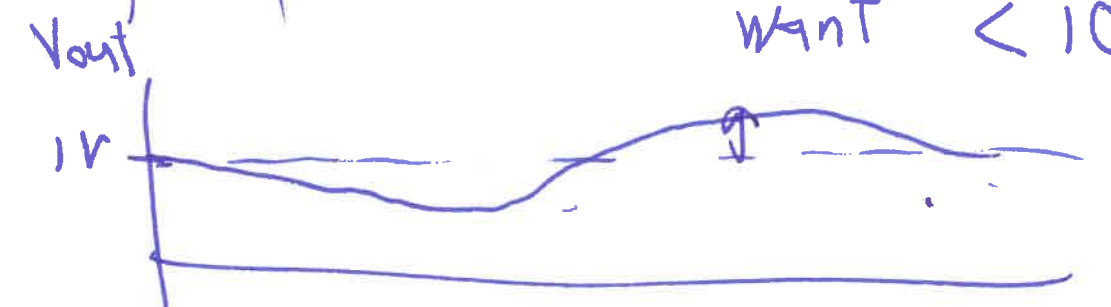

$CMRR = 20 \log \frac{1000}{10^{-4}} = 140 \text{ dB}$