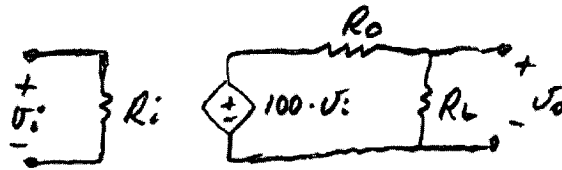


P.1 EECE 2412 : HW 1 Solutions

Fall 2018

Problem 1



$$R_L = 10 \text{ k}\Omega$$
$$A_v = \frac{v_o}{v_i} = 90$$

$$v_o = 100 \cdot v_i \cdot \left(\frac{R_L}{R_o + R_L} \right)$$

$$A_v = \frac{v_o}{v_i} = 100 \cdot \left(\frac{10000}{R_o + 10000} \right) = 90 \xrightarrow{\text{solve}} R_o = 1111 \Omega$$

$R_o = 1.11 \text{ k}\Omega$

Problem 2

$$P_{in} = \frac{(V_{in-RMS})^2}{R_{in}} = \frac{(0.1 \text{ V})^2}{100 \times 10^3 \Omega} = 100 \times 10^{-9} \text{ W} = 0.1 \mu\text{W}$$

$$P_{supply} = V_{supply} \cdot I_{supply} = 15 \text{ V} \cdot 2 \text{ A} = 30 \text{ W}$$

$$P_{out} = \frac{(V_{o-RMS})^2}{R_L} = \frac{(10 \text{ V})^2}{8} = 12.5 \text{ W}$$


disipated power : $P_d = P_{in} + P_{supply} - P_{out} = 17.5000001 \text{ W}$

efficiency: $\eta = \frac{P_{out}}{P_{supply}} \times 100\%$

$P_d \approx 17.5 \text{ W}$

$$\eta = \frac{12.5 \text{ W}}{30 \text{ W}} \times 100\% = 41.67\% = \eta$$

Problem 3

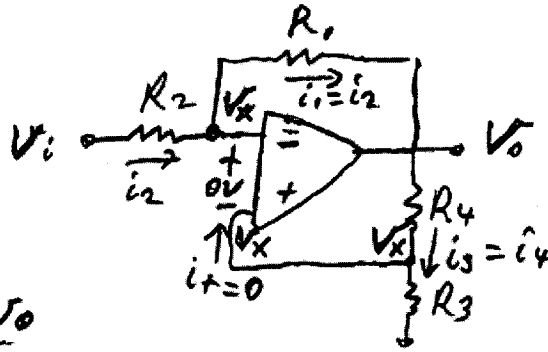

$$\textcircled{1}: V_x = \left(\frac{R_3}{R_3 + R_4} \right) \cdot V_o$$

$$i_2 = \frac{V_i - V_x}{R_2} = \frac{V_x - V_o}{R_1}$$

algebraic rearrangement $\rightarrow \frac{V_i}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \cdot V_x - \frac{V_o}{R_1}$

Substituting equ. $\textcircled{1}$ into the above equation yields:


$$\frac{V_i}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \cdot \left(\frac{R_3}{R_3 + R_4} \right) \cdot V_o - \frac{V_o}{R_1}$$

$$\frac{V_i}{R_2} = \left[\left(\frac{1}{R_1} + \frac{1}{R_2} \right) \cdot \left(\frac{R_3}{R_3 + R_4} \right) - \frac{1}{R_1} \right] \cdot V_o$$

$$\frac{V_o}{V_i} = \frac{1}{R_2 \cdot \left[\left(\frac{1}{R_1} + \frac{1}{R_2} \right) \cdot \left(\frac{R_3}{R_3 + R_4} \right) - \frac{1}{R_1} \right]}$$

P.3 Problem 4

a)

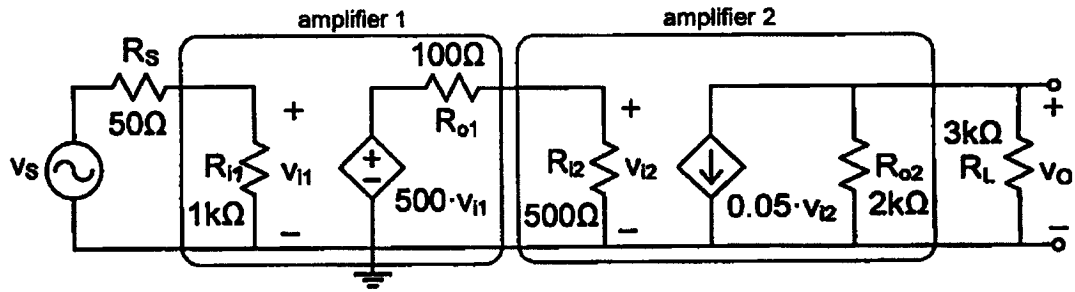

$$v_{i1} = v_s \cdot \left(\frac{R_{i1}}{R_{i1} + R_s} \right) \quad \text{sub.}$$


$$v_{i2} = 500 \cdot v_{i1} \cdot \left(\frac{R_{i2}}{R_{i2} + R_{o1}} \right) = 500 \cdot v_s \cdot \left(\frac{R_{i1}}{R_{i1} + R_s} \right) \cdot \left(\frac{R_{i2}}{R_{i2} + R_{o1}} \right)$$

$$v_o = -0.05 \cdot v_{i2} \cdot (R_{o2} \parallel R_L) = -0.05 \cdot 500 \cdot v_s \cdot \left(\frac{R_{i1}}{R_{i1} + R_s} \right) \cdot \left(\frac{R_{i2}}{R_{i2} + R_{o1}} \right) \cdot (R_{o2} \parallel R_L)$$

$$A_{vs} = \frac{v_o}{v_s} = 0.05 \cdot 500 \cdot \left(\frac{1k\Omega}{1k\Omega + 50\Omega} \right) \cdot \left(\frac{500\Omega}{500\Omega + 100\Omega} \right) \cdot \left(\frac{1}{\frac{1}{2k\Omega} + \frac{1}{3k\Omega}} \right)$$

$$A_{vs} = -2.38 \times 10^4 \quad \text{or} \quad A_{vs}(dB) = 87.54 \text{ dB} = 20 \cdot \log(|A_{vs}|)$$

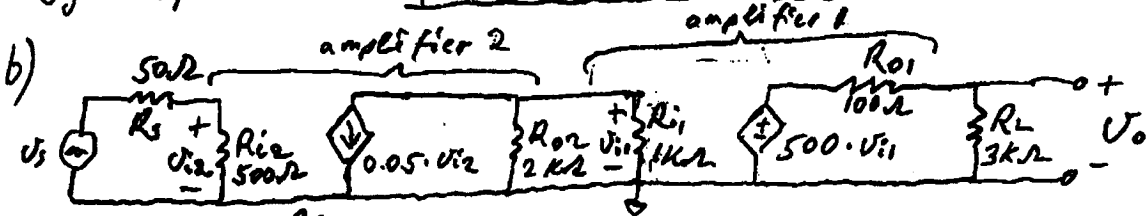by inspection: $R_i = 1k\Omega$ $R_o = 2k\Omega$



$$v_{i2} = v_s \cdot \left(\frac{R_{i2}}{R_{i2} + R_s} \right) \quad \text{sub.}$$

$$v_{i1} = -0.05 \cdot v_{i2} \cdot (R_{o2} \parallel R_{i1}) = -0.05 \cdot v_s \cdot \left(\frac{R_{i2}}{R_{i2} + R_s} \right) \cdot (R_{o2} \parallel R_{i1})$$

$$v_o = 500 \cdot v_{i1} \cdot \left(\frac{R_L}{R_L + R_{o1}} \right) = 500 \cdot (-0.05) \cdot v_s \cdot \left(\frac{R_{i2}}{R_{i2} + R_s} \right) \cdot (R_{o2} \parallel R_{i1}) \cdot \left(\frac{R_L}{R_L + R_{o1}} \right)$$

$$A_{vs} = \frac{v_o}{v_s} = -500 \cdot 0.05 \cdot \left(\frac{500\Omega}{500\Omega + 50\Omega} \right) \cdot \left(\frac{1}{\frac{1}{1k\Omega} + \frac{1}{2k\Omega}} \right) \cdot \left(\frac{3k\Omega}{3k\Omega + 100\Omega} \right)$$

$$A_{vs} = -1.47 \times 10^4 \quad \text{or} \quad A_{vs}(dB) = 20 \cdot \log(|A_{vs}|) = 83.32 \text{ dB}$$

$R_i = 500\Omega$ $R_o = 100\Omega$

Prob. 5

a) ①: $A_{vs}(s) = \frac{V_o(s)}{V_s(s)} = \frac{V_i(s)}{V_s(s)} \times \frac{V_o(s)}{V_i(s)}$, where $s = j\omega$

$$V_i(\omega) = \frac{R_i}{R_i + R_s} \cdot V_s(s) \rightarrow \text{②: } \frac{V_i(s)}{V_s(s)} = \frac{150}{150 + 50} = 0.75$$

$$V_o(s) = -0.1 \cdot V_i(s) \cdot (R_o \parallel \frac{1}{sC_L} \parallel R_L) = -0.1 \cdot V_i(s) \cdot \left(\frac{1}{\frac{1}{R_o} + sC_L + \frac{1}{R_L}} \right)$$

$$V_o(s) = -0.1 \cdot V_i(s) \times \left(\frac{\frac{1}{\frac{1}{R_o} + \frac{1}{R_L}}}{1 + \frac{sC_L}{\frac{1}{R_o} + \frac{1}{R_L}}} \right) = -0.1 \cdot V_i(s) \cdot \left(\frac{R_{eq}}{1 + sC_L R_{eq}} \right)$$

where: $R_{eq} = \frac{1}{\frac{1}{R_o} + \frac{1}{R_L}} = R_o \parallel R_L$

$$R_{eq} = 3.75 \text{ k}\Omega$$

③: $\frac{V_o(s)}{V_i(s)} = -0.1 \cdot \left(\frac{R_{eq}}{1 + sC_L R_{eq}} \right)$

Substituting ② and ③ into ①, and $s = j\omega$:

$$A_{vs}(j\omega) = 0.75 \cdot (-0.1) \cdot \left(\frac{R_{eq}}{1 + j\omega C_L R_{eq}} \right) = - \frac{0.075 \cdot R_{eq}}{1 + j\omega C_L R_{eq}}$$

$$A_{vs}(j\omega) = \frac{-281.25}{1 + j \left(\frac{\omega}{2667} \right)}$$

where: $\omega_{3dB} = \frac{1}{C_L R_{eq}}$
 $\omega_{3dB} = 2667 \text{ rad.}$

b) $f_{3dB} = \frac{\omega_{3dB}}{2\pi} \stackrel{\text{see part a)}}{=} \frac{1}{2\pi C_L R_{eq}} = \frac{2667}{2\pi} = \boxed{424 \text{ Hz} = f_{3dB}}$

c) $GBW = f_t \approx |A_{vs}(\omega=0)| \cdot f_{3dB}$

where: $|A_{vs}(\omega=0)| = \left| \frac{-281.25}{1 + j \left(\frac{0}{2667} \right)} \right| = 281.25$


Thus,

$$GBW \approx (281.25) \cdot (424 \text{ Hz})$$

$$\boxed{GBW \approx 119 \text{ kHz}}$$

15

Problem 5

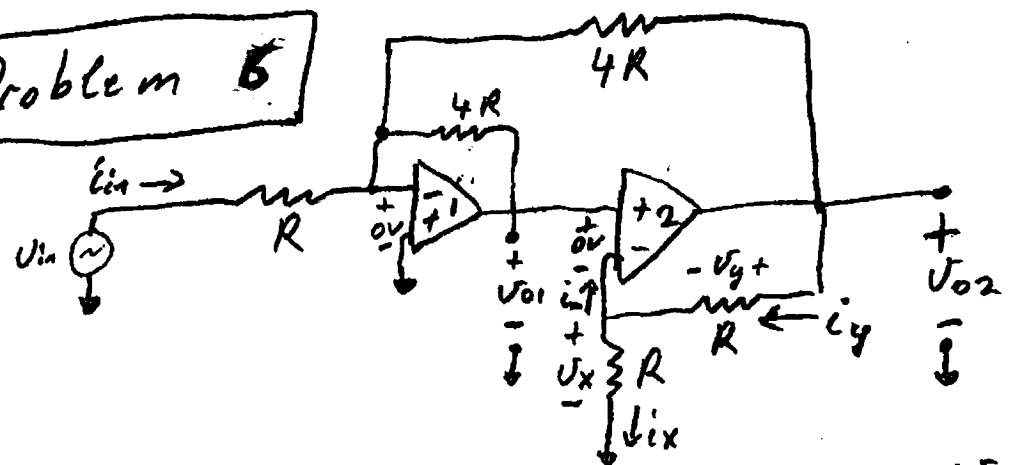

Summing-point constraint for amplifier 1: $v_- = v_+ = 0V$

↳ ①: $i_{in} = \frac{V_{in} - 0V}{R} = \frac{V_{in}}{R}$

Summing-point constraint for amplifier 2:

$0 = -V_{01} + 0V + V_x \rightarrow$ ②: $V_x = V_{01}$

$i_- = 0 \rightarrow i_x = i_y = \frac{V_x}{R} = \frac{V_{01}}{R} \rightarrow$ ③: $i_x = i_y = \frac{V_{01}}{R}$

KVL: $0 = -V_{02} + V_y + V_x$

↳ $V_{02} = V_y + V_x = i_x R + i_y R = 2i_x R = 2V_x$

④: $V_{02} = 2 \cdot V_x = 2 \cdot V_{01}$

KCL at the inverting input of amplifier 1:

$0 = i_{in} + \frac{V_{01}}{4R} + \frac{V_{02}}{4R} = \frac{V_{in}}{R} + \frac{V_{01}}{4R} + \frac{2V_{01}}{4R}$

Rearranging the above equation:

$-V_{in} \cdot 4 = 3V_{01} \rightarrow$ $A_1 = \frac{V_{01}}{V_{in}} = -\frac{4}{3}$

From equ. ④: $V_{02} = 2 \cdot V_{01} = 2 \cdot (-\frac{4}{3} \cdot V_{in}) = -\frac{8}{3} \cdot V_{in}$

$A_2 = \frac{V_{02}}{V_{in}} = -\frac{8}{3}$