
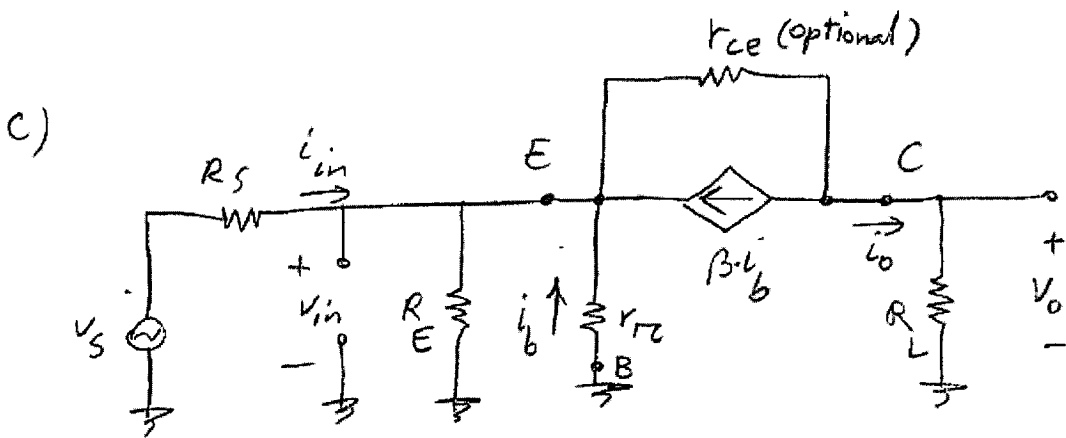
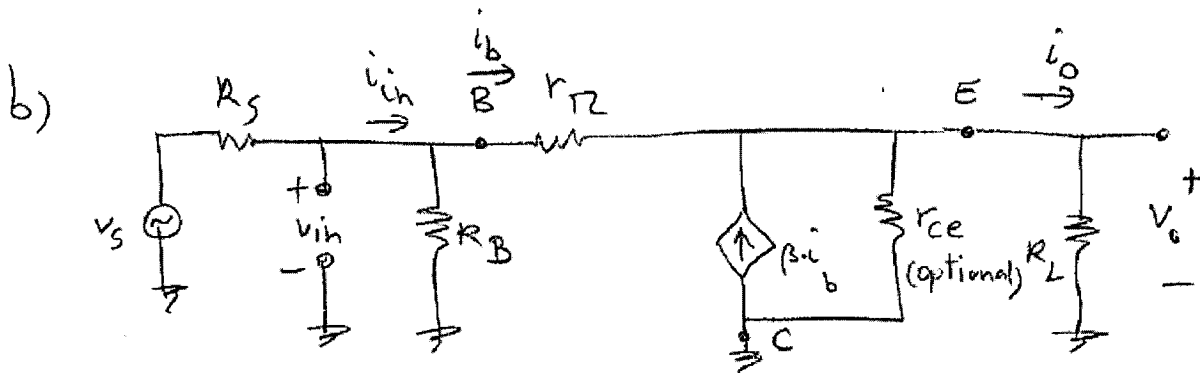


Homework 7 Solutions

①


Fall
2018

Prob. 1

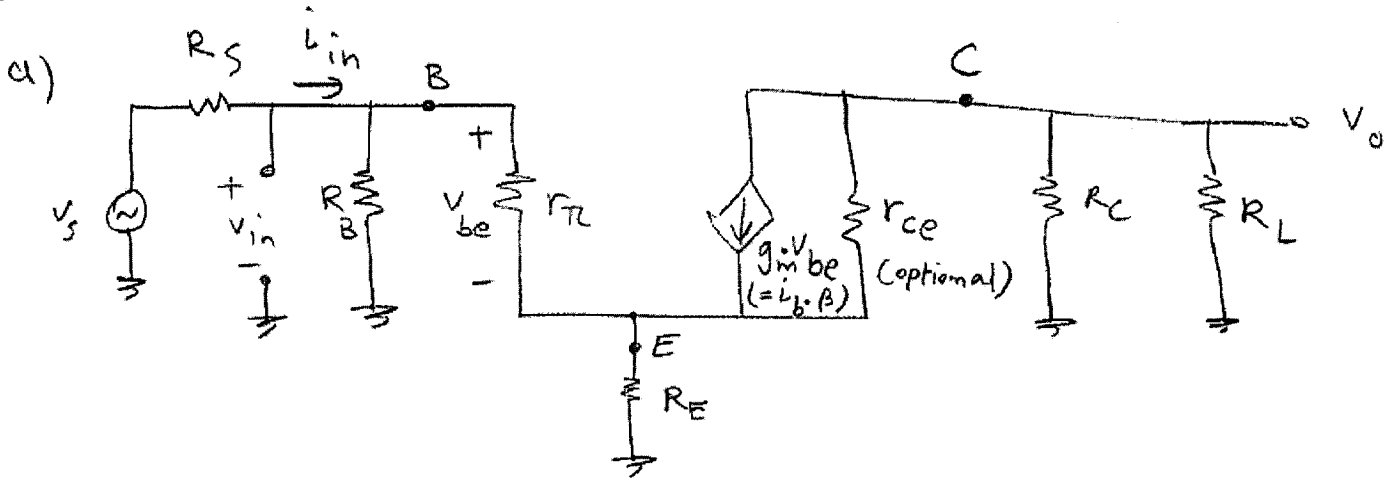

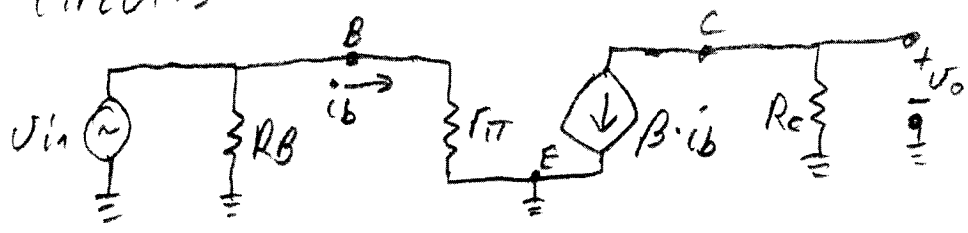Problem 2


The equivalent circuit is identical for both circuits when $V_{hum} = 0$ during small-signal analysis.



$$i_b = \frac{V_{in}}{r_{\pi}} \quad \text{Sub.}$$

$$V_o = -\beta \cdot i_b \cdot R_c = -\beta \cdot \frac{V_{in}}{r_{\pi}} \cdot R_c \rightarrow \boxed{\frac{V_o}{V_{in}} = -\frac{\beta \cdot R_c}{r_{\pi}}}$$


(a) With $V_{in} = 0$:

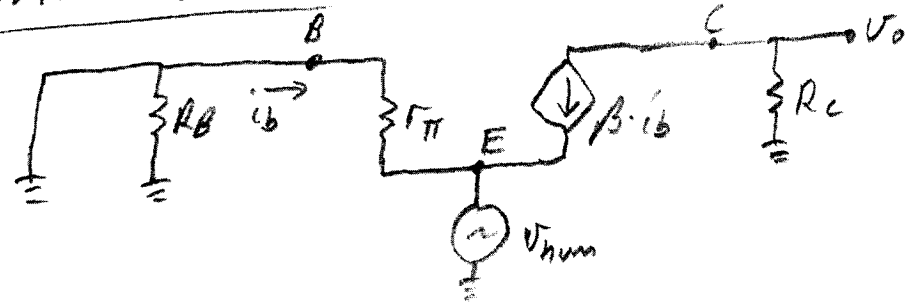

$$i_b = -\frac{V_{hum}}{r_{\pi}} \quad \text{Sub.}$$

$$V_o = -\beta \cdot i_b \cdot R_c = \beta \cdot \frac{V_{hum}}{r_{\pi}} \cdot R_c \rightarrow \boxed{\frac{V_o}{V_{hum}} = \frac{\beta \cdot R_c}{r_{\pi}}}$$

(b) With $V_{in} = 0$:

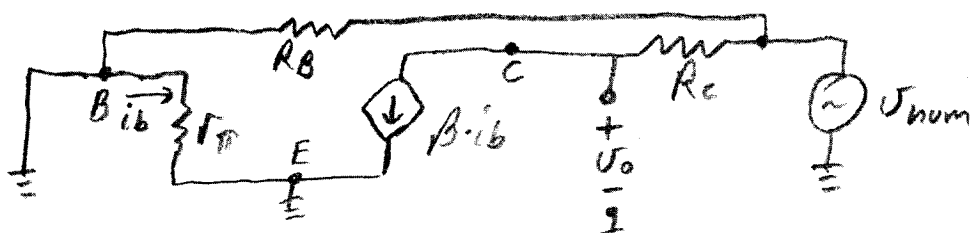


$$i_b = \frac{0V - 0V}{r_{\pi}} = 0 \rightarrow \beta \cdot i_b = 0$$

$$\text{KVL: } 0 = -V_o - \beta \cdot i_b + V_{hum} \rightarrow V_o = V_{hum} \rightarrow \boxed{\frac{V_o}{V_{hum}} = 1}$$

... Prob. 2 cont.:

3

DC analysis:

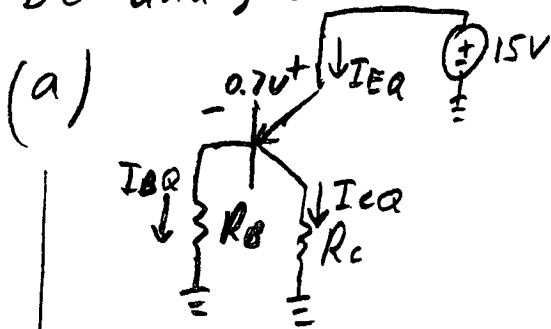

$$0 = -15V + 0.7V + I_{BQ} \cdot R_B$$


$$\hookrightarrow I_{BQ} = \frac{14.3V}{1 \times 10^6 \Omega} = 14.3 \mu A$$

$$I_{CQ} = \beta \cdot I_{BQ} = 1.43 \text{ mA}$$

$$r_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{100 \cdot 26 \text{ mV}}{1.43 \text{ mA}} = 1.82 \text{ k}\Omega$$

$$\frac{V_o}{V_{in}} = \frac{-\beta \cdot R_c}{r_{\pi}} = -258.5$$
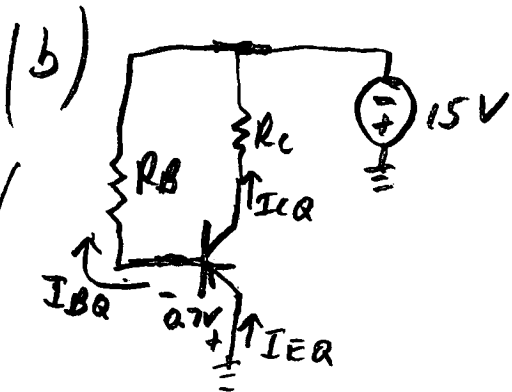
$$\frac{V_o}{V_{hum}} = \frac{\beta R_c}{r_{\pi}} = 258.5$$



$$0 = 0.7V + I_{BQ} \cdot R_B - 15V$$

$$\hookrightarrow I_{BQ} = \frac{14.3V}{R_B} = 14.3 \mu A$$

$$I_{CQ} = \beta \cdot I_{BQ} = 1.43 \text{ mA}$$


$$r_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}} = 1.82 \text{ k}\Omega$$

$$\frac{V_o}{V_{in}} = \frac{-\beta \cdot R_c}{r_{\pi}} = -258.5$$

$$\frac{V_o}{V_{hum}} = 1$$

Circuit (b) is better because it has a lower gain from V_{hum} to V_o , while having the same gain from V_{in} to V_o .

Problem (3)

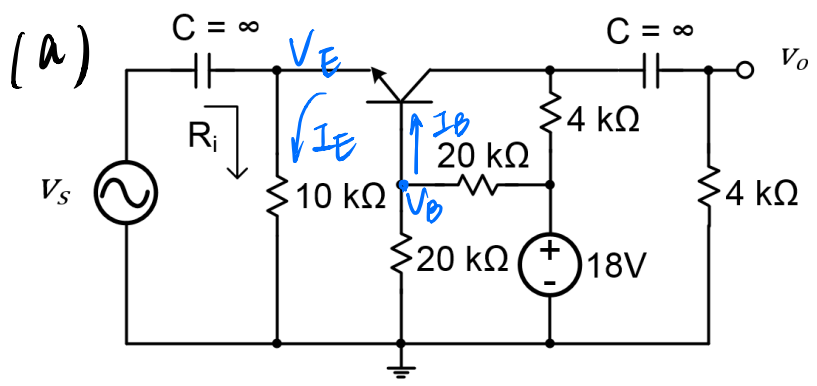

DC analysis :

Capacitors → open circuit

$$\begin{cases} I_E = \frac{V_E}{10k\Omega}, V_E = V_B - 0.7V \\ I_B = \frac{18 - V_B}{20k\Omega} - \frac{V_B}{20k\Omega} \\ I_E = (1 + \beta)I_B, \beta = 250 \end{cases}$$

$V_B = 8.9671, V_E = 8.2671$

$I_E = 0.82671 \text{ mA}, I_C = \frac{\beta}{1 + \beta} I_E = 0.82342 \text{ mA}$

$g_m = \frac{I_C}{V_T} = \frac{0.82342}{26} = 0.03167 \text{ S}$

$r_{\pi} = \frac{\beta}{g_m} = \frac{250}{0.03167} = 7.893 \text{ k}\Omega$


Small signal analysis

Capacitors → short circuit


$-V_{be} = V_s \cdot \frac{r_{\pi}}{r_{\pi} + 20k\Omega \parallel 20k\Omega}$

$V_s = -2.272 V_{be}$

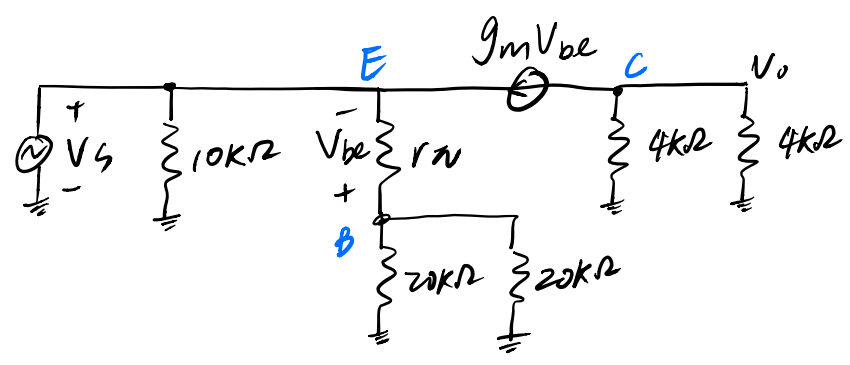$V_o = -g_m V_{be} \cdot (4k\Omega \parallel 4k\Omega) = -63.6 V_{be}$



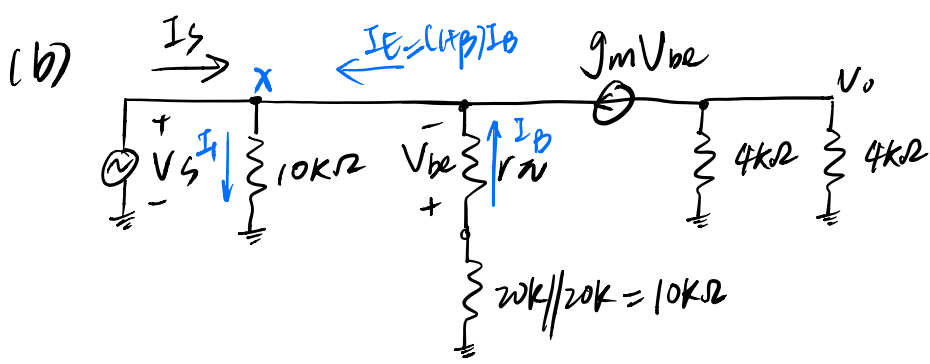$A_{Vs} = \frac{V_o}{V_s} = \frac{-63.6 V_{be}}{-2.272 V_{be}} = 27.99 = A_{Vs}$



$$\begin{cases} I_B = \frac{V_{be}}{r_{\pi}} = -\frac{V_s}{r_{\pi} + 10k\Omega} \\ I_E = (1 + \beta)I_B = -V_s \frac{1 + \beta}{r_{\pi} + 10k\Omega} \\ I_1 = V_s \cdot \frac{1}{10k\Omega} \end{cases}$$

KCL @ node x :


$I_s = I_1 - I_E = V_s \left[\frac{1}{10k\Omega} + \frac{1 + \beta}{r_{\pi} + 10k\Omega} \right]$

$R_i = \frac{V_s}{I_s} = \frac{1}{\frac{1}{10k\Omega} + \frac{1 + \beta}{r_{\pi} + 10k\Omega}} = 70.66 \Omega = R_i$

Problem (4)



(a) Biasing point

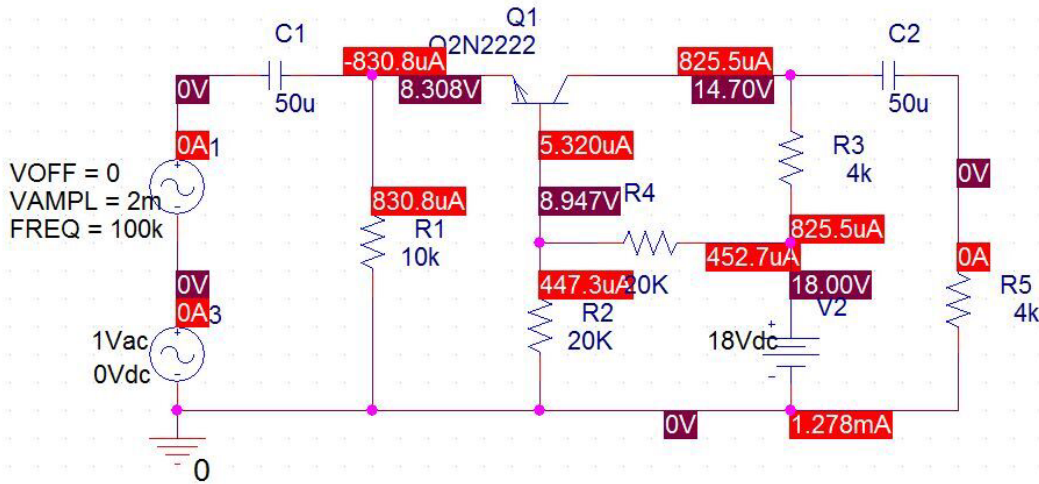

```

Q2N2222
NPN
IS 14.340000E-15
BF 255.9
NF 1
VAF 74.03
IKF .2847
ISE 14.340000E-15
NE 1.307
BR 6.092
NR 1
RB 10
RC 1
CJE 22.010000E-12
MJE .377
CJC 7.306000E-12
MJC .3416
TF 411.100000E-12
XTF 3
VTF 1.7
ITF .6
TR 46.910000E-09
XTB 1.5
CN 2.42
D .87
    
```

```

**** BIPOLAR JUNCTION TRANSISTORS
NAME Q_Q1
MODEL Q2N2222
IB 5.32E-06
IC 8.25E-04
VBE 6.39E-01
VBC -5.75E+00
VCE 6.39E+00
BETADC 1.55E+02
GM 3.18E-02
RPI 5.42E+03
RX 1.00E+01
RO 9.67E+04
CBE 4.93E-11
CBC 3.49E-12
CJS 0.00E+00
BETAAC 1.72E+02
CBX/CBX2 0.00E+00
FT/FT2 9.60E+07
    
```

$I_B > 0$
 (active/saturation region)
 $V_{CE} > 0.2V$
 (active region) ✓


$$A_{Vs} = \frac{V_o}{V_s} = \frac{-g_m V_{be} (4k \parallel 4k)}{-V_{be} \frac{r_{\pi} + 20k \parallel 20k}{r_{\pi}}} = 22.355 = A_{Vs}$$

A_{Vs} is smaller compared to hand calculation, the reasons are:

- ① $\beta_{ac} = 155$ instead of 250, which makes $r_{\pi} = \frac{\beta}{g_m}$ smaller;
- ② $V_A = 74.03V$ instead of ∞ , which makes $r_{ce} = \frac{V_A}{I_c}$ finite. \rightarrow R_{out} becomes smaller as well.

6


(b) AC simulation:

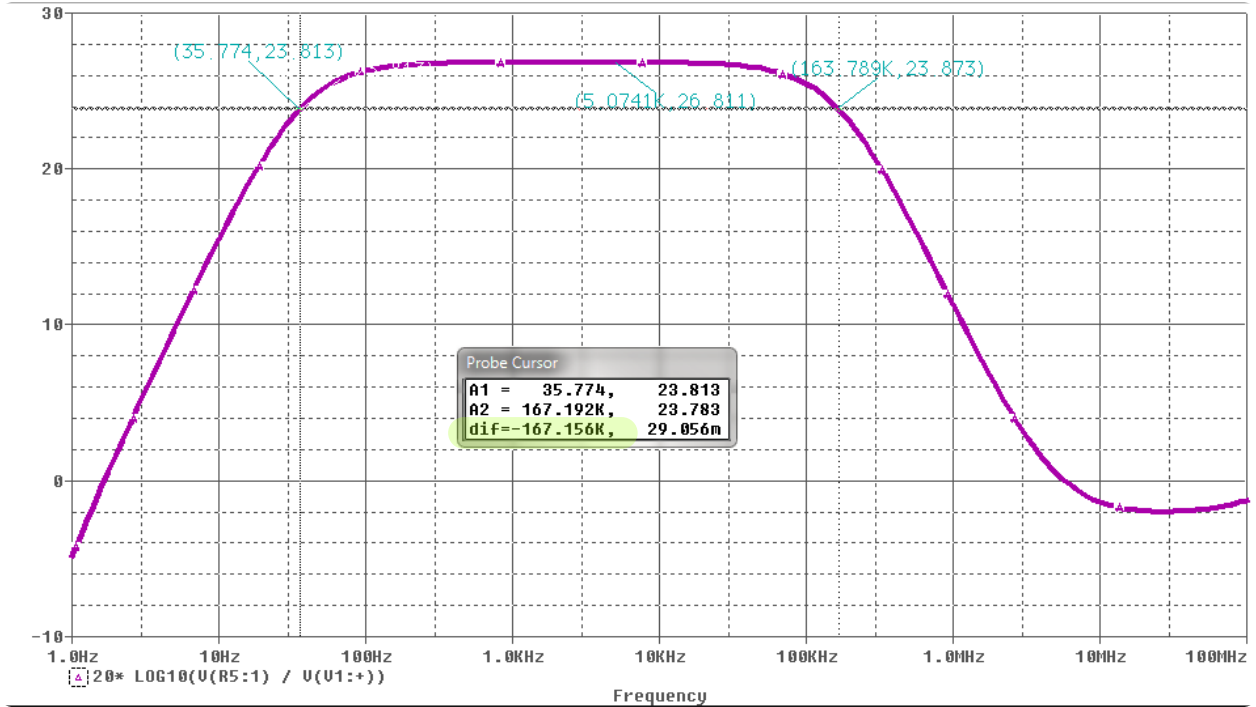

$$A_{Vs} = 26.811 \text{ dB} \rightarrow A_{Vs} = 10^{\frac{(26.811)}{20}} = \boxed{21.9}$$

$$\text{BW} = 167.156 \text{ kHz}$$

(c) transient simulation

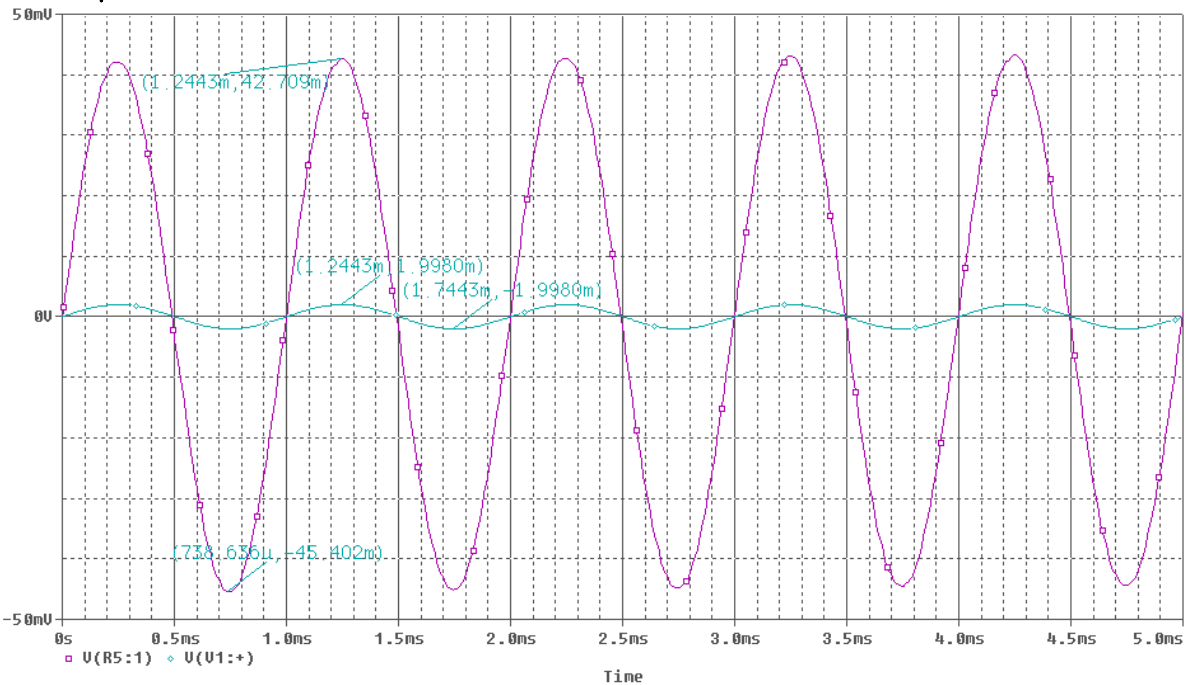


$$A_{Vs} = \frac{42.709 \text{ mV} - (-45.402 \text{ mV})}{1.998 \text{ mV} - (-1.998 \text{ mV})} = \boxed{22.04}$$

→ 26.811 dB
 agrees with the gain at 1kHz in part (b)


(d)

7

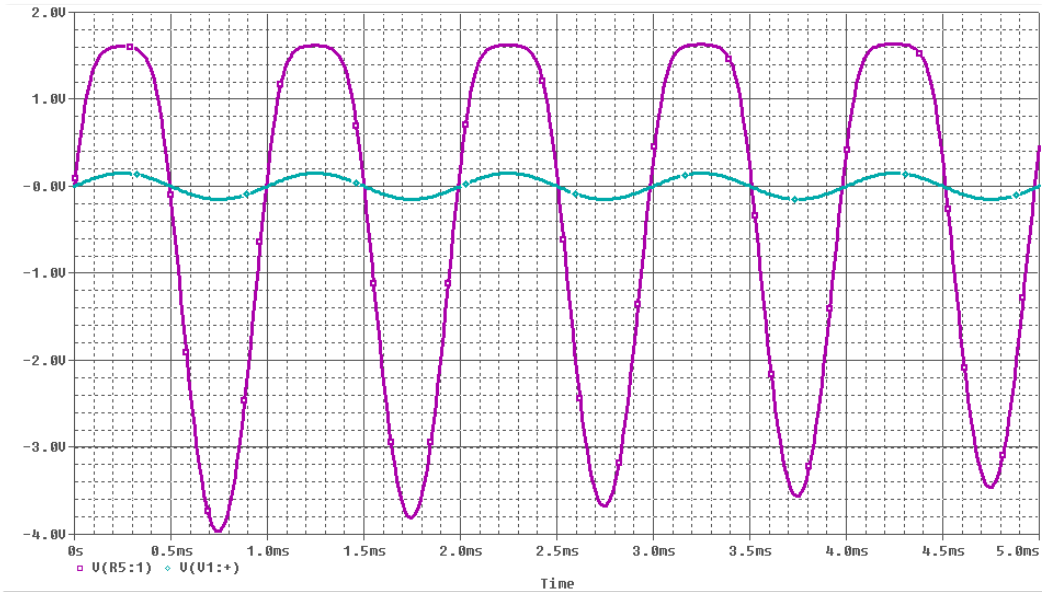


From DC analysis in part (a), we observe that headroom between collector and supply is $\Delta V = 18V - 14.7V = 3.3V$. With the gain of 22, by increasing V_s , V_o gets closer to $3.3V$ but can never exceed $3.3V$ (otherwise peak value of V_o will go beyond the supply voltage). Therefore, V_o gets saturated when V_s is close to $\frac{3.3V}{22} = 150mV$.

(e) Updated schematic:

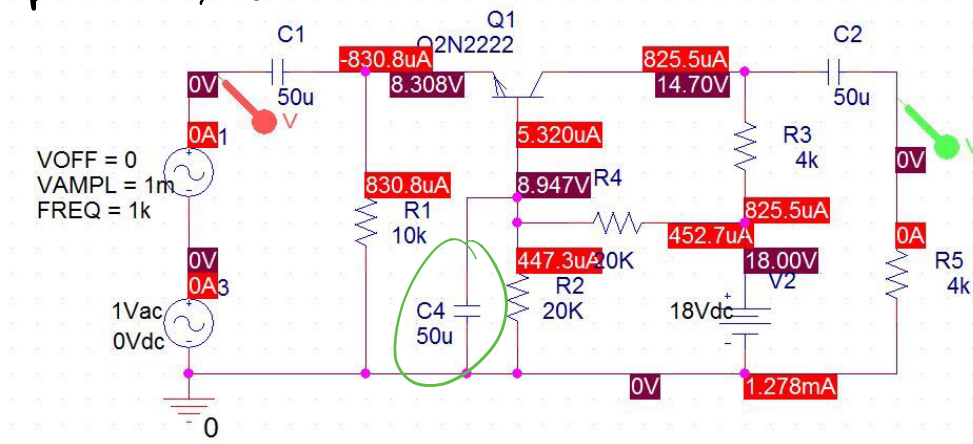

AC simulation:


8

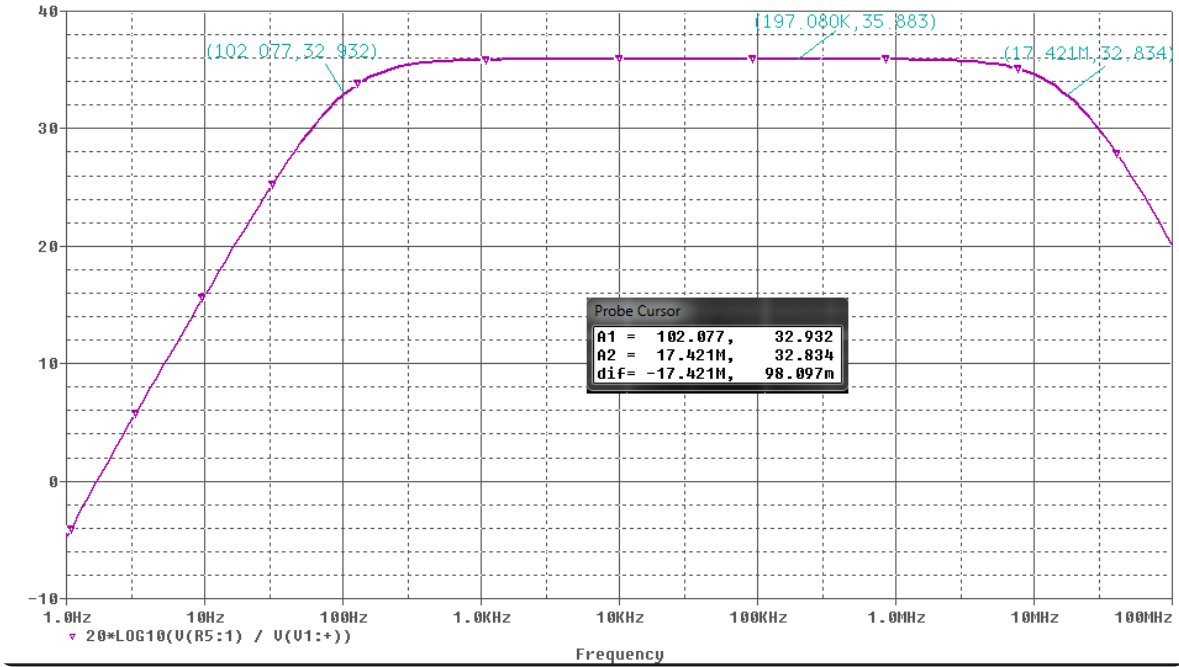

$$A_{VS} = 35.883 \text{ dB} \rightarrow A_{VS} = 10^{\frac{35.883}{20}} = 62.25 = A_{VS}$$

$$BW = 17.412 \text{ MHz}$$

transient simulation

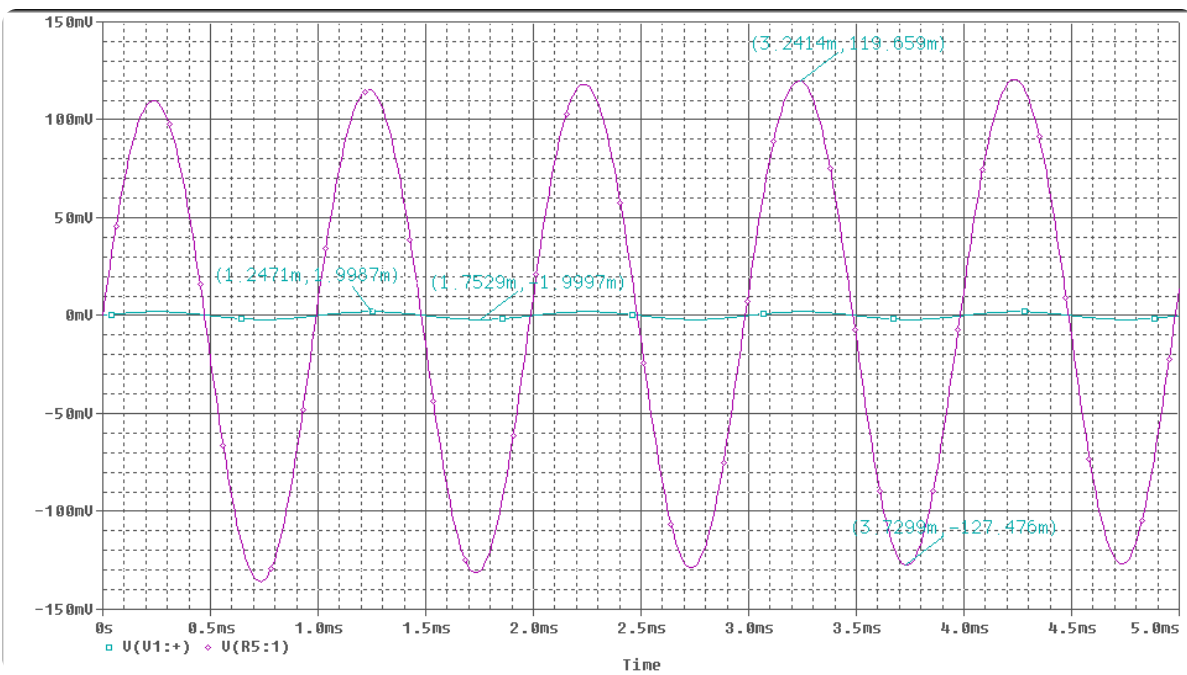

$$A_{VS} = \frac{119.650 \text{ mV} - (-127.476 \text{ mV})}{1.9987 \text{ mV} - (-1.9997 \text{ mV})} = 61.8 = A_{VS}$$