

U210 Electrical Engineering Homework Solutions

Assignment 1: 1.1.1, 1.1.2, 1.1.4*, 1.1.7, 1.1.11, 1.1.20

1.1.1 $F=9 \times 10^9$ N or 1.01×10^6 ton-force

1.1.2 $F_N = ((3)^{1/2}/a^2)$ with $F_1 = F_2 = F_3$

1.1.4 location of point charge is (2,2,-1) with $Q = (24\pi\epsilon_0)$ C

1.1.7 $v(t) = (50+t)$ C; $i = dq/dt = 1$ A

1.1.11 F at (3,4,2) = $0.0002(3a_x + 4a_y)$ N

1.1.20 230 hrs; 5 MJ

Assignment 2: 1.2.5, 1.2.6, 1.2.7, 1.2.8, 1.2.9, 1.2.13(a), 1.2.14, 1.2.18, 1.2.19

1.2.5 3 Ohms

1.2.6 10 Ohms

1.2.7 2 Ohms

1.2.8 8 Ohms

1.2.9 12.4% increase in power with matching load

1.2.13 (a) $V_{RMS} I_{RMS} = V_{RMS}^2 / R$

1.2.14 a) 4.8 kW; b) 1.44 kW; c) 7.2 kW; d) 1.8 kW

1.2.18 $V_x = 1.5$ V

1.2.19 a) -2A; b) -5 A; c) 2 A; d) 1.5 A

Assignment 3: 1.3.1, 1.3.2, 1.3.5, 1.3.6, 1.3.10

1.3.1 $V_B = 2$ V; $V_C = 8$ V; $V_G = 14$ V; $I_A = -1$ A; $I_D = -1$ A; $I_E = 2$ A; $I_F = 2$ A; $I_H = 1$ A; Power delivered to each element: A=6 W (sink); B=4 W (sink); C=-8W (source); D=8W (sink); E=8 W (sink); F=20 W (sink); G=-42 W (source); H=4W (sink); conservation of power is satisfied.

1.3.2 $V = 2$ V

1.3.5 $V_1 = 35$ V; $V_2 = -15$ V; $P_{V1} = 175$ W; $P_{V2} = 75$ W; $P_R = 250$ W; power absorbed by resistors equal power provided by sources therefore conservation of power is satisfied.

1.3.6 a) $V = 914.3$ V; b) $I_1 = 45.7$ A; $I_2 = 22.86$ A; $I_3 = 11.43$ A; c) $P_A = 27.4$ kW; $P_B = 45.7$ kW; $P_R = 73.1$ kW; power absorbed by resistors equals power provided by sources therefore conservation of power is satisfied.

1.3.10 $V_{out} = -5$ V; $I = 0.5$ mA; $P = 1.25$ mW

Assignment 4: 2.1.1, 2.1.2, 2.1.3, 2.2.2, 2.2.4, 2.2.9, 2.2.10

2.1.1 a) $R_{th} = 6$ Ohms, $V_{th} = 1$ V b) $R = 6$ Ohms c) $P = 1/24$ Watts

2.1.2 $V_{th} = 8$ V, $R_{th} = 4$ Ohms, $I_N = 2$ A

2.1.3 $V_{th} = 72$ V, $R_{th} = 4$ Ohms, $I_N = 18$ A

2.2.2 $I = 1$ Amp

2.2.4 Nodal analysis leads to $V_C = 54$ V (the voltage across the 12 Ohm R); Using mesh analysis $I_2 = 4.5$ A where $V = 12I_2 = 54$ V

2.2.9 Nodal analysis leads to $V_A=12\text{ V}$, $V_B=-6\text{V}$ where $V_B=V=-6\text{ V}$; using mesh analysis
 $I_{\text{loop}} (=I_L)=3\text{ A}$, $V_B=2I_L-4I_1=-6\text{V}$